

# Radio-Electronics®

**SPECIAL  
TEAR OUT SECTION  
COMPUTER DIGEST**

\$1.75 JULY 1984

COMPUTERS - VIDEO - STEREO - TECHNOLOGY - SERVICE

**Energy Miser For  
Air Conditioners!**  
Build R-E's add-on and  
save money this summer.

**Tune-up Your MDS  
Downconverter.**  
Simple - to - follow  
instructions let you  
extract maximum  
performance.

**Build Your Own  
Power Supplies!**  
Practical power-supply  
and voltage regulator circuits.

**Do Something New  
With Your Timex 1000!**  
R-E shows you how to  
use it as a control  
computer around  
the house.

**Mind Boggling  
TV Problems.**  
Actual case  
histories from a  
service shop with details  
on the troubleshooting  
techniques used  
to fix them.



## **PLUS:**

- ★ Hobby Corner
- ★ Equipment Reports
- ★ Designers Notebook
- ★ Service Clinic
- ★ New Idea
- ★ State-Of-Solid-State

**GERNSBACK  
PUBLICATION**





# Build your own IBM PC compatible and save hundreds of dollars.



## Heath proudly announces the NEW HS-151 Desktop and HS-161 Portable computers.

One of the world's largest software libraries has IBM's name on it. Now you can run that software on Heath's new IBM PC compatible computers, available in easy-to-build kits.

Can you build one of these computers? 85% of our first-time customers ask the same question. And the answer is 100% yes. You can.

In fact, you *should* build one. You'll save a lot of money while learning about computers in general and the Heath PC's in particular.

**Build confidence**...and your new computer...one step at a time. Two main circuit boards come to you pre-assembled and factory-tested. So that you can build the three other boards, we include a test soldering board plus helpful soldering instructions to make sure you get it right. Our instruction manuals are easy to understand, thorough and packed with cogent illustrations. And once it's built, the computer guides you

through a full range of included disk-based diagnostics.

**Expert advice** is only a phone call away, should you need it. You'll reach a trained consultant whose specialty is talking sense, not jargon.

We'll do whatever's necessary to make our pledge come true: "We Won't Let You Fail." Our entire business depends on that simple promise.

## Experience a little wonder and a lot of pride. Save

money, too, by building the highest quality personal computer. The Heath PC's have 128K RAM standard (expandable to 640K), a professional keyboard, dual 360K disk drives and optional Winchester. These machines are truly complete. Both are color capable and MS\*-DOS is included.

Check out the Heath PC computers today. IBM compatibility means they'll run the most popular software. And, with the money saved by building a kit, think of all the peripherals and software you can buy!

**HS-151 Desktop PC with standard floppy disk drive or optional hard disk.**

**CIRCLE READER SERVICE CARD.** Get more information on the most rewarding personal computers. The HS-151 Desktop PC and HS-161 Portable PC.

\*MS is a registered trademark of Microsoft Corporation.

## For computing on the go... the HS-161 Portable.



The HS-161 has the same features as the HS-151. Amber Monitor included. Convenient keyboard folds up, two disk drives fold down.



**Heathkit®**  
Heath  
Company


A subsidiary of Zenith Radio Corporation

CIRCLE 15 ON FREE INFORMATION CARD

CP-230


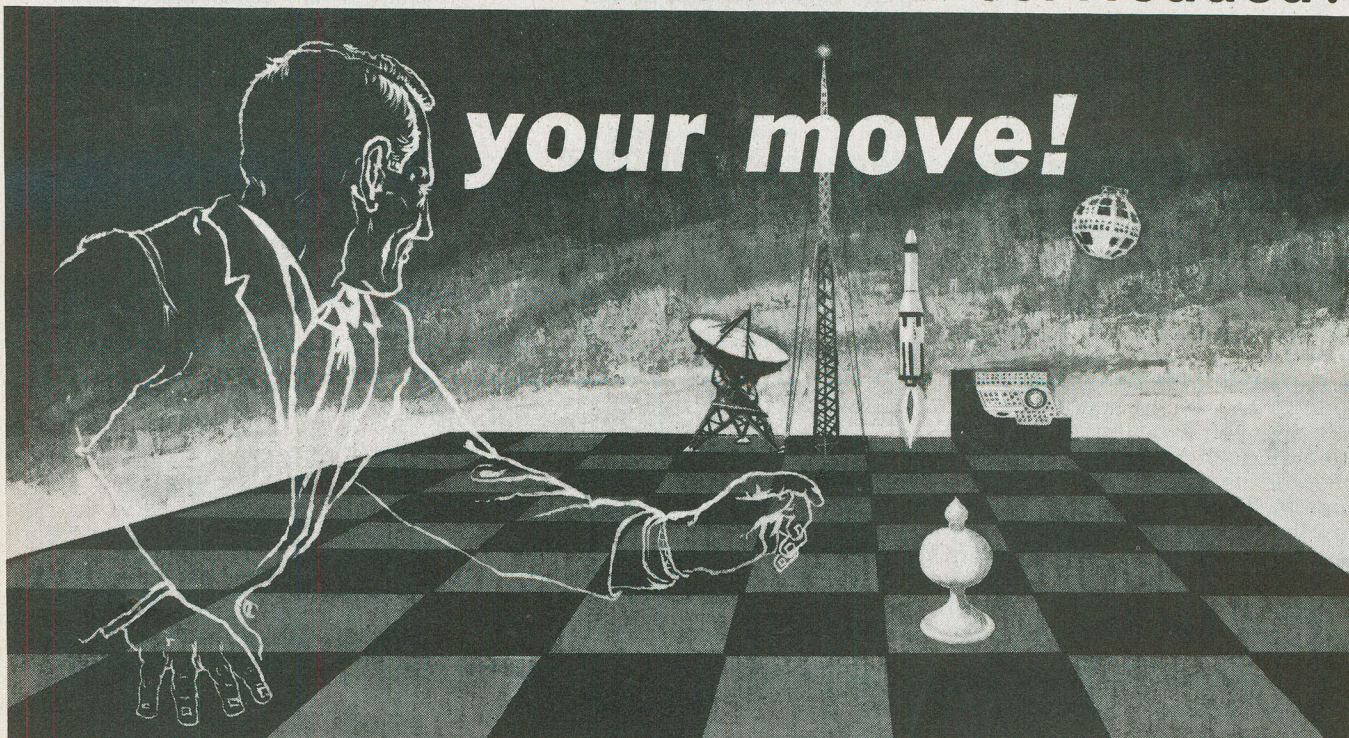
# Where's Your **ELECTRONICS** Career Headed?



## The Move You Make Today Can Shape Your Future

Yes it's your move. Whether on a chess board or in your career, you should plan each move carefully. In **electronics**, you can *move ahead* faster and further with a

### **B. S. DEGREE**

Put professional knowledge and a COLLEGE DEGREE in your electronics career. Earn your degree through independent study at home, with Grantham College of Engineering. No commuting to class. Study at your own pace, while continuing your present job.

The accredited Grantham non-traditional degree program is intended for mature, fully employed workers who want to upgrade their careers . . . and who can successfully study electronics and supporting subjects through

### **INDEPENDENT STUDY, AT HOME**

Free Details Available from:

**Grantham College of Engineering**  
2500 South La Cienega Blvd.  
P. O. Box 35499  
Los Angeles, CA 90035

### **Independent Home Study Can Prepare You**

Study materials, carefully written by the Grantham staff for independent study at home, are supplied by the College, and your technical questions related to those materials and the lesson tests are promptly answered by the Grantham teaching staff.

### **Recognition and Quality Assurance**

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council.

We are located at 2500 S. LaCienega Blvd., Los Angeles, California, but for faster response please use our mailing address: P. O. Box 35499, Los Angeles, CA 90035.

**Grantham College of Engineering** 7-84  
P. O. Box 35499, Los Angeles, CA 90035

Please mail me your free catalog which explains your B.S. Degree independent-study program.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



# NEW!

## Regency® Scanners

**Communications Electronics™**, the world's largest distributor of radio scanners, introduces new models with special savings on all radio scanners. Chances are the police, fire and weather emergencies you'll read about in tomorrow's paper are coming through on a scanner today.

We give you excellent service because CE distributes more scanners worldwide than *anyone* else. Our warehouse facilities are equipped to process thousands of scanner orders every week. We also export scanners to over 300 countries and military installations. Almost all items are in **stock for quick shipment**, so if you're a person who prefers fact to fantasy and who needs to know what's *really* happening around you, order your radio today from CE.

### NEW! Regency® MX5000-B

List price \$599.95/CE price \$379.00  
**Multi-Band, 20 Channel • No-crystal scanner**  
**Search • Lockout • Priority • AC/DC**  
**Selectable AM-FM modes • LCD display**  
**World's first continuous coverage scanner**  
Frequency range: 25-550 MHz, continuous coverage. Never before have so many features come in such a small package. The Regency MX5000 mobile or home scanner has continuous coverage from 25 to 550 MHz. That means you can hear CB, Television audio, FM-broadcast stations, all aircraft bands including military and the normal scanner bands, all on your choice of 20 programmable channels.

### NEW! Regency® MX3000-B

List price \$299.95/CE price \$181.00  
**6-Band, 30 Channel • No-crystal scanner**  
**Search • Lockout • Priority • AC/DC**  
Bands: 30-50, 144-174, 440-512 MHz.  
The Regency Touch MX3000 provides the ease of computer controlled, touch-entry programming in a compact-sized scanner for use at home or on the road. Enter your favorite public service frequencies by simply touching the numbered pressure pads. You'll even hear a "beep" tone that lets you know you've made contact.

In addition to scanning the programmed channels, the MX3000 has the ability to search through as much as an entire band for an active frequency. The MX3000 includes channel 1 priority, dual scan speeds, scan or search delay and a brightness switch for day or night operation.

### NEW! Regency® Z30-B

List price \$269.95/CE price \$169.00  
**6-Band, 30 Channel • No-crystal scanner**  
Bands: 30-50, 144-174, 440-512 MHz.  
Cover your choice of over 15,000 frequencies on 30 channels at the touch of your finger.

### JIL SX-200-B

CE price \$264.00/LOW LOW PRICE  
**8-Band, 16 Channel • No-crystal scanner**  
**Quartz Clock • AM/FM • AC/DC**  
Bands: 26-88, 108-180, 380-514 MHz.  
Tune Military, F.B.I., Space Satellites, Police & Fire, D.E.A., Defense Department, Aeronautical AM band, Aero Navigation Band, Fish & Game, Immigration, Paramedics, Amateur Radio, Justice Department, State Department, plus thousands of other radio frequencies.

### Regency® HX1000-B

Allow 60-120 days for delivery after receipt of order due to the high demand for this product.

List price \$329.95/CE price \$209.00  
**6-Band, 30 Channel • No Crystal scanner**  
**Search • Lockout • Priority • Scan delay**  
**Sidelit liquid crystal display • Digital Clock**  
Frequency range: 30-50, 144-174, 440-512 MHz.  
The new handheld Regency HX1000 scanner is fully keyboard programmable for the ultimate in versatility. You can scan up to 20 channels at the same time. When you activate the priority control, you automatically override all other calls to listen to your favorite frequency. The LCD display is even sidelit for night use. A die-cast aluminum chassis makes this the most rugged and durable hand-held scanner available. There is even a backup lithium battery to maintain memory for two years. Includes wall charger, carrying case, belt clip, flexible antenna and nicad battery. Reserve your Regency HX1000 now.

### Regency® R106-B

List price \$149.95/CE price \$92.00  
**5-Band, 10 Channel • Crystal scanner • AC/DC**  
Frequency range: 30-50, 146-174, 450-512 MHz.  
A versatile scanner, The Regency R-106 is built to provide maximum reception at home or on the road. Rugged cabinet protects the advanced design circuitry allowing you years of dependable listening.

### Regency® R1040-B

List price \$199.95/CE price \$121.00  
**6-Band, 10 Channel • Crystalless • AC only**  
Frequency range: 30-50, 144-174, 440-512 MHz.  
Now you can enjoy computerized scanner versatility at a price that's less than some crystal units. The Regency R1040 lets you in on all the action of police, fire, weather, and emergency calls. You'll even hear mobile telephones.

Programming the R1040 is easy. Merely touch the keyboard and enter any of over 15,000 frequencies on your choice of 10 channels.

### Regency® HX650-B

List price \$119.95/CE price \$79.00  
**5-Band, 6 Channel • Handheld crystal scanner**  
Bands: 30-50, 146-174, 450-512 MHz.  
Now you can tune in any emergency around town, from wherever you are, the second it happens. Advanced circuitry gives you the world's smallest scanner. Our low CE price includes battery charger/A.C. adapter.

### NEW! Regency® HX-650P-B

List Price \$179.95/CE price \$104.00  
Now, Communications Electronics offers a special packaged price on the Regency HX-650 scanner and the following items for only \$104.00. You get the Regency HX-650 scanner, a set of 4 AAA ni-cad batteries, the MA-506 carrying case, six crystal certificates, AC adapter/charger and flexible rubber antenna for only \$104.00 per package plus \$10.00 shipping/handling. To order this special package, use CE special order number HX-650P-B.

### QUANTITY DISCOUNTS AVAILABLE

Order two scanners at the same time and deduct 1%, for three scanners deduct 2%, four scanners deduct 3%, five scanners deduct 4% and six or more scanners purchased at the same time earns you a 5% discount off our super low single unit price.

### Regency® Z10-B

List price \$229.95/CE price \$149.00  
**6-Band, 10 Channel • No-crystal scanner**  
**Priority control • Search/Scan • AC/DC**  
Bands: 30-50, 140-174, 440-512 MHz.  
Cover your choice of over 15,000 frequencies on 10 channels at the touch of your finger.

### OTHER RADIOS & ACCESSORIES

Regency® C403-B Scanner	\$59.00
Panasonic RF-9-B Shortwave receiver	\$84.00
Panasonic RF-B50-B Shortwave receiver	\$129.00
Panasonic RF-799-B Shortwave receiver	\$219.00
Panasonic RF-2600-B Shortwave receiver	\$199.00
Panasonic RF-3100-B Shortwave receiver	\$279.00
Panasonic RF-B300-B Shortwave receiver	\$195.00
Panasonic RF-B600-B Shortwave receiver	\$429.00
Panasonic RF-B300-B Shortwave receiver	\$539.00
Bearcat® 210XL-B Scanner	\$219.00
Bearcat® 5/6-B Scanner	\$119.00
Bearcat® DX1000-B Shortwave Receiver	\$489.00
JIL SX-400-B Scanner	\$539.00
JIL PS-B 12 V DC Power Supply for JIL SX-400	\$39.00
SP55-B Carrying case for Bearcat Five-Six	\$15.00
MA-506-B Carrying case for Regency HX650	\$15.00
TSG-B "Top Secret" Registry of U.S. Govt. Freq.	\$15.00
RRF-B Railroad Frequency Directory	\$10.00
ESD-B Energy Services Directory	\$10.00
ASD-B Frequency Directory for Aircraft Band	\$10.00
SRF-B Survival Radio Frequency Directory	\$10.00
TIC-B Techniques for Intercept Communications	\$12.00
CIE-B Covert Intelligence, Elect. Eavesdropping	\$12.00
FB-E-B Frequency Directory for Eastern U.S.A.	\$12.00
B-4-B 1.2 V AAA Ni-Cad batteries (set of four)	\$9.00
B-6-B 1.2 V AA Ni-Cad batteries (set of four)	\$12.00
A-135C-B Crystal certificate	\$3.00
A60-B Magnet mount mobile antenna	\$35.00
A70-B Base station antenna	\$35.00
Add \$3.00 shipping for all accessories ordered at the same time.	
Add \$12.00 per shortwave receiver for U.P.S. shipping.	
Add \$3.00 shipping per scanner antenna.	

### BUY WITH CONFIDENCE

To **get the fastest delivery from CE** of any scanner, send or phone your order directly to our Scanner Distribution Center. Be sure to calculate your price using the CE prices in this ad. Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on backorder automatically unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. Ann Arbor, Michigan. No COD's. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. Non-certified checks require bank clearance.

**Mail orders to:** Communications Electronics, Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add \$7.00 per scanner for U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are three times continental U.S. rates. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-521-4414. In Canada, order toll-free by calling 800-265-4828. WUI Telex CE anytime, dial 671-0155. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today.

Scanner Distribution Center™ and CE logos are trademarks of Communications Electronics.


† Bearcat is a federally registered trademark of Electra Company, a Division of Masco Corporation of Indiana.  
‡ Regency is a federally registered trademark of Regency Electronics Inc. AD #060184-B

Copyright ©1984 Communications Electronics

**Order Toll Free... call  
1-800-521-4414**

**COMMUNICATIONS  
ELECTRONICS™**  
**Consumer Products Division**

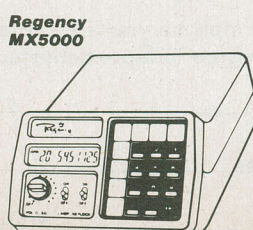818 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.  
Call TOLL-FREE 800-521-4414 or outside U.S.A. 313-973-8888





# Radio- Electronics

THE MAGAZINE FOR NEW  
IDEAS IN ELECTRONICS

Electronics publishers since 1908

JULY 1984 Vol. 55 No. 7

## BUILD THIS

- 43 **ENERGY MISER FOR AIR CONDITIONERS**  
You don't have to make yourself uncomfortable to save money on your air-conditioning bills. **Bill Owen**
- 61 **CLAMP-ON DC AMMETER**  
This ammeter eliminates the undesirable side effects of measuring DC current; it uses Hall-effect transducers and a clamp-on probe. **Hardin Stratman**

## TECHNOLOGY

- 4 **VIDEO ELECTRONICS**  
Tomorrow's news and technology in this quickly changing industry. **David Lachenbruch**
- 12 **SATELLITE/TELETEXT NEWS**  
The latest happenings in communications technology. **Gary H. Arlen**

## CIRCUITS AND COMPONENTS

- 51 **HOW TO REPAIR PC BOARDS**  
If you've ever had a PC board that you thought was ruined forever—it probably wasn't. **Robert Grossblatt**
- 54 **DESIGNING WITH LINEAR IC'S**  
Part 3. A look at the noninverting follower and some typical op-amp applications. **Joseph J. Carr**
- 65 **POWER-SUPPLY CIRCUITS**  
This article is chock full of practical power-supply circuits that you can put together now! **Ray Marston**
- 72 **HOBBY CORNER**  
Testing your telephone. **Earl "Doc" Savage, K4SDS**
- 74 **NEW IDEAS**  
Restoring tube-type auto radios.
- 76 **DESIGNER'S NOTEBOOK**  
Frequency multiplication. **Robert Grossblatt**

## VIDEO

- 47 **HOW TO TUNE YOUR MDS DOWNCONVERTER**  
You don't have to run up and down your roof with a soldering iron. **Lew G. Schuweiler**
- 69 **TROUBLESHOOTING THE TOUGH ONES**  
A look at how some TV-servicing problems that—although they took some time—were eventually solved. **Frank A. Salerno**
- 78 **SERVICE CLINIC**  
Electrostatic discharge and its problems. **Jack Darr**
- 79 **SERVICE QUESTIONS**  
Radio-Electronics' Service Editor solves readers' problems.

## COMPUTERS

- 57 **INTERFACING THE ZX81**  
The ZX81 (or Timex Sinclair 1000) computer can be turned into a very powerful machine. **Neil Bungard**

Following page 72

- COMPUTER DIGEST**  
A look at the new Sinclair QL, printing buffers, personal communications, and lots more!

## EQUIPMENT REPORTS


- 26 **Ungar Electronic Soldering System 9000**
- 33 **Sabre Electronics Calc-U-Dial Automatic Dialer**

## DEPARTMENTS

- |                                  |                  |
|----------------------------------|------------------|
| 12 Advertising and Sales Offices | 82 Market Center |
| 104 Advertising Index            | 37 New Products  |
| 105 Free Information Card        | 6 What's News    |
| 14 Letters                       |                  |
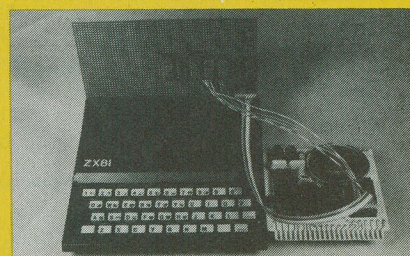
## ON THE COVER

You can save money on your air-conditioning bills and stay comfortable at the same time. No, it's not magic—it's what's known as time cycling. The energy miser lets your air conditioner operate more efficiently than it does when it is controlled by just a thermostat. Best of all, you can build the device just in time for the hot weather! The story begins on page 43.



THE TIMEX SINCLAIR 1000 or ZX81 has been described as being worse than a toy. Well, it doesn't have to be. You can put your ZX81 to work as a control computer with as many features as your imagination permits. This month, interfacing basics are discussed, and an interface circuit is presented. The story begins on page 57.

## COMING NEXT MONTH On Sale May 22

- **Electronics And The Heart.** The heart may have more in common with electronic devices than you think.
- **An Infrared Transmitter/Receiver.** How many uses for one can you come up with?
- **ComputerDigest.** Another tear-out edition of our magazine-within-a-magazine.
- **And lots more!**

**Radio-Electronics, (ISSN 0033-7862)** Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$14.97, Canada, \$17.97. Other countries, \$22.47 (cash orders only, payable in U.S.A. currency). Single copies \$1.75. © 1984 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**POSTMASTER:** Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

JULY 1984



# VIDEO ELECTRONICS

DAVID LACHENBRUCH  
CONTRIBUTING EDITOR

## RCA PULLS THE PLUG

RCA's noble experiment with the CED (Capacitance Electronic Disc) videodisc system came to a sudden end after three years of marketing and \$580,000,000 of losses when the corporation's board decided to discontinue manufacturing SelectaVision players. The company will continue to manufacture discs for existing players for at least three years, or as long as there is demand, according to RCA. The videodisc system was a victim of the unexpected success of the VCR, of which RCA is the leading brand in the United States. RCA said the unanticipated demand for VCR's, the constantly dropping prices, and the widespread availability of low-cost program cassette rentals spelled the death of the videodisc system.

RCA had reduced the price of the basic player model to \$199.95 and introduced stereo and interactive models at higher prices, but only the cheapest model sold in any volume. RCA said it would continue to sell the remaining players this year, and it expects a total of 700,000 to be in use by year's end. The competing LaserVision optical system, with players being sold by Pioneer, Magnavox, and Sylvania, continues on the market.

## THE VCR WINNERS

Once again in 1983, RCA was the most popular VCR brand in the United States, according to a survey by the trade newsletter *Television Digest*. However, RCA won by a slimmer margin this time, with an estimated 16% of 1983's sales, while Panasonic, the No. 2 brand, had 15%. In 1982, RCA held an estimated 22% of the market, to Panasonic's 17.75%. Sony was the No. 3 brand with 7%, followed by General Electric with 5.5%, and Fisher and Sanyo with 5% each.

The two American brands owned by Matsushita Electric, Panasonic and Quasar, accounted a total of 20.6% of all VCR's sold in the United States last year, and taken together they would easily come out in first place. Other brand groupings: North American Philips brands (Magnavox, Sylvania, and Philco) had a total of more than 7.5% of the market, while Sanyo's two brands (Sanyo and Fisher) totaled 10%.

Because total VCR sales in 1983 were more than double those of 1982 (4,091,000 vs. 2,035,000), virtually every brand ended up with greater sales than the year before—even those brands which lost some market share (such as Zenith, which fell from 6% to 2.6% when it temporarily dropped out of the market in preparation for its 1984 switch to VHS from Beta). According to the survey, about 19% of the VCR's sold in the U.S. last year were in the Beta format, a decline from 26% in 1982.

## BIG SCREEN, BIG PROSPECTS

Some 143,500 giant-screen projection TV sets were sold in 1983, up from 117,000 in 1982, and in the first quarter of 1984 sales were running about 14% ahead of 1983's pace. U.S. Precision Lens Co., which makes lenses for most of them, sees American homes adding TV projectors in even greater numbers this year, forecasting sales of about 178,000.


The company predicts that 75% of all projection sets sold this year will be rear-projection systems (one-piece types in which the picture is thrown from the inside of the set onto a translucent front-mounted screen) as opposed to 60% last year and 29% in 1981. It sees these advances in projection this year: Improved lenses at lower cost; more compact cabinets; better projection tubes with widespread use of liquid cooling for higher brightness; smaller spot size for better resolution; better phosphors; better screens at lower cost; more sets with optical coupling of tube to lens for higher contrast, and a new generation of chassis designed specifically for projection.

U.S. Precision also spots a trend toward somewhat smaller screen sizes in projection TV. Since a rear-projection set resembles a conventional TV, but with a bigger picture, the company quotes its manufacturing customers as feeling that "projection should more properly be considered an extension of conventional color-TV lines. They argue that we should forget about calling it projection, instead concentrating only on larger screen size."

Meanwhile, some set manufacturers' labs are working on new generations of projection television designed to be used with high-definition widescreen TV of the future. Already in sight, according to inside reports, are projection systems with better contrast, resolution, and brightness than conventional direct-view sets.

R-E



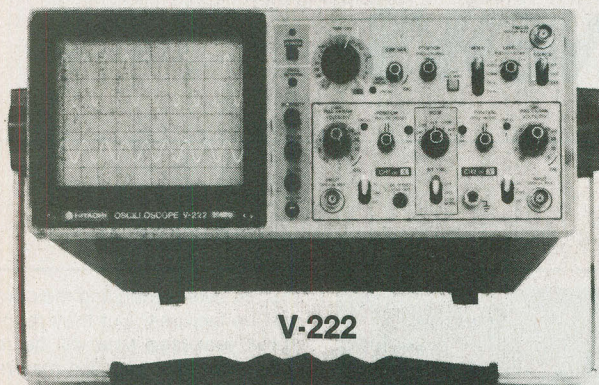

V-222

## HI-PERFORMANCE PORTABLE OSCILLOSCOPES

ALL FEATURE 6" RECTANGULAR CRT  
Full 2 year parts & labor warranty.



**\$599<sup>95</sup>**  
V-422


DC to 40 MHz,  
1mV/div, dual-trace,  
DC offset function

**\$499<sup>95</sup>**  
V-222

DC to 20 MHz,  
1mV/div, dual-trace,  
DC off. func., Alt.  
magnify function

**\$439<sup>95</sup>**  
V-212

DC to 20 MHz,  
1mV/div, dual-trace

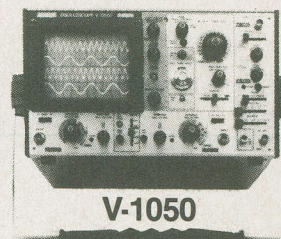

V-1050


**\$1,249<sup>95</sup>**

V-1050F  
100 MHz Quad Trace  
w/delay sweep

**\$939<sup>95</sup>**  
V-650F

60 MHz Dual Trace  
w/delay sweep

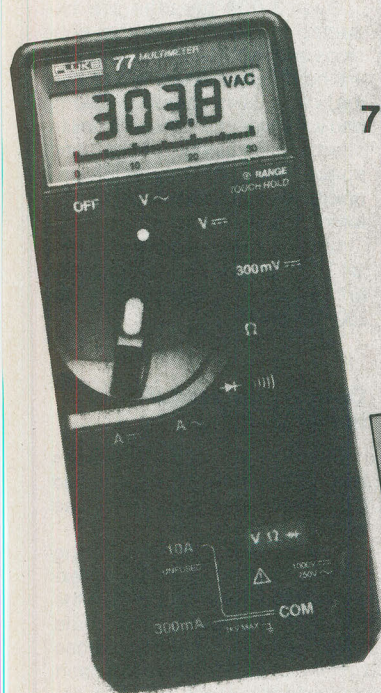PRICE DOES NOT INCLUDE  
PROBES. PROBES \$50. A PAIR  
WHEN PURCHASED WITH SCOPE.  
\$15 SHIPPING WITHIN  
CONTINENTAL U.S.



- 77 • 0.3% Accuracy  
• Manual or  
Autorange  
• 10A + mA Range  
• Beeper  
• "Touch-Hold"  
Function

**\$129<sup>00</sup>**

WE CARRY A FULL  
LINE OF FLUKE  
MULTI-METERS.  
IN STOCK NOW

- 0.5% Accuracy  
• Manual or  
Autorange  
• 10A + 300 mA  
Range  
• Beeper




75

**\$99<sup>00</sup>**

- 0.7% Accuracy  
• Autorange Only  
• 10 Amp Only

**\$85<sup>00</sup>**

73

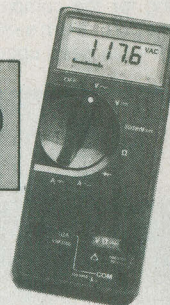

## FLUKE 70 SERIES MULTIMETERS

• Analog Display • Rotary Knob • Volts AC &  
DC • Resistance to • 32 MΩ • 10 Amps • Diode  
Test • 3200 Counts • Fast Autoranging • Function  
Annunciators in Display • Power-Up Self Test  
• 2000+ Hour Battery Life w/ Power Down "Sleep  
Mode" • New Test Leads • VDE & UL Approval



TOLL FREE HOT LINE  
**800-223-0474**

212-730-7030

26 WEST 46th STREET, NEW YORK, N.Y. 10036

THE TEST EQUIPMENT SPECIALISTS

**ADVANCE  
ELECTRONICS**



# WHAT'S NEWS

## EIA sets new standards for silicon digital IC's

The Engineering Department of the Electronic Industries Association has established JEDEC Standard No. 7, setting industry specifications for three series of new high-speed silicon-gate digital IC's.

The 54/74HC series includes buffered CMOS logic devices with the primary characteristic of  $V_{IL}$  (logical low-input voltage) and  $V_{IH}$  (logical high input voltage) ratings for good noise immunity in CMOS system designs. The 54/74HCU series includes a limited number of unbuffered (1 active logic circuit) inverters or gates where  $V_{IL}$  and  $V_{IH}$  ratings are less than those of the 'HC series. The third series is designated 54/74HCT, having  $V_{IL}$  and  $V_{IH}$  ratings of 0.8- and 2-volts respectively for direct interfacing with TTL logic IC's.

## Computer to interface home student, teacher

A new home-study system, in which student and teacher can be in direct contact, was described to Chicago security analysts by David Bright of the National Education Corp. Mr. Bright reported that the company's computer bank in Scranton, PA—which now handles testing for the company's 60,000 domestic home-study students—has been upgraded to ac-

cept on-line computer interfaces.

The new *EdNet* system will be offered to owners of IBM, Apple, Radio Shack, Commodore and Timex computers. The new system, Bright said, will permit independent home students to not only take their testing by computer, but to interface directly with instructional specialists via their home or office computers as well.

## Dr. Maiman member of Inventors Hall of Fame

Dr. Theodore H. Maiman, pioneer in laser research, was inducted into the National Inventors Hall of Fame at the 12th Inventors' Day Expo in Arlington, VA. He was honored for the invention of the ruby laser, the world's first operating laser. The first laser action occurred on May 15, 1960, at the Hughes Research Labs, Malibu, CA.

Dr. Maiman has been elected to both the National Academy of Sciences and the National Academy of Engineers. Among his many awards is the American Physical Society Oliver E. Buckley Prize for "The Most Important Contribution to Solid-State Physics in the Prior Five Years."

The National Inventors Hall of Fame is located in the United States Patent Office in Arlington, VA, and is dedicated to the persons "who conceived the great technological advances which this na-



**THEODORE H. MAIMAN LOOKS ON** as William Weigel, president of the National Inventors Hall of Fame Foundation, unveils a display honoring him. The display, which includes a replica of the original laser, will be permanently on exhibit in the lobby of the U.S. Patent Office.

tion fosters through its patent system."

The year's other inductees were William M. Burton, for an invention in the refining of gasoline; Wallace H. Carrothers, inventor of nylon, and Philo T. Farnsworth, inventor of the first all-electronic television system.

## Japan industry faces semiconductor shortage

Soaring production of VCR's, personal computers, automated office equipment, and other electronics products is hobbling the Japanese electronics industry, according to the influential Japanese newspaper *Yomiuri Shimbun*. At the end of 1983, Japan's largest semiconductor maker, NEC, admitted that "we can supply only about 70 percent of the demand."

Projected production figures are being cut back by some manufacturers. A Sony representative states: "VTR makers are unable to produce as many units as planned, because of the shortage of certain types of semiconductors." A Hitachi official said: "We cannot manufacture as many personal computers as we had planned."

Responding to the situation, NEC, Hitachi, Fujitsu, Toshiba, and other manufacturers are operating 24 hours a day, seven days a week,

and are even expanding their production facilities. But they report that a year lead time will be required, and that supplies may remain tight through 1984.

## New Orleans will host satellite conference

The sixth annual Satellite Communications Users Conference (SCUC) will be held at the Louisiana Superdome, New Orleans, August 28–30, 1984. Sponsored by the international trade journal *Satellite Communications*, it is the world's largest commercial satellite-communications gathering.

Over 3,000 persons are expected to attend the panel sessions and exhibits. Panel sessions will be directed toward broadcasting, cable, and corporate users, and will cover international satellite services, regulatory policies, and space law. The newest technological advances are being featured by 120 exhibitors.


Additional information on SCUC '84 may be obtained from Kathy Kriner, convention manager, at 303-694-1522.

## Optical print reader is held in hand

Oberon International, a London firm, has introduced a hand-held character reader suitable for use with a microcomputer.

Former character-recognizing devices have been extremely expensive and were restricted in the types of characters they could read. Particular problems arose with the operation of the transport and scanning heads. The new device uses manual instead of automatic operation to minimize or eliminate those problems.

The user of an Omni-Reader passes a light-sensitive linear array across a line of type, using a built-in ruler for accurate alignment. The light-sensitive element picks up and stores a series of vertical slices along the line of characters. Those are analyzed by a microprocessor, interpreted, and passed to the computer. Most of the standard fonts can be recognized, and some non-standard fonts can be taught to the software.

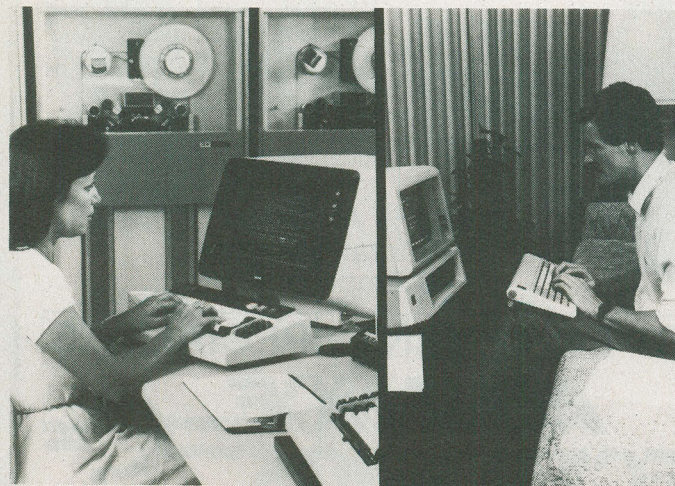


**A NEW ERA IN HOME STUDY?** Instructor specialist (at left) handles queries from the student at right in his home, via the computer link, which supports owners of most of the popular personal computers.


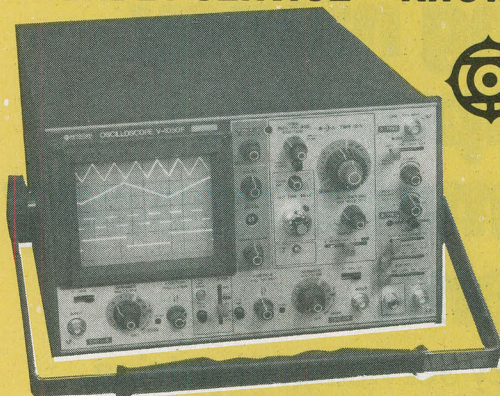
# The West Coast Alternative!


FRIENDLY SERVICE — KNOWLEDGEABLE AND COURTEOUS SALES PEOPLE



**HITACHI**  
Hitachi Denshi, Ltd.

**2 YEAR  
WARRANTY!!**

**PROBES  
INCLUDED!**

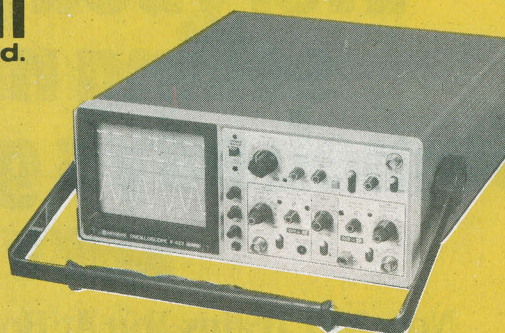

**DELAYED SWEEP  
w/TRIGGER VIEW**  
100MHz 60MHz

**3rd & 4th TRACE**  
RGHITV1050F List Price: \$1595.00

**\$1279**

**3rd TRACE**  
RGHITV650F List Price: \$1195.00

**\$985**

**NEW! LOW PROFILE  
DUAL CHANNEL**  
40MHz 20MHz

**DUAL TRACE**  
RGHITV422 List Price: \$895.00

**\$649**

**DUAL TRACE**  
RGHITV222 List Price: \$695.00

**\$545**




## DIGITAL MULTIMETERS SERIES 70 Autoranging

**3 1/3 Digit With Analog Bar Graph  
3 YEAR WARRANTY!**

- Full 3200 count instead of the normal 2000
- ULTRA-Fast analog bar graph
- Beeper included in the 75 & 77
- True touch and hold on the 77

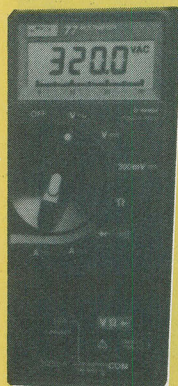
RGFLU73 .7% accuracy, **\$85.00**  
RGFLU75 .5% accuracy **\$99.00**  
RGFLU77 .3% accuracy **\$129.00**  
RGFLUC70 Custom Holster (included w/FLU77) **\$ 9.00**  
RGFLUC71 Soft Vinyl Case **\$ 9.00**



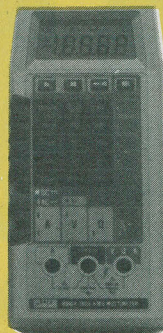
## 8060 SERIES 4 1/2 Digit .05% DMM

- True RMS
- Relative reference and continuity test
- dBm range (8060 only)
- .01 to 200 KHz frequency range (8060 only)
- Conductance range
- One Year Warranty!

RGFLU8080A w/Freq. counter **\$349.00**  
RGFLU8082A 4 1/2 Digit DMM **\$279.00**  
RGFLUA81 115V AC adaptor/Battery Eliminator **\$20.00**  
RGFLU80510 10 A current shunt **\$ 30.00**  
RGFLUC90 Vinyl carrying case **\$ 10.00**



DYNASCAN  
CORPORATION

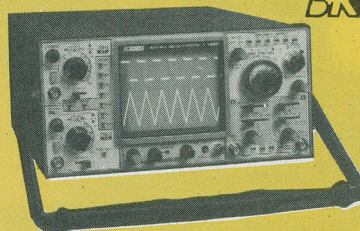

### Oscilloscopes — Probes Included

Part Number	Description	List Price	OUR PRICE
RGBKP1590P	100 MHz Eight Trace Scope	\$1995.00	<b>\$1645.00</b>
RGBKP1570P	80 MHz Quad Input Scope	\$1395.00	<b>\$1145.00</b>
RGBKP1560P	60 MHz Triple Trace Scope	\$1150.00	<b>\$1045.00</b>
RGBKP1540P	40 MHz Dual Trace Scope	\$ 950.00	<b>\$ 795.00</b>
RGBKP1522P	20 MHz Dual Trace Scope	\$ 695.00	<b>\$ 575.00</b>


### Signal & Pulse Generators:

RGBKP3010	1 MHz Function Generator	\$239.00	<b>\$189.95</b>
RGBKP3015	200 KHz Sweep/Function Generator	\$289.00	<b>\$239.00</b>
RGBKP3020	2 MHz Sweep/Function with Pulse	\$399.00	<b>\$319.95</b>
RGBKP3025	5 MHz Sweep/Function Generator	\$475.00	<b>\$399.00</b>
RGBKP3030	5 MHz Sweep/Funct. Lin/Log Sweep	\$699.00	<b>\$595.00</b>
RGBKP3300	5 MHz Pulse w/Pulse Burst	\$399.00	<b>\$329.00</b>

### Frequency Counters:

RGBKP1805	80 MHz Frequency Counter	\$290.00	<b>\$229.00</b>
RGBKP1822	175 MHz Frequency Counter	\$450.00	<b>\$325.00</b>
RGBKP1851	520 MHz Frequency Counter	\$575.00	<b>\$479.00</b>
RGBKP1855	1.2 GHz Frequency Counter	\$750.00	<b>\$639.00</b>

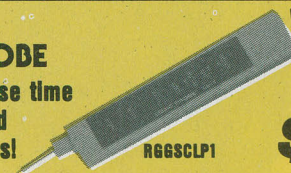**GSC LP-1  
LOGIC PROBE**  
50 nS Response time  
With Pulse and  
Memory Modes!



**WAS \$50.00  
NOW:  
\$19.95**

Terms: (Check, VISA, MasterCard or money order). Minimum order is \$15.00. CA residents add 6 1/2% sales tax.  
Prices valid through July 31, 1984.

Pre-Paid Orders — Shipping and Insurance (48 States):

\$0 to \$500 \$ 4.50  
\$500 to \$1000 \$10.00  
\$1000 and up \$15.00

Credit Card Orders Will Be Charged Appropriate Freight



**PRIORITY ONE ELECTRONICS**

9161 Deering Ave., Chatsworth, CA 91311-5887

**ORDER TOLL FREE (800) 423-5922 - CA, AK, HI CALL (818) 709-5111**

CIRCLE 57 ON FREE INFORMATION CARD



# **Everybody's making money selling microcomputers. Somebody's going to make money servicing them.**

**Now NRI Trains You At Home To Make Money Servicing, Repairing,  
and Programming Personal and Small Business Computers**





## Learn At Home to Service Any Computer

NRI can train you for this exciting, rewarding field. Train you at home to service not only microcomputers, but word processors and data terminals, too. Train you at your convenience, with clearly written "bite-size" lessons that you do evenings or weekends, without going to classes or quitting your present job.

Your training is built around the latest model of the world's most popular computer. It's the amazing TRS-80™ Model 4, now with disk drive and the capabilities and features to perform a host of personal and business functions. No other small computer has so much software available for it, no other is used and relied on by so many people. And it's yours to keep for personal and business use.

You get plenty of practical experience. Under NRI's carefully planned training, you even install a *disk drive*

as an alternative to the Model 4. The same technique for getting inside is enhanced by using the new NRI-developed Computer Access Card. Only NRI offers you a choice to fit your specific training needs.

## Become the Complete Computer Person

In addition to training in BASIC and advanced machine language, you gain hands-on experience in the operation and application of the latest computers for both business and personal jobs. You're trained to become the fully rounded, new breed of technician who can interface with the operational, programming, and service facets of all of today's computers. You're ready to take your place in the new electronic age.

## Other Opportunities

NRI has been giving ambitious people new electronic skills since 1914. Today's offerings also include TV/Audio/Video Systems servicing with training on our exclusive Heath/Zenith computer-programmable 25" diagonal color TV... Industrial Electronics, Design Technology... and other state-of-the-art courses.


Training now includes either the TRS-80 Model 4 Microcomputer with *Disk Drive* or the TRS-80 Color Computer with Computer Access Card; professional LCD multimeter; the NRI Discovery Lab; and hundreds of demonstrations and experiments.

Seems like every time you turn around, somebody comes along with a new computer for home or business use. And what's made it all possible is the amazing microprocessor, the tiny little chip that's a computer in itself.

Using this new technology, the industry is offering compact, affordable computers that handle things like payrolls, billing, inventory, and other jobs for business of every size... perform household functions including budgeting, environmental systems control, indexing recipes. And thousands of hobbyists are already owners, experimenting and developing their own programs.
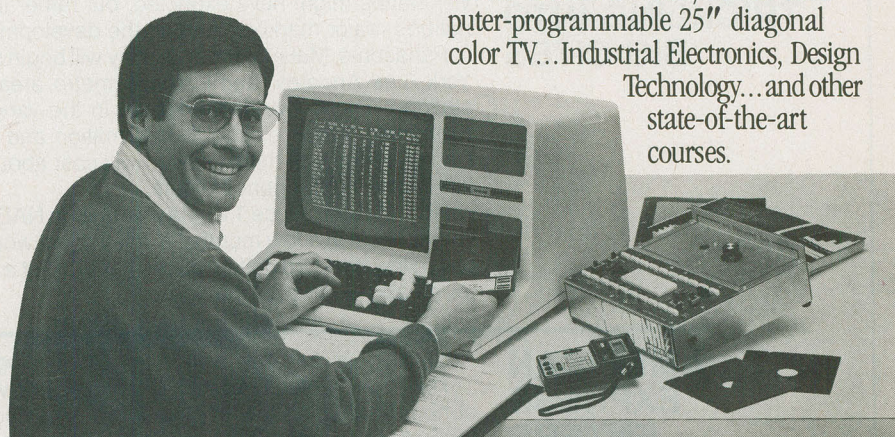
## Growing Demand for Computer Technicians

This is only one of the growth factors influencing the increasing opportunities for qualified computer technicians. The U.S. Department of Labor projects over a 600% increase in job openings for the decade; most of them *new* jobs created by the expanding world of the computer.



verifying its operation at each step. Using the NRI Discovery Lab® that also comes as part of your course, you build and study circuits ranging from the simplest to the most advanced. You analyze and troubleshoot using the professional 4-function LCD digital multimeter you keep to use later in your work. Then you use the lab and meter to actually access the interior of your computer... build special circuits and write programs to control them. You "see" your computer at work and demonstrate its power.

## Same Training Available With Color Computer

NRI offers you the opportunity to train with the TRS-80 Color Computer

## The Catalog is Free. The Training is Priceless.

Send the postage-paid card for our 104-page catalog showing all courses with equipment and complete lesson plans. There's no obligation other than to yourself. See how NRI can help you take advantage of the exciting job and earnings opportunities in the exploding field of microcomputers. If card has been removed, please write to us.



**NRI SCHOOLS**  
McGraw-Hill Continuing  
Education Center  
3939 Wisconsin Ave.  
Washington, DC 20016

(TRS-80 is a trademark of the Radio Shack division of Tandy Corp.)



# SATELLITE/TELETEXT NEWS

GARY ARLEN  
CONTRIBUTING EDITOR

## CBS, IBM, SEARS TEAM UP

In a move that could speed up nationwide development of videotext—and redefine the nature of videotext technology—Sears, CBS, and IBM have joined forces to develop a new service. The system will use home computers rather than dedicated videotex terminals and could include “true video” pictures rather than the conventional computer-graphic images of today’s videotext.

The Sears/CBS/IBM venture will take at least two years to put together, meaning that the first tests will take shape during 1986. All three companies have tested other videotex systems. By teaming up, they bring strong resources to the videotex business. Sears will concentrate on home banking and financial services, along with catalog merchandising. CBS will contribute software and news/information services, while IBM develops computer hardware, software, and networking facilities.

At the heart of the joint venture is a plan to deliver computer software and data-processing power into the home for education, personal productivity, and home management. The triumvirate will recruit other financial and information firms, computer companies, and organizations to offer a variety of services on the system, which doesn’t yet have a name.

## TELETEXT TRICKLING INTO BIG CITES

Teletext services are popping up around the U.S. this spring—not in the rush that some visionaries might have expected, but rather in a deliberate progression, arriving first in the nation’s major markets. Among the developments:

Panasonic, Matsushita, and Sony will begin selling NABTS-format teletext decoders in New York, Los Angeles, and Chicago metro areas, where CBS and NBC both own local TV stations. Those two networks are in the vanguard of promoting teletext material, and are coordinating their electronic information and ad packages with the decoder introductions. Decoders from all three makers will cost about \$900, at first, and will work only with certain late-model component-TV sets.

RCA may introduce TV sets with built-in NABTS teletext decoders as part of the 1985 model line, due out in a few months. Such a move would bring the price of teletext reception down to only a few hundred dollars above the price of a non-teletext set, and would eliminate the need for an add-on teletext decoder.

## AMERICAN EXPRESS ENTERS VIDEOTEX

American Express may have to modify its slogan to “Don’t *stay home* without us.”

The financial-services giant is plunging into videotex services in a big way, preparing to offer at-home shopping, travel-planning, bill-paying, and even insurance and stock brokerage through its subsidiaries. American Express is also repackaging material from its massive worldwide inventory of information—including restaurant reviews, flight schedules, travel tips and business ideas—to put online through various videotex and teletext systems around the U.S.

Working with hotel chains, restaurants, travel firms, and others who accept American Express cards and travelers checks, the company is also creating new systems to deliver travel, entertainment, and business services to videotex customers. In addition, monthly videotex service charges will be billed to your American Express card, just as you can now put your monthly MCI or AT&T long-distance phone bills on a monthly account.

All of American Express’ services are being assembled under the trade name “Advance.” The first services are now available to Viewtron videotex customers in south Florida, and later this year will go online to Time Mirror Videotex users in southern California.

## DBS DEVELOPMENTS

United Satellite Communications Inc., the first-comer in the DBS sweepstakes, began marketing its five-channel service in the Indianapolis area. USCI, which plans to eventually roll out its service nationally, has recruited Radio Shack as its major retail-sales agent—meaning that the DBS service will be sold through Radio Shack stores when the system is offered in other parts of the country. At its start-up, USCI offered two channels of movies, one channel of ESPN all-sports programming, plus two channels that carried a mixture of text news-reports, children’s programming, music videos, an electronic program-guide, and other material. USCI, now using a Canadian Ku-band bird (14/12 GHz), is not currently scrambling its signal, although it plans to introduce scrambling later.



R-E




1 mV/DIV.  
VERTICAL  
SENSITIVITY

**1 mV**  
VERTICAL  
SENSITIVITY

V-MODE  
DISPLAYS  
UNRELATED  
SIGNALS

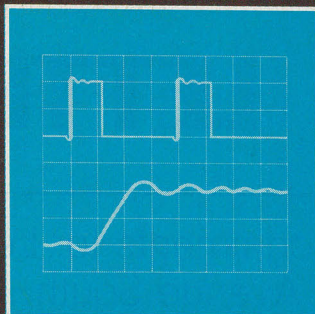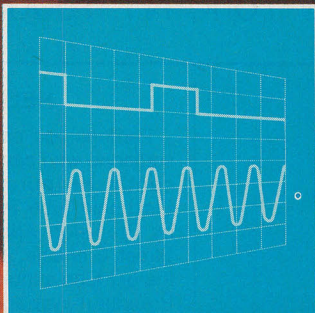

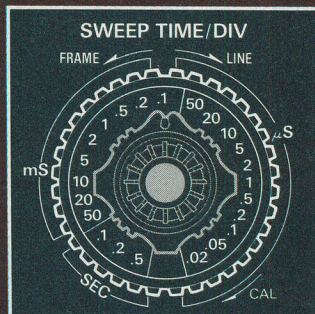
DELAYED  
SWEEP  
WITH TRACE  
SEPARATION



HIGH ACCELERATION  
VOLTAGE  
DUAL TRACE ON 1580  
TRIPLE TRACE ON 1560  
DUAL TRACE ON 1540  
X10 SWEEP  
MAGNIFICATION

DUAL  
TIME BASE

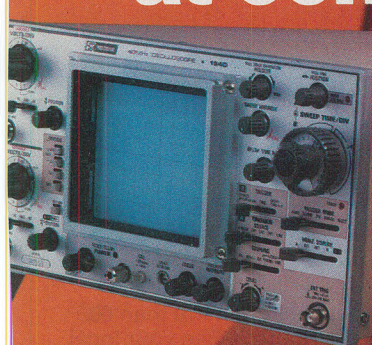**Three new B&K-PRECISION scopes  
loaded with features  
at competition-busting prices.**



60MHz 1560  
\$1,150



100MHz 1580 \$1,595



40MHz 1540  
\$950

FOR MORE INFORMATION, see the  
latest B&K-PRECISION catalog. For  
your free copy, contact your local  
distributor or B&K-PRECISION.

**B&K PRECISION** DYNASCAN  
CORPORATION

6460 West Cortland Street • Chicago, Illinois 60635 • 312/889-9087

International Sales, 6400 W. Cortland St., Chicago, Illinois 60635  
• Canadian Sales, Atlas Electronics, Ontario  
South and Central American Sales, Empire Exporters, Plainview, NY 11803

CIRCLE 16 ON FREE INFORMATION CARD




# LETTERS

Address your comments to: Letters, **Radio-Electronics**,  
200 Park Avenue South, New York, NY 10003
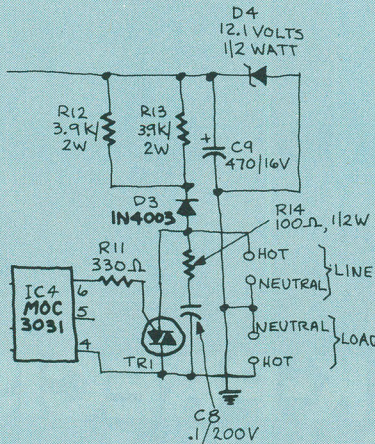
## OOOOOPS!

A potentially dangerous error worked its way into the proximity power-switch schematic presented in the "New Ideas" column in the May 1984 issue of **Radio-Electronics**. In the lower right-hand corner of Fig. 1, the neutral line is connected directly to the load's hot line, short-circuiting the output. The neutral line should *not* be connected to the hot line. Instead, it should be connected to the circuit ground. (See figure to right.)—Editor




## HELP WANTED

Perhaps you can help us or direct us to someone who can. Our problem is this: Recently we purchased a Model 10-40 Electronic Tube Tester. It was manufactured by Precision Apparatus Co., 70-31 84th Street, Glendale, 27 L.I., New York. On one of the old tube supplements it is indicated that Precision Apparatus is a subsidiary of Pacotronics Inc., same address.

The instrument seems to be in fine condition, but the last Tube Supplementary Booklet is dated 1964. What we need are updated Tube Supplements. I wrote to the above named company about eight weeks ago, and as of this writing, have received no response from this.

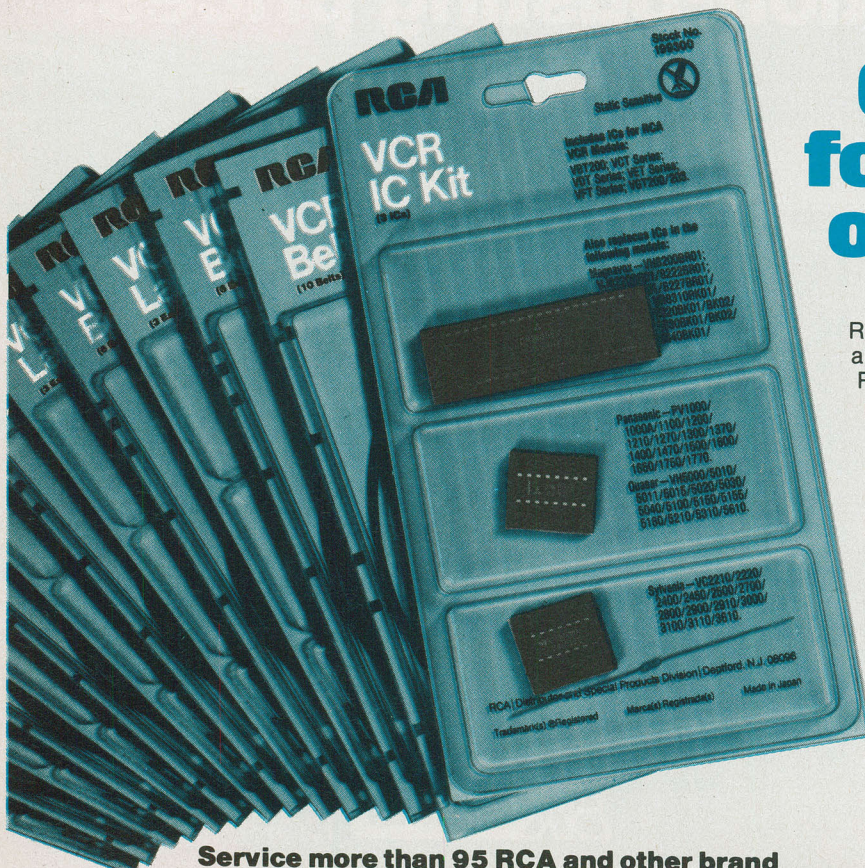If you could offer us any information on this  
*continued on page 16*



## One source for thousands of VCR parts.

RCA VCR parts are available from more than 600 authorized RCA parts distributors. See your local RCA distributor for RCA's new VCR parts kits — they're easy to use and reuse. Each package has a handy slide top — and features detailed cross-references to other manufacturers' model numbers and stock numbers.

One more thing. Kit prices are lower than the total cost of the individual parts. So see your RCA distributor today. Also ask for a copy of the VCR Parts Cross Reference of more than 8000 VCR parts (Form 1F6627) and VCR Tool Catalog (Form 1F6857). Or write: RCA Distributor and Special Products Division, 2000 Clements Bridge Road, Deptford, NJ 08096.

**Service more than 95 RCA and other brand models with these VCR Parts Kits:**


199094 and 199095 Belt Kits, 199096 Lamp Kit, 199097 Fuse Kit, 199300 IC Kit

# RCA VCR Parts


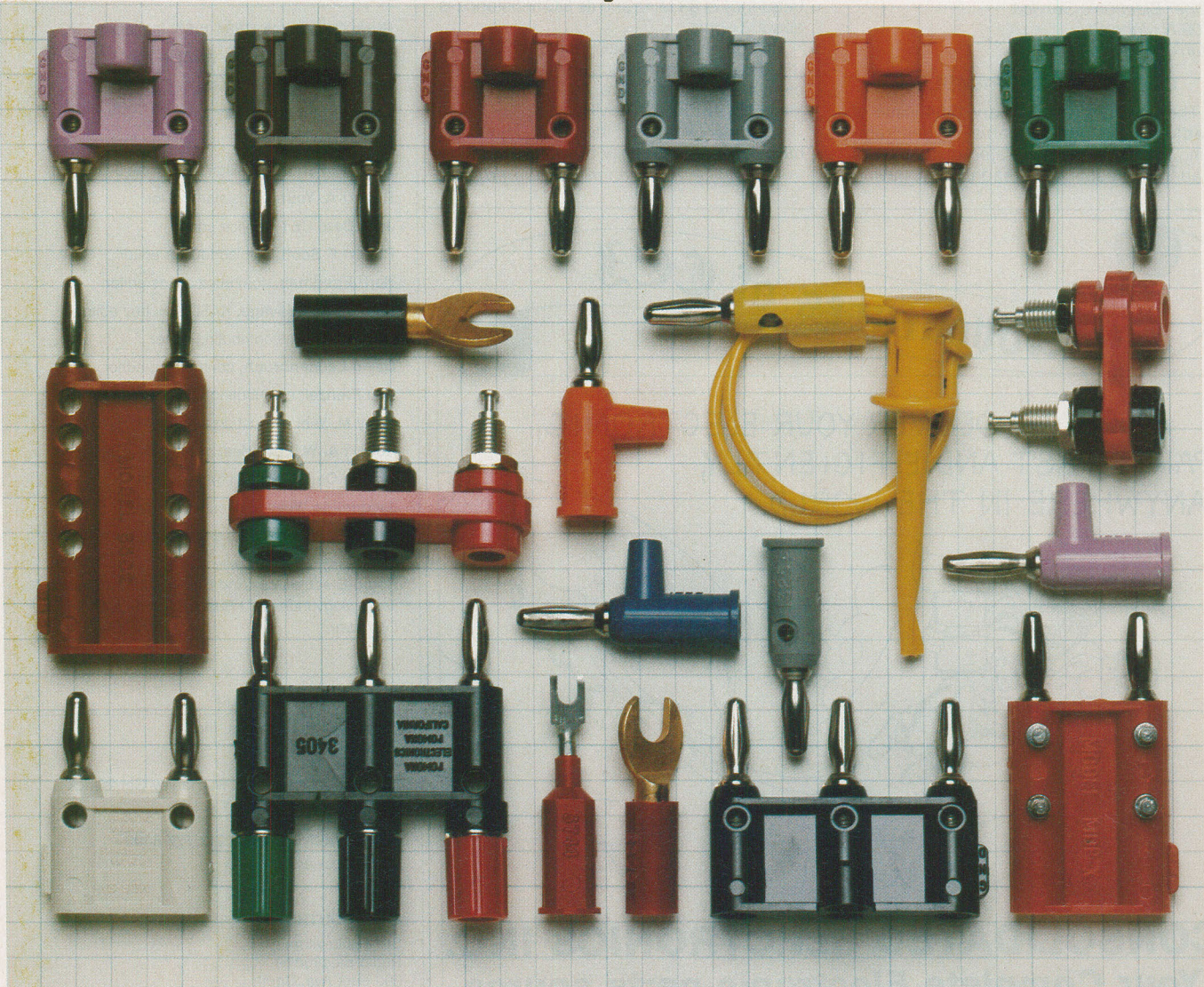
# THE POMONA PROMISE

Our constant goal is to provide the design engineer with the best banana plugs and jacks made in this country. Or anywhere.



And we've been doing it for a long time. Since 1951 in fact.

That's when we promised there wouldn't be anyone in the world who could design and produce banana plugs and jacks the way we could.

The world agreed.

Naturally, as the years have passed, we've improved upon our original designs. So much so that today, our banana plugs and jacks are out there alone. In their own class.

The same can be said for every other product we design and

produce. And each and every one of them is trusted by the professionals of the electronics industry.

At ITT Pomona Electronics, we know there is no such thing as standing pat. We also know that your needs change and your expectations become greater as the demands become more severe. To this end we will continue to create a better way. A better product.

That's a promise.

All of our products are described and illustrated in our General Catalog, and it's free. Just call (714) 623-3463 or 623-6751.

TWX 910-581-3822. Write to us at ITT Pomona Electronics, a Division of ITT Corporation, 1500 E. Ninth St., Pomona, CA 91766.

In Europe: ITT CANNON BELGIUM S.A./N.V. Rue Colonel Bourg Str. 105 Space A (B.3) 1140 Brussels, Belgium. Phone: 02-735-6094.

Our products are available through your favorite electronics parts distributor.

**ITT** Pomona Electronics

CIRCLE 72 ON FREE INFORMATION CARD



## LETTERS

*continued from page 14*

subject it would be deeply appreciated.

By the way, the serial number of the instrument is 1347, if that will be of any help.

MAL MILNER

Milner Electronic Service

1109 N. John St.

Frankfort, IN 46041

### CABLE-TV DESCRAMBLING

The article in the February 1984 issue of **Radio-Electronics** on cable-TV descrambling methods has generated quite a bit of reader interest. Many readers are having

trouble with the circuit because they cannot find certain parts or acceptable substitutes. That is partly our error, because we did not spell out some of the parts-specifications in the article. Let's take a look at some of the hard-to-find parts.

First of all, coil L1 has an inductance of  $12 \mu\text{H} \pm 10\%$ . It has a minimum Q of 30 measured at 2.52 MHz. Its typical self-resonant frequency is 33 MHz and its DC resistance is about 2 ohms.


Coil L2 has a nominal inductance of  $0.071 \mu\text{H}$ . It is made from  $3\frac{1}{2}$  turns of 0.6-mm diameter wire on a 6-mm core. Its unloaded Q is a minimum of 120 at 100 MHz.

The other two coils in the circuit, T1 and T2, have a center frequency of 10.7 MHz with a

*continued on page 22*
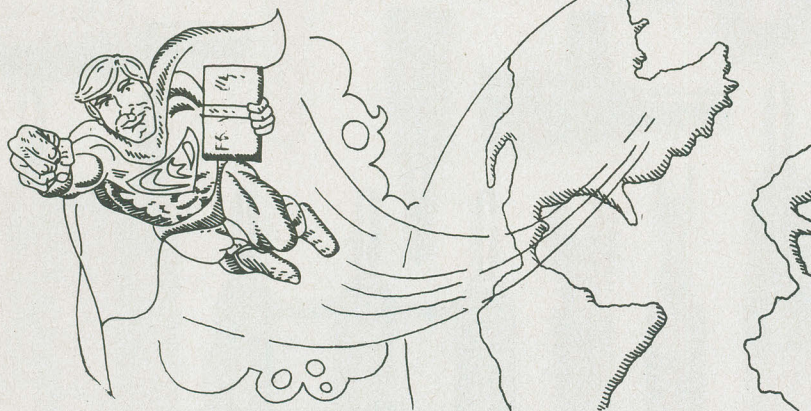
## Adventures of CEI

AT CEI, WE DELIVER YOUR ELECTRONIC PARTS FAST AND EFFICIENTLY, ANYWHERE IN THE WORLD.



**CONSOLIDATED ELECTRONICS INC.**  
Your Complete Electronic parts source  
705 WATERVLIET AVE., DAYTON OH 45420

TELEX : 288-229

CALL TOLL  
FREE TODAY!



FOR OUR  
CURRENT CATALOG

NATIONAL WATS LINE

1-800-543-3568

OHIO WATS LINE

1-800-762-3412

## Radio-Electronics

A  
**GERNSBACK**  
PUBLICATION

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief

Larry Steckler, CET, publisher

Arthur Kleiman, editor

Carl Laron, WB2SLR, associate editor

Brian C. Fenton, assistant technical editor

Robert A. Young, assistant editor

Jack Darr, CET, service editor

Robert F. Scott, semiconductor editor

Herb Friedman, communications editor

Earl "Doc" Savage, K4SDS, hobby editor

Gary H. Arlen, contributing editor

David Lachenbruch, contributing editor

Lou Frenzel, contributing editor

Ruby M. Yee, production manager

Robert A. W. Lowndes, production associate

Dianne Osias, production assistant

Jacqueline Weaver, circulation director

Arline R. Fishman, advertising coordinator

Cover photo by Robert Lewis

**Radio-Electronics** is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.

200 Park Ave. South

New York, NY 10003

Chairman of the Board, M. Harvey Gernsback

President: Larry Steckler

ADVERTISING SALES 212-777-6400

Larry Steckler  
Publisher

### EAST/SOUTHEAST

Stanley Levitan

Radio-Electronics

200 Park Ave. South

New York, NY 10003

212-777-6400

### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen

Radio-Electronics

540 Frontage Road—Suite 325

Northfield, Illinois 60093

312-446-1444

### PACIFIC COAST

Mountain States

Marvin Green

Radio-Electronics


15335 Morrison St., Suite 227,

Sherman Oaks, CA 91403

818-986-2001





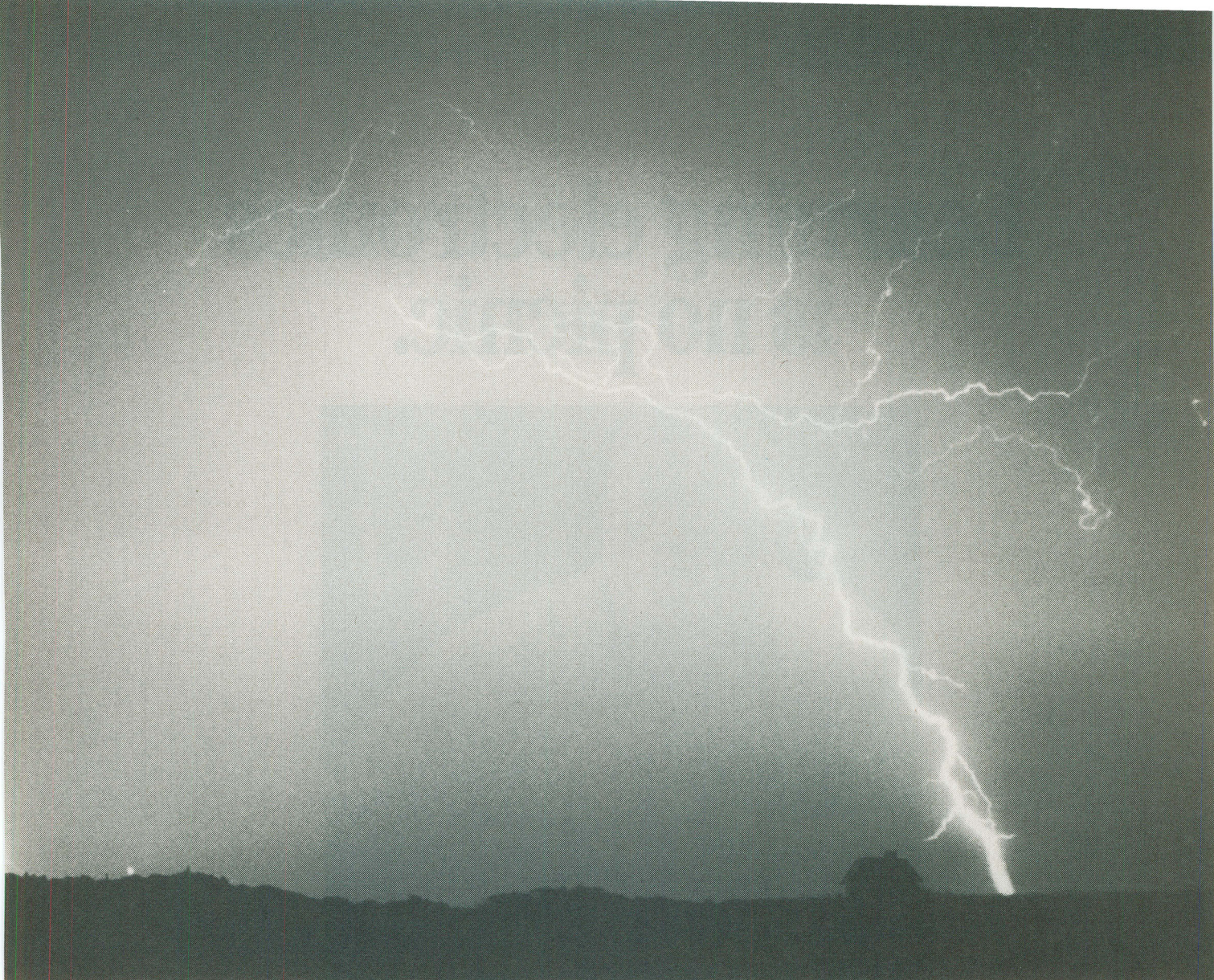

## People don't know the importance of 40% more surge protection until lightning strikes.

Compared to most other surge suppressors, Philips ECG Surge Suppressors handle 40% greater surge current. They tame 53% more surge energy. Each has a positive overload protector that automatically shuts off equipment in the rare event of a massive overload surge. And each clamps spikes to 24% lower voltage. Philips ECG delivers almost twice the protection at a competitive price.

A good thing to have when lightning strikes.

Sell maximum protection. Call Philips ECG today for the name of your nearest distributor: 1-800-225-8326 (in Massachusetts, 617-890-6107).

**If it's ECG<sup>®</sup>, it fits.  
And it works.**



*Philips ECG Surge Suppressors  
are available in 2- and 3-prong units.*


# PhilipsECG

*A North American Philips Company*

CIRCLE 32 ON FREE INFORMATION CARD



**Learning electronics  
is no picnic.**

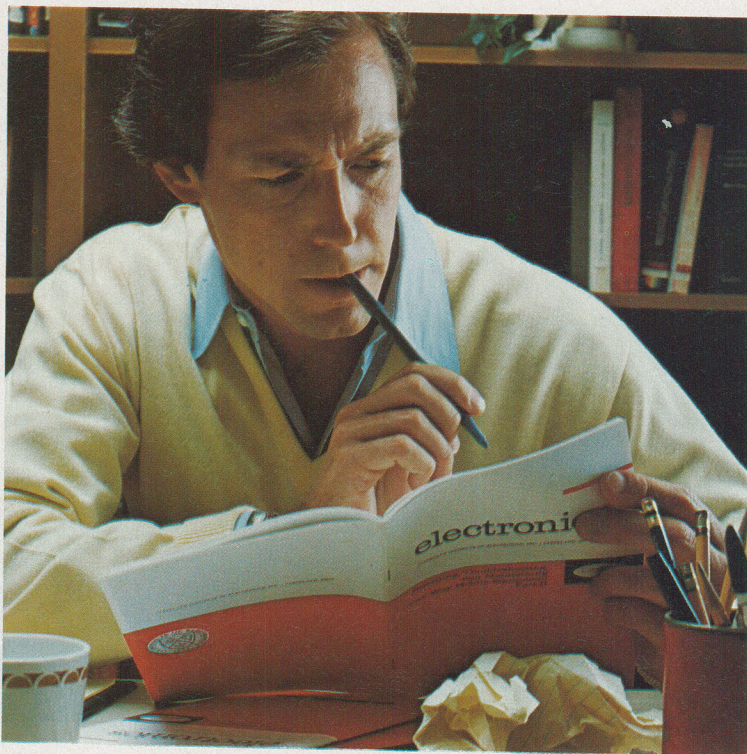

**At any level it takes  
work and a few  
sacrifices. But with  
CIE, it's worth it.**



Whoever said, "The best things in life are free," was writing a song, not living a life. Life is not just a bowl of cherries, and we all know it.

You fight for what you get. You get what you fight for. If you want a thorough, practical, working knowledge of electronics, come to CIE.

You can learn electronics by spending some hard-working time at home. Or, would you rather go bowling? Your success is up to you.

At CIE, you *earn* your diploma. It is not handed to you simply for putting in hours. But the hours you do put in will be on your schedule, not ours. You don't have to go to a classroom. The classroom comes to you.

### Why electronics training?

Today the world depends on technology. And the "brain" of technology is electronics. Every year, companies the world over are finding new ways to apply the wonders of electronics to control and program manufacturing, processing...even to create new leisure-time products and services. And the more electronics applications there are, the greater the need will be for trained technicians to keep sophisticated equipment finely tuned and operating efficiently. That means career opportunities in the eighties and beyond.

### Which CIE training fits you?

Beginner? Intermediate?

Advanced? CIE home study courses are designed for ambitious people at all entry levels. People who may have:

1. No previous electronics knowledge, but do have an interest in it;
2. Some basic knowledge or experience in electronics;
3. In-depth working experience or prior training in electronics.

You can start where you fit and fit where you start, then go on from there to your Diploma, an Associate Degree if you want it, and career.

### Many people can be taught electronics.

There is no mystery to learning electronics. At CIE you simply start with what you know and build on it to develop the knowledge and techniques that make you a specialist. Thousands of CIE graduates have learned to master the simple principles of electronics and operate or maintain even the most sophisticated electronics equipment.

### CIE specializes in electronics.

Why CIE? CIE is one of the largest independent home study schools that specializes in electronics. Nothing else. CIE has the elec-

tronics course that's right for you.

Learning electronics is a lot more than memorizing a laundry list of facts about circuits and transistors. Electronics is interesting! It is based on recent developments in the industry. It's built on ideas. So, look for a program that starts with ideas and builds on them. Look to CIE.

### Programmed learning.

That's exactly what happens with CIE's Auto-Programmed® Lessons. Each lesson uses famous "programmed learning" methods to teach you important principles. You explore them, master them completely, before you start to apply them. You thoroughly understand each step before you go on to the next. You learn at your own pace.

And, beyond theory, some courses come fully equipped with electronics gear (the things you see in technical magazines) to actually let you perform hundreds of checking, testing, and analyzing projects.

### Experienced specialists work closely with you.

Even though you study at home, you are not alone! Each time you return a completed lesson, you can be sure it will be reviewed, graded, and returned with appropriate instructional help. When you need additional individual help, you get it fast and in writing from the faculty technical specialist best qualified to answer your question in terms you can understand.

### CIE offers you an Associate Degree.


One of the best credentials you can have in electronics — or any other career field — is a college degree. That's why CIE gives you the opportunity to earn an Associate in Applied Science in Electronics Engineering Technology. Any CIE career course can offer you credit toward the degree...more than half of the number needed in some cases.

You can also prepare for the government-administered FCC (Federal Communications Commission) Radiotelephone License, General Class. It can be a real mark in your favor...government-certified proof of your specific knowledge and skills.
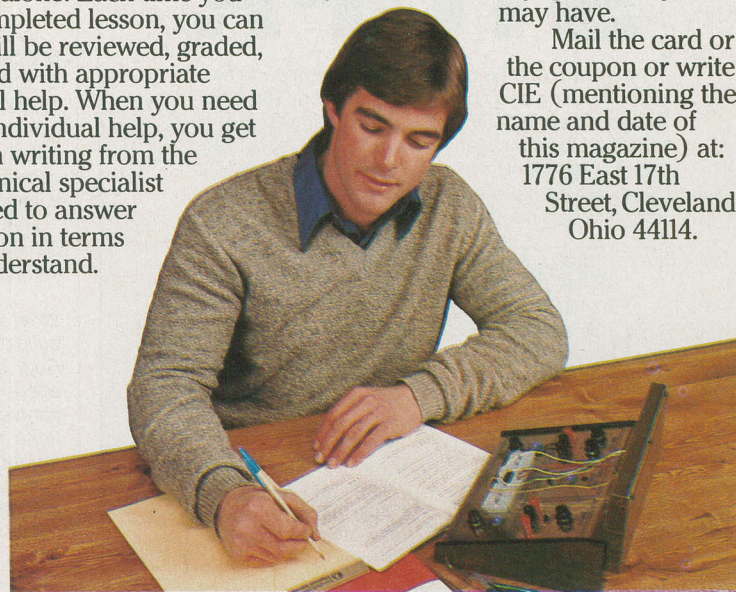
### Today is the day. Send now.

Fill in and return the postage-free card attached. If some ambitious person has removed it, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail the card or the coupon or write CIE (mentioning the name and date of this magazine) at:  
1776 East 17th  
Street, Cleveland,  
Ohio 44114.



**CIE** **Cleveland Institute of Electronics, Inc.**

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

YES...I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program... plus my FREE package of home study information.

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_


Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_ / \_\_\_\_\_

Check box for G.I. Bill bulletin on Educational Benefits: ☐ Veteran ☐ Active Duty

**MAIL TODAY!**

RE 88



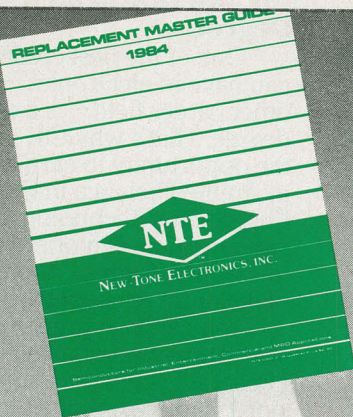

# THE RIGHT STUFF.

The growth of NTE quality replacement parts has been nothing short of astronomical. And the proof is in our new 1984 Replacement Master Guide, destined to be the standard directory for technicians across the country. In excess of 3,000 quality NTE types are cross-referenced to more than 220,000 industry part numbers.

## YOU'LL FIND ALL THE RIGHT STUFF FOR REPLACEMENT, MAINTENANCE AND REPAIR:

- Transistors
- Thyristors
- Integrated Circuits
- Rectifiers and Diodes
- High Voltage Multipliers and Dividers
- Optoelectronic Devices
- Zeners
- Microprocessors and Support Chips
- Memory IC's
- Thermal Cut-Offs
- Bridge Rectifiers
- Unijunctions
- RF Transistors
- Microwave Oven Rectifiers
- Selenium Rectifiers
- NEW! The Protector 6000™ Transient Voltage Protection Strip

Look for our Replacement semiconductors in the bright green polybags and cartons that list rating limits, device type, diagrams and competitive replacement right on the package. NTE quality parts are available from your local NTE distributor and come backed by our exclusive two-year warranty. Ask for your FREE NTE Replacement Master Guide and take off with NTE!



NEW-TONE ELECTRONICS, INC.  
44 FARRAND STREET • BLOOMFIELD, NEW JERSEY 07003

## LETTERS

*continued from page 16*

tuning range of  $1 \mu\text{H} \pm 6\%$  measured at 7.96 MHz. The unloaded Q is  $60 \pm 20\%$  at 10.7 MHz.

Transistor Q2, the BFQ85, which is no longer manufactured by SGS/ATES has the following absolute-maximum specifications:

- Collector-emitter voltage,  $V_{CE}$ : 15 V
- Collector-base voltage,  $V_{CB}$ : 20 V
- Emitter-base voltage,  $V_{EB}$ : 3 V
- Collector current,  $I_C$ : 40 mA
- Power dissipation,  $P_D$ : 200 mW
- DC Current gain,  $h_{FE}$ : 40 (minimum) to 200
- Current-gain-bandwidth product,  $f_T$ : 4 (minimum) to 5 GHz
- Noise Figure, NF: 3 dB @ 1 GHz.—Editor

## STAY AS YOU ARE

Your "Stay as you are", comment in the March 1984 issue, expresses my sentiments exactly. I have been a subscriber for a number of years and sincerely hope that **Radio-Electronics** will stay as it is *now* and has been in the past.

ROBERT L. SITLER  
Beaver, PA

## IDEAL SWITCH

In the "What's News" department of the March 1984 issue, you mention a new General Electric solid-state switch that handles 12,000 watts. I didn't think a switch was suppose to handle any power at all. An ideal switch would handle infinite voltage with no current when open, infinite current with no voltage when closed.

How much is  $0 \times \infty$ ?

JOHN R. SIMPSON  
Tampa, FL

*What is an ideal switch? If you ever find or build one, let us know so we can both get rich. Real switches cannot handle infinite voltages—the insulation will break down and the contacts will arc. Real switches also have a finite resistance and cannot pass infinite amounts of current—they will melt. Solid-state switches suffer from similar breakdown problems. The GE insulated-gate transistor (IGT) switch described is rated at 25 amperes, 500 volts continuous, or 12,500 watts. That's not quite infinite, but it's a considerable improvement over earlier IGT's. (Incidentally,  $0 \times \infty$  is known as an indeterminate form and is undefinable.)*—Editor

## OWNER'S MANUAL NEEDED

I purchased a Precision R.F. Signal Generator, model E-200C. The former owner did not have the owner's manual; it was either lost or misplaced, and the family was unable to find it.

I made several phone calls to the New York area and located the former factory, but the present occupants say that the Precision Company moved several years ago and left no forwarding address.

Will you ask your readers if there is an extra owner's manual for a Precision model E-200C somewhere in their shops?

R.F. STONEMAN  
Roscommon, MI

Now we can detect a breast cancer smaller than this dot.

At such an early stage, your chances of living a long, healthy life are excellent. But we need your help. The only proven way to detect a cancer this small is with a mammogram. A mammogram is a low-radiation x-ray of the breast capable of detecting a cancer long before a lump can be felt. If you're over 50, a mammogram is recommended every year. If you're between 40 and 50, or have a family history of breast cancer, consult your doctor. In addition, of course, continue your regular self-examinations.

 American Cancer Society

R-E




# Radio-Electronics mini-ADS



**THE ULTIMATE IN VIDEO SWITCHING.** Finally a Video Switch with precision solid state electronic switching and a touch of class. "The Beta Bunny" features "one touch" control membrane panel; excellent video clarity; bright LED true position indicators; luxurious solid oak or simulated dark walnut wood enclosure; 6 inputs and 3 outputs. Kit form **\$99.95**, Assembled **\$129.95**. Add **\$4.95** shipping/handling. **BETA ELECTRONICS, 2081-A 3RD ST., RIVERSIDE, CA. 92507 (714) 788-2701.**

CIRCLE 22 ON FREE INFORMATION CARD

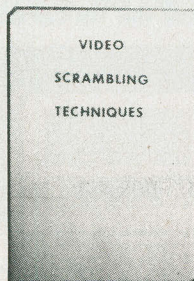


**SUBSCRIPTION TV MANUAL.** This information packed book details the methods used by subscription TV companies to scramble and descramble video signals. Covers the Sinewave, Gated Pulse, SSAVI system, and the methods used by most cable companies. Includes circuit schematics, theory, and trouble shooting hints. **Only \$12.95** plus **\$1.50** first class P&H. Info **\$2.00**, refundable. **RANDOM ACCESS, Box 41770-R, Phoenix, AZ 85080.**

CIRCLE 31 ON FREE INFORMATION CARD



**FREE 1984 ELECTRONIC TOOL & INSTRUMENT CATALOG** is packed with over 5,000 quality technical products for assembling, testing and repairing electronic equipment. All products fully illustrated with photographs, detailed descriptions and pricing to allow for easy ordering by phone or mail. Most orders are shipped within 24 hours. 100% satisfaction guarantee. **CONTACT EAST, 7 Cypress Drive, Burlington, MA 01803. (617)272-5051.**

CIRCLE 50 ON FREE INFORMATION CARD

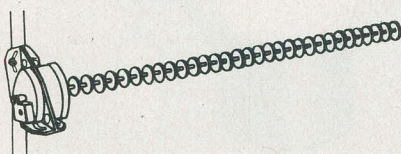


**MAE-3, YAGI MICROWAVE ANTENNA** — High quality up to 60 dB gain 1.9-2.5 GHZ-50 mile range possible clear TV picture, pre assembled probe with down converter, 1.9-2.5GHZ, power supply and RF amplifier, 1.9-2.5GHZ, 30dB gain, with co-ax cable included. All mounting hardware, for fast and easy installation. Special **\$89.95**. Available by phone or mail order only. Check or money order, 5% Shipping and Handling on all orders. **KASHIWAGI ELECTRONICS CORP., 3555 So. Highland Suite 14 Las Vegas, Nevada 89103, 702-367-1241.**

CIRCLE 63 ON FREE INFORMATION CARD
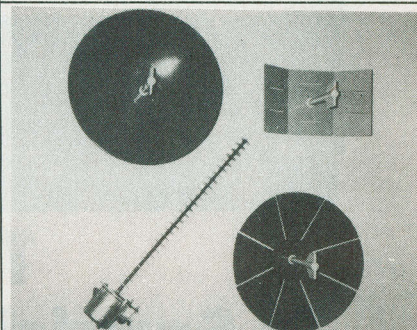
## CALL NOW AND RESERVE YOUR SPACE


- 6 x rate \$605 per each insertion.
- Reaches 235,323 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **212-777-6400** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.



Bring in those hard to get channels with these low priced amateur microwave T.V. receivers. **HMR Mini—\$64.95; HMR Daisy Dish—\$69.95; Spectra Dish—\$89.95; MDS 52 ROD—\$89.95.** All systems complete and fully guaranteed. Free Shipping. Cable converters call or write for quantity pricing. Add \$4.00 for COD orders. Call today. **H.M.R. Sales, 221 East Camelback, Suite 1, Phoenix, Arizona 85012, Phone 602-993-0398.**

CIRCLE 38 ON FREE INFORMATION CARD

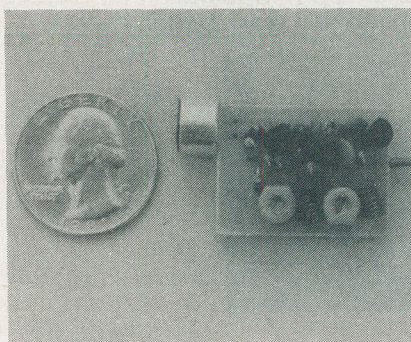

**THE MOST EXCITING KIT YOU WILL EVER BUILD** The model WAT-50 miniature FM transmitter uses a 4-stage circuit NOT to be confused with a simple wireless microphone. Up to 1 mile range. So sensitive, it will pick-up a whisper 50 feet away! Use with any FM radio. Complete kit only **\$29.95** tax incl. **FREE SHIPPING.** **DECO INDUSTRIES, BOX 607, BEDFORD HILLS, NY 10507.**

CIRCLE 24 ON FREE INFORMATION CARD




**APPLIANCE REPAIR HANDBOOKS—13** volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. **\$2.65 to \$5.90 each.** Free brochure. **APPLIANCE SERVICE, PO Box 789, Lombard, IL 60148. 1-(312) 932-9550.**



**ZENITH Z-TAE CABLE T.V. Descrambler.** Brand new tag along. For Complete information and our Catalog SEND 5.00 to **R&M Distributors, P.O. Box 266-R15, Boston, MASS. 02190. REMIN-1032.**



# 1946. Sams Introduces PHOTOFACT®

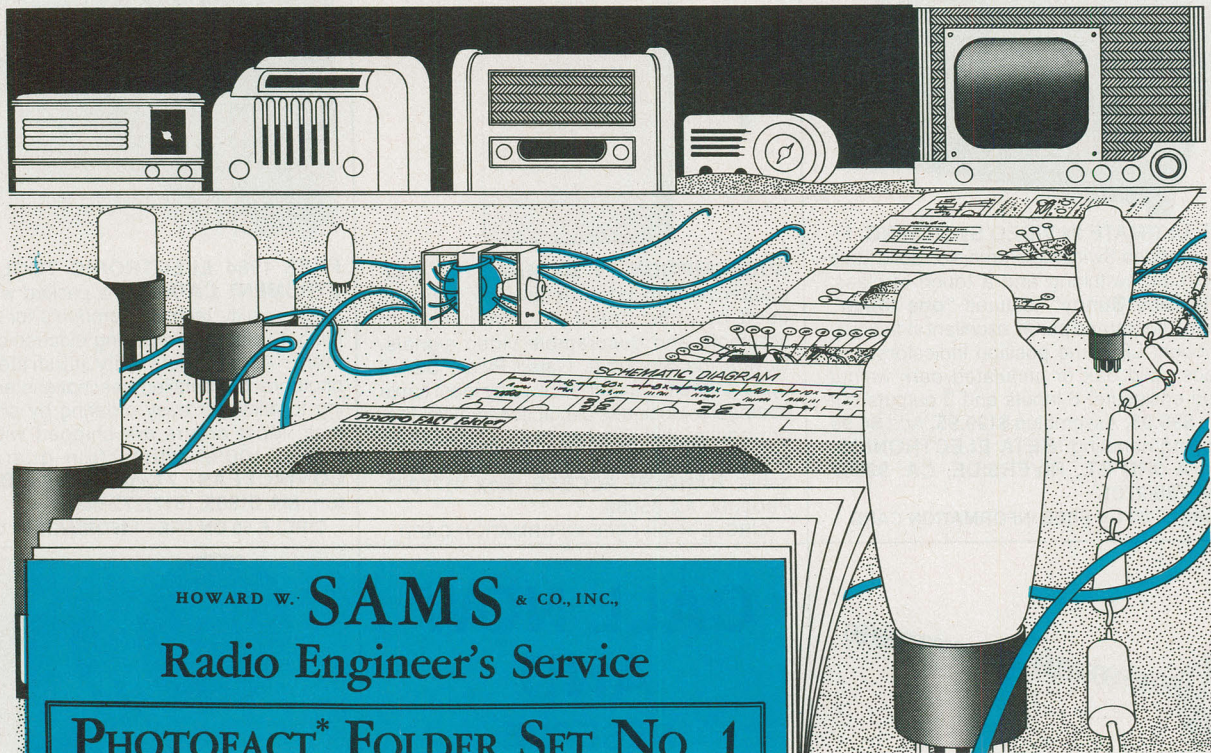

## The Inside Track To Servicing Your Microcomputer

### The Inside Track To Servicing Your Microcomputer.


It started in the early days of television. Sams began reconstructing and documenting how technology works and published its first PHOTOFACT TV service manual.

But Sams didn't stop there. Sams continued to apply its technical expertise in new areas. And in 1967, released the first computer book.

Now Sams has combined its knowledge of computers and technical servicing to bring you **COMPUTERFACTS**—the first and only technical manual series for servicing today's microcomputers and peripherals.
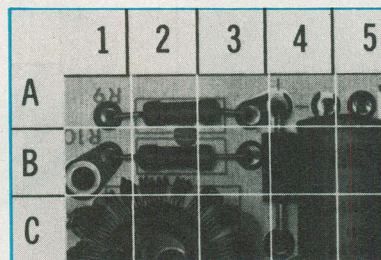
### The Facts Remain Clear.

Buy Sams **COMPUTERFACTS** and you've got the inside track to servicing and maintaining your computer yourself. Because with **COMPUTERFACTS**, you have everything you need to understand how your computer is put together and how you can make it work better.





Offer good in USA only. Prices and availability subject to change without notice.  
In Canada, contact Lenbrook Electronics, Markham, Ontario L3R 1H2.

Apple is a registered trademark of Apple Computer, Inc. Commodore is a registered trademark of Commodore Business Machines, Inc. Atari is a registered trademark of Atari, Inc. Osborne is a registered trademark of Osborne Computer Corporation. Diablo is a registered trademark of XEROX CORPORATION. TI 99/4A is a registered trademark of Texas Instruments, Inc. PHOTOFACT is a registered trademark of Howard W. Sams & Co., Inc. **COMPUTERFACTS** is a trademark of Howard W. Sams & Co., Inc.



# 1984. Sams Introduces COMPUTERFACTS™

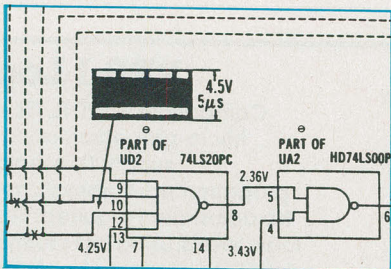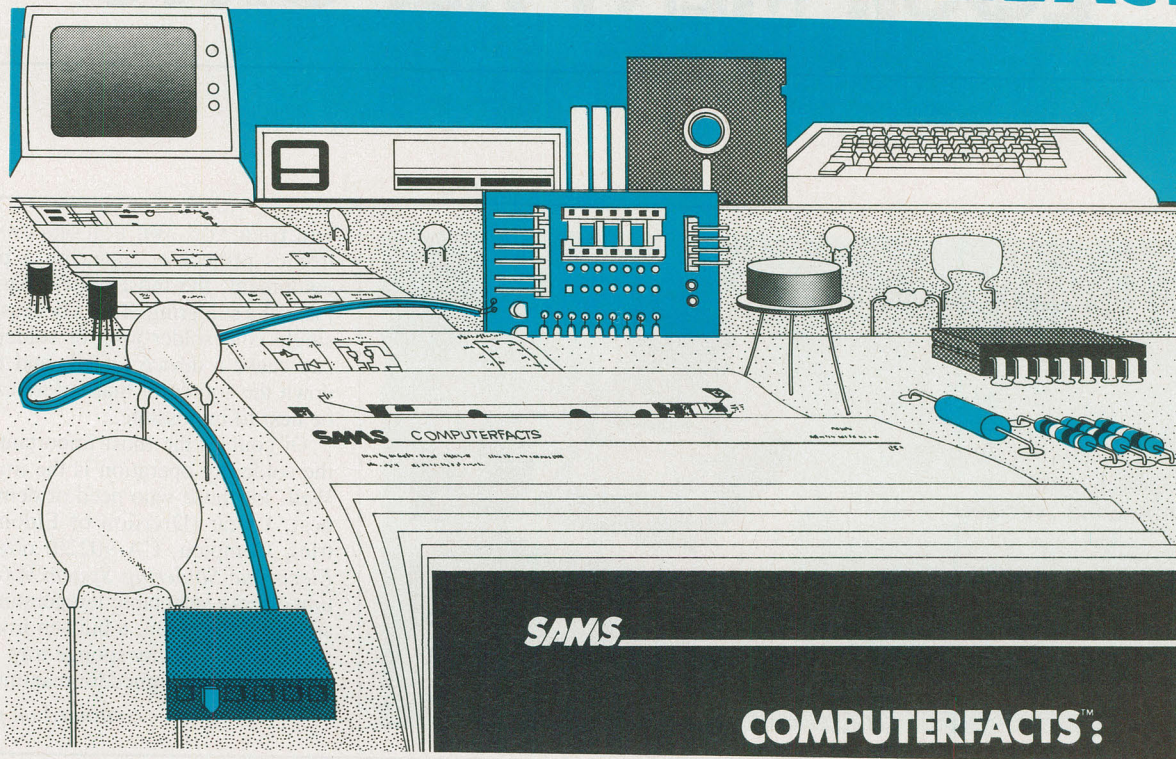

COMPUTERFACTS are available for every major computer and component made including data storage devices, modems, and printers by Apple®, Osborne®, Commodore®, Atari®, Diablo®, TI 99/4A®, and others.

And like PHOTOFACT, COMPUTERFACTS cover every circuit, chip and control thoroughly and accurately with pages of:

- Fully-diagrammed schematics
- Disassembly instructions
- Logic charts
- Parts descriptions

- Terminal guides
- Troubleshooting hints

So you can spot and service problem areas in minutes.

## COMPUTERFACTS Give You More.

If you want more out of your computer, get more into it with COMPUTERFACTS. Only COMPUTERFACTS can be used alone or with your favorite computer guide to improve operation, change configuration, replace defective parts, and more.

**So get Sams COMPUTERFACTS and get on the fast track to better computing. To order, visit your local Sams dealer. Or call OPERATOR 164 at 317-298-5566 or 800-428-SAMS.**

## SAMS™

**What Technology Is All About.**

HOWARD W. SAMS & CO., INC.  
4300 West 62nd Street, P.O. Box 674  
Indianapolis, IN 46268

CIRCLE 25 ON FREE INFORMATION CARD



# EQUIPMENT REPORTS

## Ungar Electronic Soldering System 9000

This soldering system lets you set the iron temperature precisely

CIRCLE 101 ON FREE INFORMATION CARD




WHETHER YOU ARE BUILDING AN electronics project or repairing a piece of equipment, the most critical part of the job is the soldering. That's because even a single cold solder joint or solder bridge can cause a device to fail, and tracking down the source of that failure can often be next to impossible.

Of course, the most important part of the soldering operation is the iron itself. Well, for those who need or demand the best, Ungar (Division of Eldon Industries, Compton, CA 90220) offers their *Electronic Soldering System 9000*. That unit offers a selectable-temperature precision soldering iron, a built-in iron stand, and a large capacity sponge tray.

The unit is designed for maximum flex-  
*continued on page 32*
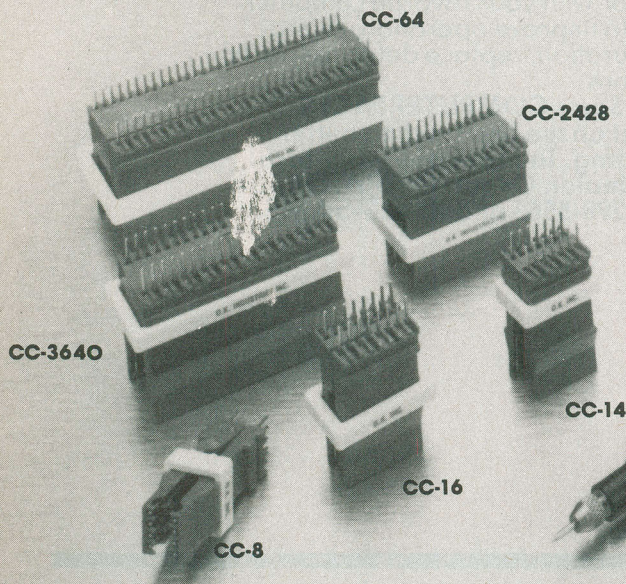
## IC Test Clips

Unlike "clothespin" type test clips which can stress IC's and even accidentally loosen or extract them, the CHIP-CLIP attaches by means of a snap-action locking ring that ensures reliable contact but with virtually no stress to the device under test.



## PRB-1 Logic Probe

Compatible with DTL, TTL, CMOS, MOS and Micro-processors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated. Eliminates need for heavy test equipment. A definite savings in time and money for Engineer and Technician.



## PLS-1 Logic Pulser

PLS-1 is a multi-mode high current pulse generator packaged in a hand-held instrument. Signal injection is by means of a pushbutton switch near the probe tip. Pulse polarity is automatic. Holding the button down delivers a series of pulses of 20 pps to the circuit under test.

3455 Conner Street, Bronx, New York, 10475, U.S.A.  
Telex 125091 OK NYK. Telex 232395 OK NY UR.  
Phone (212) 994-6600.

CIRCLE 7 ON FREE INFORMATION CARD

OK  
Industries  
Inc.





# We gave solderless breadboarding a new name.

Proto-Board® breadboards, by Global Specialties. The leading name in solderless breadboarding.

You find them wherever electronics is important. From labs to production lines to classrooms to home workshop benches. Their name, synonymous with solderless breadboarding. And for good reason.



Proto-Board breadboards introduced engineers, technicians and hobbyists to a new way

of designing and building electronic circuits: as fast as they can think. Testing, modifying and expanding as quickly as new thoughts occur. Saving precious time and money by freeing creativity from manual labor.

Global Proto-Board products are arrays of solderless sockets and bus strips that emulate PC board layouts

while permitting instant insertion and removal of components from the largest DIP to the smallest discretes. With a rugged construction built to provide positive connections and withstand day-in, day-out professional use—even as test fixtures. And mounted on sturdy metal backplanes, for extended high-frequency use and extra durability.

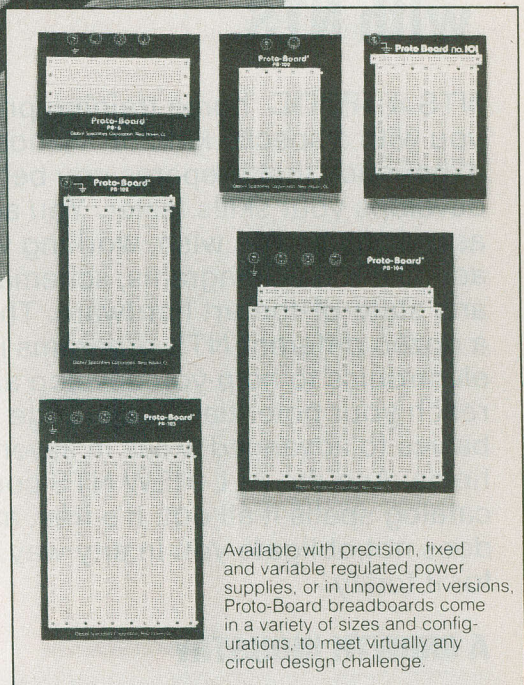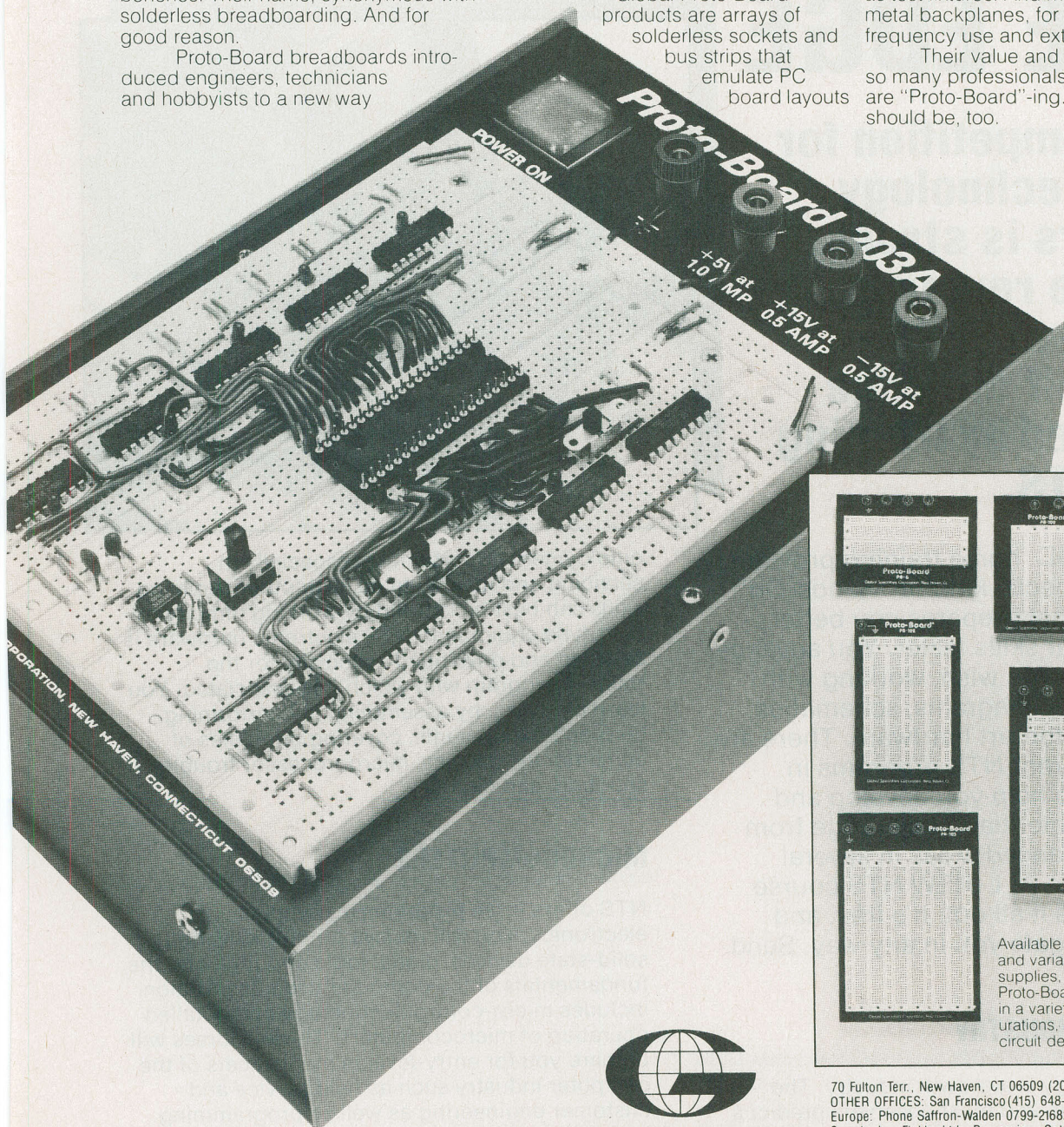Their value and versatility are why so many professionals and hobbyists are "Proto-Board"-ing. And why you should be, too.



Available with precision, fixed and variable regulated power supplies, or in unpowered versions. Proto-Board breadboards come in a variety of sizes and configurations, to meet virtually any circuit design challenge.



**GLOBAL SPECIALTIES**  
An Interplex Electronics Company

\*Suggested U.S. resale. Prices, specifications subject to change without notice.

70 Fulton Terr., New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227  
OTHER OFFICES: San Francisco (415) 648-0611, TWX 910-372-7992  
Europe: Phone Saffron-Walden 0799-21682, TLX 817477  
Canada: Len Finkler Ltd., Downsview, Ontario

CIRCLE 33 ON FREE INFORMATION CARD

JULY 1984


27



# In Computer Electronics...

## NTS INTRONIC™ HOME TRAINING GIVES YOU THE EDGE

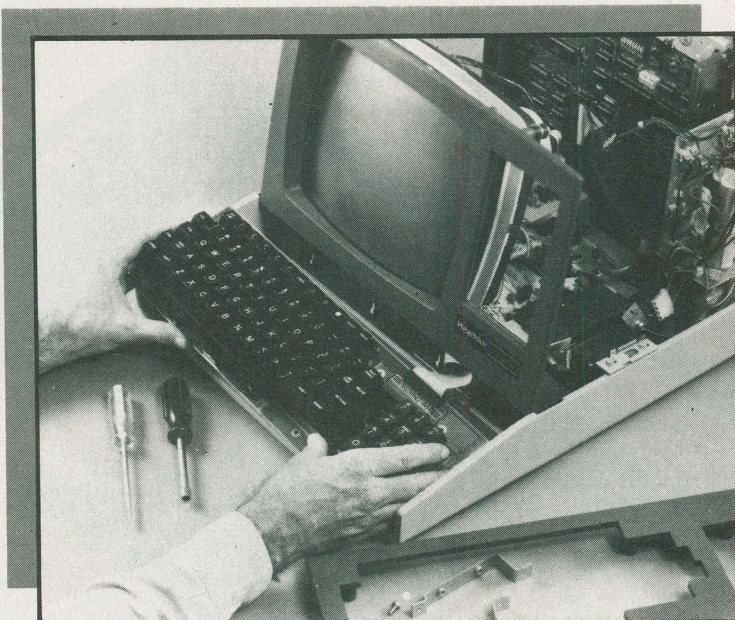**The competition for High-Technology careers is strong, and the rewards are great. Give yourself the edge you need by training with NTS.**



NTS INTRONIC home training provides you with a special kind of "Hands-On" experience that prepares you better, develops your skills faster. You advance as quickly as you wish, working with actual circuits, diagrams, schematics, and state-of-the-art hardware. There are a dozen different NTS programs in electronics to help you develop and reach your potential. They range from basics to advanced areas in several fields. And the ALL-NEW NTS course catalog spells it all out. It's free, and does not obligate you in any way. Send for it today.

### **A GROWTH INDUSTRY**

High-Technology is a growth industry. The evidence is clear, and most observers predict a steady expansion due to a relatively strong flow of investment capital into computers, electronics and precision instruments. Sales of computers alone will reach an estimated ten million units this year. This means challenges and new

employment opportunities, especially in servicing and maintenance. Computer servicing skills can best be learned by working directly on field-type equipment. NTS electronic hardware is selected and developed especially for the training program with which it is associated. You learn by doing, by assembling, by performing tests and experiments, covering principles of computer electronics, microprocessor troubleshooting, and circuitry.

### **MICROCOMPUTERS**

NTS offers three programs in computer electronics. You will receive training covering solid-state devices, digital logic circuitry, and the fundamentals of the computer itself. Instruction includes micro-control technology and detailed operation of microcomputers. These courses will prepare you for entry-level in many facets of the computer industry such as field service and customer engineering as well as programming. In addition to written texts your course includes the NTS/HEATH disc-drive computer which you assemble as part of the training process. The assembly and use of the computer will serve to reinforce practical application of principles.



## MICROPROCESSOR TECHNOLOGY


The field of industrial and microprocessor technology encompasses the application of electronic microprocessor control principles. Your course takes you from fundamentals of digital electronics and associated circuitry through the application of the microprocessor as a control device. You will learn how to move and manipulate instructions and information. The microprocessor trainer included in your course is a microcomputer system designed as a practical tool for learning the use of software and hardware techniques utilized in the linking of microprocessors to various systems.

## DIGITAL ELECTRONICS

The NTS Compu-Trainer is a fascinating solid-state device which you will build in order to perform over ninety logic circuit experiments. These experiments serve to emphasize an area of electronics which is essential to the understanding of state-of-the-art control equipment; they are also extremely important to those wanting to pursue a career in computer servicing. Separate courses involving the Compu-Trainer are also available in Microcomputer Servicing and Digital/Analog Electronics.
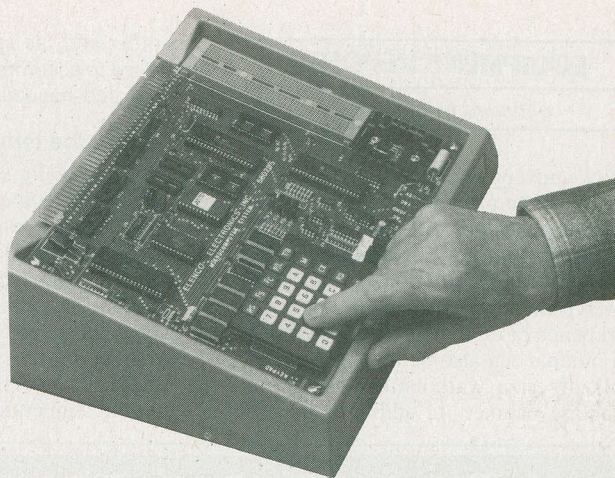
## ROBOTICS & VIDEO TECHNOLOGY

Other NTS courses cover a wide range of specialization. In Robotics, the NTS/Heath Hero I is included to train you in robotic applications in




manufacturing processes. In Video technology, a new course features the advanced NTS/Heath Z Chassis "Smart Set" color TV with computer space command remote control and space phone. This is an excellent program for those interested in a career in video servicing with microcomputer basics.
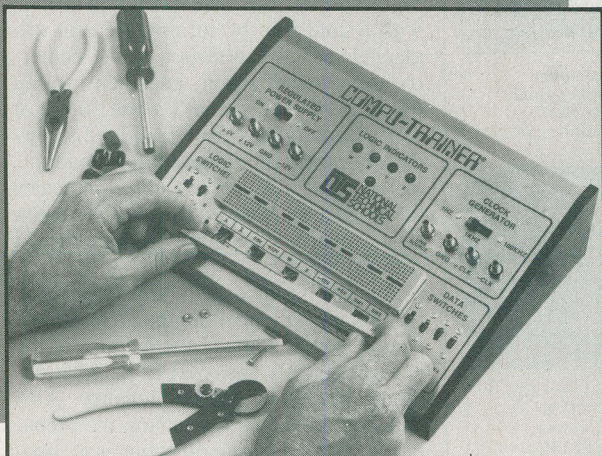
## EARN CEU CREDITS

America's industrial giants are turning more and more frequently to home study as an effective way to upgrade employee skills. You benefit from the experience NTS has gained in its 79 years as a leader in technical training. The skills and experience gained in the building of kits and test equipment provide you with training that cannot be duplicated. And, depending on the program you select, you can earn up to 30 CEU credits for successful completion. Complete details included in the catalog.



Use the mail-in card or fill out and mail the coupon. Indicate the field of your choice. (One, only please.) FREE full color catalog will be sent to you by return mail.



NO OBLIGATION

NO SALESMAN WILL CALL

**NTS NATIONAL TECHNICAL SCHOOLS**

TECHNICAL TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools

4000 So. Figueroa St., Los Angeles, CA 90037

**NATIONAL TECHNICAL SCHOOLS** Dept 206-074  
4000 South Figueroa Street, Los Angeles, CA 90037

Please send FREE color catalog on course checked below:

- |   |   |
|---|---|
| <input type="checkbox"/> Robotics                       | <input type="checkbox"/> Computer Electronics |
| <input type="checkbox"/> Digital Electronics            | <input type="checkbox"/> Video Technology     |
| <input type="checkbox"/> Auto Mechanics                 | <input type="checkbox"/> Home Appliances      |
| <input type="checkbox"/> Air Conditioning/Solar Heating |   |

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Phone ( ) \_\_\_\_\_

- ☐ Check if interested ONLY in classroom training in Los Angeles  
☐ Check if interested in G.I. Bill Information.



## EQUIPMENT REPORTS

continued from page 26

ibility and convenience. The soldering station can be placed directly on a workbench using the base provided, or, if desired, the system control module, which houses the unit's electronics, can be removed from the base and placed under the workbench or on a shelf. The system control module can also be mounted under a shelf or on a wall using an optional mounting bracket. In addition, the iron

holder and the sponge tray can be positioned to accommodate either right-handed or left-handed users.

### Setting the temperature

But what really sets that unit apart is the adjustable temperature scale. Since the idling temperature can be adjusted over a range of 420°F to 800°F (215.5°C to 426.6°C), the user can set the idling temperature according to the requirements of a specific application. The settings are arranged in increments of 20°F over two ranges. Once set, the system will maintain the temperature to within  $\pm 10^\circ\text{F}$ .

Ungar										9000
OVERALL PRICE										
EASE OF USE										
INSTRUCTION MANUAL										
PRICE/VALUE										
	1	2	3	4	5	6	7	8	9	10
	Poor		Fair		Good			Excellent		

An LED-bargraph-type display is used to show the actual iron temperature. That type of display is used so that you can see clearly and directly that the unit has reached or is maintaining the selected temperature. A pulsating LED on the display indicates slight variations in iron temperature.

The system control module and base are made of attractive black and beige plastic. As is appropriate in this type of device, all the plastics are self-extinguishing to reduce any chance of a fire. Also for safety, the system is three-wire grounded, burn-resistant cords are used, and circuit-breaker protection is provided.

Operation of the unit is simplicity itself. The unit is switched on using a front-panel POWER switch, and the desired temperature is selected using the RANGE switch and TEMPERATURE slide control. Once the well-balanced iron with cool grip has reached the proper temperature, you're set to go. All controls and the readout are located on the system-control module.

Calibration of the unit is done against room-temperature. The procedure is done with a cold iron by turning the unit off, placing the RANGE switch in the center CALIBRATION position, and then turning the unit on. Once that's done, the ADJ control is rotated—using a slotted screwdriver—until the temperature readout, disregarding the the last zero, indicates the room temperature. That is, for a room temperature of 70°F, the readout should indicate 700°F.

As you might expect, the instruction manual is really no more than a four-page flyer. It covers some of the features of the unit, and briefly goes over its installation, use, calibration, and maintenance. Also included are some pointers on the preparation and care of soldering-iron tips. There is no information regarding the theory of operation, or a schematic. A list of user-replaceable parts, and their Ungar part numbers, is provided.

With its list price of \$190.00, the *Electronic Soldering System 9000* is obviously not aimed at the occasional user. But, if you do a lot of building or repairing, and you are serious about the work that you do, then this unit, with its combination of precision and convenience features, is going to be hard to beat. **R-E**

# Scan the World.



## R-2000

SSB, CW, AM, FM, digital VFO's, 10 memories, memory/band scan, optional 118-174 MHz coverage...

The R-2000 is an innovative all-mode SSB, CW, AM, FM receiver that covers 150 kHz-30 MHz, with an optional VC-10 VHF converter unit to provide coverage of the 118-174 MHz frequency range.

### R-2000 FEATURES:

- Covers 150 kHz-30 MHz in 30 bands. UP/DOWN band switches. VFO's tune across 150 kHz-30 MHz.
- All mode: USB, LSB, CW, AM, FM.
- Digital VFO's. 50-Hz, 500-Hz or 5-kHz steps. F. LOCK switch.
- Ten memories store frequency, band, and mode data. Each memory may be tuned as a VFO. Original memory frequency may be recalled.
- Lithium batt. memory back-up. (Est. 5 yr. life).
- Memory scan. Scans all or selected memories.
- Programmable band scan. Scans within programmed bandwidth.
- Fluorescent tube digital display of frequency (100 Hz resolution) or time. DIM switch.
- Dual 24-hour quartz clocks, with timer.
- Three built-in IF filters with NARROW/WIDE selector switch. (CW filter optional.)
- Squelch circuit, all mode, built-in.
- Noise blanker built-in.
- Tone control.
- Large front mounted speaker.
- RF step attenuator. (0-10-20-30 dB.)
- AGC switch. (Slow-Fast.)
- "S" meter, with SINPO "S" scale.
- High and low impedance antenna terminals.
- 100/120/220/240 VAC, or 13.8 VDC (Option) operation.
- RECORD output jack
- Timer REMOTE output (not for AC power)
- "Beeper"
- Carrying handle.



### R-1000

High performance receiver • 200 kHz-30 MHz • digital display/clock/timer • 3 IF filters • PLL UP conversion • noise blanker • RF step attenuator • 120-240 VAC (Optional 13.8 VDC).



### R-600

General coverage receiver • 150 kHz-30 MHz • digital display • 2 IF filters • PLL UP conversion • noise blanker • RF attenuator • front speaker • 100-240 VAC (Optional 13.8 VDC).

### Optional accessories:

- VC-10 118-174 MHz converter.
- HS-4, HS-5, HS-6, HS-7 headphones.
- DCK-1 DC cable kit.
- YG-455C 500-Hz CW filter.
- HC-10 World digital quartz clock.
- AL-2 Surge Shunt

# KENWOOD

TRIO-KENWOOD COMMUNICATIONS  
1111 West Walnut/Compton, CA 90220  
Telephone: (213) 639-9000


CIRCLE 96 ON FREE INFORMATION CARD



## Sabre Electronics Inc. Calc-U-Dial Automatic Dialer

An automatic call dialer  
that's also a call timer  
and a calculator

CIRCLE 102 ON FREE INFORMATION CARD

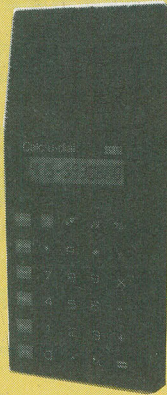

IN THESE DAYS OF HIGH LONG-DISTANCE phone bills, it's not uncommon to subscribe to one of the independent long-distance telephone services. But using one of those services usually involves entering a long billing or access number. That is an inconvenience, and there is always a chance that you might forget the number or make a mistake entering it. Also, using those services requires a phone that generates DTMF (*Touch-Tone*) tones. If you only have pulse (rotary) equipment you are out of luck. That is, unless you have a device such as the *Calc-*

*U-Dial* from Sabre Electronics (344 El Camino Real, San Carlos, CA 94070). But, as we'll soon see, that device is far more than just a telephone dialer.

### A dialer

The unit is a hand-held device that generates DTMF tones. No direct connection to telephone equipment is needed. When dialing a number, the unit's rear speaker is held up to the mouthpiece of the telephone's receiver.

Up to six 16-digit numbers can be stored. The storing process is simplicity

itself. The device is turned on and placed in the store mode by pressing the **STOR** button. Then, using the calculator-type keypad, a storage "location" from one to six is selected and the number entered. Once the number is entered, the store mode is exited and the unit is turned off by pressing the **STOR** button a second time. So that you don't forget where each number is stored, an area for writing down that information is provided on the back of the unit.

The unit is capable of generating all of the DTMF tone pairs, including \* and #. In addition, if you require a pause in your dialing sequence, it can be stored using a **P** button on the keypad.

As easy as entering a number is, dialing one is even easier. All you do is hold the unit's speaker to the telephone's mouthpiece, press **AUTO**, and key in the memory location of your number; the dialer does the rest. Once the number has been dialed, it is shown on the unit's 10-digit LCD readout. For stored numbers longer than 10 digits, a  $\pm$  key can be used to alternately view the first and second part of the number if you wish.

The dialer also has an automatic redial feature. That allows you to redial the last number called by simply pressing the **REDL** key.

*continued on page 36*

# GET THE SAME VIDEO TRAINING THE PEOPLE AT SONY GET.


Now you can be trained by Sony even if you aren't employed by Sony.

Because we're making our vast library of training videotapes available to you. The very tapes that teach our own engineering, service and sales personnel.

The tapes cover the products and concepts of video and its related technologies. You can learn the basics of video recording. Color systems. Digital video and electronics. Television production. And more.

Plus you can learn how to service cameras, VTR's, and other video products. As professionally as Sony does.

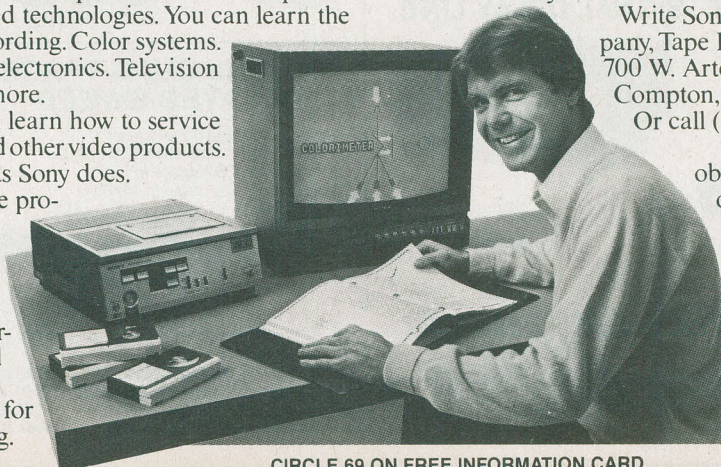The tapes are produced entirely by Sony and contain up-to-the-minute information. They communicate clearly and simply. And some of them are even programmed for interactive learning.



And learning through video can be done at your own pace, in the convenience of your home, shop or school. Reviewing is quick and easy. And the tapes are always available for reference.

Send for your catalog, which lists more than 250 titles. In your choice of 3/4" or 1/2" formats.

Write Sony Video Products Company, Tape Production Services, 700 W. Artesia Boulevard, Compton, California 90220. Or call (213) 537-4300.

Of course, there's no obligation. Except the obligation you have to yourself: to find out about the best training available in one of the country's fastest-growing, most lucrative fields.

**SONY**  
Video Communications  
Sony is a reg. trademark of Sony Corp.

CIRCLE 69 ON FREE INFORMATION CARD



# UNGAR DESOLDERING & SOLDERING

## Special Pricing... Special Free Offer

### Hot VAC Desoldering System



Model 4000

Built-in vacuum pump eliminates the need for shop air. Compact design and portability make it ideal for use at any location where there is an AC electrical plug-in outlet.  
**Self-Contained, Super-Quiet Air Pump:** The vacuum pump is not only virtually maintenance free, it is remarkably quiet. The pump operates only when the handle switch is actuated.  
**Temperature Control:** Variable solid-state control that adjusts the tip temperature from 500° - 1000°F. An electric circuit assures that transient spikes are fully suppressed thereby making the system safe for desoldering voltage-sensitive components.

Reg \$599.95  
**OUR SPECIAL PRICE**

**\$379<sup>95</sup>**

### Electronic Temperature Controlled Soldering System with Built-in Controller

**OUR SPECIAL PRICE \$89<sup>95</sup>**



Model 9100

Includes: base unit with built-in controller, micro-size handle with THERMO-DURIC heater, 1/16" #9012 screwdriver tip, sponge and tip tray, sponge, and Iron Holder. A low cost alternative in an operator-adjustable, temperature controlled soldering system.  
 • Electronic, closed-loop temperature control for maximum precision • Temperature is operator-adjustable from 400°F to 800°F • Continuous, variable control so you can select the exact temperature you need • Neon "on-off" light • Iron Holder can be right- or left-hand mounted to accommodate all operators.

**FREE** UNGAR 9100  
 with purchase of  
 Ungar 4000

TOLL FREE (800) 645-9518

**FORDHAM**



260 Motor Parkway, Hauppauge, N.Y. 11788

in N.Y. State 800-832-1446

■ VISA ■ COD ■ Master Charge  
 ■ Money Order N.Y. State residents add appropriate sales tax.  
 COD's extra (required 25% deposit)

ADD FOR SHIPPING AND INSURANCE

\$250.00 ....	\$4.50
\$251.00 to 500.00 .....	6.50
501.00 to 750.00 ....	8.50
751.00 to 1000.00 ....	12.50
over 1000.00 .....	15.00

# FORDHAM DISCOUNTS DISCOUNT PRICES ON HITACHI SCOPES


We will beat any advertised price

**SPECIAL OFFER!**  
*For a limited time only*
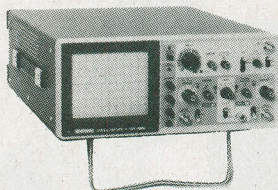
### 35 MHz DUAL TRACE SIGNAL DELAY LINE

Vertical sensitivity 5m V/div to 5V/div and 1m V/div to 1 V/div with 5X amplifier • Trigger modes Auto-matic, Normal, TV (+), TV(-).

REG \$895  
**OUR PRICE**  
**\$599<sup>95</sup>**  
 WITH PROBES




V-355F

### 60 MHz DUAL TRACE DELAYED SWEEP

High sensitivity • 1 mV/div (10 MHz) • 5 ns/div sweep rate  
 • 3rd channel display (trigger view) • Variable trigger hold-off  
 • Full TV triggering • Single sweep • Auto-matic focus correction.

**OUR PRICE**  
**\$995**  
 WITH PROBES

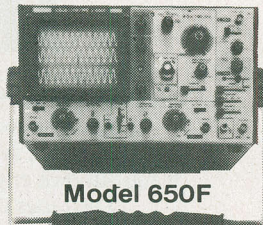


Model 650F

### 100 MHz QUAD TRACE DELAYED SWEEP

Large, bright 8x10 cm screen  
 • Quad trace operation/Ch1, Ch2, A trigger and B trigger • High sensitivity 500 μ V/div (5 MHz)  
 • Full TV triggering.

**OUR PRICE**  
**\$1299<sup>95</sup>**  
 WITH PROBES

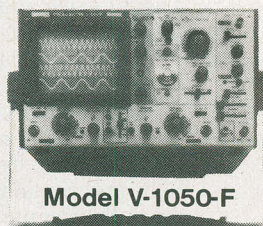

Model V-1050-F

TOLL FREE (800) 645-9518

**FORDHAM**



260 Motor Parkway, Hauppauge, N.Y. 11788

in N.Y. State 800-832-1446

■ VISA ■ COD ■ Master Charge  
 ■ Money Order N.Y. State residents add appropriate sales tax.  
 COD's extra (required 25% deposit)

ADD FOR SHIPPING AND INSURANCE

\$250.00 ....	\$4.50
\$251.00 to 500.00 .....	6.50
501.00 to 750.00 ....	8.50
751.00 to 1000.00 ....	12.50
over 1000.00 .....	15.00



# SUPERSALE

We will beat any advertised price

## BECKMAN Circuitmate® DMM

MODEL DM73  
**\$69<sup>95</sup>**

• Smallest digital multimeter on the market • Probe-style design makes it ideal for taking measurements in hard-to-reach test areas.



**\$64<sup>95</sup>**

• 3½-digit, pocket-size multimeter • 0.8% Vdc accuracy • diode test • hFE test • conductance • 10 amps AC and DC ranges • Autopolarity • Auto-Zero • Auto-decimal.



**\$79<sup>95</sup>** MODEL DM25

• 3½-digit, pocket-size multimeter • 0.5% Vdc accuracy • diode test • capacitance • continuity beeper • conductance • 10 amps AC and DC ranges • auto-polarity • auto-zero • auto-decimal.




## B&K PRECISION

100 MHz FREQUENCY COUNTER

OUR PRICE

MODEL 1803  
REG. \$169.95

**\$144<sup>50</sup>**

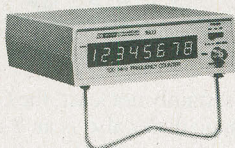


• 5 Hz to 100 MHz range • 8 digit LED display • Leading zero blanking • Low pass filter • BNC Connector Input • Overflow Indicator • Battery or AC powered • Charger/AC Adaptor included with Model 1803.

NTSC COLOR BAR GENERATOR

MODEL 1251  
REG. \$995.00

OUR PRICE

**\$849<sup>95</sup>**

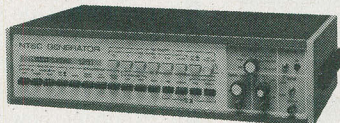



• Generates a wide variety of test signals and patterns for comprehensive testing, servicing and adjustment of virtually all types of television and video equipment • Video patterns include standard NTSC color bars, -IWQ, and staircase at two levels of burst phase chrominance • A full assortment of convergence patterns, raster colors gated or full field multiburst.

## HITACHI

PORTABLE OSCILLOSCOPES

MODEL V-222 (20 mHz)  
REG. \$695.00

MODEL V-422 (40 mHz)  
REG. \$895.00

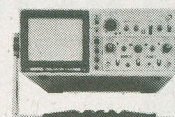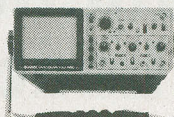

## CALL FOR SPECIAL PRICING

• New series of scopes provides high performance and light weight • Large 6-inch rectangular, internal graticule CRT • Autofocus circuit and scale illumination • DC offset function • Voltage and frequency reading outputs • High accuracy - ±3% • High sensitivity - 1 mV/div.

## BP DIGITAL CAPACITANCE METER



MODEL DCM-601  
REG. \$149.95

OUR PRICE

**\$79<sup>95</sup>**

• Digital display easy and correct readout • High accuracy: 100 PPM 0.5% • LS-circuit provides high reliability and durability • LCD display provides low power consumption.

## FORDHAM

550 MHz FREQUENCY COUNTER



MODEL FM-8  
REG. \$199.95

OUR PRICE

**\$149<sup>95</sup>**

• 8-digit high frequency counter with a switch selectable input using single BNC • Completely assembled • Pre-Calibrated, Pre-tested.

## LEADER

NTSC WAVEFORM MONITOR

MODEL LBO-5860  
REG. \$2050.00

OUR PRICE

**\$1850**




Permits displaying vertical interval test and reference signals by front panel line selector.

NTSC VECTORSCOPE

MODEL LVS-5850  
REG. \$2050.00

OUR PRICE

**\$1850**

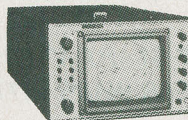

Convenient method for observing and measuring the relative phase and amplitude of chrominance signal components.

## FLUKE 70

73

• Analog Display • Rotary Knob • Volts AC & DC • Resistance to 32 MΩ • 10 Amps • Diode Test • 3200 Counts • Fast Autoranging • Function Annunciators in Display • Power-Up Self Test • 2000+ Hour Battery Life w/Power Down "Sleep Mode" • New Test Leads • VDE & UL Approval

**\$79<sup>95</sup>**

• 0.7% Accuracy • Autorange Only • 10 Amp Only



75

**\$95<sup>00</sup>**

• 0.5% Accuracy • Manual or Autorange • 10A + 300 mA Range • Beeper



77

**\$125<sup>00</sup>**

• 0.3% Accuracy • Manual or Autorange • 10 A + 300mA Range • Beeper • "Touch-Hold" Function



## VIZ DC TRIPLE POWER SUPPLYST

MODEL WP-708  
REG. \$489.00  
OUR PRICE

**\$399<sup>95</sup>**



• Dual DC Voltmeter • Triple DC Power Supply • Three separate completely isolated DC power supplies; two 0-20V at 0-2A, one fixed 5V at 4A.

## WELLER SOLDERING STATION

SOLDERING STATION

MODEL EC1000  
OUR PRICE

**\$109<sup>95</sup>**

• Identical to the EC2000 except LED Digital temperature readout • The EC1000 is dial controlled.



MODEL EC2000  
OUR PRICE

**\$139<sup>95</sup>**

• Continuously variable tip temperature from 350 to 850 F • Positive temperature coefficient sensor inside the tip provides temperature feedback to maintain tip temperature at a set point.



# FORDHAM

260 Motor Parkway, Hauppauge, N.Y. 11788

Master Charge  
VISA  
COD  
Money Order  
Check

N.Y. State residents add appropriate sales tax.

ADD FOR SHIPPING AND INSURANCE:  
\$0-\$250.00 ..... \$ 4.50  
\$251.00 to \$ 500.00 ..... \$ 6.50  
\$501.00 to \$ 750.00 ..... \$ 8.50  
\$751.00 to \$1000.00 ..... \$12.50  
over \$1000.00 ..... \$15.00

TOLL FREE

**(800) 645-9518**

in N.Y. State call 800-832-1446

Free Catalog on Request

JULY 1984



## EQUIPMENT REPORTS

continued from page 33

Finally, numbers that are not stored in memory can be dialed by placing the unit in the manual mode. That's done by pressing the MANL button and keying in the digits. One potential problem in using the device in that manner is that keying in a long number while holding the rear speaker against the telephone's mouthpiece can be inconvenient. Fortunately, the redial feature also works with

numbers entered in the manual mode. Thus, all you need do is to enter the number, turn off the unit, then hold the speaker up to the telephone's mouthpiece and press REDL. When used in that manner, the redial feature acts as a seventh storage location.

### A call timer

If the *Calc-U-Call* were just a dialer it would still be a handy device. However, the unit does much more. For instance, it is also a call timer. Thirty seconds after a call has been made using either the AUTO or REDL keys, the dialed number display

blanks and is replaced by the duration of the call in minutes and seconds. The unit will time calls up to 50 minutes long. After 50 minutes, the unit will turn itself off. The call timer can be turned off before 50 minutes by simply pressing the OFF button.

Sabre	Calc "U" Dial									
OVERALL PRICE										
EASE OF USE										
INSTRUCTION MANUAL										
PRICE/VALUE										
	1	2	3	4	5	6	7	8	9	10
	Poor		Fair			Good			Excellent	

### A calculator

Lastly, but certainly not least, the *Calc-U-Dial* automatic dialer also is an 8-digit calculator. In addition to the normal arithmetic functions (+, -, ×, ÷), the unit can square, do square roots, and take percentages. In addition, the unit can accommodate scientific-notation entry and display. When scientific notation is used, the exponent (power) of 10 is shown at the far right of the display.

The small manual that comes with the *Calc-U-Dial* does a good job of explaining how to use the unit, and detailed examples are given for a variety of circumstances. As you would expect in a consumer unit of this type, no technical information is provided.

All-in-all this is an interesting and useful device that works exactly as claimed. The *Calc-U-Dial* is covered by a 90-day warranty and has a suggested retail price of \$49.95.

R-E

## Instrument Mart and Leader



## For Instruments You Can Count On

PRICES START AT \$210.00

2-YEAR WARRANTY

LEADER frequency counters lead a shielded life and are built to last. That's why **INSTRUMENT MART** recommends them to customers in severe RF and educational environments.

Buying a counter can be a confusing job. There are optional time base stabilities, different gate times and resolutions, and any number of variables that affect performance. Call **INSTRUMENT MART** to discuss which of our more than 20 counters are right for your application. We've been doing it for over 15 years.

All available at competitive prices. Call us and compare.




The Professional Test Equipment Source

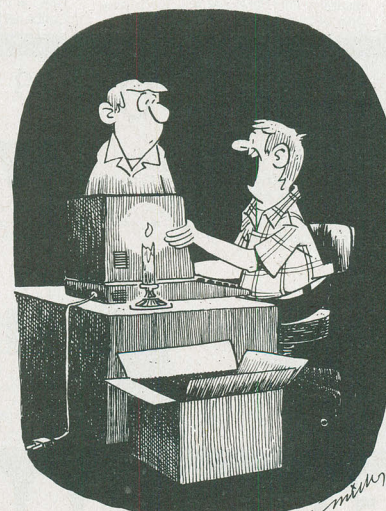**The Instrument Mart**

295 Community Drive, Great Neck, New York 11021  
(516) 487-7430 Outside N.Y. (800) 645-6535

Sales, Service, Rental/Leasing Programs  
... and Pre-Owned Test Equipment also Available



"Sure, they turned off the power. But by ignoring my electric bills, I accumulated enough to buy this unit!"




# NEW PRODUCTS

For more details use the free information card inside the back cover

**SIGNAL GENERATOR**, model 1260 features gen lock; RGB outputs; blackburst; gated or full-field multiburst; a full assortment of convergence patterns and raster colors; NTSC color bars, IWQ and staircase; selectable in-

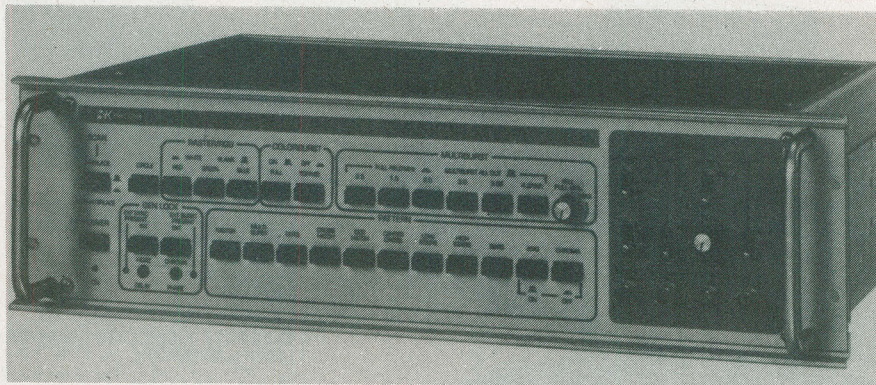type of test signal and pattern needed for complete testing, servicing, and adjustment of all types of television and video equipment, including TV receivers, VTR's, VCR's, VDP's, CCTV, MATV, and CATV systems and com-



CIRCLE 111 ON FREE INFORMATION CARD

terlaced or progressive vertical scan, and auxiliary input and output signals.


The model 1260 generates virtually every

ponents. It is priced at \$1695.00. —**BK Precision**, 6460 West Cortland Street, Chicago, IL 60635.

**UNINTERRUPTIBLE POWER SYSTEM**, the **LINE-SAVER™**, model LS-240, is a standby system for use in the home and small-business computer market. It is available for 120/240 volt, 60/50Hz systems, and has 240-VA, 150 watt capacity. The unit uses pulse-width modulation (PWM) technology to regulate the AC output voltage for greater efficiency to various load conditions. The PWM-AC output will also increase battery efficiency to increase back-up time: 5–10 minutes full load, 20–25 minutes half load, 35–40 minutes ½ load.

In addition there is an internal 12-volt sealed rechargeable battery, four voltage-surge protected and EMI/RFI filtered AC outlets, audible and visual power-failure warnings systems, test-mode indicator and switch, and replaceable external fuses.

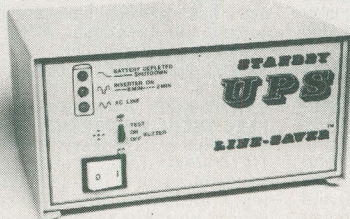The unit comes complete with a 6-foot, detachable, 3-prong, heavy-duty cord-set with a




CIRCLE 112 ON FREE INFORMATION CARD

CEE-22 connector.

The suggested retail price of the model LS-240 is \$395.00. —**Kalglo Electronics Co., Inc.**, Dept. LS, 6584 Ruch Rd., E. Allen Twp., Bethlehem, PA 18017.

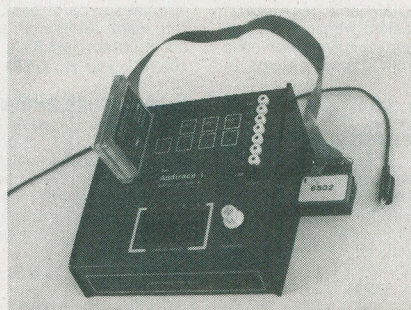**ADDRESS TRACER**, the *Addtrace I*, is a hardware address tracer to aid in troubleshooting machine-language programs. The operator can track program loops with the aid of the hexadecimal thumbwheel switches and LED's that indicate all coincident address lines.



CIRCLE 113 ON FREE INFORMATION CARD

Intended mainly for applications involving single-board computers, *Addtrace I* is connected directly to the microprocessor IC via a

*continued on page 42*

# EKI

**ELECTRONIC KITS INTERNATIONAL, INC.**  
(Formerly PPG Electronics)

**NEW!**

**AM RADIO  
6 TRANSISTOR  
#854/754**

A "Fun to Build" super sensitive 6-transistor AM radio. Exciting hands-on experience. Learn the how and why of a radio by building it yourself. All parts necessary are included, so tune in and discover the fun of building your own! Features: Low power consumption, low cost, easy step-by-step instructions with each kit, alignment procedure and troubleshooting instructions included. Circuit operations explained, wrist strap and cabinet included.



**NEW!**

## FROG PHONE W/CB & CASE

This kit has over 76 electronic parts including: speaker, microphone, microswitch, 12 button keypad, two circuit boards, transformer, two LED's eight transistors, one integrated circuit, twelve diodes, five electrolytic capacitors and sixteen resistors. Comes with step-by-step instruction and learning manual.

**#815/715  
NEW!**



Learn about:  
• Large scale integration pulse generator IC's  
• Matrix keyboards and decoders  
• Dial tone generation  
• Busy tone generation  
• Ring pulse generation  
• How to repair electronic telephones

## OVER 50 KITS AVAILABLE

### KIT #

- |                                      |  |
|--------------------------------------|--|
| 801 Pocket Dice                      | 842 12-volt Color Organ                    |
| 802 Signal Injector                  | 844 T.V. Jammer                            |
| 803 Space War Gun                    | 846 12-volt Strobe Stick                   |
| 804 Metal Detector                   | 850 Whooper Alarm                          |
| 805 Logic Probe                      | 852 Combination Lock/Alarm Control         |
| 806 Burglar Alarm                    | 856 Electronic Tennis                      |
| 808 Decision Maker                   | 858 Digital Roulette                       |
| 809 LED Pendulum Metronome           | 860 5-24 Volt Regulated Power Supply       |
| 811 Double Decision Maker            | 861 Big Sound Portable Organ               |
| 812 Siren Oscillator                 | 862 Full-wave Meter Speed Control          |
| 814 Robot Blinker                    | 866 Digital Slot Machine                   |
| 816 Mini-wink                        | 868 Digital Dice                           |
| 818 Fish Caller                      | 870 Nerve Taster                           |
| 820 Shimmer Lights                   | 876 8-digit Digital Clock                  |
| 821 Christmas Tree                   | 878 Digital Bird                           |
| 822 One Channel Color Organ          | 880 12-volt, 2-amp Regulated Power Supply  |
| 824 Automatic Siren                  | 882 Musical Horn                           |
| 826 Fuzz Box                         | 884 Sound Activated Color Organ, 1-channel |
| 828 9-Volt Power Supply              | 886 Audio Amp/Intercom                     |
| 830 Multi-purpose Power Supply       | 888 Librarian Tormentor                    |
| 834 Color Organ 3-channel, 1-control | 890 Stop-action Timing Tester              |
| 836 3-channel, 4-control Color Organ | 892 Telephone Hold Button                  |
| 840 Variable Strobe Light            | 894 Phaser Gun/Sound Generator             |
|                                      | 896 Binary Clock                           |

## FREE CATALOG OF ALL KITS

Available nationwide at your local electronics store.  
(Or send \$1.00 shipping & handling to address below.)

**EKI ELECTRONIC KITS INTERNATIONAL, INC.**

791 RED ROCK ROAD  
ST. GEORGE, UTAH 84770

**Call TOLL FREE  
1-800-453-1708**  
For store nearest you.

**Special Prices for Educators**

CIRCLE 58 ON FREE INFORMATION CARD



# Professional Books That Help You Get Ahead—And Stay Ahead!

## Join the **Electronics and Control Engineers' Book Club®** and...

- Keep up with current technology
- Sharpen your professional skills
- Be ready for new career opportunities
- Boost your earning power

**THE MCGRAW-HILL COMPUTER HANDBOOK: Applications, Concepts, Hardware, Software.** Edited by H. Helms. 992 pp., 475 illus. Everything you need to know about today's computer science and engineering is here in this massive treasure trove of information. Covers everything from Boolean algebra to hardware selection techniques to artificial intelligence. A handy reference work that brings you right up to the minute!  
279/721 Pub. Pr., \$79.50 Club Pr., \$49.95

**INTUITIVE IC ELECTRONICS: A Sophisticated Primer for Engineers and Technicians.** By T. M. Frederiksen. 208 pp., illus. Covering both the simplest and the most complicated IC designs, this lively, easy-to-read volume provides a sophisticated, nonmathematical explanation of the basic internal mechanisms common to all semiconductor devices.  
219/230 Pub. Pr., \$24.95 Club Pr., \$18.95


**ANTENNA ENGINEERING HANDBOOK, 2/e.** Edited by R. C. Johnson and H. Jasik, with contributions by 57 recognized authorities. 1,408 pp., 946 illus. This widely acclaimed Handbook gives you the guidance you need to solve problems in antenna design and application. It provides detailed information on physical fundamentals, patterns, structures, and design techniques for practical modern antennas.  
322/910 Pub. Pr., \$95.00 Club Pr., \$62.50

**RADIO HANDBOOK, 22/e.** By W. Orr. 1,136 pp., more than 1,300 illus. Here's the latest edition of what is universally regarded as the most useful reference in the industry. It's a "course" in communications, a fact-packed reference, and a how-to guide—all in a single book!  
582442-6 Pub. Pr., \$39.95 Club Pr., \$33.95

**MICROPROCESSOR APPLICATIONS HANDBOOK.** Editor-in-Chief, D. F. Stout. 472 pp., 284 illus. At last—a reference guide to microprocessor applications to help you make your systems timely, versatile, and cost-effective.  
617/988 Pub. Pr., \$39.95 Club Pr., \$31.45

**MICROPROCESSOR AND MICRO-COMPUTER DATA DIGEST.** By W. H. Buchsbaum and G. Weissenberg. 336 pp., 93 block diagrams, 106 pin configurations. If you work with electronic devices that use microprocessor or microcomputer integrated circuits, this much-needed book contains all the detailed technical data for every microprocessor IC that is currently listed as a "standard," off-the-shelf item.  
582835-9 Pub. Pr., \$29.95 Club Pr., \$22.50

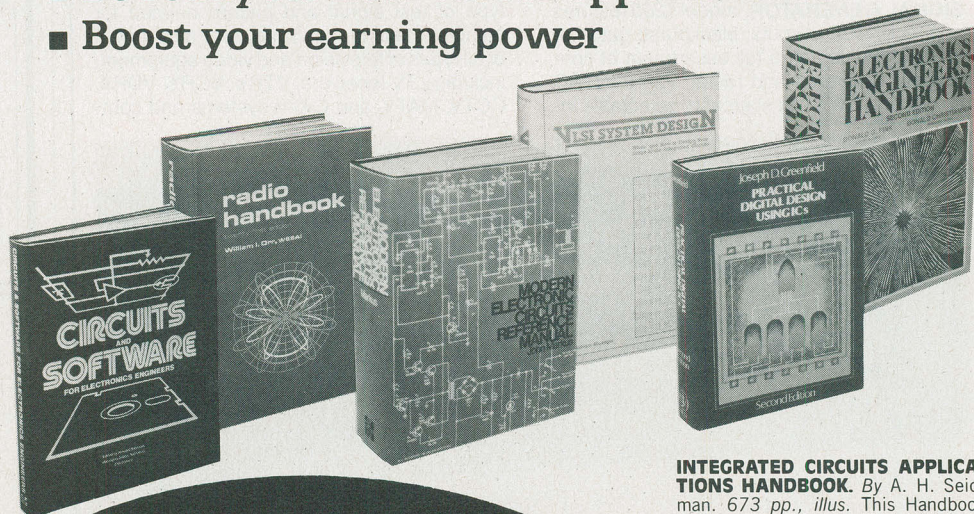**VLSI SYSTEM DESIGN: When and How to Design Very-Large-Scale Integrated Circuits.** By S. Muroga. 496 pp., illus., includes self-test problems. This book provides a straight-forward explanation of how to design the integrated circuit chips that are causing this electronics revolution. It focuses on every significant aspect of LSI/VLSI system design.  
582823-5 Pub. Pr., \$34.95 Club Pr., \$26.50



New members!  
Any one of these great  
professional books  
for only ... **\$2<sup>89</sup>**  
as a premium with your  
1st selection!

Spectacular values up to **\$95.00**

**HANDBOOK OF PRACTICAL ELECTRICAL DESIGN.** By J. F. McPartland. 416 pp., 300 illus. This volume provides a step-by-step explanation of designing electrical systems for industrial, commercial, and residential applications. Packed with helpful tips for saving time and complying with code requirements from branch circuits to wiring size.  
456/95X Pub. Pr., \$39.50 Club Pr., \$27.50

**DIGITAL LOGIC DESIGN.** By B. Holdsworth. 338 pp., 192 illus. All of the recent advances in digital design techniques are presented here in depth. It's both a text covering basic concepts and a practical guide to design techniques for combinational, clock-driven, and event-driven circuits.  
582852-9 Pub. Pr., \$39.95 Club Pr., \$27.50

**ELECTRONIC COMMUNICATIONS SYSTEMS.** By W. D. Stanley. 566 pp., illus. Emphasizing the signal-processing functions of modulation and demodulation operation, this book presents the essentials of electronic communications in a logical, step-by-step sequence.  
582834-0 Pub. Pr., \$25.95 Club Pr., \$20.95

**MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL.** By J. Markus. 1,264 pp., 3,666 circuit diagrams. Complete with values of components and suggestions for revisions—plus the original source of each circuit in case you want additional performance or construction details.  
404/461 Pub. Pr., \$74.95 Club Pr., \$57.95

**ELECTRONICS ENGINEERS' HANDBOOK, 2/e.** Edited by D. G. Fink & D. Christiansen. 2,272 pp., 2,189 illus. This updated and enlarged edition covers all the latest knowledge in the field, including new advances in integrated circuits, pulsed and logic circuits, laser technology, telecommunications, and much more.  
209/812 Pub. Pr., \$79.90 Club Pr., \$57.50

**DIGITAL CIRCUITS AND MICRO-PROCESSORS.** By H. Taub. 608 pp., heavily illus. This fast-paced, carefully written guide gives you thorough explanations of all the basic principles of digital systems and logic design—plus a solid introduction to microprocessors and microprocessor-based designs.  
629/455 Pub. Pr., \$34.95 Club Pr., \$26.50

**INTEGRATED CIRCUITS APPLICATIONS HANDBOOK.** By A. H. Seidman. 673 pp., illus. This Handbook presents information on everything from TTL, ECL, MOS, and CMOS logic families to semiconductor and bubble memories. The emphasis is on applications, with a minimum of theory. The math used is essentially limited to simple arithmetic and elementary algebra.  
582860-X Pub. Pr., \$39.95 Club Pr., \$29.95

**INTRODUCTION TO RADAR SYSTEMS, 2/e.** By M. I. Skolnik. 698 pp., 244 illus. This new edition of a widely used text on radar from the systems engineer's point of view brings you full discussions of the many major changes that have occurred in the field recently.  
579/091 Pub. Pr., \$40.95 Club Pr., \$31.00

**CIRCUITS AND SOFTWARE FOR ELECTRONICS ENGINEERS.** By H. Bierman. 352 pp., 200 illus., outsized 8½ x 11 format. This collection of over 340 proven—reliable circuits, computer programs, test methods, and design tools have been selected because of the ingenious ways they adapt devices to other uses.  
052/433 Pub. Pr., \$35.00 Club Pr., \$27.95

**HANDBOOK OF ELECTRIC POWER CALCULATIONS.** Edited by A. Seidman, H. Mahrous and T. G. Hicks. 448 pp., 300 illus. Here are 285 tested and proven procedures for handling the electric power problems most frequently encountered in actual practice. You'll find ingenious, time-saving ways to calculate fuel costs, motor efficiency, and power output.  
560/617 Pub. Pr., \$39.50 Club Pr., \$29.95

**STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e.** By D. G. Fink and H. Beaty. 2,448 pp., 1,414 illus. Today's most widely used source of electrical engineering information and data serves you as no other single work when you need detailed, timely, and reliable facts.  
209/74X Pub. Pr., \$74.95 Club Pr., \$53.95



**ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS.** By C. R. Hafer. 336 pp., more than 200 illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.

254/303 Pub. Pr., \$29.95 Club Pr., \$21.50

**PRACTICAL DIGITAL DESIGN USING ICs, 2/e.** By J. D. Greenfield. 717 pp., illus. This revised and expanded Second Edition of a popular guide shows how to get the most out of a wide range of popular integrated circuits. What's more, it contains the specialized know-how today's designer needs to interface ICs with microprocessors.

582853-7 Pub. Pr., \$25.95 Club Pr., \$19.95

**OPTICAL FIBER SYSTEMS: Technology, Design, and Applications.** By C. K. Kao. 197 pp., illus. From a basic explanation of optical fiber systems to the economic ramifications of their use, this volume provides full coverage of a rapidly changing field.

332/770 Pub. Pr., \$29.50 Club Pr., \$23.95

**MCGRAW-HILL ENCYCLOPEDIA OF ELECTRONICS AND COMPUTERS.**

By S. P. Parker, Editor-in-Chief. 960 pp., 1,266 illus., outsized 8½ x 11 format. It's a single-volume library that covers the entire world of electronics from Edison's pioneering work in electricity right up to optical fiber communications, control systems, lasers, radar, TV receivers, artificial intelligence, and computer storage technology.

454/876 Pub. Pr., \$59.50 Club Pr., \$41.50

**DIGITAL CONTROL SYSTEM ANALYSIS AND DESIGN.** By C. L. Phillips and H. T. Nagle, Jr., both Auburn University. 556 pp., 316 illus., 7 ready-to-run computer programs. It analyzes and designs closed-loop systems to which digital computers have been added to modify system dynamics. The book develops a wide range of control-system techniques applicable to linear, time-invariant, discrete-time system models.

582944-4 Pub. Pr., \$39.95 Club Pr., \$31.95


**HANDBOOK OF MICROCOMPUTER-BASED INSTRUMENTATION AND CONTROLS.** By J. D. Lenk. 307 pp., 227 illus.

Digital or microcomputer-based instrumentation and control systems can be very complicated—or relatively simple—depending on the application. In this book both systems are described and illustrated—and many examples of actual systems now in use in industry are included throughout.

582866-9 Pub. Pr., \$22.95 Club Pr., \$18.95

**COMPUTER METHODS FOR CIRCUIT ANALYSIS AND DESIGN.** By J. Vlach and K. Singhal. 656 pp., 148 illus. Computational methods have become an integral part of circuit analysis and design. And a solid understanding of the basics of computer-aided design is a must for engineers who want to achieve their career objectives. This self-teaching book provides that know-how in a logical, easy-to-follow presentation.

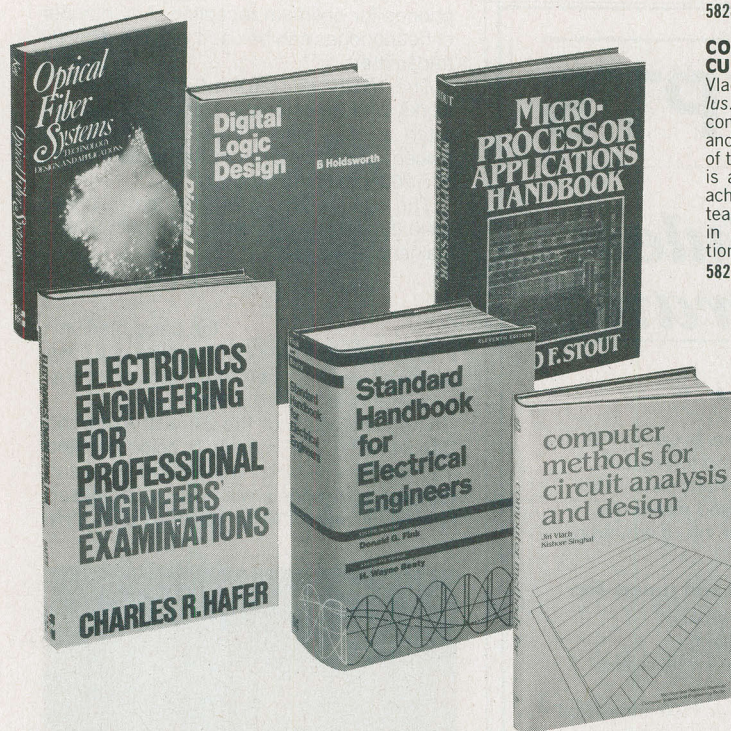582855-3 Pub. Pr., \$42.50 Club Pr., \$33.95



## Why YOU should join now!

■ **BEST AND NEWEST BOOKS IN YOUR FIELD** — Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

■ **BIG SAVINGS** — Build your library and save money too! Savings ranging up to 30% or more off publishers' list prices — usually 20% to 25%.

**BONUS BOOKS**—You will immediately begin to participate in our Bonus Book Plan that allows you savings up to 70% off the publishers' prices of many professional and general interest books!

■ **CONVENIENCE** —12-14 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and Alternate Selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an Alternate Selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three books (including your first selection) during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the first selection plus two additional books.

### Other McGraw-Hill Book Clubs:

Architects' Book Club • Byte Book Club • Chemical Engineers' Book Club  
• Civil Engineers' Book Club • Mechanical Engineers' Book Club

For more information, write to:

McGraw-Hill Book Clubs, P.O. Box 582, Hightstown, New Jersey 08520

## Be sure to consider these important titles as well!

**LARGE SCALE INTEGRATION: Devices, Circuits, and Systems.** By M. J. Howes & D. V. Morgan. 582851-0 Pub. Pr., \$35.95 Club Pr., \$29.95

**MICROWAVE SEMICONDUCTOR ENGINEERING.** By J. F. White. 582553-8 Pub. Pr., \$32.50 Club Pr., \$25.95

**MICROPROCESSOR SUPPORT CHIPS: Theory, Design, and Applications.** By T. J. Byers. 095/183 Pub. Pr., \$39.50 Club Pr., \$31.00

**ENGINEERING FORMULAS, 4/e.** By K. Gieck. 232/199 Pub. Pr., \$16.95 Club Pr., \$13.50

**ELECTRONICS CIRCUITS NOTEBOOK.** Edited by S. Weber. 192/448 Pub. Pr., \$35.50 Club Pr., \$27.50

**ANALYSIS AND DESIGN OF DIGITAL INTEGRATED CIRCUITS.** By D. A. Hodges and H. G. Jackson. 291/535 Pub. Pr., \$31.00 Club Pr., \$23.95

**HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN.** By D. E. Stout & M. Kaufman. 617/97X Pub. Pr., \$39.50 Club Pr., \$29.00

**ENGINEERING MATHEMATICS HANDBOOK, 2/e.** By J. J. Tuma. 654/298 Pub. Pr., \$34.50 Club Pr., \$26.95

**PCM & DIGITAL TRANSMISSION SYSTEMS.** By F. F. Owen. 479/542 Pub. Pr., \$34.95 Club Pr., \$25.95

**SIGNALS AND SYSTEMS.** By A. Oppenheim, A. Willsky, and I. Young. 582674-7 Pub. Pr., \$32.50 Club Pr., \$25.95

**DIGITAL COMMUNICATIONS.** By J. Proakis. 509/271 Pub. Pr., \$37.50 Club Pr., \$29.50

### MAIL THIS COUPON TODAY

#### McGraw-Hill Book Clubs

#### Electronics and Control Engineers' Book Club®

P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for the \$2.89 premium and my first selection at the discounted member's price, plus local tax, shipping, and handling charges. I agree to purchase a minimum of two additional books during my first year of membership as outlined under the Club plan described in this ad. A shipping and handling charge is added to all shipments.

Write Code No. of  
\$2.89 selection here

Write Code No. of  
first selection here



Signature \_\_\_\_\_

Name \_\_\_\_\_

Address/Apt. # \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members.

E33675



## NEW PRODUCTS

continued from page 37

40-pin DIP clip. A special plug-in module adapts the unit so that it is suitable for use with most microprocessors.

There are seven output jacks on the front panel for monitoring pulse duration and timing relationships with an oscilloscope. There are sixteen input lines and six user-definable control lines.


*Addtrace I* is available in kit form for \$199.95. (Factory-wired prices are available on request.)—**BMH Company, Inc.**, 224 Vas-

sar Street, Reno, NV 89502.

**CORDLESS STEREO HEADPHONE** system works with any audio source: stereo systems, TVs, and radios. It consists of a transmitter and stereo headphone receiver, or transmitter and stereo receiver for use with any headphones.

The components use infrared light to transmit audio information normally carried by wire. The transmitter, *IRT-200*, installs easily; hookup is by phone plug, and adapters are included. With both headphones and receivers, the range is about 35 feet. The system can be used for either stereo or mono.

The stereo headphones, model *IRH-210*

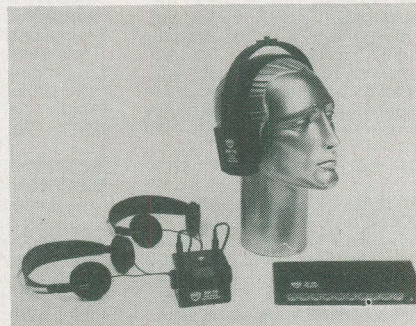

CIRCLE 114 ON FREE INFORMATION CARD

have full frequency response, 50-15,000 Hz. The infrared sensor is on top of the headphones for optimum reception. Any number of headphones can be used with the *IRT-200* transmitter.

The *IRSR-220* infrared stereo receiver works with any stereo earphones. Two can listen at once with the unit, which can be placed up to 35 feet from the audio-source/*IRT-200* transmitter hookup.

The system has a retail price of under \$100.00.—**Nady Systems**, 1145 65th Street, Oakland, CA 94608.

**TWO-WAY FM RADIOS**, the basic medium-power Midland *SYN-TECH* mobiles and base stations have had their transmit and receive bandwidths increased.

The bandwidth of the 50-watt low-band (29-54 MHz) VHF models is being doubled from 1 MHz to 2 MHz. The 40-watt mid-band (66-88 MHz) models will have an increased bandwidth from 2 MHz standard to 8 MHz



CIRCLE 115 ON FREE INFORMATION CARD

(transmit) and 3 MHz (receive). The 40-watt high-band VHF bandwidths will increase from 4.5 MHz to 7 MHz (transmit) and 6 MHz (receive). The 30-watt UHF model's bandwidth increases from 10 MHz (transmit) 5 MHz (receive) to 15 MHz (transmit), 8 MHz (receive). All other ratings of the new wider-bandwidth models remain at full published specifications.

Inexpensive conversions kits are available for field installation on existing units. The total cost of the enhanced-bandwidth conversion kits, including installation, is expected to be under \$20.00.—**Midland LMR**, 1690 N. Topping, Kansas City, MO 64120. **R-E**

The  
Professionals'  
Choice


# PTS

## "PTS rebuilt modules are better than brand new..."

I use PTS modules and tuners because of their automatic updates. Compared to original manufacturers' new and rebuilt parts, PTS is better. Quality and turnaround makes the difference. PTS does a better job of rebuilding 'cause that's all they do."
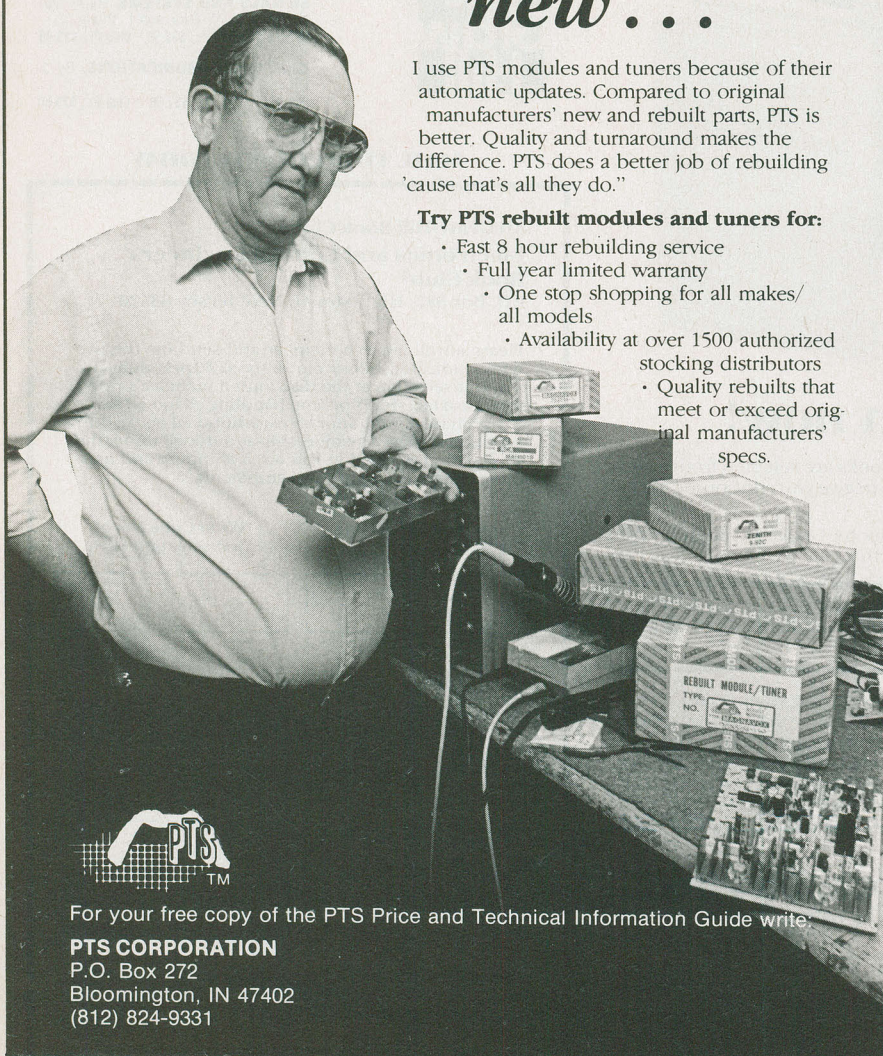
### Try PTS rebuilt modules and tuners for:

- Fast 8 hour rebuilding service
- Full year limited warranty
- One stop shopping for all makes/all models
- Availability at over 1500 authorized stocking distributors
- Quality rebuilds that meet or exceed original manufacturers' specs.



For your free copy of the PTS Price and Technical Information Guide write:

**PTS CORPORATION**  
P.O. Box 272  
Bloomington, IN 47402  
(812) 824-9331

CIRCLE 43 ON FREE INFORMATION CARD



# BUILD THIS

## ENERGY MISER



## For Air Conditioners

*You can cut your air-conditioning bills—while still staying comfortable—by using this device to control the cycling time of your central air-conditioning system.*

BILL OWEN

MANY PEOPLE DREAD THE SUMMER months. It's not because of the heat—it's because of what happens to utility bills once the air conditioner starts running. But as we'll show you, you can keep your bills down while still staying cool. The only requirements are that you have central air conditioning and that the air conditioning uses 24-volt DC control circuits.

When we say we feel hot or cold, we are really describing how comfortable we feel—not necessarily the air temperature. That's because the human body is a poor thermometer: Along with the temperature, it responds to humidity, air movement, and fresh air. For example, we've all heard of the wind-chill factor (a formula which takes into account the effects of air movement on how cold we feel). And all of us have experienced being uncomfortably hot when it's 79°F, and muggy (humid) but quite comfortably cool when it's 78° and dry. (And we've all heard too many times—and we're bound to hear it many more times as the weather

heats up—the expression “It's not the heat, it's the humidity.”)

### Problems with a thermostat

Air conditioning equipment is controlled by a thermostat which, unlike us, can respond *only* to changes in air temperature. If we attempt to economize by increasing the thermostat setting, we will save money. But we'll also reduce the amount of time that the compressor runs, increase humidity, reduce air movement, and allow room air to grow stale. The device that we'll describe uses the proven principal of *time cycling* to keep a comfortable effective air temperature while reducing the actual air-conditioner operating time. It cycles the air conditioner more frequently to reduce humidity, increase air movement and remove stale air. Comfort is maintained with reduced compressor operating-time, resulting in significant savings.

Another problem with a thermostat is that it can respond only to changes in temperature near its location. Because of

that, it often cannot provide fine control—it permits the room temperature to vary from uncomfortably cold to uncomfortably hot with no in-between. However, with the flexible COOLING CYCLE control of the device that we'll build, the exact amount of cooling can be easily programmed.

The device that we'll build is effective (and most efficient) when used in conjunction with a ceiling fan. When used that way, you can program the air conditioner to run for minimum-length cycles (to introduce dry, fresh air as needed) but you can still stay comfortable because of the increased air movement that the ceiling fan provides.

Another application for the device is in humid areas where it is necessary to run air conditioning when you are away from home to prevent mildew and damage to furniture, carpets, drapes and artwork. The extended-cycle feature is ideal for unoccupied homes or buildings. In that setting, the “energy miser” will cycle the air conditioner on for 5 minutes, followed



by a 30-minute off period. Valuable furnishings and possessions will be protected because the air conditioner will run at regular, predictable, and economical intervals, whereas a thermostat may or may not operate depending upon temperature variations.

A feature normally found only in expensive energy management systems is the fan run-on timer. Normally, when the air conditioner's compressor shuts down, the fan motor stops as well. That leaves cool air trapped in the duct work and cold compressor-coils. However, the fan run-on timer of the device that we'll build lets the fan run for 90 seconds after the compressor stops—allowing the fan to pull cool air into the living space. That feature alone can help you realize significant energy savings, and thus saving you enough money so that you can recoup your investment in a very short time.

### A look at the circuit

Figure 1 is the schematic of the cycling-time control circuit. Three monostable timers (IC1, IC2, and IC3) correspond to the three timed intervals. The first timer, IC1, controls the fan-on time—the amount of time that the fan runs on after

the compressor shuts off. The second timer, IC2, controls the compressor-on time and the third timer, IC3, controls the compressor-off time. Let's take a look at how it works.

When power is initially applied, the R4-C1 time constant keeps the trigger input (pin 2) of IC2 (which controls the compressor-on time) low enough to ensure triggering. The output from IC2 switches high for a period of time determined by the parallel combination of capacitors C4 and C5 and series resistors R1 and R7. Depending upon the position of control R1 (the COOLING-CYCLE control), the compressor-on time will be between 5 minutes and 20 minutes.

At the end of the on cycle, IC2 pin 3 switches low, triggering IC1 (pin 2) through capacitor C9. Pin 3 of IC1 switches high for 90 seconds (as determined by C11 and R13). At the end of the 90-second fan-on period, IC1 pin 3 switches low, triggering IC3. The output of IC3 (which controls the compressor-off time) will go high for a time interval that is selected by S1. In the CYCLE 1 position, that compressor-off interval is 15 minutes, as determined by C6 and R6. In the CYCLE 2 position, the compressor-off interval is 30

minutes, as determined by C6 and the series combination of R3 and R6.

During the compressor-on interval, IC2 pin 3 is high, which turns on transistor Q1, energizing relay RY1 and the associated LED indicator. Relay RY1 completes the 24-volt control circuit for the compressor-motor contactor. Similarly, during the fan-on interval, relay RY2 and its LED indicator are energized through transistor Q2. During the compressor-off interval, IC2 pin 3 is in its low state, and LED1, the COMPRESSOR-OFF LED, is lighted.

The three timers continue in sequence (compressor on, fan on, compressor off) until power is interrupted. When power is reapplied, the compressor-on timer will begin the sequence.

We don't have to build a power supply for our cycling controller—it obtains its power from the control-voltage transformer inside the air conditioner. One side of that 24-volt AC secondary is brought out directly to the thermostat and is (usually) labeled R. (See Table 1 for some common thermostat markings.) The other side of the secondary is available indirectly through the heater contactor-coil (labeled W).


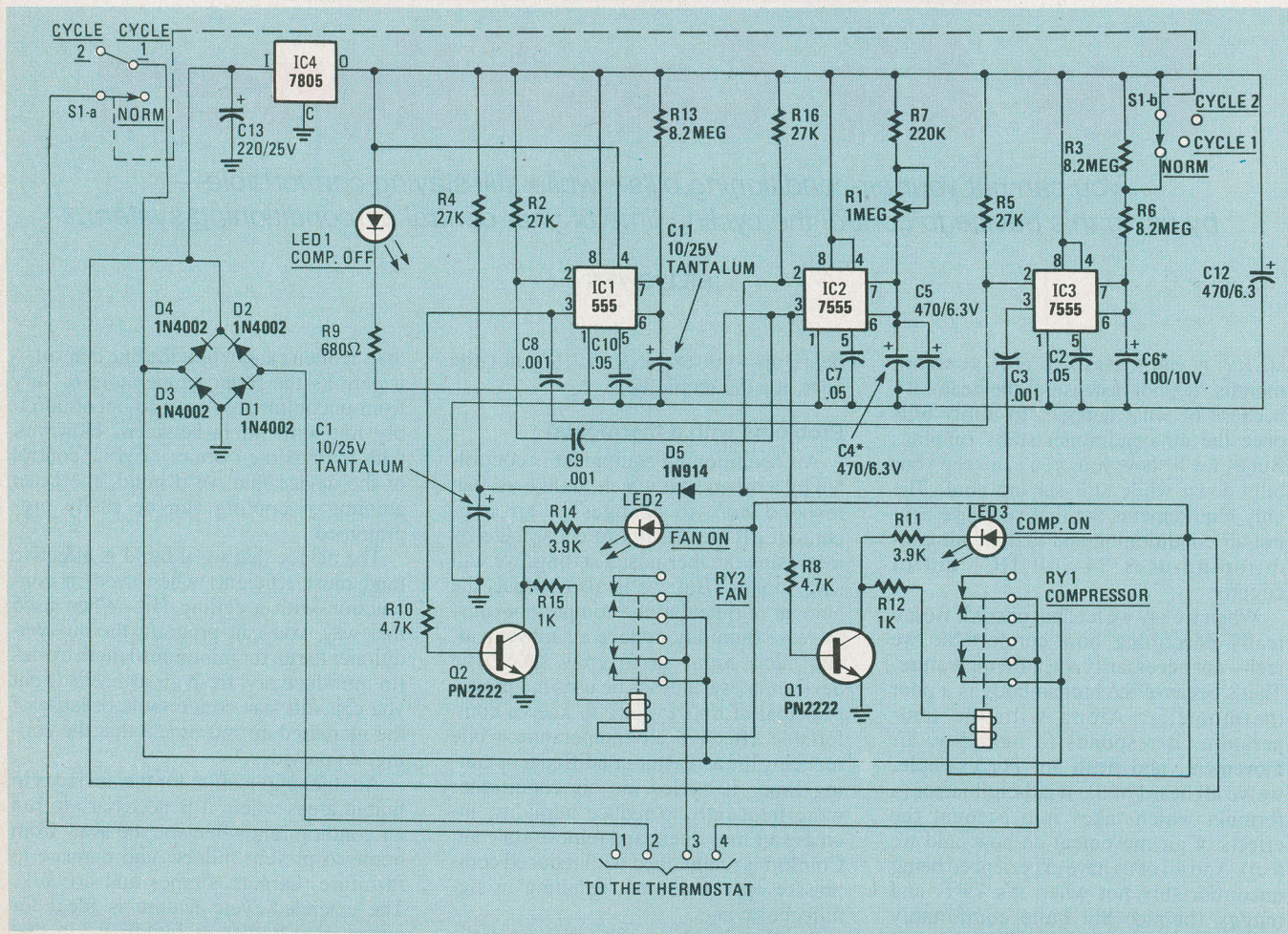


FIG. 1—THREE TIMERS ARE USED to provide compressor-on, compressor-off, and fan-on intervals. Two of the timers are 7555 types because of the long time constants required. Note that the capacitors marked with an asterisk (\*) are low-leakage electrolytics.

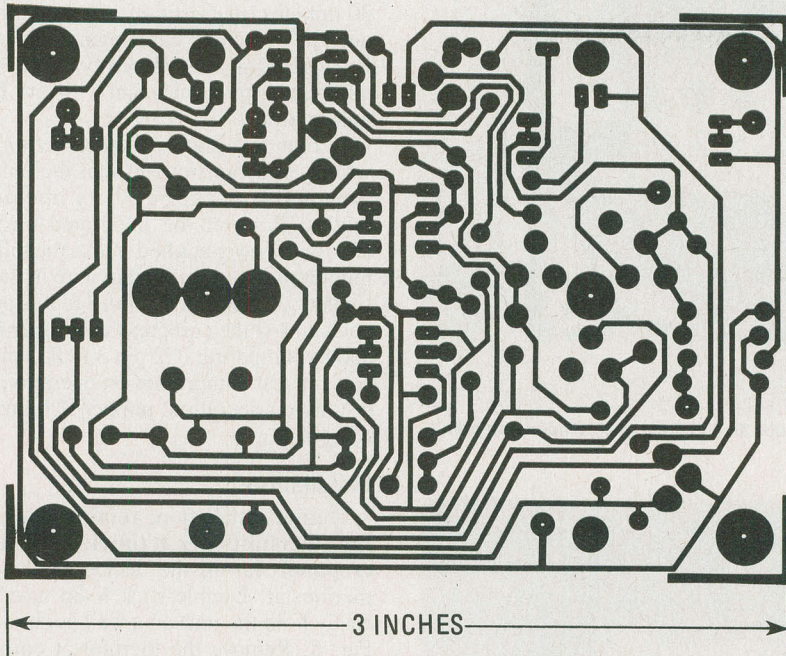

### Possible thermostat-terminal markings

Cable/Color	Possible thermostat-terminal markings				
1/Red	R5	R	RH	4	M
2/White	4	W	W	W	H
3/Green	G	G	G	G	F
4/Yellow	Y6	Y	Y	Y	C



Since the “energy miser” will not be used during reverse-cycle or heat-cycle operation of the air conditioner, we can use a small amount of current (about 50 mA) through the heater contactor (relay) coil. (If more current were drawn through the heater contactor-coil, it might energize the contactor.) Of course, you can use a small transformer instead. Diodes

## PARTS LIST

R1—1 megohm, potentiometer  
R2,R4,R5,R16—27,000 ohms  
R3,R6,R13—8.2 megohms  
R7—220,000 ohms  
R8,R10—4700 ohms  
R9—680 ohms  
R11,R14—3900 ohms  
R12,R15—1000 ohms

C1,C11—10  $\mu$ F, 25 volts, tantalum  
C2,C7,C10—.05  $\mu$ F, ceramic disc  
C3,C8,C9—.001  $\mu$ F, ceramic disc  
C4,C5,C12—470  $\mu$ F, 6.3 volts, low-leak-  
age electrolytic  
C6—100  $\mu$ F, 10 volts, low-leakage elec-  
trolytic

IC1—555 timer  
IC2, IC3—7555 timer (CMOS version of 555)

D1-D4—1N4002

Q1,Q2—PN2222

S1—PC-mount, 3P3T

LED1-LED3—miniature red LED's

**Miscellaneous**—PC board, cabinet, knobs, machine screws, hookup wire, IC sockets, etc.

The following is available from NRG Electronics, P.O. Box 24138, Ft. Lauderdale, FL 33307; drilled and etched PC board, \$9.95; complete kit, \$29.95; wired and tested unit, \$49.95. Include \$1.50 to cover postage and handling and \$2.00 for C.O.D. orders.

You can easily build this energy-saving device by using a printed circuit board. A PC board isn't essential—point-to-point wiring can be used—but a board is recommended, if only for its neatness and ease of troubleshooting. A suitable foil pattern is shown in Fig. 2. To assemble the project, simply follow the parts-placement diagram of Fig. 3. However, if you plan to mount the board in a cabinet (and that's surely recommended), you should prepare the cabinet before you start soldering. You'll want to mark the locations of R1, S1, and the three LED's on the front panel. Then drill the front panel at those points to fit your components.

Make sure to use good quality rosin-core solder and a fine-tipped pencil-type soldering iron. Place and solder the resistors and diodes first followed by the IC sockets, capacitors and transistors. Be sure to observe polarity with the dipped tantalum and electrolytic capacitors, the transistors, and the diodes. Place and solder potentiometer R1 on the foil side of the PC board. Mount switch S1 on the component side of the PC board and solder. (Figure 4 shows the component side of the



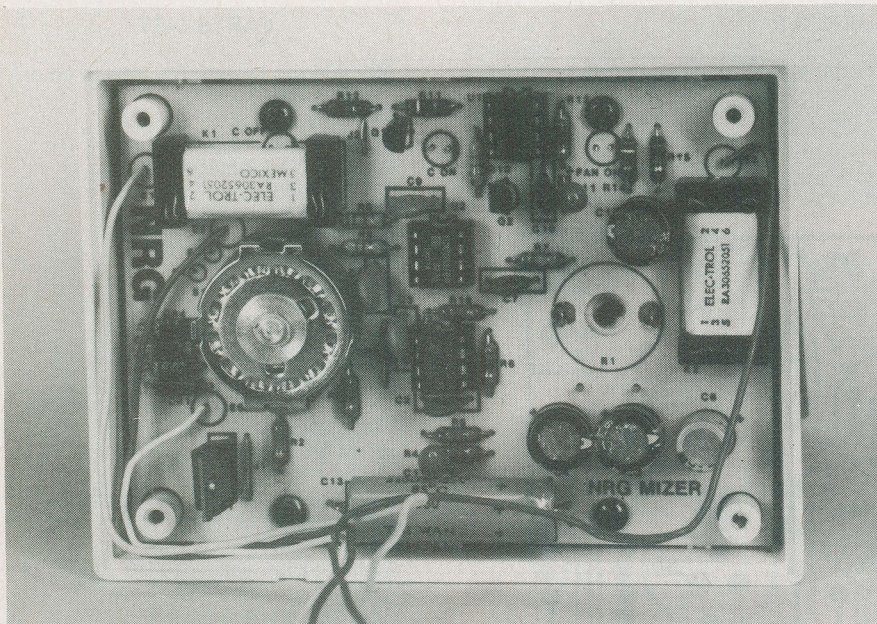


FIG. 4—COMPONENT SIDE. Although the unit is small (about 3×4 inches), the components aren't densely packed.



FIG. 5—USING A PLASTIC case for the project allows you to simply use double stick foam tape to mount it to the wall.

completely assembled PC board.) Next install the three LED's on the foil side of the PC board. Note that the LED's must be polarized correctly. Temporarily fit the PC assembly into the cabinet top and push the LED's into the holes in the cabinet. Clinch the LED leads and carefully remove the PC assembly from the cabinet and—without changing their adjustment—solder the LED leads to the foil. Relays can now be placed at RY1 and RY2 and soldered.

Use excess component leads as wire jumpers and solder at the locations marked "J" on the parts-placement diagram. Finally, install the four wires that

you'll use to hook up the device to your thermostat. The leads should be color-coded: The leads marked 1, 2, 3, and 4 on the schematic and parts-placement diagram should be red, white, green, and yellow respectively.

Before installing the unit, it's a good idea to check its operation. Let's now see how to go about doing that:

With controls R1 and S1 set at MIN and NORMAL, connect the red and white wires to an 18-24 volt AC or DC source. (If none is available, two 9-volt transistor radio batteries in series will suffice.) Switch to CYCLE 1 and note that the COMPRESSOR-ON lamp will light.

The proper LED-lighting sequence will start with COMPRESSOR ON, which will stay lit for between 5 and twenty minutes (depending on the setting of the COOLING-CYCLE control) That will be followed by the lighting of the FAN-ON LED for 2 minutes while at the same time "COMPRESSOR OFF" is lit for 15 minutes (in CYCLE 1) or 30 minutes (in CYCLE 2). After IC3 times out, the cycle will begin again when IC2 is triggered again. Remember that those times are approximate and will vary from unit to unit.

If that test shows that something is wrong, you can troubleshoot the unit by "manually triggering" its operating modes. Remove the integrated circuits and, with power applied, make the following jumps using fine gauge wire in the IC sockets. Jumpering IC2 pin 3 to IC2 pin 1, you can test the compressor-off operation and by jumpering IC2 pin 3 to IC2 pin 4, you can test compressor-on operation. To test fan-on operation, jumper IC1 pin 3 to IC1 pin 4.

### Installation

During installation, **remove power to the air conditioner at the circuit-breaker panel.** Install the device next to the thermostat. Double-stick foam tape will easily hold the unit on a wall as shown in Fig. 5. Remove the thermostat cover to expose the wire terminals on or behind the wall mounting plate. Cut the wires from the unit to a convenient length and make the connections to the thermostat indicated in Table 1. (It may be necessary to trim some plastic from the thermostat cover or base to allow for wire passage. Switch the "energy mizer" to NORMAL and restore power to the air conditioner. Set the air conditioner to "cool," and the fan to "auto" and set the thermostat high enough so that it does not come on. Set the "energy mizer" to MIN and CYCLE 1. When that's done, the air conditioner should come on and the COMPRESSOR-ON LED should light.

### Tips

The thermostat acts as a high limit and will override the device if the room temperature rises above the set temperature. When using the heat cycle, switch the "energy mizer" to NORMAL.

The CYCLE 2 mode provides an extended-off period (about 30 minutes) that is useful for unattended dwellings for humidity control. If the unit is set to MIN and CYCLE 2, the air conditioner compressor will run for 5 minutes followed by a 30 minute off period.

The most economical operation is achieved by setting the fan on auto rather than continuously on. The fan-on timer will keep the fan running for about two minutes after the compressor stops to purge cool air from the duct work and compressor coils.

R-E



## Tune Up Your MDS Downconverter

LEW G. SCHUWEILER

*Tuning microwave downconverters can be a real headache—but it doesn't have to be. We'll look at a way to get around some of the problems normally associated with that task.*

THE POPULARITY OF MICROWAVE DOWN-converters for use in receiving Multipoint Distribution Service (MDS) signals has grown enormously over the past couple of years. Check the classified section of any electronics magazine and it's sure to have advertisements for downconverter parts and kits. As a result, there are a growing number of kits and home-brew converters in the hands of electronics enthusiasts. The only problem is that once the kit is assembled, the builder is then faced with the awesome task of making sure that the circuit works properly. To understand the proper procedure for tuning and troubleshooting a receiver, it's best to review some background information about downconverter circuits first.

### The downconverter system

The main function of a downconverter is to convert microwave signals down to a frequency that's low enough to be received by your television set. As shown in Fig. 1, a typical downconverter consists of a microwave antenna, a mixer, a VCLO (Voltage-Controlled-Local-Oscillator), a variable power-supply, and an antenna





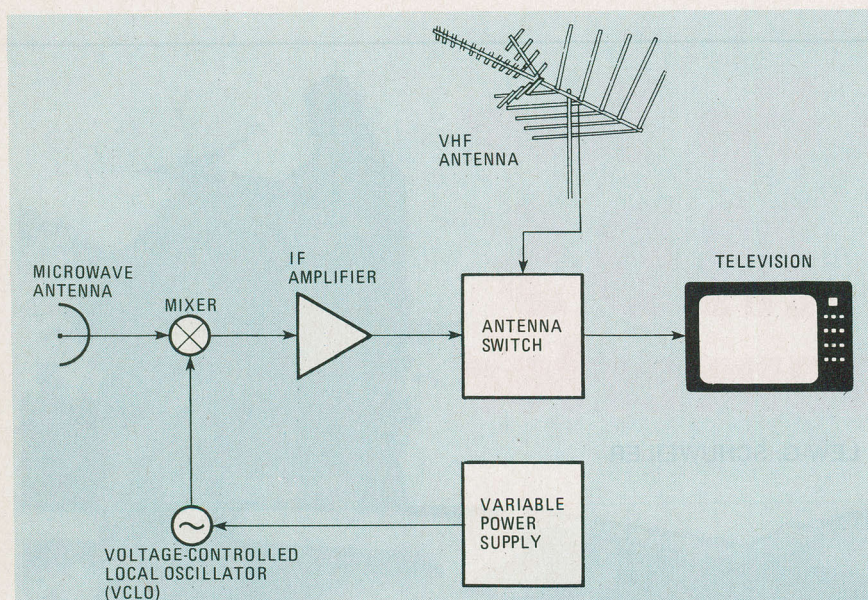


FIG. 1—BLOCK DIAGRAM of a microwave receiver system. The power supply and antenna switch are often enclosed in the same case.

switch. The incoming signal is received by the microwave antenna and fed to a twin-diode mixer. Essentially, what the mixer does is to double the frequency of the VCLO, and then output the difference between that frequency and the received microwave signal to the IF (Intermediate Frequency) amplifier. That output is usually equal to that of VHF Channel 3 (61.25 MHz). The IF amplifier boosts the signal to a usable level and feeds it to an antenna switch that's used to permit easy switching between the downconverter and the VHF antenna. The VCLO frequency is controlled by a variable power-supply. Adjusting the power-supply voltage causes the VCLO frequency to change, which in turn causes the output (IF) frequency to change. That allows you to fine-tune the downconverter, which can drift somewhat due to temperature changes.

### Checking basic circuit operation

After constructing the kit, follow the normal post-construction procedures, which includes making sure that all components are installed in the right position and properly soldered. When checking solder connections, be sure that there are no solder bridges, particularly between the power and ground traces. In addition, the circuit-board layout is critical to the performance of the converter. Board conductors or strip lines behave as inductors and capacitors—altering their size with excess solder changes their values and affects circuit performance.

Also, circuit components such as transistors, diodes, and chip capacitors should be handled with care because they're very fragile. For example, transistor leads can be easily broken off during handling, and chip capacitors can be

damaged by excessive heat in soldering—so be careful. Once you are convinced that you have made no construction errors, use a volt/ohm meter (VOM) to check the basic DC operation of the circuit.

When checking the basic operation of the circuit: Make sure that the power supply is operating properly by monitoring its output voltage and making sure that it swings several volts as the tuning knob is rotated back and forth. The next step is to connect the downconverter board to the power supply and place it in a position that allows you easy access to the circuit components. The position of the power-supply's tuning knob isn't important now. Apply power to the system and measure the base-to-emitter ( $V_{BE}$ ) voltage of each transistor with the VOM—it should be about 0.6 volt.

Figure 2 shows how to distinguish the transistor's collector from its base and emitter. For some transistors, the collector is indicated by the dot directly in front of it—the base is the lead directly across

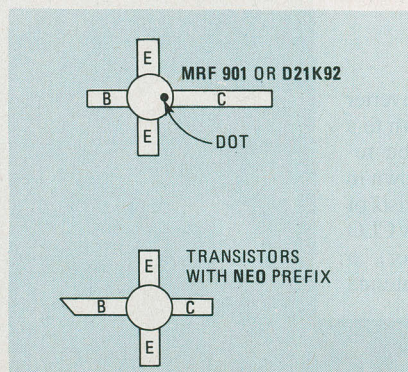


FIG. 2—ALMOST ALL RF transistors will identify their leads in one of these two ways.

from the collector, and the remaining two tabs are the emitter leads. Transistors with the prefix NEO are set up in much the same way, except that the base (instead of the collector) is designated by an angled lead.

If  $V_{BE}$  is zero or several volts, check the circuit again for bad solder connections, bridges, or missing components. If everything is soldered in properly but the voltages are incorrect, suspect a bad transistor. If everything thus far is working properly, use the VOM to check the collector-to-emitter voltage ( $V_{CE}$ ) of the transistors. (Refer again to Fig. 2 if necessary.) The collector-to-emitter voltage should be several volts lower than the power-supply voltage. To make the comparison between the two voltages, measure the supply voltage at the point where it enters the converter board and then measure the base-to-emitter voltages of each transistor. If the collector-to-emitter voltage of any transistor is the same as the power supply voltage, you could have an open collector in that transistor—therefore, it should be replaced. On the other hand, if  $V_{CE}$  is zero, the collector of the transistor could either be shorted to ground at some point on the circuit board, or the transistor may be shorted internally and therefore should be replaced. If the voltages are correct, the transistors are operating with the proper DC bias and the circuit is now ready for tuning.

### Tuning the downconverter

The normal tuning procedure is a hit-or-miss one, which involves a combination of lengthening or shortening a tuning conductor on the downconverter board and adjusting the variable power-supply.

Adjusting the power supply is no problem; but after each change in the length of the tuning conductor, the downconverter/antenna assembly must be placed in an area where it can receive microwave signals. That's necessary so that you can see whether the changes that you've made have done the trick.

Doing so can be particularly frustrating if you have to hoist the assembly up a 30-foot mast each time! Most people have line-of-sight view of the transmitter from their roof as they stand on it. Even with that ideal situation, a few problems can be encountered, such as having to run up and down a ladder each time you make a correction in the circuit.

To avoid that situation, you'll need a soldering iron on the roof and someone in the house watching the TV while you make the changes. Otherwise, you'll need the variable power-supply and a TV on the roof with you so that you can do it all yourself. Once the circuit is tuned, there's often trouble in positioning the antenna for maximum signal strength. Therefore, it's best not to even consider that problem at this point.



TABLE 1

Frequency—MHz	Use
1690 - 1700	Meteorological satellites
1691.0	GOES satellite
1694.5	METOSAT satellite
1700 - 1710	Space research
1710 - 1850	Government and armed forces
1990 - 2110	Studio-to-transmitter links; intercity relay
2130 - 2150	Point-to-point, fixed
2150 - 2180	Omnidirectional, fixed
2150 - 2156	MDS channel 1
2156 - 2160	MDS channel 2A
2156 - 2162	MDS channel 2
2180 - 2200	Point-to-point, fixed
2200 - 2290	Government and armed forces
2205	NASA space shuttle video
2215	NASA space shuttle video
2217.5	NASA space shuttle audio
2287.5	NASA place shuttle audio
2290 - 2300	Space research
2300 - 2450	Amateur radio operation
2304	Amateur DX
2375	Amateur television
2400 - 2450	Amateur FM repeaters
2450 - 2500	Radar
2500 - 2690	Instructional TV, fixed (ITFS)
2500 - 2506	ITFS ch. A1
2506 - 2512	ITFS ch. B1
2512 - 2518	ITFS ch. A2
2518 - 2524	ITFS ch. B2
2524 - 2530	ITFS ch. A3
2530 - 2536	ITFS ch. B3
2536 - 2542	ITFS ch. A4
2542 - 2548	ITFS ch. B4
2548 - 2554	ITFS ch. C1
2554 - 2560	ITFS ch. D1
2560 - 2566	ITFS ch. C2
2566 - 2572	ITFS ch. D2
2572 - 2578	ITFS ch. C3
2578 - 2584	ITFS ch. D3
2584 - 2590	ITFS ch. C4
2590 - 2596	ITFS ch. D4
2596 - 2602	ITFS ch. E1
2602 - 2608	ITFS ch. F1
2608 - 2614	ITFS ch. E2
2614 - 2620	ITFS ch. F2
2620 - 2626	ITFS ch. E3
2626 - 2632	ITFS ch. F3
2632 - 2638	ITFS ch. E4
2638 - 2644	ITFS ch. F4
2644 - 2650	ITFS ch. G1
2650 - 2656	Operational service, fixed
2656 - 2662	ITFS ch. G2
2662 - 2668	Operational service, fixed
2668 - 2674	ITFS ch. G3
2674 - 2680	Operational service, fixed
2680 - 2686	ITFS ch. G4

TABLE 2

UHF	Local	3rd harmonic	UHF	Local	3rd harmonic
Channel oscillator (MHz)		(MHz)	Channel oscillator (MHz)		(MHz)
14	517	1551	49	727	2181
15	523	1569	50	733	2199
16	529	1587	51	739	2217
17	535	1605	52	745	2235
18	541	1623	53	751	2253
19	547	1641	54	757	2271
20	553	1659	55	763	2289
21	559	1677	56	769	2307
22	565	1695	57	775	2325
23	571	1713	58	781	2343
24	577	1731	59	787	2361
25	583	1749	60	793	2379
26	589	1767	61	799	2397
27	595	1785	62	805	2415
28	601	1803	63	811	2433
29	607	1821	64	817	2451
30	613	1839	65	823	2469
31	619	1857	66	829	2487
32	625	1875	67	835	2505
33	631	1893	68	841	2523
34	637	1911	69	847	2541
35	643	1929	70	853	2559
36	649	1947	71	859	2577
37	655	1965	72	865	2595
38	661	1983	73	871	2613
39	667	2001	74	877	2631
40	673	2019	75	883	2649
41	679	2037	76	889	2667
42	685	2055	77	895	2685
43	691	2073	78	901	2703
44	697	2091	79	907	2721
45	703	2109	80	913	2739
46	709	2127	81	919	2757
47	715	2145	82	925	2775
48	721	2163	83	931	2793

### Tuning the easy way

There is an easier way to tune your downconverter. You'll need the downconverter along with its power supply, and two television sets. One TV set, which we'll call TV-1, will be used to view the microwave programming. The UHF tuner of the other set (TV-2) will be used as an artificial microwave-signal source. It contains a local oscillator operating at the chosen UHF channel frequency, plus the TV IF (45.75 MHz). TV-2's local oscillator provides enough energy at its third harmonic to serve as a microwave signal. (One of the \$69 black-and-white sets will work great.)

In building a downconverter kit, it is important to keep in mind the frequency at which the circuit will be operating. To do so, you must first decide which type microwave transmission you wish to receive, such as one of the NASA space-shuttle frequencies or perhaps one of the MDS channels. Table 1 is a listing of microwave-frequency allocations that can be used for that purpose. Also, whether one of the MDS channels or some other programming is desired, it will be necessary to decide which UHF channel will be used as a microwave-signal source—Table 2 is provided for that purpose. Let's look at an example of what we mean. Suppose, for instance, that you want to receive one of

the MDS channels, whose operating frequencies (as shown in Table 1) range between 2150 MHz and 2162 MHz. Selecting a midpoint frequency of 2156 MHz will be accurate enough for the purposes of this tuning procedure. (The reason for that will become more obvious in a moment.)

Now that you've chosen the microwave signal-source, refer to Table 2 to determine the UHF channel that TV-2 is to be tuned to. In the above example, we chose 2156 MHz as our center frequency, so we'll look for that frequency in Table 2 under the "3rd harmonic" heading. As you can see, the closest that we can come to that frequency is either 2145 MHz (Channel 47) or 2163 MHz (Channel 48). Let's use Channel 48. Note: Although this tuning exercise attempts to tune in the desired frequency with the variable power-supply tuned to its mid-voltage point, the converter's actual low-to-high voltage tuning range is extremely broad. Hence, the Channel 48 local-oscillator frequency is accurate enough. Now let's tune the converter by performing the following steps:

**1. Connect the equipment** as shown in Fig. 3. As you can see, TV-1 is connected to the output of the converter, while TV-2 is connected the antenna/downconverter terminal of the power supply through the feedhorn/downconverter assembly.



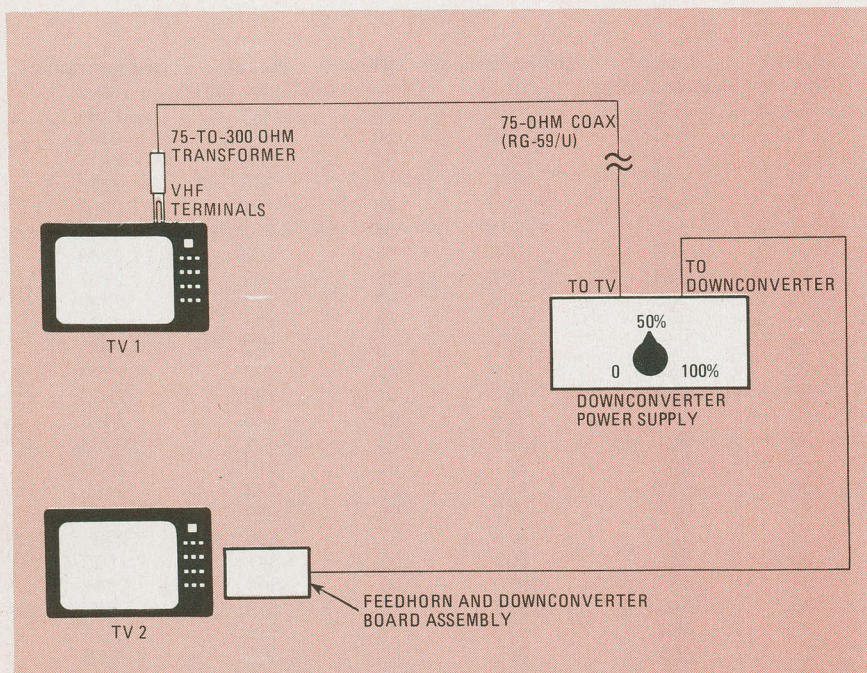


FIG. 3—TEST SETUP for tuning the downconverter. Here the feedhorn assembly is placed close to TV-2 to pick up the artificial microwave signal.

**2. Apply power to all equipment.**

**3. Turn TV-1 to the channel** to which the downconverter is to be tuned (2–6).

**4. Turn the UHF tuner of TV-2** to the channel chosen from Table 2 (in this case Channel 48). If that channel is an active channel in your area, be sure that there is no antenna connected to TV-2.

**5. Place the quarter-wavelength stub** or board dipole (antenna) as close as possible to the UHF tuner of TV-2 as shown. (It will probably not be necessary to disassemble the TV—a sufficiently strong signal will be radiated through the case.)

**6. Rotate the power-supply control** slowly back and forth while watching TV-1. If tuning is possible within the set voltage range, the TV screen will: a) go nearly or completely blank—raster with little or no snow; b) show streaks of color; or c) flicker. The TV's sound will: a) nearly or completely mute; b) buzz; or c) sound like a local radio-station or adjacent television-channel.

**7. If tuning is not achieved,** set the power supply to its mid-voltage range. Change the VHF tuner of TV-1 in either direction one channel at a time, while adjusting the power-supply voltage back and forth slightly for each channel. If tuning is achieved, proceed to step 10—if not, refer to steps 8 and 9.

**8. If tuning cannot be achieved,** check the component values of all passive components to see if they are correct and also make sure that they are not damaged. Capacitors can easily be checked for shorts; however, it's a little more difficult to check for open capacitors. Using the highest resistance scale on your meter, carefully observe the meter for a slight

deflection just as you touch the test probes to the capacitor leads. If there is no deflection replace that component.

**9. The final items to be checked** if tuning cannot be achieved are the diodes. To do so, first remove the diodes from the circuit board. Then using the lowest resistance-range on the VOM, connect each diode (one at a time) to your test probes facing in one direction—all anodes to either the black or red lead. Then reverse the leads and check them again. (The anode can be distinguished from the cathode by the stripe at the cathode end.) With the stripe facing in one direction, the diodes should have a low resistance and in the other a high resistance. Replace any defective component, then repeat steps 4 through 8.

**10. Once tuning is achieved,** set the power supply control to its mid-voltage range and again set TV-2 to the appropriate channel (48 in our example). Add solder to or remove trace material from the tuning conductor on the downconverter circuit board until the converter is tuned. (The tuning conductor is a short length of wire or slug on the converter board.) That gives you the greatest tuning range, so that if the oscillator drifts because of temperature changes you can fine-tune the converter. That concludes the tuning procedure.

### Summary

This article has described a simple tuning procedure for microwave downconverters. It can be seen that several unnecessary headaches can be avoided by simply following good soldering and wiring practices beforehand. The job is much

### WHAT IS MDS?

MDS, an acronym for Multipoint Distribution Service, is a local microwave television service. MDS operators are authorized to use microwave frequencies for data communications or television programming within a community.

There are two MDS channels—2150–2156 and 2165–2162 MHz. There is also provision for channel to transmit information from an MDS subscriber's home to the operator, thus leaving open the possibility of an interactive service.

The MDS signal is transmitted in the standard NTSC format but with some differences. The transmission passband is inverted, with the result being lower vestigial-sideband video with the audio carrier being located 4.5 MHz below the video carrier, which in turn is located 1.25 MHz below the top band-edge. That scheme is a mirror image of a standard TV broadcast. The audio and video thus must be inverted by the downconverter before being fed to a TV receiver.

These days, the primary use for MDS is for distribution of pay-TV programming. MDS operates line-of-sight, with only paying subscribers authorized to receive the transmissions. MDS subscription costs are generally lower than other over-the-air forms of pay-TV (i.e. UHF-TV) because the operator's outlay is generally lower. The reason for the lower cost is that an MDS transmitter outputs only a fraction of the power of a UHF pay-TV station—10 to 100 watts as compared to hundreds of thousands of watts.

Because of that, and other cost-related reasons, MDS has become extremely popular. MDS common-carriers lease their transmission facilities to pay-TV programmers in most major markets around the country. Most MDS systems boast between 10,000 and 30,000 subscribers, each paying between \$15 and \$25 a month for the service.

The FCC does not consider MDS to be a broadcasting service. It instead considers it to be a common carrier and thus the frequencies it uses are not public. Because, in part, of that interpretation, MDS operators have successfully prosecuted manufacturers, sellers, and users of unauthorized reception equipment.

easier if troubleshooting requirements are kept to a minimum. Also, an important point to note about the procedure is that it can be used for any microwave frequency you choose. In addition, an antenna rotor, such as that available from Radio Shack, mounted with your microwave antenna could be helpful in some cases.

Depending on your location, it might be very interesting to experiment with your downconverter by tuning it to receive things like television studio-to-transmitter links, university instructional TV, or (of course) amateur broadcasts. In any event, it opens up several doors for the inventive microwave experimenter. **R-E**



# HOW TO

# REPAIR

## PC BOARDS

*Here are some techniques that can help you rescue that "ruined" board*

**ROBERT GROSSBLATT**

THOSE WHO MAKE THEIR OWN PRINTED-circuit boards know that it's a detailed and painstaking process. It's not hard—just detailed and painstaking. And, as everyone knows, the effects of Murphy's Law are directly proportional to the number of steps in the procedure. Fortunately, printed-circuit boards are one of the few electronics components that can be easily repaired. You can't repair the substrate in an IC and replacing the electrolyte in a capacitor is difficult—even if you use special tools. You can, however, easily correct various PC-board foulups.


If we approach the problem logically, it's immediately obvious that there are really only two things that can possibly go wrong with a board:

1. There's copper where there should not be.

2. There's no copper where there should be.

Basically, those problems are the result of either a bad etch or a bad layout.

In the case of a bad etch, before any repair is attempted, you have to ask yourself if it is worth the trouble. A simple repair to a trace on the board is fairly easy to do, but trying to correct catastrophic problems is, quite frankly, more trouble than it's worth. There's no hard and fast rule to help you decide whether or not your board is beyond salvage. If you have vast areas of unetched copper (see Fig. 1) or your traces are hair-thin and grainy looking (see Fig. 2), the board should probably be considered a write-off. If, on the other hand, things aren't that bad and the board is complex and difficult to produce, you're probably looking at a good

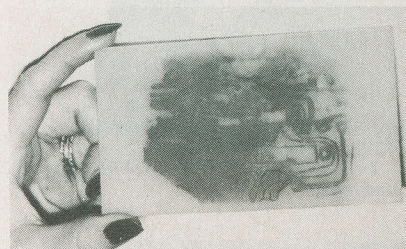

**FIG. 1—AN UNDERETCHED BOARD that is beyond repair**

candidate for a repair.

### Removing excess copper

Removing excess copper is a straightforward operation. If there are a lot of small pieces of copper left on the board between the traces you'll have to cut them out using an X-acto knife. Make sure the



blade is sharp, because the copper, even though soft, is still difficult to cut. If you've got a lot of copper to remove, make sure you have a good supply of blades on hand because the edge won't last too long. Remember that you'll be cutting through the copper and into the board material itself. Glass epoxy is hard stuff. If the board material is phenolic your blade will last a little longer but will still dull out pretty quickly.

Cut through the unwanted copper bridge on both sides and carefully lift it up by working the tip of the blade under the corner of the copper at the cut as shown in Fig. 3. Once you lift the corner, you'll find that the copper will peel off the board easily. Make sure you get all the copper off the board—a small piece of loose copper can cause all sorts of terrible problems later on. Longer traces can be removed the same way—just cut them at the ends and peel them off the board.

If you've got large areas of unwanted copper on your board, resist the temptation to remove all of it. Not only do you run the risk of damaging the board, but unconnected copper can come in very handy for all those brilliant last-minute variations that you just have to add to the circuit. And, if all those reasons aren't enough, remember that it's always wiser to *leave well enough alone*. If the excess copper isn't hurting anything, isolate it from the rest of the layout and forget about it. Take your X-acto knife and cut away the traces that connect the unwanted plane of copper to the rest of the foil. Flick the bridges off the board and go on to more important things.

If you feel that you *absolutely* have to get rid of large areas, there are two options—grinding and etching. Large areas of copper that can be easily isolated on the board can be etched away. It's simply a

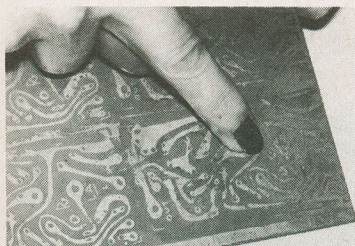


FIG. 2—AN OVERETCHED BOARD that is beyond repair.

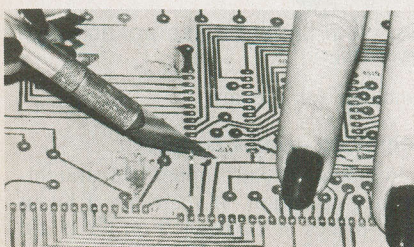


FIG. 3—TO REMOVE AN UNWANTED TRACE, cut it and lift a corner of the copper at the cut.

matter of covering the areas of the board you want to protect with waterproof tape, steel-wooling the areas you want to get rid of, and dumping the board back into the etchant. The only important thing to remember here is to make sure that the tape you use is *waterproof*. If it's not, you can be sure that your etchant—and that holds true for all of them from ferric chloride to ammonium persulphate—will ooze its way through the tape with predictable results.

The best tape to use is that thin plastic packing tape—the kind that can be only cut with a knife. Don't use the tape that has the nylon cords running through it because you can't completely smooth it out on the board. Lay the tape on the board, overlap it at the edges, and rub it to get rid of the air bubbles (see Fig. 4). Take your X-acto knife and cut away the tape wherever you want to remove the copper (see Fig. 5). You can also paint lacquer over the areas you want to protect—that works just as well but it takes a lot longer. If you're anything like the author, the necessity of having to go back and correct mistakes makes you frustrated and impatient. You want *immediate* results. The half hour or so that it takes for the lacquer to dry is just too long—if it only took five minutes it would still be too long. If you do go that route, however, make sure and use a lacquer with a color. Clear lacquer is nice but you can't always be sure which areas are covered—especially when the board is in the etchant. It is the understatement of all time to say that it's disheartening to make a mistake correcting a mistake.

The second way to get rid of copper is to grind it off. It's mentioned here only to give us the opportunity to tell you to avoid it completely. I know it's possible to put a grinding wheel on a small hand tool and pulverize veritable oceans of copper—not only is it fast but it's nice to let electricity do the work. However, *avoid* the temptation to do that! Besides having the board look terrible when you finish (sometimes an important consideration), one slip and you'll grind right through the board itself (always an important consideration).

### Replacing copper

Missing copper is a much easier problem to handle. Once again you have to decide whether or not the repairs are worth the trouble. An etch that leaves you with just the ghostly remains of your foil pattern is beyond hope. The same goes for a board that is criss-crossed with cut traces and has doughnuts that are measurable only in angstroms.

There's more at stake here than whether or not two points on the board are connected by copper. The thinner the trace gets, the less current it can handle. If you've got components on the board that use a lot of current, the thickness of the

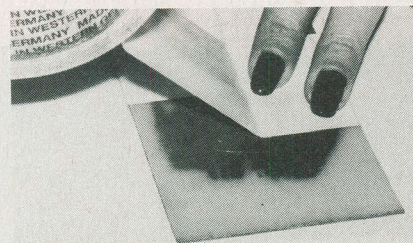


FIG. 4—TO REMOVE LARGE AREAS of unwanted copper, first cover the board with waterproof tape.

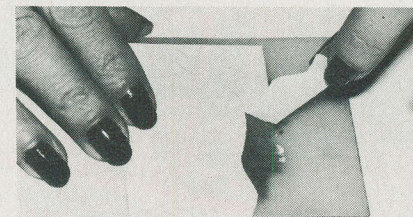


FIG. 5—ONCE THE BOARD is completely covered, use an X-acto knife to remove the tape over the areas you want to re-etch.

trace is one of the things you should have had in mind when you did the layout for the foil pattern. It's always a touchy thing to route relatively serious amounts of current through thin traces. Assuming the copper doesn't burn up (extreme case), it's at least going to get hot (usual case). And when heat rears its ugly head all kinds of nastiness can follow. The conductance of the copper can change and lead to some oscillation and/or other similar nightmares. Linear and TTL circuits draw relatively heavy amounts of current in spurts and those spikes are potential sources of trouble. Thin traces can lead to audio clipping, false triggering, and a whole host of other equally disturbing phenomena—all directly because of current starvation.

When those things occur, the last thing you'll suspect is the traces on the board. Many a board has been ripped apart and many a component has been substituted for over and over before the real source of the problem was found. The moral here is that the problems that can come from thin traces often masquerade as faults in design—you can waste a lot of valuable bench time tracking down the real source of the trouble.

Before ending this soliloquy on the evils of thin traces, there's one more thing you should be aware of. Thin traces can generate heat—and heat can weaken the bond between the copper and the board. And, as we said before, loose copper can do a lot of damage to costly components.

Probably the easiest and most direct way to repair a damaged trace is to solder a piece of wire to the board. You just take a length of wire of the correct thickness and use it to jump the gap in the foil. There are, however, rules that should be followed:



1. Never use uninsulated wire.
2. Never tack solder directly to the foil.
3. Never leave slack in the wire.

Let's take these rules one at a time.

Using uninsulated wire is just asking for trouble. If the foil density of your board is high, it will only take a small shift in the wire's position to short it to another trace. Hook-up wire and cut-off component legs are always lying around your bench but try to avoid using them. It makes a lot more sense to keep a small spool of insulated wire handy just for making repairs to your board. Cut off the length you need and strip the insulation from the ends. If you're using multi-stranded wire, make sure you tin the ends before you solder it to the board. Loose strands of wire are as dangerous as loose bits of copper.

That brings us to our second rule. If you tack solder directly to the foil, you'll be depending on the foil for strength. Just one inadvertent tug on the wire and—you guessed it—the foil is going to lift off the board as shown in Fig. 6 and cause what is referred to in the technical journals as a big problem. The strength in a printed-circuit board comes from the base material, not the foil. Always drill holes for the ends of the wire, regardless of whether your jumper is going to be on the foil or component side of the board. If you put the jumper on the component side treat it like any other component. Put the ends through the holes in the board and solder them to the foil. If you can't drill holes directly through the foil, (if the trace is too thin, for example), locate the holes right next to the trace and bend the ends of the wire over the foil. If your wire has to go on the foil side, drill the holes and let the ends of the wire poke through to the component side. The repair won't be as solid but it will still be better than just tack soldering. Bend the ends of the wire flat against the component side of the board and put a blob of solder on them making sure that it is slightly larger than the hole (see Fig. 7). That jury-rigged strain relief may look strange but it only has to work once to prove its worth.

The most carefully made repair is wasted if you don't pay attention to the third rule. Loose wire will always get snagged on something. If you're lucky, and you've led a good life, *only* the wire will pull loose. More likely, the foil will pull off the board and generate an unnecessary number of gray hairs on your head. If your wire is running on the component side of the board that will be less of a problem, but it's still good practice to make the wire only long enough to span the distance between the two holes. Don't use the same "right angle" principle for the jumpers that you did when you originally laid out the foil pattern. There's absolutely no way the wire repair is going to look as neat as an unbroken trace, so go

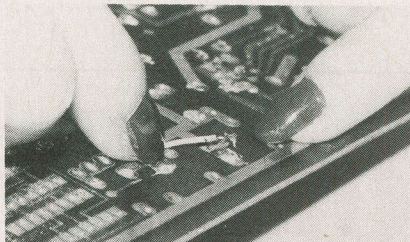


FIG. 6—IF YOU MAKE YOUR REPAIRS by tack soldering wire, lifted foil is likely to be the result.

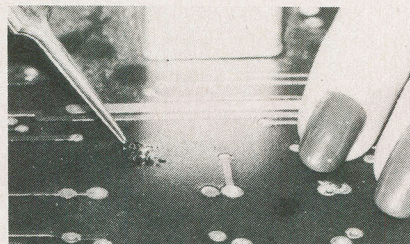


FIG. 7—MAKING A JURY-RIGGED strain relief using solder.



FIG. 8—USE NAIL POLISH to secure the wire to the board. It works better than any glue we've tried.

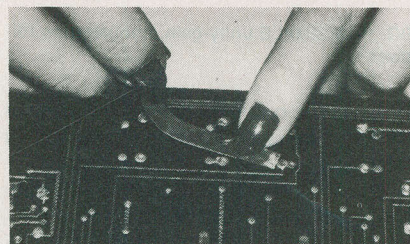


FIG. 9—USING SELF-ADHESIVE copper foil to make a repair.



FIG. 10—SILVER PAINT, though expensive, is excellent for repairing hairline cracks in traces.

directly from point A to point B.

After you've made the repair, make things even better by securing the wire to the board. The best way to do this is with clear nail polish (see Fig. 8). All the glues we've tried—from two-part epoxy to the cyanoacrylate super glues—don't seem to adhere well to glass-epoxy board. It might

be a different story with phenolic board, but we don't use it. The nail polish is strong enough to hold the wire securely to the board but can still be easily removed if you want to make a change later on. Just use a few drops at various points along the length of the wire to keep it from flopping around. Make sure you put some on the solder where the wire is connected to the foil. Since it's the weakest part of the repair, it needs the most help.

There are several alternatives to wire when you have to add copper to the board. For one reason or another they're not as attractive a choice as wire.

Some manufacturers make copper foil sheets with an adhesive back. You just cut out the shape you need with an X-acto knife, peel off the paper covering the adhesive on the back, and stick it on the board as shown in Fig. 9. That stuff is really dynamite when you need large areas of copper added to the board but it's difficult to cut out a replacement for a convoluted trace, and more difficult yet if you have to cut out something that's only a sixteenth of an inch thick. Another disadvantage of that method is that the foil doesn't adhere well to an uneven surface. If you do use that stuff to repair your board, don't rely on the adhesive—when your repair is finished, put a few drops of nail polish along its length to hold it to the board. That is really important if the copper is going to handle enough current to warm it up. If you've got a smooth surface, copper foil is a reasonable way to make a repair. If you have to add large planes of copper, it's the only way to make a repair.

Silver paint is a super way to repair hairline breaks in traces (see Fig. 10). If there's room to maneuver on your board, you can also use it to draw in a missing trace. Using it is simplicity itself—you apply it with a thin brush and carefully draw in the traces that are missing or over the ones that are broken. If you happen to slop a bit onto a neighboring trace, it can easily be scraped off when the paint dries. You can repair traces as thin as your artistic ability permits. If your hand is steady enough to follow the serpentine meanderings of a trace, silver paint is the method to use. When it dries it's almost as conductive as the copper it's replacing and you don't have to worry about it getting loose on the board. Now that we've told you why it's so wonderful, we'll tell you why it's not.

To start off with, you can't solder to it and it can't handle as much current as the copper it's replacing. Remember that copper foil comes in different thicknesses—the thicker the copper, the more current it can handle. Traces made from silver paint are thin—certainly much thinner than the copper. You could keep adding layers of silver paint, but that

*continued on page 81*



# CIRCUITS

# DESIGNING WITH LINEAR IC'S

This month, we look at the noninverting follower and some op-amp applications.

JOSEPH J. CARR

**Part 3** SO FAR IN THIS SERIES we have introduced you to the basic op-amp, the inverting follower, and some of the more common problems associated with op-amp circuits. This month, we will consider the noninverting follower and look at some applications for op-amps in AC circuits.

## Noninverting follower

The inverting follower has one serious drawback—low input-impedance. Since the noninverting input is grounded, the summing junction (the junction of the feedback resistor, input resistor, and the op-amp inverting input) will also be at ground potential. The input impedance is therefore limited to the value of the input resistor. Since input bias currents effectively limit the maximum value of the resistor, they also limit the input impedance. The input impedance of an inverting follower rarely exceeds 1 megohm, with 10 kilohms much more common.

The solution is to turn to the noninverting follower configuration. In that type of circuit, the signal is applied to the noninverting input, so the output will be in phase with the input. The extremely high input impedance of the op-amp (as high as  $10^{12}$  ohms) makes the impedance seen by the signal source equally high.

A simple noninverting follower is shown in Fig. 1. That circuit is called a unity-gain noninverting follower. The output signal is fed back directly to the inverting input. The voltage gain of the circuit, as its name implies, is unity.

The properties of the unity-gain circuit are: extremely high input-impedance, low output-impedance, and a voltage gain of one. Since the output impedance,  $Z_O$ , is

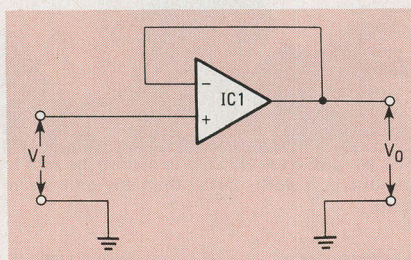


FIG. 1—A SIMPLE unity-gain, noninverting follower.

low, and the output voltage is the same as the input voltage, the power gain is greater than one.

The unity-gain noninverting follower has at least two main applications: buffering and impedance transformation. A buffer is an amplifier whose job is to isolate an electronic circuit from its load. An oscillator, for example, may use an output buffer to prevent frequency shifts caused by changing load impedances. Often, op-amp-based instruments will use a unity-gain buffer as a matter of good design, so that external factors will not affect the circuit as much.

As for impedance transformation, since the input impedance is very high, and the output impedance is very low, the unity-gain noninverting follower is a high-to-low-impedance converter.

A noninverting follower with gain is shown in Fig. 2. In that circuit, the signal is applied directly to the noninverting input of the op-amp. We must, therefore, treat the inverting input as if it were also at  $V_I$ .

The feedback network is the same as for the inverting follower (see part two of this series in the May 1984 issue of **Radio-**

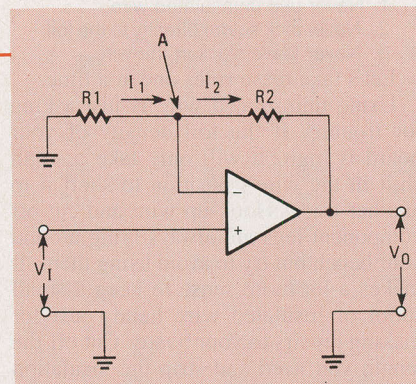


FIG. 2—A NONINVERTING FOLLOWER with gain. If the desired amount of gain is known, the values of  $R_1$  and  $R_2$  can be found through using equation 7.

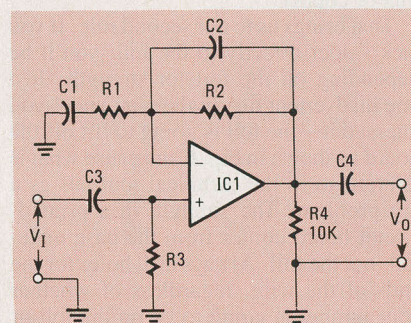


FIG. 3—FOR AC APPLICATIONS, this noninverting follower with gain circuit can be used.

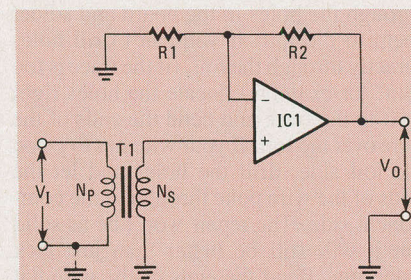


FIG. 4—THIS AC AMPLIFIER provides no frequency shaping, but it can be combined with the circuit that is shown in Fig. 3 if some shaping is desired.

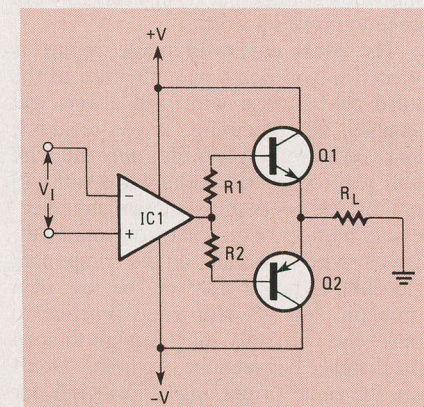


FIG. 5—WHEN AN OP-AMP must drive a load such as a loudspeaker, some means of boosting output power, such as using a complementary symmetry transistor amplifier, is required.



**Electronics**), except that the "input" side of R1 is grounded. As before, Kirchoff's Current Law (KCL) requires that:

$$I_1 = I_2 \quad (1)$$

by ohms Law,

$$I_1 = V_i/R_1 \quad (2)$$

and,

$$I_2 = \frac{V_o - V_i}{R_2} \quad (3)$$

Substituting equation 2 into 3:

$$\frac{V_i}{R_1} = \frac{V_o - V_i}{R_2} \quad (4)$$

Solving for  $V_o$ :

$$V_o = \frac{V_i R_2}{R_1} + V_i \quad (5)$$

$$V_o = V_i \left( \frac{R_2}{R_1} + 1 \right) \quad (6)$$

Equation 6 is the transfer function for the noninverting follower with gain, and should be committed to memory; the actual gain portion of the equation is:

$$A_v = \frac{R_2}{R_1} + 1 \quad (7)$$

We can use equation 7 to set resistor values. That's because that equation can be rewritten so that it can be used to find the values of R2 and R1 required for a specified gain. Since we can pretty much set the value of R1 arbitrarily (although the value of that resistor is usually between 100 ohms and 10 kilohms), we should solve for the value of R2:

$$R_2 = R_1 (A_v - 1) \quad (8)$$

One constraint that we should remember is that non-standard value resistors are difficult to come by. We should not, for instance, count too much on obtaining a 29002-ohm unit. The easiest way to proceed, then, is by trial and error, reworking equation 8 several times, using standard values for R1, until a standard-valued R2 is also found. Sometimes, a given gain requirement will not result in a pair of standard values for the two resistors. In that case, a variable resistor, a parallel or

series combination of standard-valued resistors that yields the calculated value, or the standard-valued resistor that comes closest to the calculated value, can be used.

If the project has more than one stage, there is another alternative. The total gain is the product of the gains of the individual stages. That means we can work with all of the resistor values in all of the stages until we find a combination that gives us the proper total gain using only standard-valued resistors. There, of course, is no guarantee that such a combination exists, but it is likely that after a bit of searching one can be found.

Like the unity-gain circuit, the noninverting follower with gain circuit will provide buffering and impedance transformation, but also (as its name implies), voltage gain. A noninverting follower with gain circuit, for use in AC applications, is shown in Fig. 3. Note that while four capacitors are used there, one or more of them can, in some cases, be deleted.

Some low-frequency response shaping is performed by capacitors C1 and C3, while high-frequency shaping is done by C2. In all cases, the -3-dB breakpoint is given by equation 9 below (note that that equation is given here in its general form), and the response falls off at a rate of about -6-dB-per octave.

$$f = \frac{1}{2\pi RC} \quad (9)$$

Another AC amplifier is shown in Fig. 4. That circuit provides no frequency shaping, but it can be combined with the circuit of Fig. 3 if some is needed. The gain of this stage must account for the voltage transformation of T1. The gain of the stage is then

$$A_v = \left( \frac{R_2}{R_1} + 1 \right) \left( \frac{N_s}{N_p} \right) \quad (10)$$

where  $N_p$  is the number of turns in the primary,  $N_s$  is the number of turns in the secondary, and all other terms are as defined before.

Here, we can manipulate the transformer's turns ratio as well as the values of the resistors to get the gain we need. Be aware, however, that the turns ratio is multiplicative, so gains get high in a hurry as the turns ratio gets higher. That situation can lead to saturation of the amplifier. If we have a gain of two in the op-amp, and a

turns ratio of 10:1, then the overall gain is 100. That is fine, provided that the input-signal amplitudes are small enough. Applying a 1-volt peak signal to the input will cause the amplifier to try outputting 100-volts of signal, which is clearly impossible on a  $\pm 15$ -volt power supply.

## Power amplifiers

Operational amplifiers do not usually produce much output power, usually less than 100 milliwatts. When it is necessary to drive a load such as a loudspeaker, then some means of boosting the output power must be found.

One traditional solution is shown in Fig. 5. In that figure, we see a complementary symmetry transistor amplifier being directly driven by an operational amplifier. That power amplifier operates in class B, which means that each transistor conducts over just one-half of the cycle.


The complementary symmetry class-B amplifier works because of the relative natures of NPN and PNP transistors. An NPN transistor turns on harder as the base is made more positive than the emitter, while a PNP transistor turns on harder as the base is made more negative than the emitter. In other words, the NPN device turns on during the positive half-cycle while the PNP one turns on during the negative half-cycle. Thus the bases of the two devices must be connected in parallel.

A major problem with the circuit shown in Fig. 5 is the need for external discrete components (i.e. the transistors), which take up space. In addition, the circuit will not work well without other components to eliminate crossover distortion. Sometimes, the most practical solution is to use a special IC power amplifier. Some of those are special audio devices, while others are merely power op-amps and may be used in a number of applications.


There are a number of special power IC's on the market, so we will pick only one, National Semiconductor's LM379. That 14-pin device can output up to 6 watts-per-channel. The LM379 contains two amplifiers, so it can be used in stereo designs.

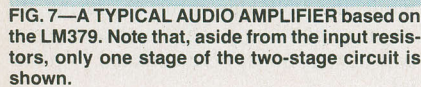A block diagram of the LM379 is shown in Fig. 6. Note that that device has only one power terminal ( $V_{CC}$ ), so that it is not technically an op-amp. Nonetheless, the device behaves like an op-amp and is as simple to use.






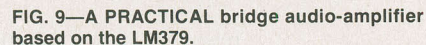Let's first consider the half-bridge case; that uses a normal totem-pole amplifier (here Q1/Q2). In a totem-pole amplifier, the two output transistors are connected in series across the power supply, and the load (the loudspeaker) is connected to the



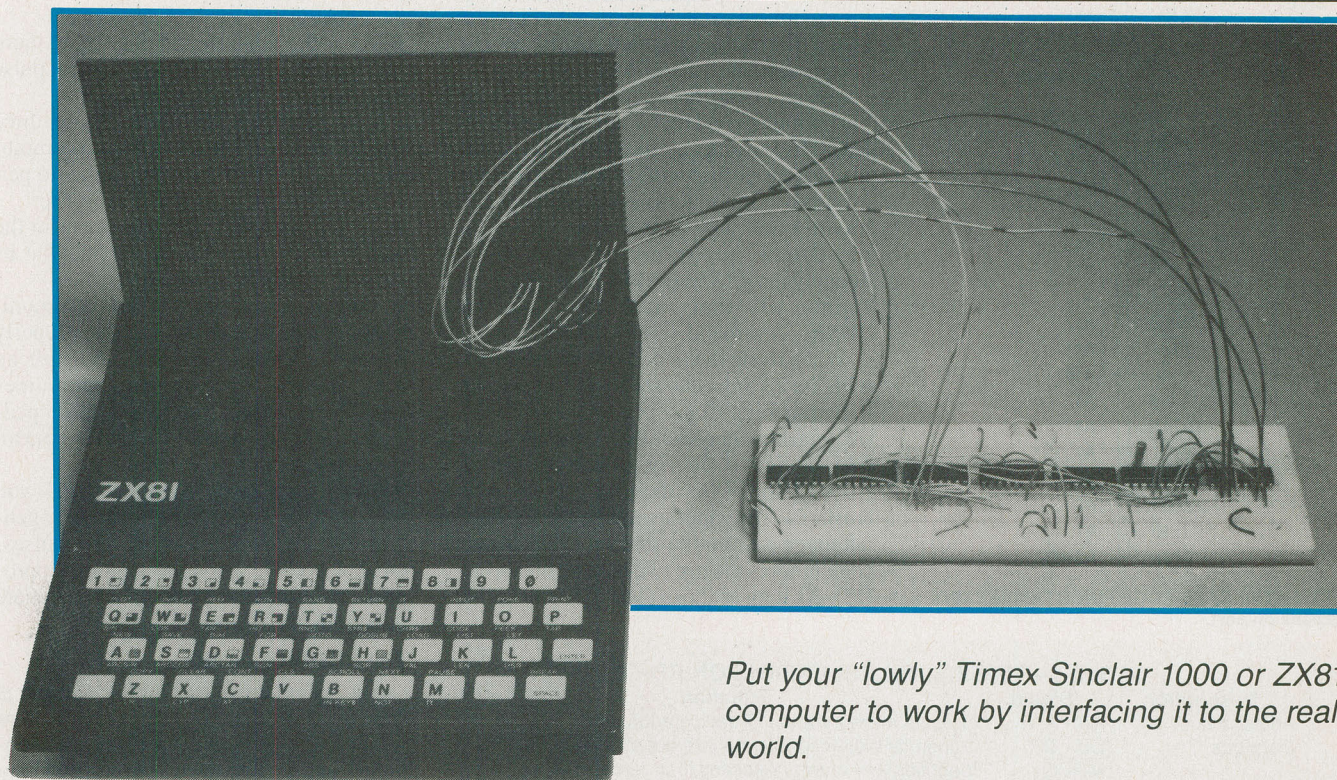In the next part of this series we will turn our attention to the DC differential amplifier. **R-E**





*Put your "lowly" Timex Sinclair 1000 or ZX81 computer to work by interfacing it to the real world.*

## Interfacing the ZX81

NEIL BUNGARD

THE SINCLAIR ZX81 (OR TIMEX SINCLAIR 1000) was the first computer to be sold for less than \$100. It was quite a bargain at that price. Perhaps you're one of the many people who bought one so that you (or your kids) could learn something about computers. Or perhaps you've seen the computer on sale for a very attractive price and have only recently considered buying it just to see what it was like.

If you did buy the machine when it first became available, you may have outgrown it by now. After all, it's not the most practical computer available. Some of its problems—including its membrane keyboard and wobbling 16K RAM extension—can make using the computer almost a chore.

However, the ZX81 is unbeatable for the hobbyist who wants to experiment—as we will do—with computers, computer interfacing, and Z80 machine language. And now that the computer is no longer being produced, you can often find it selling for as little as \$30 (and maybe even less).

Let us note that for the remainder of the

article, we'll refer to the Timex-Sinclair 1000 as the ZX81, if for no other reason than because it's shorter. There is little difference between the two machines, save that the 1000 has 2K of built-in RAM as compared to the ZX81's 1K.

### What we'll do

In this article, we'll show you how to interface the ZX81 to a clock/calendar integrated circuit, a temperature indicator, a light controller, and a heater controller. You might find use for such devices in photographic dark rooms, home weather stations, and home security systems.

In addition to interfacing those special devices to the ZX81, hardware and software interfacing principles will be covered in general. That means that you can make use of the inexpensive ZX81 for any particular monitor or control application that you have in mind—you won't be limited to the specific applications that we'll discuss. It's true that we won't end up with something as elegant as the home-control computer that was presented in **Radio-Electronics** in April through June. But we will have something to quiet the people who scoff at the ZX81 and call it a useless machine.

Using a computer for monitoring and control has become much simpler than it once was because of the number of interesting microprocessor-compatible integrated-circuits now available. For example, we'll be using OKI's MSM5832 clock/calendar integrated-circuit (IC).

### Where to begin

You will, of course, need a ZX81 computer and a TV. You should also have a standard cassette-tape player so that you can store your programs. You might also consider building the 8K non-volatile RAM accessory that was described in the July and August 1983 issues of **Radio-Electronics**. It makes storing and using machine code much more convenient.

On the back of the ZX81 is a card-edge with 44 "fingers." That gives you access to (for all practical purposes) all of the pins of the Z80 microprocessor. Figure 1 shows the pinout of the card edge, while the signals and functions are listed in Table 1. When you interface to the port, you are essentially interfacing directly to the Z80 CPU. To get the most out of the project, you might consider obtaining a Z80 technical manual and other reference material relating to the Z80.



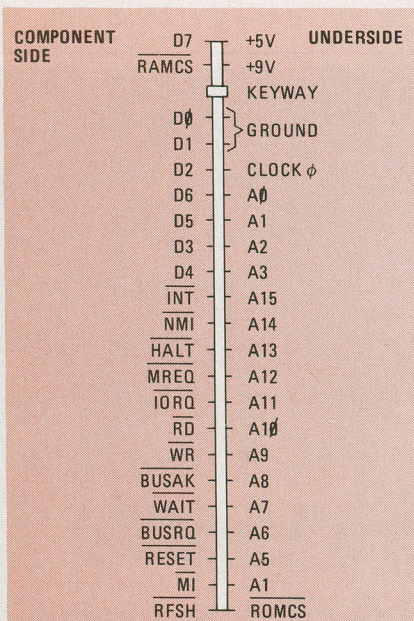


FIG. 1—THE CARD-EDGE PINOUT of the ZX81's expansion port.

TABLE 1—TIMEX/SINCLAIR EXPANSION PORT

Description	Signal	Function
Address bus	A0 - A15	Outputs memory and I/O device addresses
Data bus	D0 - D7	Transmits bidirectional data into/out of CPU
	MREQ	Identifies any memory-access in progress
	IORQ	Identifies any I/O operation in progress
	RD	Indicates that the CPU wants to read data
System control	WR	Indicates that the CPU wants to output (write) data
	MI	Identifies the op-code fetch cycle of instruction
	RFSH	Also used with IORQ to acknowledge interrupt
System clock	φ	Synchronizes dynamic-memory refresh
	RESET	3.25 MHz clock (output)
	INT	Resets CPU when pulled low
CPU control	NMI	Interrupt request input
	WAIT	Interrupt request input; cannot be disabled
	HALT	Initiates wait state in machine cycle
Bus control	BUSRQ	Indicates CPU has executed a HALT instruction
	BUSAK	Request to CPU for control
RAM/ROM select	RAMCS	Acknowledgement of release of control by CPU
	ROMCS	If pulled high will disable computer's on board RAM
Power	+9V	If pulled high will disable computer's ROM
	+5V	Unregulated
	GROUND	Regulated

## Interfacing principles

The procedures for interfacing to a microcomputer are relatively straightforward. Once you learn the techniques, you'll be able to apply what you learn here to other computers. However, the ZX81 has some unique idiosyncrasies that can give you a real headache unless you are forewarned. We will list those idiosyncrasies now for those that have done some microprocessor interfacing. If you don't understand them now, don't worry—we'll explain later them in more detail when we review general interfacing principles.

The first thing that makes interfacing with the ZX81 not as straightforward as interfacing with just the Z80 CPU is that the ZX81 does not use absolute address decoding in its memory scheme. Con-

sequently doing any type of memory-mapped input/output (I/O) is practically impossible. That leaves you with only the Z80's IN and OUT instructions for getting peripheral data in and out of the microcomputer. Unfortunately, the ZX81 does not include IN and OUT commands with its BASIC language instructions. That means that all I/O will have to be accomplished from machine-language subroutines that will be incorporated within the BASIC program you write. Fortunately the ZX81's BASIC language does supply you that capability with the "USR" command.

When using the IN and OUT instructions with the ZX81, some strange things occur in two specific situations: 1) if you use the OUT machine language instruction with an odd device code (in other words, if A0 = 1), the ZX81 monitor system will crash. 2) Any input using the IN machine language instruction and an even device code ignores the top two data bits (D6 and D7). As long as those characteristics (that

are unique to the ZX81) are known, they can be circumvented. They will not be a problem for our applications. If one is not aware of those characteristics, however, they can be maddening and take weeks to figure out.

## Interfacing basics

Interfacing to a microcomputer can be analogous to tossing a baseball. If you try to catch the ball before it is within your reach—or after it has gone past—you will miss it. Data moving in and out of the microprocessor works much the same way. When the microprocessor wishes to input or output data, it always does three operations:

- It places the address of the device with which it wishes to communicate on the eight lower bits of the address bus.

- It places the data it wishes to send to (or receive from) the external device on the data bus.

- After the address and data buses have had time to settle, it sends a control pulse to initiate the data transfer.

The microprocessor does those three operations every time it wishes to communicate. But it is your responsibility to perform the following tasks in response:

- You must decode the address from the address bus and signal the device that its particular address is being sent.
- You must be certain that the communication lines of the device are properly connected to the data bus, and if it is an input device, its communication lines must be disabled (set to a high-impedance) until it receives an input-control pulse from the microcomputer.
- When interfacing to the Z80 CPU, you must decode three control signals to generate the input and output control pulses. Once decoded, you must send the appropriate control pulse to the device to initiate data transfer.

## The interface circuit

The schematic of the interface circuit is shown in Fig. 2. Let's take a look at it to see how the principles that we just mentioned apply. Two sections of a quad OR gate, IC1-a and IC1-b, receive three control signals from the microcomputer on its inputs. It decodes those three signals, such that when IORQ and WR are true (low) an OUT control pulse is generated. When IORQ and RD are true (low) an IN control pulse is generated. Those input- and output-control pulses initiate the data transfers. Each of the control pulses goes to a 74LS138 3-to-8-line decoder (IC3 and IC4). Figure 3 shows how the 74LS138 operates: When E1 and E2 are high (logic 1) the logic levels of inputs A, B, and C do not matter. However, if E1 and E2 are low (which is the condition when either IN or OUT is true), the inputs A, B, and C are decoded such that one of the outputs on the 74LS138 goes low. As shown in the table in Fig. 3, the output that goes low depends on the code at the inputs A, B, and C (pins 1, 2, and 3).

Referring back to the schematic in Fig. 2, you will notice that the 74LS138 inputs are connected to A2, A3 and A4 of the ZX81 address bus. This means that—assuming that A0, A1, A5, A6 and A7 are all logic zeros—the device codes as, shown in Table 2, can be generated by the ZX81 and will be decoded by the 74LS138.

So with two OR gates and two 74LS138's you have the capability of generating eight output- and eight input-device code pulses. In other words, you have the capability of sending an output to eight separate devices from the ZX81 and receiving an input from eight separate devices. In the interface circuit in Fig. 2, three of the output-device code pulses (IC4, pins 13, 14 and 15) and one of the



## PARTS LIST

IC1—74LS32 quad OR gate  
 IC2—74LS04 hex inverter  
 IC3, IC4—74LS138 3-to-8-line decoder/multiplexer  
 IC5—74LS74 dual D-type flip-flop  
 IC6—MSM5832 microprocessor real-time clock/calendar  
 IC7—74LS75 4-bit bistable latch  
 IC8—74LS373 octal D-type latch  
 IC9—74LS11 triple 3-input AND gate  
 IC10—74LS245 octal bus transceiver  
 XTAL1—32.768 kHz

**Miscellaneous:** Card-edge connector for ZX81, wire-wrap sockets, universal plug-board, etc.

The following are available from Active Electronics, PO Box 8000, Westborough, MA 01581 (1-800-343-0874): MSM5832 clock/calendar IC, \$12.95; 32.7680 kHz crystal, \$3.45. Add \$3.75 for postage, handling, and insurance.

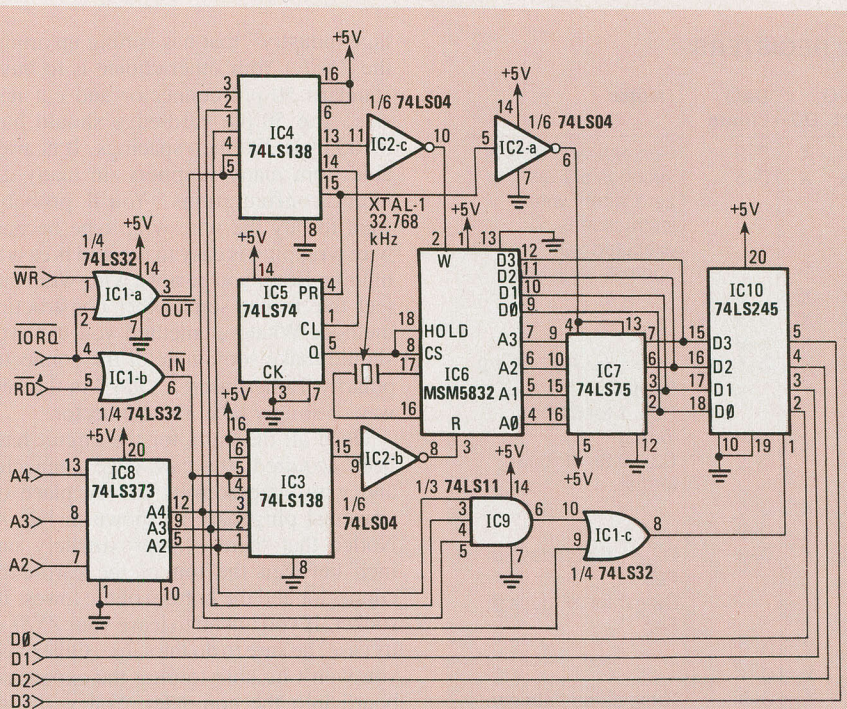


FIG. 2—INTERFACE-CIRCUIT SCHEMATIC. The connections to the computer include three address lines, three control lines, and four data lines. Note that +5 volts can also be taken from the computer.

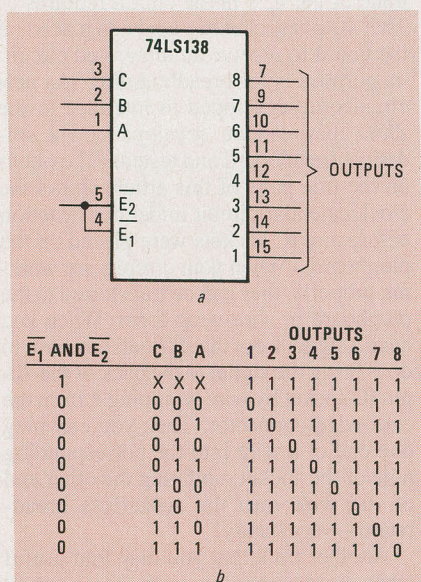


FIG. 3—THE 74LS138 3-to-8-line decoder/multiplexer. By using three address lines and two control lines, we can generate 8 input- and 8 output-device codes.

input-device code pulses (IC3 pin 15) are used. The remaining input and output device code pulses will be used in future interface projects.

Once the device-code pulses are generated via the input and output 74LS138's, they are sent to the clock/calendar circuit to get information into and out of the MSM5832 clock/calendar IC.

The remainder of the circuit in Fig. 2 is specifically for interfacing the MSM5832 to the ZX81. For example, when output-device code pulse 00H is generated (at IC4, pin 15), it goes to pin 4 of IC5, a

TABLE 2

A4	A3	A2	Device Code (Hex)
0	0	0	00
0	0	1	04
0	1	0	08
0	1	1	0C
1	0	0	10
1	0	1	14
1	1	0	18
1	1	1	1C

Note: A7, A6, A5, A1, and A0 = 0

74LS74 flip-flop. (Note: A hexadecimal number is indicated by a capital "H" following the digits.) When the flip-flop receives a low-going pulse on pin 4, it sets its output (pin 5)—and thus the cs and HOLD inputs of the MSM5832 clock/calendar IC—to a logic 1. A logic 1 on those inputs selects the MSM5832 and holds all of its internal registers stable during the input or output operation.

In addition to going to pin 4 of the 74LS74, the device-code pulse is inverted and sent to pins 4 and 13 of a IC7, a 74LS75 4-bit latch. When the 74LS75 receives a high-going pulse on pins 4 and 13, it catches the data present on its inputs (pins 2, 3, 6, and 7). Those input pins are connected (through a buffer) to the four lower-order bits of the data bus of the ZX81.

The information transferred from the ZX81 to the latch is the code or address for the MSM5832 clock/calendar register to which it wishes to send or receive information. A listing of the register options and their codes are shown in Table 3. Once the register code is sent to the 74LS75, it will remain present on its outputs until a new register code is sent.

Once the register code is sent, the MSM5832 is ready for communication and data can be sent to the selected register by generating an output-device code pulse 08H (pin 13, IC4). You may receive information from the selected register by generating an input-device code pulse 00H (pin 15, IC3). When you have completed your input or output operations, an output-device code pulse 04H (pin 14, IC4) is generated to reset the 74LS75 flip-flop output back to a logic zero. That deselects the MSM5832 and allows it to resume normal timing operations—which brings us to an important point: If the MSM5832 is kept on hold (CS and HOLD set to logic 1) for more than 1 second, its normal timing will be interrupted and you will lose a second for each second that those pins are held to a logic 1.

Two IC's in the interface, IC8 and IC10, have not been discussed, yet they are important. Those two IC's are bus buffers—they protect the ZX81 from damage resulting from wiring errors in the interface circuit. For example, IC8 (74LS373) buffers the address lines and is unidirectional, while IC10 (74LS245) buffers the data-bus lines and is bidirectional. The 74LS245 allows information to flow from the ZX81 data bus to the interface circuit on all OUT instructions. But it only allows information to flow from the interface circuit to the ZX81 on certain IN instructions. Those IN instructions are determined by the IN address lines A2 through A4, and a decoder circuit constructed of IC9 (74LS11) and IC1-c (74LS32).

If any address line is a logic 0 and an IN is generated, the 74LS245 allows information to flow from the interface circuit to the ZX81 data bus. That means that if the ZX81 is trying to generate an IN instruction with A2, A3, and A4 all logic 1's, an input will not be accomplished.



TABLE 3—MSM5832 REGISTERS

Address Inputs				Internal Counter	Data I/O				Data Limits	*Notes
A3	A2	A1	A0		D3	D2	D1	D0		
0	0	0	0	Seconds	X	X	X	X	0-9	Seconds and tens of seconds are reset to zero when write instruction is executed with address selection
0	0	0	1	Tens of seconds	—	X	X	X	0-5	
0	0	1	0	Minutes	X	X	X	X	0-9	
0	0	1	1	Tens of minutes	—	X	X	X	0-5	
0	1	0	0	Hours	X	X	X	X	0-9	D2 = 1 for PM; D2 = 0 for AM D3 = 1 for 24-hour format D3 = 0 for 12-hour format
0	1	0	1	Tens of hours	*	*	X	X	0-1/0-2	
0	1	1	0	Day of week	—	X	X	X	0-6	
0	1	1	1	Days	X	X	X	X	0-9	
1	0	0	0	Tens of days	—	*	X	X	0-3	D2 = 1 for 29 days in Feb D2 = 0 for 28 days in Feb
1	0	0	1	Months	X	X	X	X	0-9	
1	0	1	0	Tens of months	—	—	—	X	0-1	
1	0	1	1	Years	X	X	X	X	0-9	
1	1	0	0	Tens of years	X	X	X	X	0-9	X Indicates data can be either 1 or 0

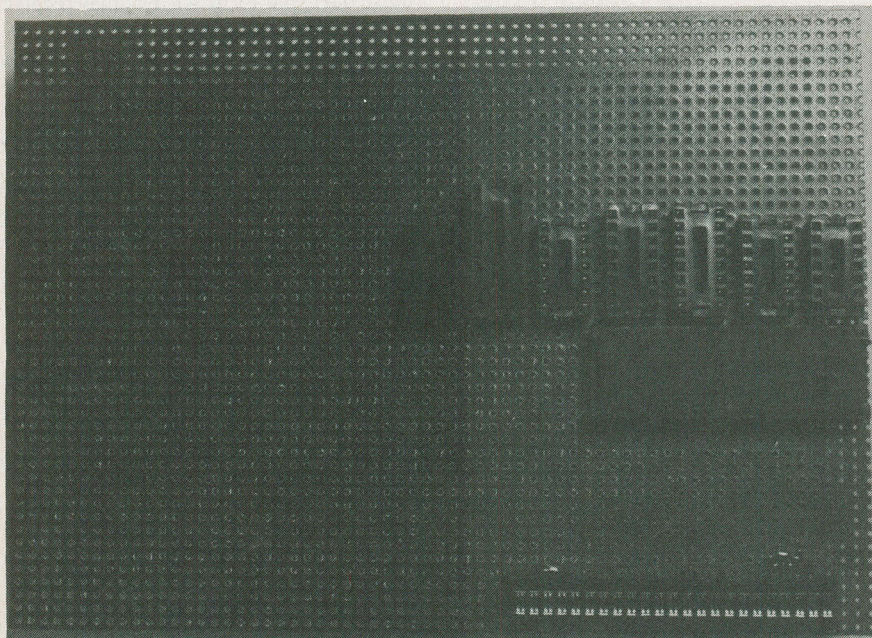


FIG. 4—THE INTERFACE BOARD. Wire wrapping is probably the easiest way to construct the interface. Be sure to leave space between the connector and the lowest IC socket so you can plug the board into the computer.

Even though the 74LS138 can decode and generate a device code pulse for that address when those three address lines are all logic 1's, the 74LS245 will not let the information pass. Keep that in mind when interfacing with the circuit.

### Building the interface

To wire anything to the card-edge port of the ZX81, you'll need a 44-pin card-edge connector. However, you cannot use a standard 44-pin connector. If you look closely at the card-edge fingers, you will

notice that, in addition to the 44 fingers, there is a keyway. That keyway takes up exactly one pin location—it's used so that you won't plug anything in backward. It means that the connector you need is actually a 46-pin type. The problem is that standard connectors are available in 44- and 50-pin configurations but are not available with 46 pins.

You can do one of two things. You can buy a special connector that will fit the ZX81. (Such a connector is not too easy to find, but they are available from the "cot-

tage industry" that has sprung up around the ZX81.) Your other choice is to buy a standard 50-pin connector and cut it to size. The 50-pin card-edge should have 0.100 by 0.200 inch spacings. It is available from many suppliers, in many different configurations. You'll probably want to buy the wire-wrap type because wire wrapping is easy to use and is easy to modify. But if you're not a wire-wrap fan, feel free to use some other construction method. Whatever method you use, you should make some note of the connector polarity. Either insert a "key" in the keyway or simply label the connector.

Once all the parts for the circuit have been acquired, the card-edge connector and wire-wrap sockets can be placed on universal plugboard as shown in Fig. 4. Notice that there is approximately one inch between the top of the card-edge connector and the bottom of the lowest IC socket. If you intend to leave your ZX81 in its case, be sure to do the same. Otherwise you won't be able to plug the expansion board into the computer. You will also notice that a 40-pin IC socket has been placed on the plugboard, even though none of the IC's in the circuit requires it. That 40-pin socket has *not* been placed on the board to receive an integrated circuit; its purpose is for breadboarding. As new circuits are developed to interface to the ZX81 they can be developed on a solderless breadboard and tested. (The photo on the title page of this article shows the clock/calendar circuit under construction before any IC sockets were placed on the plugboard.) When your circuits are working properly, they can be transferred to the plugboard in wire-wrap form. When you need a signal from the ZX81 all you have to do is bring the signal to the back of the 40-pin IC socket by wire wrapping it from the card-edge connector. Then you can plug one end of a wire into the corresponding hole of the socket, and plug the other end of the wire into the solderless breadboard—very handy!

Another trick that you may find useful when wire wrapping is to use a small amount of quick-setting epoxy glue on the backs of the IC sockets before mounting them. That ensures a sturdy mount which makes wire wrapping easier. Labeling each IC and marking the number one pin of each IC makes the task of wire wrapping much easier; and in addition this aids in reducing wiring errors. Plastic slip-on pin identifiers are recommended.

Now that we have the basic hardware design completed, we can turn to what is often the most time-consuming and least understood aspect of any microprocessor-based project: the software—the program that makes your interface do what it has been designed to do. Next month, after we look at the software, we'll be able to put the interface to work as a temperature sensor, a security system, and more. **R-E**




# BUILD THIS

## Clamp-on DC Ammeter

*This ammeter uses Hall-effect transducers to let you measure DC current using a clamp-on probe.*

HARDIN STRATMAN

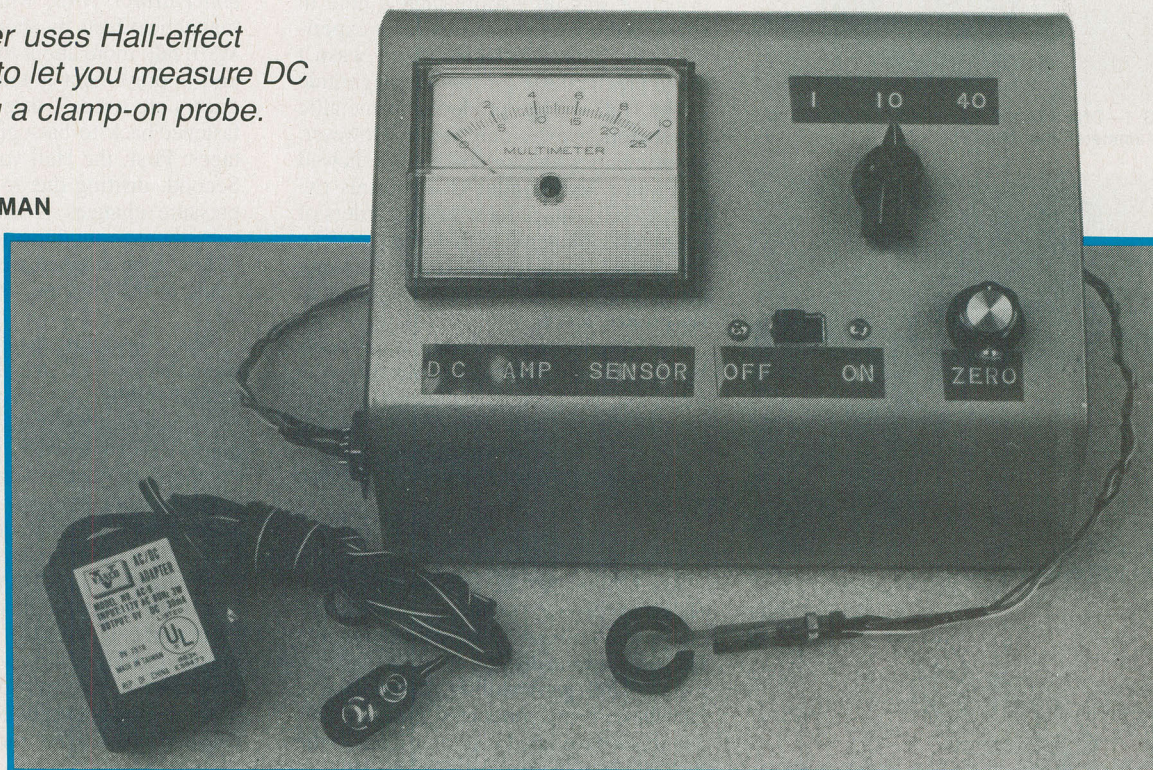

THE CONVENTIONAL METHOD OF MEASURING direct current in a circuit is to connect an ammeter in series with the current flow, as shown in Fig. 1. That means that if you want to measure the circuit's current, you have to shut the current off before connecting or disconnecting the ammeter. If the point of current measurement is at a high voltage, the ammeter case must be insulated from ground to prevent arcing. And it also must be insulated from people who might come in contact with it.

Another problem with inserting a conventional ammeter in series with the current flow is that the internal resistance and inductance of the meter can alter some characteristics of the circuit under test in an undesirable manner. For example, it can add inductance in a video circuit or resistance in a high-current circuit. A remote meter-reading at any distance may be difficult to obtain.

### The clamp-on ammeter

With clamp-on ammeters, there's no exposure to dangerous voltages when measuring current; there's no need to disturb the insulation; there's no inserted impedance. Clamp-on ammeters eliminate the undesirable characteristics of DC ammeters because they measure the current

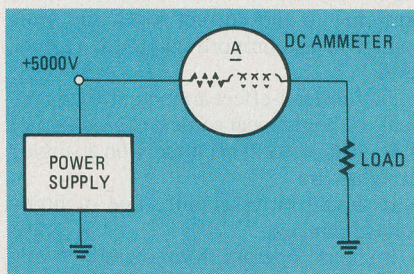


FIG. 1—THE CONVENTIONAL METHOD of measuring current can add undesirable resistance and inductance to the circuit. The ammeter case may also be at a dangerous voltage level.

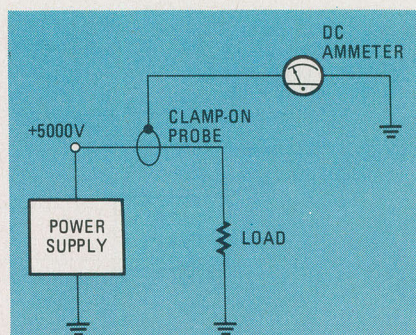


FIG. 2—THE CLAMP-ON AMMETER does not add inductance or resistance to the circuit, and it's isolated from high voltages.

flowing in a wire without breaking the circuit connection, as shown in Fig. 2.

Clamp-on ammeters for measuring alternating current have been around for a long time. Those devices are generally low cost, reasonably accurate, and easy to construct since they operate on a mutual-inductance principle the same as a transformer. But there have only been a limited number of DC clamp-on ammeters available. One example of a fine laboratory-type DC clamp-on ammeter is shown in Fig. 3: Hewlett Packard's *HP-428B*, which can measure current from 1 milliamp to 10 amps. Its list price is around \$1800. The *HP-428B* first converts the magnetic field around the conductor to an AC voltage that is proportional to the DC current. If you connect a voltmeter or oscilloscope to a front-panel output, you can measure low-frequency (under 400 Hz) AC current, too. The unit's probe needs occasional de-gaussing.

Just recently, some DC clamp-on ammeters that make use of the *Hall effect* principle—as our ammeter will do—have become available. The list price of those instruments is about \$200 to \$500. Figure 4, for example, shows F.W. Bell's *Current Gun* model *CG-103A*. That is a clamp-on current probe that uses a Hall-effect gen-



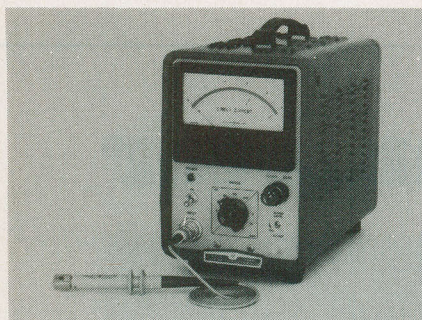


FIG. 3—ONE EXAMPLE OF a lab-type DC clamp-on ammeter: the HP-428B.

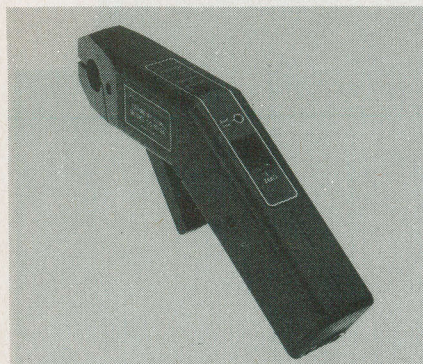


FIG. 4—THIS CLAMP-ON CURRENT PROBE uses Hall-effect sensors.

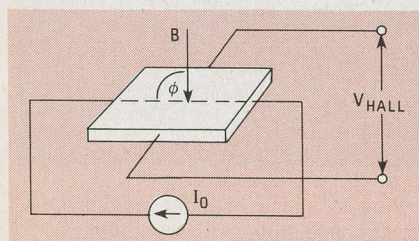


FIG. 5—IF A CURRENT-CARRYING conductor is placed in a magnetic field, a Hall voltage is generated that is perpendicular to both the current flow and the magnetic field.

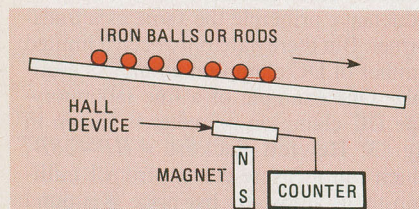


FIG. 6—BECAUSE THE OUTPUT of early Hall transducers varied widely with temperature and pressure variations, their use was limited to acting as switches. Here, the iron balls or rods concentrated the field from the magnet.

erator and lets you read DC and AC currents on a standard voltmeter or oscilloscope. The list price of that probe is about \$220.

### The Hall effect

The Hall effect is one of those great discoveries that had to wait for its time to come. Edward H. Hall, in 1879, found that if a current-carrying conductor is placed in a magnetic field that is perpen-

dicular to the direction of current flow, a voltage is developed across the material in a direction perpendicular to both the initial current direction and the magnetic field, as shown in Fig. 5. That voltage is now known as the Hall voltage to commemorate the discoverer of the effect.

For close to 100 years, the Hall effect principle was little more than a note in some textbooks and a curiosity for experimenters. That's because there wasn't much practical use for it—the magnitude of the Hall voltage produced in metallic conductors is extremely small. However, experiments with semiconductor materials showed that some semiconductor materials exhibit a Hall voltage three or four orders of magnitude greater than that of metal. The advances in semiconductor technology permitted the construction of practical Hall transducers.

Early semiconductor Hall transducers had a tendency to drift considerably with vibration, pressure, and changes in temperature. That limited their use to acting as switches in counting devices. An example of how they could be used is shown in Fig. 6.

### Using the Hall effect

We no longer have to limit the use of Hall transducers to switches. A useful DC clamp-on ammeter can be built using Hall-effect transducers.

If a Hall generator is placed near a current-carrying conductor, the Hall voltage that's developed is proportional to the magnitude of the magnetic field surrounding the conductor. Since that field is proportional to the current level, the Hall voltage is also proportional to the current level.

For our Hall-effect ammeter to be practical, it should meet some design criteria:

- It must perform accurately on a single, straight wire.
- It should be essentially free of high-voltage dangers.
- It should operate from a single 9-volt battery for a reasonable length of time.
- It should be simple to operate, calibrate, and "zero set".
- It should be fairly low-cost.

We can start with a simple design like

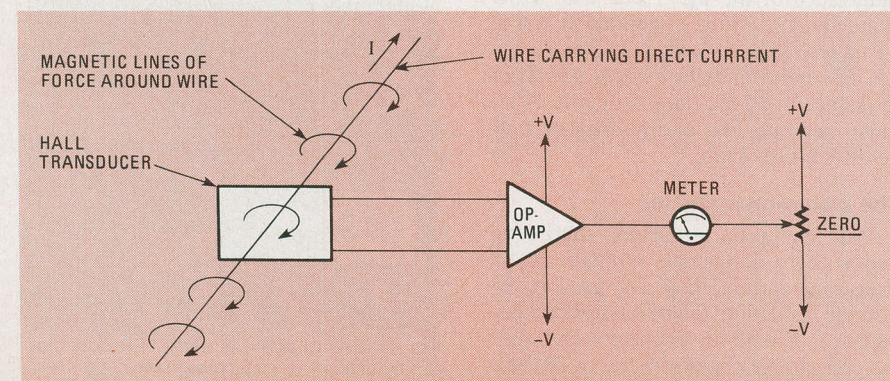


FIG. 7—SIMPLIFIED HALL-EFFECT DC ammeter.

that shown in Fig. 7. The voltage induced by the magnetic lines of force around wire generates a voltage that is amplified by the Hall transducer. However that type of circuit is not too practical: It can be used only if the current is extremely large. Figure 8 shows an improved simplified circuit. The first improvement is the use of a concentrator core, which increases the magnetic effects by about a factor of four. We'll talk more about that shortly. A second improvement is that two Hall transducers are used. Using two transducers, fastened back-to-back gives us two advantages: First, the Hall voltage is doubled. Second, drifting due to temperature and pressure changes is drastically reduced because each input of the differential op-amp will be effected similarly. The schematic of the final circuit is shown in Fig. 9.

When designing the meter, several Hall transducers were tried. Most of them drifted wildly. A 9SS-series transducer manufactured by the Micro Switch Company (Div. Honeywell, 11 W. Spring St., Freeport, IL) demonstrated considerable improvement over all others and was chosen for the final circuit. Figure 10 shows the Hall transducer.

The output voltage of the 9SS as a function of the magnetic field is linear over an input range of  $-400$  to  $+400$  gauss. The diagram in Fig. 11 shows the four blocks that make up the transducer: Hall-effect element, voltage regulator, amplifier, and output transistor. Its transfer function is:

$$V_{OUT} = (6.25 \times 10^{-4} B + 0.5)V_S$$

where  $V_S$  is the supply voltage and  $B$  is the magnetic flux density in gauss.

### The flux concentrator

The flux density produced by low-level currents is usually not sufficient to allow the use of a Hall transducer to measure the current. However, if a toroidal is used to enclose the conductor and act as a flux concentrator, good results can be obtained, and the basic clamp-on circuit of Fig. 5 can be made into a practical and useful measuring instrument.

Different materials, sizes, and shapes



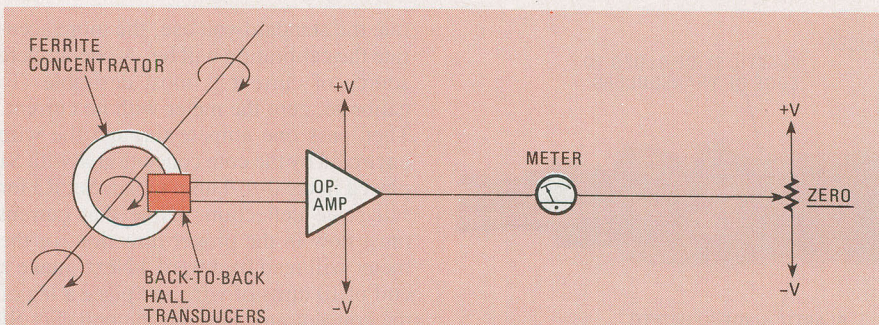


FIG. 8—THIS IMPROVED HALL-EFFECT-AMMETER circuit uses two back-to-back Hall transducers and a ferrite concentrator core.

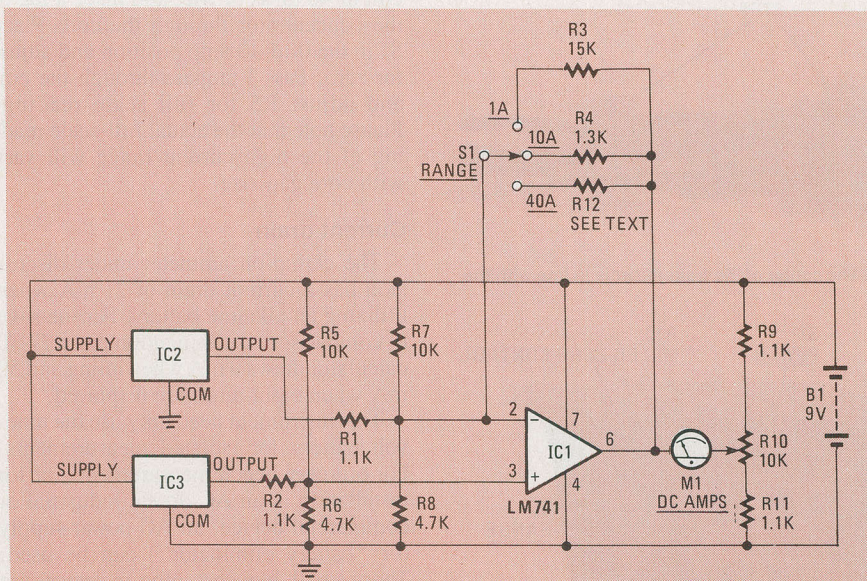


FIG. 9—COMPLETE AMMETER SCHEMATIC. Parts values are not critical, but for more accurate calibration, use variable resistors for R3, R4 (and R12, if you don't use a jumper).

were tried for the concentrator for the external probe. The standard of comparison was to pass one ampere of current through a single wire surrounded by the core under test. Ordinary steel, power-transformer steel, silicon steel and "mu" metal all retained enough residual magnetism after the passage of 1 ampere through the wire to upset the zero calibration of the meter after removal of current. The only materials that retained no measurable residual magnetism were ferrite and a special nickel core.

Different core sizes from .5 to 1 inch in diameter were used with no measurable difference in results. Changing the core gap size caused the instrument sensitivity to vary in a linear manner. If the gap size was doubled, the meter reading was reduced to one-half.

The final probe constructed by the writer used a  $\frac{7}{8}$ -inch outside-diameter ferrite core with a  $\frac{1}{16}$ -inch gap.

### Building the ammeter

You can build the DC ammeter for less than \$60, including the case. In addition to being used as an ammeter, you can use the instrument as a gaussmeter—it will

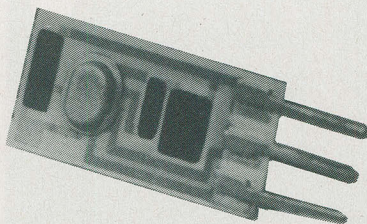


FIG. 10—THE HALL-EFFECT SENSOR from Micro Switch, the LOHET (Linear Output Hall Effect Transducer).

indicate the presence, relative intensity, and polarity of an external magnetic field.

The probe is the most difficult part of the instrument to build. In the prototype, the Hall transducers were first glued back-to-back with epoxy glue and plastic slides were glued on the sides of the transducers, as shown in Fig. 12. The core was then glued to a piece of  $\frac{1}{32}$ -inch fiberglass which slid into the side pieces. That permits the Hall transducers to move into the gap in the ferrite after the wire has been passed through. When the transducers are properly positioned, their centers should be in line with the core. The closed probe is shown in Fig. 13.

When you build your clamp-on am-

### PARTS LIST

All resistors are  $\frac{1}{4}$ -watt, 5%, unless otherwise noted.

R1, R2, R9, R11—1100 ohms

R3—15,000 ohms

R4—1300 ohms

R5, R7—10,000 ohms

R6, R8—4700 ohms

R10—10,000 ohms, potentiometer

R12—see text

### Semiconductors

IC1—LM741 op-amp

IC2, IC3—Hall transducer, sensitivity 3 mV/gauss (Micro Switch 91SS12-2)

### Other components

M1—Meter, 100 microamperes movement. (Note that meters with movements up to 1 mA may be used.)

S1—Three-position rotary switch

S2—SPDT toggle or slide switch

B1—Battery, 9 volts, transistor type

**Miscellaneous:** Concentrator cores, case, wire, solder. Concentrator cores with a permeability of 2500 or greater all performed equally well. It appears that a permeability greater than 2500–3000 fails to capture any additional magnetic flux lines.

The core used in the probe shown in the pictures is a Stackpole 57-3336 type 24B material with a permeability of 5000 and a 0.187-inch gap. These may be obtained from Perm Mag Central Corp., 1213 Estes Ave., Elk Grove Village, IL 60007. The single-unit price is \$11 postpaid (IL residents add 7% sales tax).

A pair of Hall-effect transducers (Micro Switch 91SS12-2) is available from Peerless Radio Corporation, 19 Wilbur Street, Lynbrook, NY 11563, for \$16 postpaid. (NY residents add 8% sales tax).

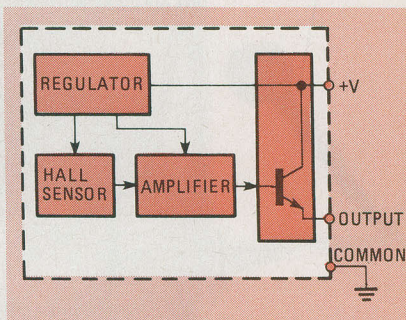


FIG. 11—BLOCK DIAGRAM of Micro Switch's LOHET 91SS12-2.

meter, you may want to use your imagination when constructing a probe for the device. The one shown here works, but is not necessarily the most elegant. You may want to build the entire ammeter into a handheld probe. For example, F.W. Bell Inc. (6120 Hanging Moss Rd., Orlando, FL 32807) sells such a meter. They simply added a digital meter to the probe that was shown in Fig. 4.

Cores for the probe should be purchased with a pre-cut gap, because cutting



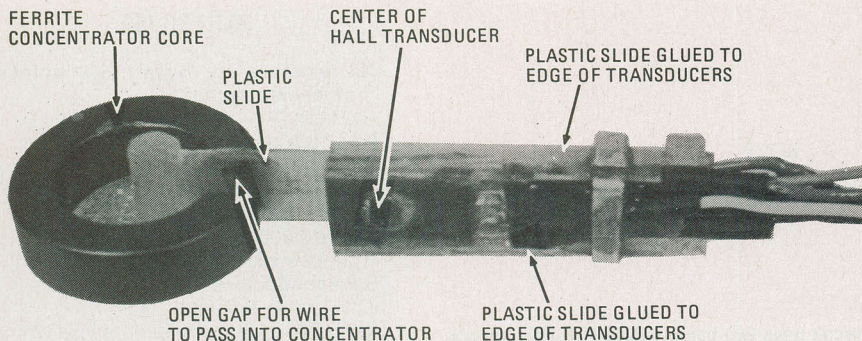


FIG. 12—THE CLAMP-ON PROBE is shown with the gap open.

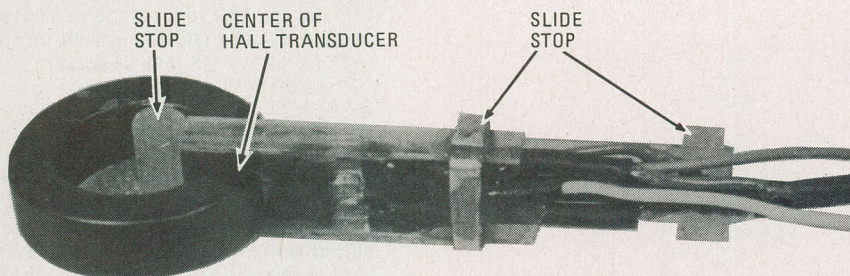


FIG. 13—THE CLAMP-ON PROBE is shown here closed. The center of the transducer is in line with the ferrite core.

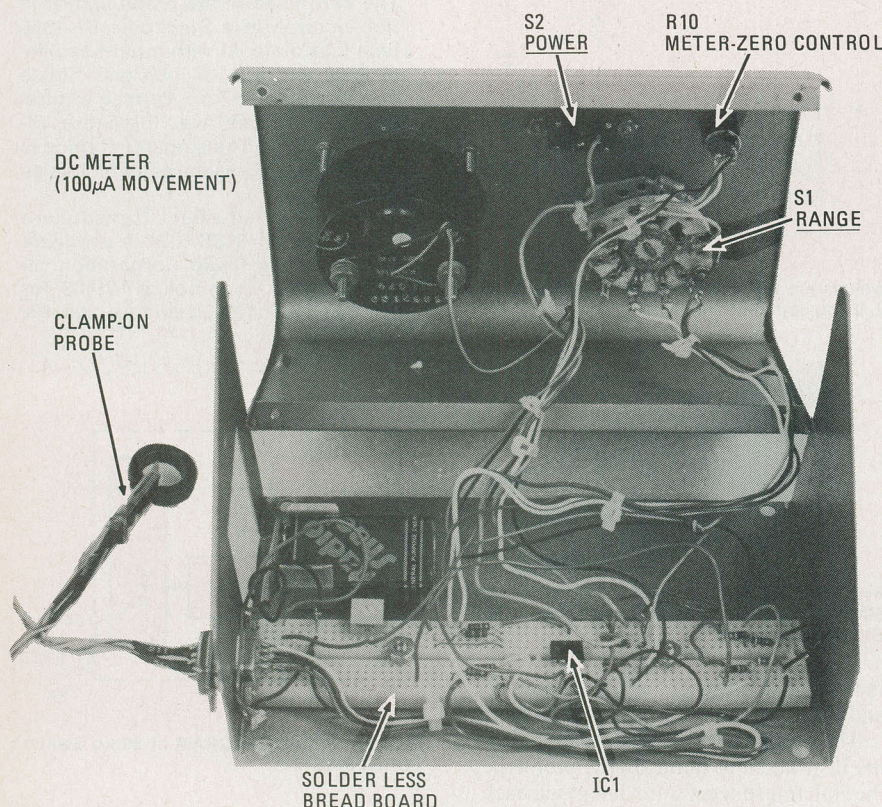


FIG. 14—THE AUTHOR'S PROTOTYPE. The construction method is obviously not critical.

through ferrite material without special tools is extremely difficult.

We won't go into detail on the construction of the rest of the instrument. It is rather straightforward and is not critical. We'll leave it to the ability of the persons wanting to build a clamp-on ammeter. As you can see in Fig. 14, the author's prototype simply used a solderless bread-board for the op-amp circuit.

### Calibration procedures

Calibration of the ammeter is determined mainly by the size of feedback resistors R3, R4, and R12 and by the concentrator-core gap. Resistor R12 will generally be zero (a jumper) for the highest current range desired.

Potentiometers should be substituted for R3 and R4 to increase the calibration accuracy. And, of course, the more accu-

rate the standard you use, the more accurate the calibration will be. A one-ampere source of current is most desirable. To calibrate, zero the meter with no current. Then pass one ampere through the wire encircled by the core concentrator with S1 placed in the 0-to-1 amp range. Set R3 for full scale deflection. (Note that current must flow in the proper direction, or the meter will read backward.) Next, make a coil of 10 turns of wire and place a leg of the concentrator through the coil. Set S1 to the 0 to 10 ampere range and zero the meter. Pass 1 ampere through the coil. Set R4 to full scale deflection. Construct a coil of 40 turns of wire and place a leg of the concentrator through the coil. Place S1 in the 0-to-40 amp position and adjust for zero. Pass 1 ampere through the coil and adjust R5 for full scale reading. Please note that the actual full-scale reading of the high current range will vary with core gap size.

### Current drain

The clamp-on ammeter under discussion has a current drain of 21 mA when utilizing an alkaline battery. For the sake of comparison, we'll mention that a TI-30 calculator draws 9 mA when idling and 50 mA when eight nines are displayed.


This instrument need only use the nine-volt battery for isolated measurements. For ordinary bench measurements, or for installation in an AC driven industrial or commercial device, an AC power-supply (or "battery eliminator") can be used. Those small, low-cost, plug-in devices are capable of delivering 30 to 40 mA. But for best results and drift-free measurements, use a regulated supply.

### High voltage warning

One of the advantages of a clamp-on ammeter is the ability to indicate current in a high voltage circuit without insulating the measuring meter. However, the safety factor is only as good as the wire insulation involved. When using the instrument to measure current in a high-voltage circuit make sure the wire insulation has an adequate safety factor to prevent arcing or danger to the operator.

R-E

HOME  
COMPUTERS

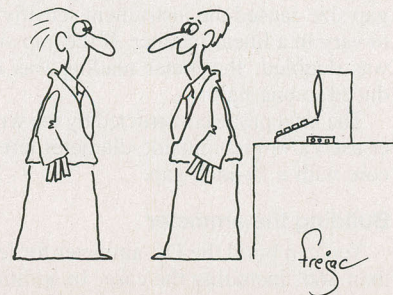

"We guarantee that all components will remain state-of-the-art for three hours."



# ALL ABOUT

## POWER-SUPPLY CIRCUITS

*Designing practical power-supply and voltage-regulator circuits is not difficult—but finding practical information on those circuits often is. We'll change that with an in-depth look at practical power supplies and voltage regulators.*

RAY MARSTON

TWO OF THE MOST COMMON CIRCUIT DESIGN tasks are those of designing basic power-supply circuits and designing voltage-regulator circuits. Both of those design tasks are reasonably simple. A basic power supply consists of little more than a combination of a transformer, rectifier, and filter so all the designer has to do is use a few simple rules to select the component values that will suit his own particular design requirements.

Voltage-regulator circuits may vary from simple Zener networks (designed to provide load currents up to only a few milliamperes) to fixed-voltage high-current units (for powering logic boards, etc.), or to variable-voltage, high-current units designed for general-purpose laboratory supplies. We'll look at practical versions of all those examples.

### Power supply circuits

Basic power-supply circuits are used so that equipment that requires a DC voltage can safely operate from the AC power lines (rather than from batteries). They are simply designed to convert the AC power-line voltage into an electrically isolated DC voltage with the value required by the actual circuitry of the equipment. The basic power-supply circuitry consists of little more than a transformer-rectifier-filter combination: The transformer is used to convert the AC line voltage into an electrically isolated and more useful (convenient) AC value, and the rectifier-filter combination is used to convert the new AC voltage into a smooth DC value.

Figures 1 through 4 show the three most useful transformer-rectifier-filter com-

binations that you will ever need. The circuit shown in Fig. 1 provides a single-ended DC supply from a transformer and bridge-rectifier combination. Its performance is virtually identical to the circuit shown in Fig. 2, which uses a center-tapped transformer.

The circuits of Figs. 3 and 4 provide bipolar DC supplies. Note that Fig. 4 is essentially the same as Fig. 3, except that discrete diodes (D1–D4) are used instead of a bridge rectifier. A bridge rectifier can keep things neater, but it can often be cheaper to use discrete diodes in high-current applications. Throughout the remainder of the article, we'll show only circuits that use discrete diodes. Where a bridge rectifier can be substituted, we'll show the diodes in the usual bridge configuration, as we did in Fig. 1.

The rules for designing both the single-ended and bipolar supplies are simple, as you'll see in a moment.

### Transformer-rectifier selection

The three most important parameters of a transformer are its *secondary voltage*,

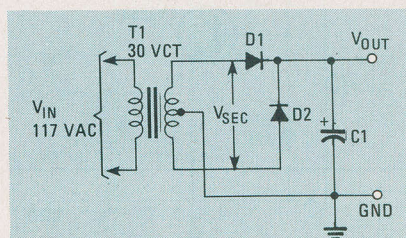


FIG. 2—THIS CIRCUIT, which uses a center-tapped transformer, performs identically to that shown in Fig. 1.

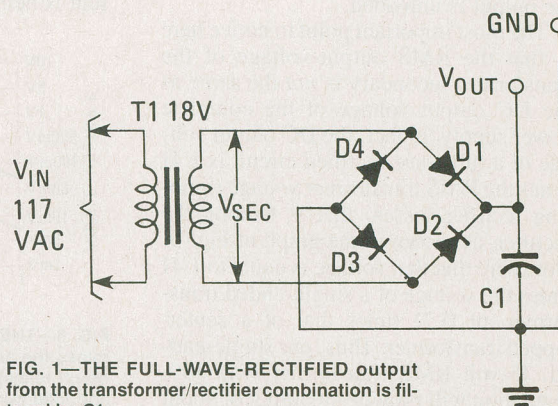


FIG. 1—THE FULL-WAVE-RECTIFIED output from the transformer/rectifier combination is filtered by C1.

its *power rating*, and its *regulation factor*. The secondary voltage is always quoted in volts RMS at full rated power load. The power load is quoted in terms of VA (Volt-Amperes) or watts. Thus, a 15 V, 20 VA transformer has an output of 15-volts

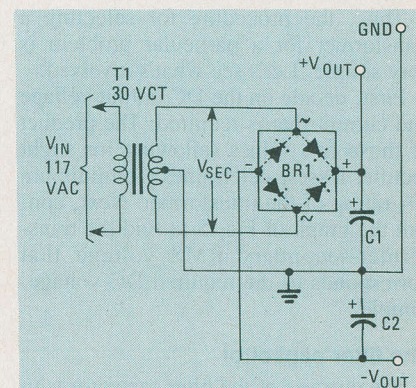


FIG. 3—THIS BIPOLAR SUPPLY uses a bridge rectifier, but separate diodes could be used instead.

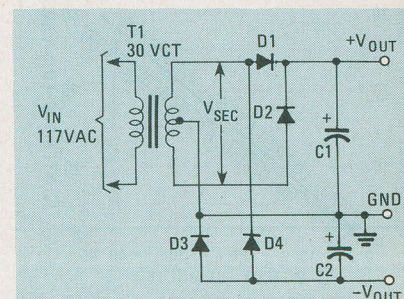


FIG. 4—FOUR DISCRETE DIODES replace the bridge rectifier of the previous circuit. Note, however, that the two circuits are equivalent.



RMS when it is supplying 20 watts. When the load is removed (and the supplied power is reduced to zero) the secondary voltage will rise by an amount specified by the regulation factor. Thus, the output of a 15-volt transformer with a 10% regulation factor (a typical value for the regulation factor) will rise to 16.5 volts when the output is unloaded.

The most important point to notice here is that the RMS output-voltage of the transformer secondary is *not* the same as the DC output voltage of the complete power supply. In fact, the DC output voltage of a full-wave-rectified circuit is 1.41 times the RMS transformer voltage (ignoring rectifier losses) that is feeding the rectifier, as shown in the graph of Fig. 5. Note here that that voltage is equal to 1.41 times the voltage of a single-ended transformer, or 0.71 times that of a center-tapped transformer. Thus, our single-ended, 15-volt RMS transformer with 10% regulation will provide an output of about 21 volts at full rated load (just under 1 amp at 20 VA rating) and an output of 23.1 volts at zero load.

When rectifier losses are taken into account, the output voltages will be slightly lower than shown in the graph. In the "two-rectifier" circuit of Fig. 2, the losses amount to about 600 millivolts, while in the "bridge" circuits of Figs. 1, 3, and 4, the losses amount to about 1.2 volts. The rectifiers should, for maximum safety, have current ratings at least equal to the DC output currents.

Thus, the procedure for selecting a transformer for a particular problem is very simple. Let's see what's involved.

First, decide on the DC output voltage and current that is required: The product of those two values (allowing for slight rectifier losses) determines the minimum VA rating of the transformer. Next, consult the graph of Fig. 5 to find the transformer-secondary RMS voltage that corresponds to the required DC voltage. Simple?

### The filter capacitor

The purpose of the filter capacitor is to convert the full-wave-rectified signal of the rectifier into a smooth DC voltage.

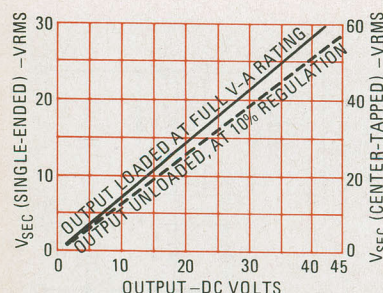


FIG. 5—TO USE THIS GRAPH, determine the required loaded DC output voltage. Then read across to find the corresponding transformer secondary voltage.

The two most important parameters of the capacitor are its working voltage and, of course, the value of its capacitance. The working voltage rating must be greater than the off-load output voltage of the power-supply circuit. The capacitance value determines the amount of ripple that will appear on the DC output when current is being drawn from the circuit.

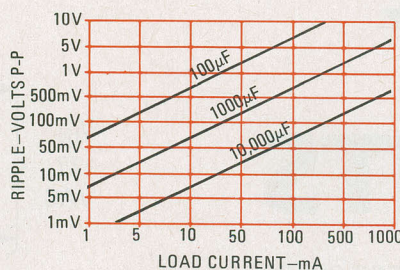


FIG. 6—THE FILTER-CAPACITOR value determines the amount of ripple at the output. This graph relates capacitor value to ripple voltage and load current in a full-wave-rectified, 50-60 Hz powered circuit.

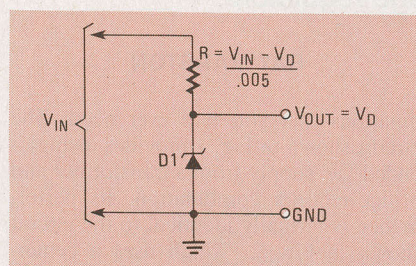


FIG. 7—USING A ZENER DIODE is an easy way to obtain a fixed reference voltage. This reference circuit is biased at about 5 mA.

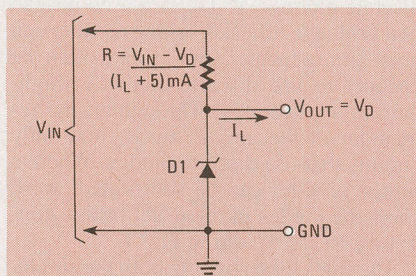


FIG. 8—THIS BASIC Zener regulator circuit can supply load currents of a few tens of milliamps.

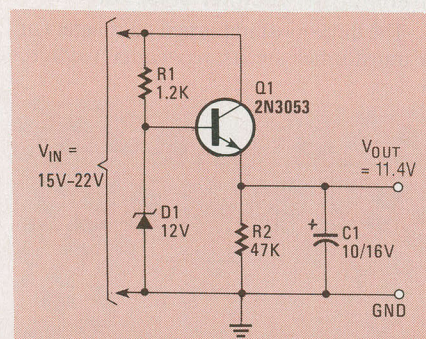


FIG. 9—THE SERIES-PASS Zener-based regulator circuit gives an output of 11.4 volts and can supply load currents up to about 100 mA.

As a rule of thumb, in a full-wave-rectified power supply operating from a 50-60 Hz power line, an output load-current of 100 mA will cause a ripple waveform of about 700 mV peak-to-peak to be developed from a 1000-µF filter capacitor. The amount of ripple is directly proportional to the load current and inversely proportional to the filter capacitor's value. That is shown in the "design guide" of Fig. 6.

In most practical applications, the ripple should be kept below 1-1.5 volts peak-to-peak under full load conditions. If very low ripple is required, the basic power supply can be used to feed a 3-terminal voltage regulator, which can easily reduce the ripple by a factor of 60 dB or so at very low cost.

### Voltage-regulator circuits

Voltage regulators may vary from simple Zener-based circuits designed to provide load currents up to only a few milliamps, to fixed-voltage high-current circuits designed around "fixed" 3-terminal regulator IC's, or to variable-voltage high-current circuits designed around "variable" 3-terminal regulator IC's. We'll look at practical versions of all three types of circuits.

### Zener-based circuits

A Zener diode can be used to provide a fixed reference voltage by using the simple circuit shown in Fig. 7. In that circuit, a current of roughly 5 mA is passed through the Zener diode from the supply through the current-limiting resistor R. The supply voltage,  $V_{IN}$ , may be subject to fairly wide variations, causing the Zener current to vary over a similarly large range. So long as  $V_{IN}$  is always more than a few volts greater than the Zener voltage and provided that the Zener power rating is not exceeded, that variation has only a moderate influence on the output voltage of the Zener, which typically has an effective output impedance of only a few tens of ohms.

A Zener can be used as a very simple voltage regulator, providing maximum load currents up to a few tens of milliamps, by merely selecting the value of the resistor R as shown in Fig. 8. When the designed maximum load current is being drawn, only 5 mA flows through the Zener: When zero load current is being drawn, the Zener passes 5 mA plus the full maximum designed load current and thus dissipates maximum power: It is important to ensure that the power rating of the Zener is not exceeded under this no-load condition.

In most practical voltage-regulator applications, the Zener is simply used to apply a reference voltage to a high-gain non-inverting buffer amplifier, which then supplies the required output power. The simplest example of this type of cir-



cuit is shown in the series-pass regulator circuit of Fig. 9. Here, Q1 is wired as a voltage follower, its emitter remaining at about 600 mV below its Zener-defined base voltage under all load conditions. The Zener network provides the base-drive current to Q1. That current is equal to the output load current divided by the current gain of the Q1 "buffer" stage. Clearly, the higher the gain of Q1, the better will be the output regulation of the circuit.

One way of improving the regulation of the circuit would be to use a Darlington transistor in place of Q1. An even better solution is to use the op-amp plus transistor buffer stage shown in Fig. 10. There, the op-amp and Q1 are wired as a unity-gain non-inverting DC amplifier with a near-infinite input impedance and near-zero output impedance. The output voltage tracks within a few millivolts of the Zener reference value. The safe output current is limited to about 100 mA by the power rating of Q1. Higher currents can be obtained if Q1 is replaced with a power Darlington transistor.

The circuit shown in Fig. 10 is very versatile. It can be made to generate any desired fixed voltage up to about 30 V maximum by simply using a suitable Zener value and ensuring that the unregulated supply voltage is at least 5 volts greater than the Zener value (up to 36 volts maximum).

The circuit can be used as a variable-voltage supply by simply wiring a potentiometer across the Zener, with its slider taken to the non-inverting input of the 3140 op-amp. That op-amp can accept inputs all the way down to zero volts, enabling (for example) a 0–25 volt supply to be easily implemented.

### Fixed 3-terminal regulator circuits

Fixed-voltage regulator design has been greatly simplified in recent years by the introduction of 3-terminal regulator IC's such as the "78xx" series of positive regulators and the "79xx" series of negative regulators. Those IC's incorporate features such as built-in fold-back current limiting and thermal protection. A wide

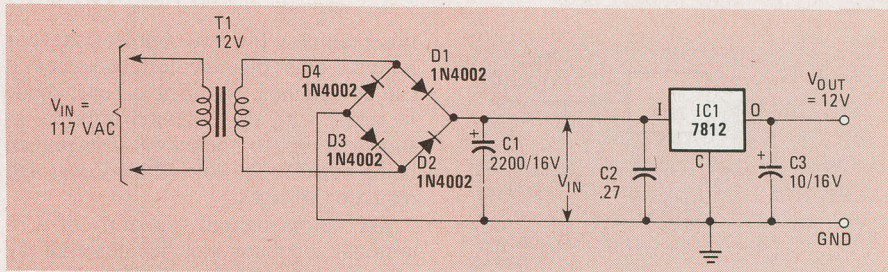


FIG. 11—A THREE-TERMINAL positive regulator circuit.

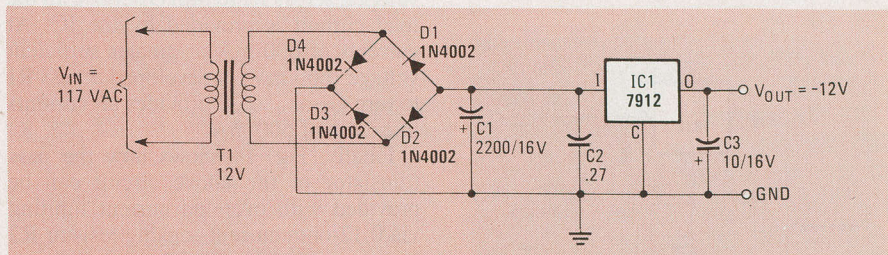


FIG. 12—A THREE-TERMINAL negative regulator circuit.

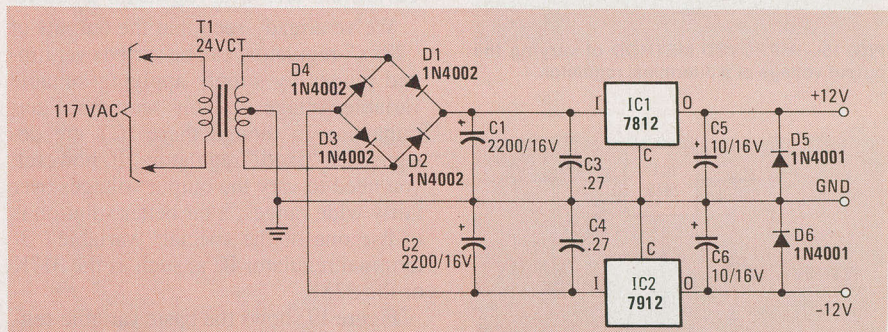


FIG. 13—COMPLETE  $\pm 12$ -volt, 1-amp bipolar power supply using 3-terminal regulator IC's.

range of 3-terminal fixed-voltage regulator IC's are available: Standard current ratings for those regulators are 100 mA, 500 mA, 1 A and 3 A and standard output voltage ranges for those devices are 5, 6, 8, 12, 15, 18, and 24 volts.

Three-terminal regulators are remarkable easy to use, as shown by the basic circuits in Figs. 11–13, which show the connections for making positive, negative, and bipolar regulated power-supply circuits respectively: The IC's shown in those examples are 12-volt units with cur-

rent ratings of 1 amp, but the basic circuits are valid for all other voltage ratings, provided that the unregulated input voltage is at least 3 volts greater than the desired output voltage.

Note that a 0.27- $\mu$ F or greater ceramic disc capacitor should be connected close to the input terminal of the IC, and a 10- $\mu$ F or greater electrolytic to the output. Also note that those regulator IC's typically provide about 60 dB of ripple rejection, so 1 volt of input ripple will appear as a mere 1 millivolt of ripple on the regulated output.

The output voltage of a 3-terminal regulator is referenced to the "common" terminal of the IC, which is normally (but not necessarily) grounded: Most regulator IC's draw quiescent currents of only a few mA, which flow to ground via that "common" terminal. The regulator output voltage can thus easily be raised above the designed value by simply biasing the "common" terminal with a suitable voltage, making it easy to obtain "odd-ball" output voltages from the regulator. Figs. 14 to 16 show three possible ways of achieving this.

In Fig. 14 the bias voltage is obtained by passing the IC's quiescent current (typ-

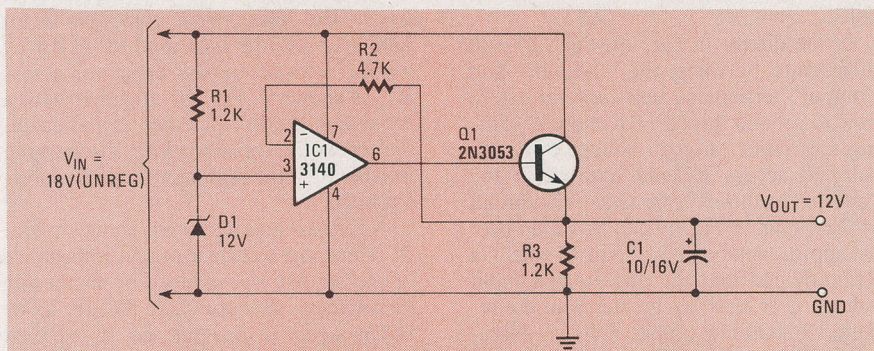


FIG. 10—THIS OP-AMP-BASED REGULATOR gives an output of 12 volts at load currents up to 100 mA with excellent regulation.



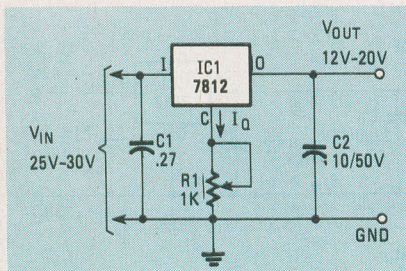


FIG. 14—A SIMPLE WAY to vary the output voltage of a 3-terminal regulator.

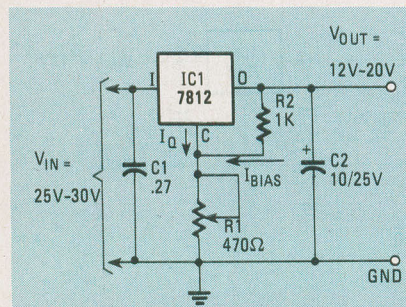


FIG. 15—IMPROVED METHOD of varying the output voltage of a 3-terminal regulator.

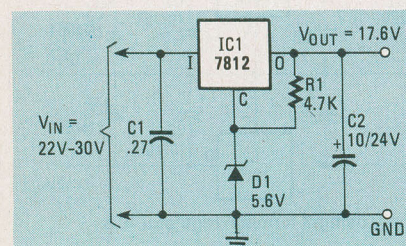


FIG. 16—TO INCREASE THE VOLTAGE output of a 3-terminal regulator, a Zener diode can be wired in series with the COMMON terminal.

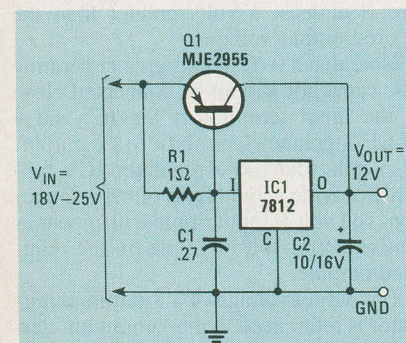


FIG. 17—TO BOOST THE OUTPUT-CURRENT capacity of a 3-terminal regulator, an external transistor can be used, as shown in this circuit that can supply a regulated 12 volts at 5 amps.

this example). If a fixed output voltage is required other than the designed value, it can be obtained by wiring a Zener diode in series with the common terminal as shown in Fig. 16, the output voltage then being equal to the sum of the Zener and regulator voltages.

The output current capability of a 3-terminal regulator can be increased by using the circuit of Fig. 17. Resistor R1 is wired in series with the regulator IC. At low currents, insufficient voltage is developed across R1 to turn Q1 on, so all the load current is provided by the IC. At currents of 600 mA or greater sufficient voltage (600 mV) is developed across R1 to turn Q1 on, so Q1 provides all currents in excess of 600 mA.

Finally, Fig. 18 shows how the pass transistor of the above circuit can be provided with overload current limiting via 0.12-ohm current-sensing resistor R2 and turn-off transistor Q2.

### Variable 3-terminal regulator circuits

We've already seen that the outputs of "78xx" regulators can be varied over limited ranges by simply applying suitable variable voltages to their "common" terminals, even though these IC's are designed as "fixed" regulators. If, however, you need to vary the output voltages over fairly wide ranges, a far better solution is to use one of the special "variable" 3-terminal regulator IC's, such as the 317K or the 338K.

Figure 19 shows the basic variable-regulator circuit that is applicable to those two devices. Both devices have built-in fold-back current limiting and thermal protection and are housed in TO3 steel packages, the major difference between the devices being that the 317K has a 1.5 amp current rating compared to the 5 amp rating of the 338K.

The major feature of both devices is that their "output" terminals are always 1.25 volts above their "adjust" terminals, and their quiescent or adjust-terminal currents are a mere 50 microamps or so. The 317K has an input-voltage range of 4-40 volts and an output-voltage range of 1.25-37 volts. The 338K has the same input range, but an output-voltage range of 1.25-32 volts.

In the circuit in Fig. 19, the 1.25-volt difference between the "adjust" and "output" terminals causes several mA to flow to ground through R1, thereby causing a variable "adjust" voltage to be developed across R1 and applied to the "adjust" terminal. In practice, the output of the circuit in Fig. 19 can be varied over the approximate range 1.25 to 33 volts via R1, provided that the unregulated input voltage is at least 3V greater than the required maximum output voltage. Naturally, alternative voltage ranges can be obtained by giving R2 and/or R1 alternative values, but it should be noted that

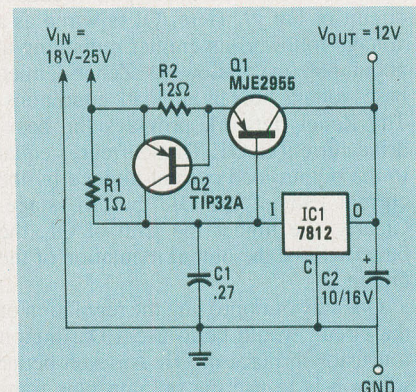


FIG. 18—OVERLOAD PROTECTION has been added to the circuit of Fig. 17.

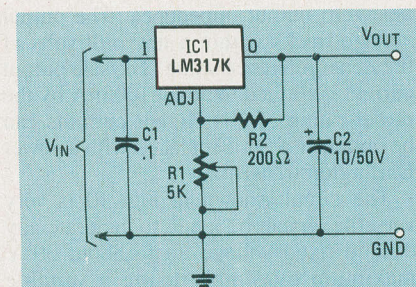


FIG. 19—BASIC APPLICATION of a variable-voltage 3-terminal regulator.

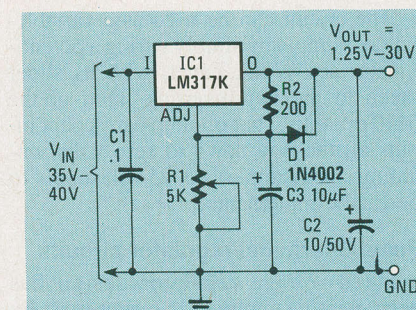


FIG. 20—THIS VARIABLE-VOLTAGE regulator has ripple rejection of 80 dB.


for best stability the R2 current must be at least 3.5 mA.

The basic circuit that we just looked at can be usefully modified in a number of ways. The basic ripple-rejection factor (about 65 dB) be increased to 80 dB by wiring a 10-μF bypass capacitor across R1, as shown in Fig. 20, together with a protection diode connected as indicated, to prevent the capacitor from discharging into the IC if the regulator output is short-circuited.

A further modification is shown in Fig. 21. Here, the transient output impedance of the regulator is reduced by increasing the value of capacitor C2 to 100 μF; diode D2 is used to protect the IC against damage from the stored energy of this capacitor if an input short occurs.

*continued on page 80*



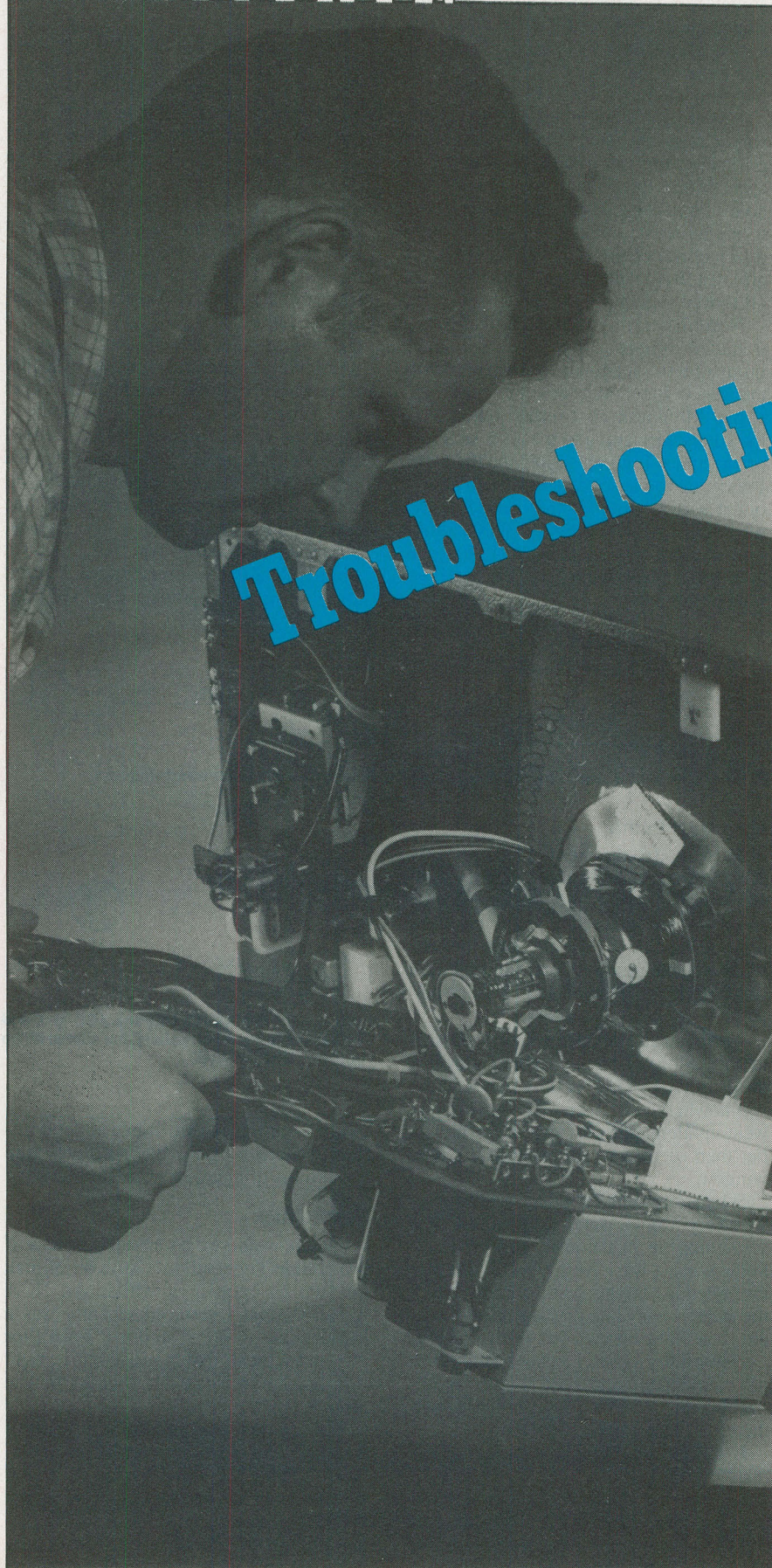

## Troubleshooting the Tough Ones

PEOPLE WHO PLAY WITH STATISTICS OFTEN come up with numbers that speculate on how many years out of a person's lifetime are spent eating, sleeping, blinking, or whatever. I wonder if someone could estimate how many accumulated years a TV technician might spend working on those nearly impossible sets, doing things like waiting countless hours for those insufferable intermittents to break down. The figure would be astonishing, I'm sure. If we could get paid for all of that time lost, even at two bucks an hour, it would be an awful lot of money.

Let's take a look at some case histories.

*Some TV problems can be fixed in a matter of minutes, with others it can take hours, days, or even weeks. In this article, we'll take a look at some of those "time killers," and see how they were eventually set straight.*

### FRANK A. SALERNO

The first involves a Zenith 25KC45 that started out routinely enough. The color was supposed to be drifting in and out. After sitting and watching the set for twenty minutes the customer was told that on that particular chassis, and others like it, the modules have a tendency to develop poor contacts. So, the modules were slid off and on again in order to re-establish the contacts and everything seemed fine.

A week later the same call came in. This time the set had been on for a couple of hours when I arrived, and I was lucky to catch it in not-so-living black and white. The act of merely changing channel caused the color to pop back in, and nothing could be done to re-create the problem. I decided to change the 9-86



module, which carries the bulk of the color circuitry, and left confidently. That would not be the first time that that module was found to be the troublemaker.

You guessed it, a few days later another call on that set came in. Once again, the receiver was in its "black-and-white" mode when I arrived. This time, I avoided changing channels and instead gingerly adjusted the fine tuning. The picture remained black and white. Slowly, I felt my way around inside when suddenly the color reappeared—again to stay.

The 9-89 module basically contains the color-output circuitry, and it usually misbehaves by causing changes in one of the primary colors, but still it does process the color signal. So I thought it a good idea to try a new one.

The next call really started to get vexing. There was no doubt about the fact that all of the color circuitry was located on the two modules already changed. Taking the set to the shop, for the time being, was out of the question. That's because that type of problem has an annoying habit of clearing up somewhere between there and here, so I was determined to do everything I could on-site.

In that set all of the customer controls, mounted at the front of the cabinet, are returned to the chassis through molex connectors. I poked around the wire bundle leading to the connectors, and for a brief moment I saw the color fade out and then in again. At last I thought that I was beginning to get somewhere, even though I was unable to repeat what had just happened in that split second. I plugged the molex connectors out and in a few times in the hope of cleaning their contacts up and left once more feeling confident.

For a week there was no news, but then it came. Lost for any more ideas, I was forced to pull the chassis. My reluctance to do so in the first place was well grounded. Once the jig was set up the long process of watching and waiting began. For days nothing happened while the best part of my workbench was being tied up. Still, I used some of the time to record some measurements. I scoped the input of the 9-86 module and made a sketch of what I saw. I did the same with the input, as well as the output, of the 9-89. If and when the color finally disappeared I would then make some comparisons and know where I was losing it.

But the color doggedly stayed put. At one point I was almost ready to give up and return the chassis, but I knew that that would have solved nothing, so I stayed with it, keeping an eye on it as much as I could. One day, upon returning to the shop after walking out for a few minutes, I was happy to see the picture in black and white. Quickly I turned on the scope, afraid that at any moment the color would pop back in and my chance would be lost.

Unfortunately, the scope did not tell me

much. The waveforms were changed somewhat; a little crimped in one instance, slightly distorted in the other, but at none of my three test points (see Fig. 1) was there a total lack of signal to give me the clear diagnosis I was looking for.

I went back to the wire bundle. There was a reaction. The bundle was gently pushed to the side, and the color faded away. When the bundle was released the color came back. Back and forth I went, trying to isolate out of this bundle of two dozen or more wires which were the most affected. Being all wrapped together, they all moved together.

Nevertheless, by using a feather touch it started to appear that it was the small group of wires leading to a connector atop the variac tuner that was the most sensitive. Moreover, as it turned out, it was the single wire going to the AFC terminal on the tuner. Tugging slightly on the wire, I was able to cause the color to go in and out at will. Tightening the connector and resoldering its terminals solved the problem. I still don't know why, it being an AFC problem, resetting the fine tuner did not restore color.

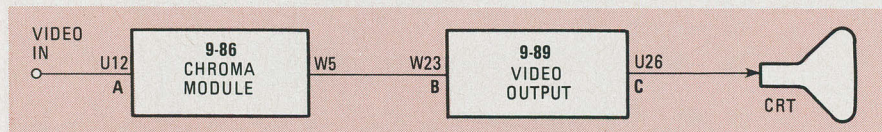


FIG. 1—POINTS A, B, and C were monitored in a hope to find where color was being lost.

### Not the antenna

Turning to the next case, a Sony KV1720, hooked up to an external antenna, was flickering and flashing badly. Now and then the picture would get snow and then quickly clear up. Outside, the wind was whipping around, and the rain was coming down in sheets. It was a perfect day for antenna trouble.

I grabbed an umbrella and went outside to have a look. I circled round and round the property looking for the antenna, but it was nowhere to be seen. The lead-in wire went up alongside one wall of the house, but then seemed to just stop at the attic window.

When questioned about it the customer was very vague, saying that there was something up in the attic, but he didn't know what it was. Well, what it was was the antenna, hanging comfortably from the rafters, cozy and dry, not being bothered one bit by the swirling storm outside.

Downstairs again, I removed the external connections and tried the set on its "rabbit ears." The flickering was still there so I took the set with me.

It was now my belief that the signal was breaking up in either the tuner or the IF strip. By disconnecting the tuner and hooking up a tuner sub, I was able to stabilize the picture. Wanting to be certain, I switched tuners back and forth a

few times. The results were conclusive so the set's tuner was pulled out and sent for repair.

Four days later I reinstalled the tuner, held my breath and pulled the switch. I lost my breath when the picture began to flicker and flash as badly as before. I retraced my steps by hooking up the tuner sub one more time. The picture was then rock solid.

It was time to rethink my diagnosis. Obviously, it was not the tuner itself that was creating the problem, but something that was tied into it: B-plus voltages, antenna transformer, AGC, etc. Taking voltage measurements proved useless since the flickers were of such short duration. Also, with the picture bouncing so wildly there wasn't a stable voltage in the entire set. A better idea, I thought, would be to substitute each of the tuner feeds. First I eliminated the antenna block. Next, I fed the tuner external B-plus voltages. Finally, when I disconnected the AGC line and put a three-volt battery in its place, the picture firmed up (see Fig. 2). So it was the RF AGC that was the reason for it all. Pushing on, I found the RF-AGC tran-

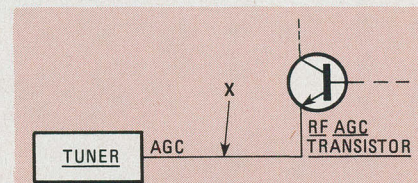


FIG. 2—BY BREAKING OFF the AGC at X and hooking in a three-volt battery, the source of the problem was isolated.

sistor to be the culprit. It had an intermittent junction, causing precisely the symptoms of a defective antenna.

### A little luck

Where would we be, in our business, if we couldn't depend on a little bit of luck to step in once in a while. An RCA CTC53X that I serviced recently was a typical case in point, and if it wasn't for the lucky break that came along I might still be bent over that set, looking for the trouble.

The picture was pulling very badly. I studied it for a while, stroking my chin, when I came up with a hunch. A similar chassis that I had serviced some years ago had a thermal condition, causing the picture to pull much like this one was doing now, but only when it was well heated up.



It took several trips to the shop to fix that one, it being one of those nasty now-you-see-it-now-you-don't kind of repairs. In any case, it turned out, at least that time, to be the sync-separator transistor that was developing a leak.

Now, with nothing more than my hunch to go on, I changed the transistor, hoping to save myself the trouble of hauling the set away, but it was not to be. With the new transistor in place the picture wiggled around as badly as before so the set had to go.

On the bench, I put the scope to work. The sync output looked awful, with peaks and humps of video tearing into the sync level. The sync input looked just as bad. In fact, I went farther and farther back, looking for a clean signal, but couldn't find one. Even at the base of the first video amp, where one is accustomed to finding nice straight-edged sync tips, the video content was rolling up and down into the sync, making the whole thing look bent out of shape.

What was going on here? The problem was not likely to be in the filter capacitors, but maybe it was in the AGC. With my voltmeter I went through the whole video/AGC/sync strip, failing to turn anything up. They all checked out. After three hours of looking, I was still not sure of exactly what I was looking for.

Through it all, I was noticing something else besides the pulling. On some channels, not all, there appeared to be some strange-looking interference superimposed over the picture. That interference looked like an odd mixture of corona discharge-radiation, ignition noise, and barkhausen. What was more, when the antenna was removed, instead of the blank, snow-filled raster I had expected to see, I was getting very dark waves of diagonal lines moving across the screen.

Since I was getting nowhere looking for the pulling I decided to leave the antenna off and hunt for the interference instead. Find the cause of that, I thought, and I will find the other. With the scope, I began to poke around the video section, looking for signals, when suddenly, through the

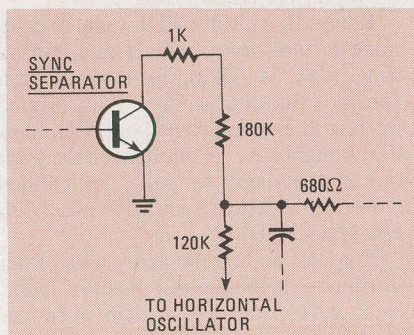


FIG. 3—WHEN THE 180-kilohm resistor changed value, it caused the 680-ohm resistor to burn out, knocking out the horizontal oscillator.

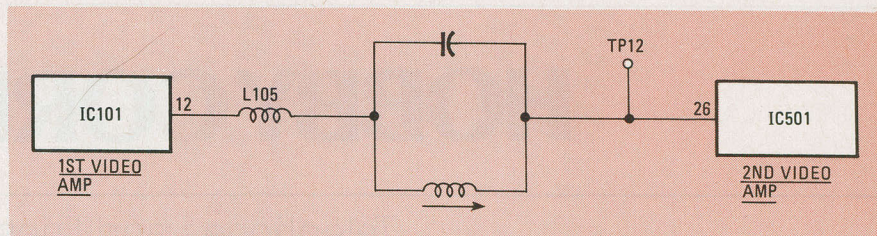


FIG. 4—AFTER WEEKS OF TESTING, the loss of picture was finally traced to an erratic L105.

corner of my eye I saw a puff of smoke. I quickly yanked the plug. What did I do now, I wondered. Had I shorted something out with the probe? I didn't think so, so I decided to try again.

With the plug back in, I now found myself with no high voltage, and the output tube began to glow red. Working in short steps, so as not to blow the tube, I found that the horizontal oscillator plate-voltage was missing. Now I knew where the smoke came from. A 680-ohm resistor, supplying B-plus voltage to the oscillator/sync board was burned open. But the question of what had happened still remained. The ohmmeter told me that there was a low reading from the cold side of that resistor to ground. Checking further, I found what should have been a 180 kilohm resistor that was now white ash. And where did that resistor go? Why, to the sync-separator collector! (See Fig. 3.)

I can only guess at what had taken place. The 180-kilohm unit was probably arcing internally, accounting for the strange interference. With the antenna disconnected, hence no signal, the arcing and interference went into regeneration, causing the resistor to overheat badly until it finally caved in. One thing was certain, once it was replaced the picture straightened out perfectly.

Why didn't the problem show up in my voltage checks? Was it really the removal of the antenna that sped things up? I'll never know.

### One big headache

The granddaddy of the marathon intermittents has got to be the one I ran into in Gold Star model CR-820 that I came to know so well. It was brought to me having sound but no video—just a white raster. For several weeks, the customer told me, the video had been alternating between getting dull and then getting bright, flickering and flashing, until it finally went out altogether.

Naturally, by the time I removed the back cover, turned on my equipment, spread out the schematic, and planned my attack, the picture jumped back in and stayed that way for the first couple of days. Nevertheless, I tucked the set into a corner, belly up, and let it play whenever I was in the shop.

I took as my first area of concentration TP12, which was dead center between the IC101, which contained the first video

amp and the IC carrying second video amp, IC501. I kept the scope probe hooked on and waited.

For days, nothing. A slight flicker here, a flash there, contrast might drop a bit, but nothing to really sink my teeth in. One time I saw the picture fall off about 50 percent, and the waveform do the same, but both quickly recovered. IC501 was a plug-in unit and easy to replace so I went for that one first. Even though it was past TP12 there was the chance that it was loading the signal down.

I thought I had it. For days the set worked fine. I buttoned it up and prepared to call the customer to arrange for pick-up, only to see the flickering return the next time I tried it. So, it wasn't that IC. Perhaps it was the other. Belly up again, scope connected, the wait was on. Occasionally the symptoms turned up briefly, but whenever I moved the scope lead over to another point the picture would lock in place for the next couple of days. After two weeks of that, the picture finally reached a point where it settled down for good.

It was time to let go, I thought. I would have the customer take the set home, live with it until such time when it would quit for good, and make it a little easier to repair. Meanwhile I clipped a memorandum to the schematic for future reference, reminding me that I had a feeling that the video was being lost somewhere between IC101 and IC501. What meager measurements I was able to come up with led to that conclusion. Between them, as shown in Fig. 4, were a small coil, a tuneable transformer, and TP12.

The decision to call the customer having been made, I turned the set on for one last try. That's right—flickering and changes in contrast. In anticipation of that, I had soldered a tiny pigtail wire to the output of IC101 so that I would have something to hold onto with the scope probe. That done, I was ready for some more waiting.

It took two more days before I saw the contrast drop appreciably. The scope pattern stood firm. As had happened so many times before, the moment I moved the probe the picture went solid. Once again, it stayed that way for days.

It was the end of a long and exasperating week. The set was playing well, the scope face steady and bright. I started to

*continued on page 77*



# HOBBY CORNER

## Telephones and lines

EARL "DOC" SAVAGE, HOBBY EDITOR

NOW THAT THERE ARE SEVERAL TELEPHONE companies instead of just one with which to deal, there seems to be increased interest in how telephones work and how to work on them. You may want to do some extra reading on the subject.

William Bass (SC) has asked how he can check his telephone equipment. Like many of us, William has bought his own phone since the "divestiture" of AT&T in January. He foresees a potential problem when he has a breakdown in service. That is, when the telephone company comes to repair his line, he gets a large service charge only to be told that the trouble is in his phone (which they don't repair).

Well, it could happen just that way, and that would be embarrassing—to say nothing of the expense. Contrary to your suggestion William, we would not advise you to stick test equipment on the phone company's line. There is too great a chance that you will create a problem that is even worse than the one you already have. However, you can do the job without any test equipment at all.

The way to go about it is to try another phone on your line. At present, you can buy a neat one-piece phone with a saddle-type holder for about \$10. Not only does one of those phones make a good extension; but with two in the house, you can disconnect them one at a time and use it to see if the problem is in the line or the

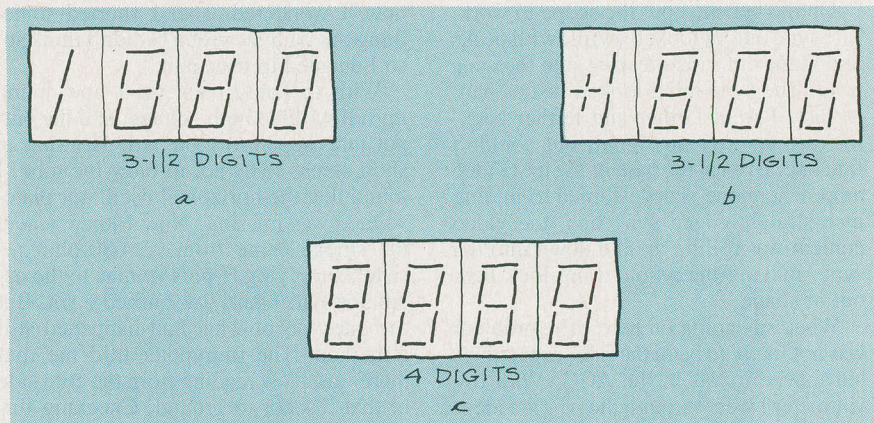


FIG. 1

phone itself. It is highly unlikely that two of them would go bad at the same time, barring a lightning strike or something equally catastrophic. And even then, you could check against such a coincidence by disconnecting one of your phones and trying it out at a friend's house.

### "Half" digits

Along with others, Robert Reiter (NY) has asked about the "1/2" in display descriptions that say 3 1/2 or 4 1/2 digits. That can be confusing, especially when you first run into it. However, it certainly does not mean that you literally have half of a digit. Let's look at an example.

Say, for instance, that a 12-hour clock has four display modules as shown in Fig. 1-a; the left-most digit never displays anything higher than a 1. That is, it is either blank or 1—never 2, 3, and so on. Therefore, that left digit need not contain all the normal segments. If the digit has only the two segments to make a 1, the clock is said to have a 3/2-digit readout. The "1/2" simply means that some of the segments of a digit are missing. Another example would be a digital meter; the left digit may be able to display +1 and -1 but no higher or lower number (Fig. 1-b). It, too, would be called a half digit. On the other hand, if the left position has all the segments (see Fig. 1-c) so that it could be used in a 24-hour clock, for example, the clock has a 4 digit readout. That's all there is to it.

### Measuring capacitance, inductance

Every electronics hobbyist is sure to need some type of test (measuring) instru-

ment at one time or another. While, some of you may be satisfied with just a VOM, most of us have additional instruments and would like to have others. The more you are able to check and test and measure, the more likely you are to end up with successful projects.

Having a variety of test equipment does not guarantee success, but it does help. And that can save you a great deal of time, too. Few things are more frustrating than having a project fail because of a component that looks good but is open, shorted, or out of tolerance. It is good to be able to check components one by one whenever necessary.

Test instruments can cost a bundle once you get beyond the basics. And if you are like me, you are attracted to instruments that have more than one use: It's like killing two birds with one stone, so to speak. That's why I am going to give one answer to two different questions.

Robert Blackwell (MD) wants to determine the inductance of coils, and Winston Jones (GA) is looking for a way to measure the value of capacitors. If my original interest in electronics had not been in radio, I might have recommended the traditional instruments for such applications. However, why don't you guys use a Grid Dip Meter (GDM)?

Not least among the many uses of that instrument is the measurement of inductance and capacitance. You are, of course, aware that when a capacitor and a coil are connected in parallel, they have a resonant frequency ( $f_r$ ). (That's how radios are tuned.) A GDM will enable you to mea-

### AN INVITATION

To better meet your needs, "Hobby Corner" has undergone a change in direction. It has been changed to a question-and-answer form. You are invited to send us questions about general electronics and its applications. We'll do what we can to come up with an answer or, at least, suggest where you might find one.

If you need a basic circuit for some purpose, or want to know how or why one works, let us know. We'll print those of greatest interest here in "Hobby Corner." Please keep in mind that we cannot become a circuit-design service for esoteric applications; circuits must be as general and as simple as possible. Please address your correspondence to:

Hobby Corner  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003



# COMPUTER DIGEST

VOL. 1 No. 3

July 1984

NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

## THE NEW SINCLAIR QL COMPUTER...

AN in-depth look AT THIS UNDER-\$500  
COMPUTER THAT INCLUDES 128K OF RAM,  
TWO TAPE DRIVES, AND HIGH-RES GRAPHICS.

## ARE PRINTING BUFFERS FOR YOU???

Nifty devices THAT FREE UP YOUR COMPUTER  
FOR OTHER TASKS WHILE DOCUMENTS ARE  
BEING PRINTED OUT.



A  
GERNSBACK  
PUBLICATION

## COMMUNICATIONS SOFTWARE....

A look AT THE SOFTWARE THAT LETS YOUR  
COMPUTER TALK TO OTHER COMPUTERS.



# Radio-Electronics Software Store



New for our readers....A mailorder source of software for Atari 400, Atari 800, IBM P C, Commodore VIC-20, Apple II, and other personal computer systems.
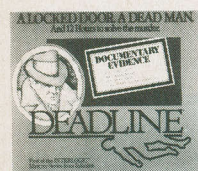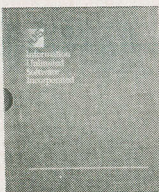
## IBM PC



☐ **FLIGHT SIMULATOR** by Microsoft ... List \$49.95. Our price ... \$43.00. Highly accurate simulation of flight in a single-engine aircraft. Working instruments. Real-time flight conditions. (IBM P C, 64k, color graphics, disc)

☐ **EASYWRITER II** by Information Unlimited ... List \$350.00. Our price ... \$300.00. Turns your computer into a word processor. You see everything on the screen. There are no imbedded commands. (IBM P C, disc)



☐ **DEADLINE** by Infocom ... List \$49.95. Our price ... \$43.00. A locked door. A dead man. You have 12 hours to solve the mystery. One false move, and the killer strikes again. (IBM P C, 48k, disc)

☐ **ALGEBRA**, Vol. 1 by Edware ... List \$39.95. Our price ... \$34.00. A first year algebra tutorial covering definitions, number line operations, sets, etc. (IBM P C, 48k, color graphics, disc)



☐ **MICRO/TERMINAL** by Microcom ... List \$94.95. Our price ... \$83.00. Allows access to remote mainframes and minis, information data banks, and other personal computers. (IBM P C, disc)

☐ **PC TUTOR** by Comprehensive Software ... List \$79.95. Our price ... \$69.00. Interactive program teaches you how to use your IBM Personal Computer, including hardware and software. (IBM P C, 64k, disc)



## APPLE



☐ **PRISONER2** by Interactive Fantasies ... List \$32.95. Our price ... \$28.00. Escape is hardly possible. The island keeps you under surveillance. Just try and get out! (Apple II, 48k, disc)

☐ **PRISONER2** by Interactive Fantasies ... List \$39.95. Our price ... \$34.00. (Atari disc)

☐ **THE MASK OF THE SUN** by Ultrasoft Inc ... List \$39.95. Our price ... \$34.00. An animated adventure through a series of hi-res screens. An ultimate adventure challenge. (Apple II, 48k, disc)



☐ **MASTERTYPE** by Lighting Software ... List \$39.95. Our price ... \$34.00. A typing instruction system in an exciting hi-res game format. Learn to type while battling waves of attacking enemy words. (Apple II, 48k/64k, disc)

☐ **THE GRAPHICS MAGICIAN** by Penguin Software ... List \$59.95. Our price ... \$53.00. Make your own animated graphics. Handles up to 32 independent objects. Stores hundreds of color pictures. (Apple II, 48k, disc)



☐ **RENDEZVOUS** by Edware ... List \$39.95. Our price ... \$34.00. In four phases, simulates an actual space-shuttle flight from Earth Liftoff through Orbital Rendezvous and Approach to Alignment Docking with a space station. Hi-res graphics (Apple II, disc)

☐ **SAT WORD ATTACK SKILLS** by Edware ... List \$49.00. Our price ... \$43.00. A tutorial for mastering vocabulary, deciphering new or unfamiliar words, and taking tests. (Apple II, disc)




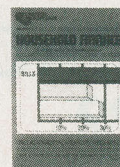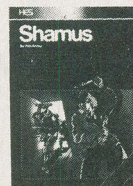
## COMMODORE VIC-20



☐ **PIPES** by Creative Software ... List \$39.95. Our price ... \$34.00. Connect a pipeline from the water supply tank to every house. Watch out for leaks. Use as little pipe as possible. 5 skill levels. (Commodore VIC-20 cartridge)

☐ **SHAMUS** by Human Engineered Software ... List \$39.94. Our price ... \$34.00. Only you can stop the Shadow's mad reign of terror. Two levels with 20 rooms each. A joystick challenge. (Commodore VIC-20 cartridge)



☐ **HOUSEHOLD FINANCE** by Creative Software ... List \$17.95. Our price ... \$15.00. Home utility program records and analyzes your monthly income, expenses and budget in 16 categories. (Commodore VIC-20 tape cassette)

☐ **HOME OFFICE** by Creative Software ... List \$29.95. Our price ... \$25.00. Combines VICPRO, a flexible and efficient word processor with VICDATA a powerful and sophisticated information storage and retrieval system. (Commodore VIC-20, cassette tape, 8k additional memory required)



## ATARI



☐ **SUBMARINE COMMANDER** by Thorn EMI ... List \$49.95. Our price ... \$43.00. A submarine patrol simulator to hunt and destroy enemy ships. 9 skill levels. Plug-in cartridge. (Atari Cartridge 400/800)

## APPLE

☐ **MINER 2049** by MicroLab ... List \$39.95. Our price ... \$34.00. Chase into a Uranium mine thru 10 levels of traps and capture Yukon Yohan. Scale ladders, jump from moving platforms, and win—if you can. (Apple II, 48k, disc)



## Radio-Electronics Software Store

200 Park Avenue South  
New York, NY 10003

Number of items ordered ☐

Total Price of Software ..... \$

Sales Tax (NY State Residents Must Include) .....

Shipping (\$2.00 per item) .....

TOTAL ENCLOSED (Sorry, No COD's) ..... \$

Name .....

Address .....

City ..... State ..... ZIP .....

SORRY - NO CREDIT CARD OR COD ORDERS



# CONTENTS

Vol. 1 No. 3

July 1984

## 6 The Sinclair QL

Can Sinclair's QL do for the office what his ZX80 personal computer did for the home? Find out what the QL has to offer. **Marc Stern**

## 8 Printer Buffers

Don't waste your time printing a document! You can put your computer back to work while your document is printing.


**Herb Friedman**

## 11 PC: "Personal Communications"


You can open the window on the world to your personal computer. All it takes is a modem and the proper software. The emphasis on this article is E-mail. **Herb Friedman**

## 4 Editorial

## 15 Computer Products

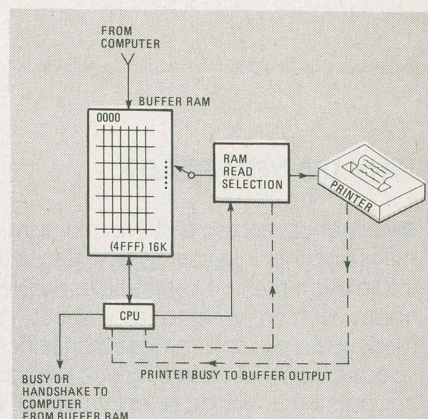

Page 8

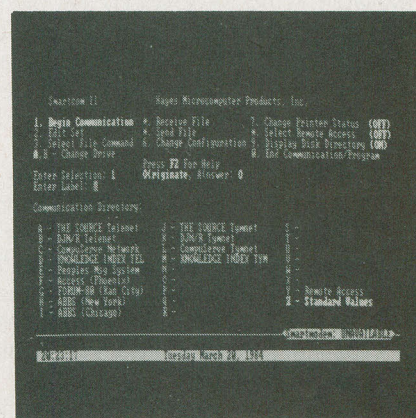

Page 11

## ON THE COVER

Sinclair started many revolutions: He was first with pocket calculators and flat-screen TV's. But perhaps he'll be best remembered for the first under-\$100 computer: the ZX81/Timex Sinclair 1000. He is trying to start a new revolution with the Sinclair QL—an office computer for less than \$500. The QL comes equipped with 128K RAM, two micro-sized tape drives, and an RS-232 serial port. Integrated software—word-processing, spreadsheet, database, and graphics programs—is also included. ROM-resident SuperBASIC is standard as well. We'll take a look at the machine in detail, starting on page 5.

### COMPUTERDIGEST

NEW KIND OF MAGAZINE FOR ELECTRONIC & PROFESSIONALS

#### THE NEW SINCLAIR QL COMPUTER...

An in-depth look at this under-\$500 computer that includes 128K of RAM, two tape drives, and high-res graphics.

#### ARE PRINTING BUFFERS FOR YOU???

Nifty devices that free up your computer for other tasks while documents are being printed out.

#### COMMUNICATIONS SOFTWARE....

A look at the software that lets your computer talk to other computers.



# EDITORIAL

## WHY DO YOU READ?

■Most of us read so that we can learn. When we find an article in a magazine that interests us, we read it in the hope that we'll pick up a bit of information that we didn't have before. Naturally, we have to be particular about what we want to learn about—we can't spend our entire lives reading. So we select those magazines that deal directly with our own specific fields of interest. Since we cannot read *everything*, it becomes important that we be selective about who our "teachers" are.

As we all know, there are a great many computer-oriented magazines available. Almost everybody that owns a computer gets a "great" idea for a new computer magazine, and thinks it's the best thing to come down the pike since the invention of sliced bread. Some of those ideas are indeed worthy. Some of the magazines that result will actually last. And some will soon fall by the wayside. How do you select which ones to read?

One of the tests that you can apply, is to look at what magazine editors call a "masthead." That's where they list the names of the people responsible for the publication you are reading. We're rather proud of our masthead, from the publisher right through all of the staff. Those people have been in electronics publishing almost since they learned to write, have worked their way, through the ranks, to the positions they now hold—accumulating years of experience in computers and electronics in the process.

The people who actually write our articles are also experts. (Many of the names, you'll notice, are not new.) They've been writing for many years, and most of our writers are employed in responsible positions at some of the top companies in the computer field. They know what they're talking about, and have learned how to communicate that information in the written word.

What I'm trying to tell you is that **ComputerDigest** is a professionally-developed publication; it's written, edited, and published by professionals for you. We want you to get the most out of it. All you have to do is read it! And by all means, let us know what you think.

BYRON G. WELS  
EDITOR

# COMPUTER DIGEST

**Hugo Gernsback** (1884-1967)  
founder

**M. Harvey Gernsback**, editor-in-chief

**Larry Steckler**, CET, publisher

**Art Kleiman**, editorial director

**Byron G. Wels**, editor

**Brian C. Fenton**, technical editor

**Carl Laron**, associate editor

**Robert A. Young**, assistant editor

**Ruby M. Yee**, production manager

**Robert A. W. Lowndes**, production  
associate

**Dianne Osias**, production  
assistant

**Joan Roman**, circulation director

**Arline R. Fishman**,  
advertising coordinator

Gernsback Publications, Inc.  
200 Park Ave. South  
New York, NY 10003

Chairman of the Board:  
M. Harvey Gernsback  
President: Larry Steckler

## ADVERTISING SALES 212-777-6400

Larry Steckler  
Publisher

### EAST/SOUTHEAST

Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
212-777-6400

### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
Radio-Electronics  
540 Frontage Road—Suite 325  
Northfield, Illinois 60093  
312-446-1444

### PACIFIC COAST Mountain States

Marvin Green  
Radio-Electronics  
15335 Morrison St., Suite 227,  
Sherman Oaks, CA 91403  
818-986-2001



■In the modern world of electronics and microcomputers there are a number of innovators and inventors who keep developing ideas that revolutionize the industry. One of those innovators, whose contributions will continue to be felt for years is Clive Sinclair. In the early 1970's, he took advantage of the four-bit microcomputer technology that was then coming to the fore and developed the first pocket calculator. If that were not enough, later in the 1970's, he was credited with developing the first miniature, flat-screen television set.

In 1981, Sinclair, ever the innovator, apparently looked at how far the cost of the microprocessor had fallen and decided the time was ripe for a low-cost personal computer. Thus, the ZX80 was born—the first computer under \$200. By using a membrane keyboard, plastic case, and a very compact operating system, the price of the computer could be kept down. Sinclair's next machine, the ZX81 could be sold for even less—it was the first \$100 computer. One of the reasons that it could be sold so cheaply was that it contained only four IC's—the Z80 microprocessor, a 2K RAM IC, the 8K operating system, and a custom IC that took the place of 14 TTL IC's that were in the ZX80.

Other companies soon realized the potential market for low-priced computers. Commodore Business Machines, Texas Instruments, Atari and a host of other companies all began to produce machines that eventually brought true computing power to home users at well below \$200 in cost.

By the end of 1982 and into 1983, the battle in the home computer marketplace became so intense that most of the major manufacturers involved in the dog-fight fell by the wayside and pulled out of the business. Texas Instruments dropped out, as did Mattel Electronics, and Atari suffered major reverses. Even Timex (which had taken over the distribution of the ZX81 in the U.S.) pulled out, leaving the field to Commodore and Radio Shack.

Despite that, Sinclair proved his point: He showed that microcomputers could be low-cost devices and provide average people with real computing power.

### **Sinclair does it again**

Now that 1984 is half over, it looks as if Sinclair has done it again, but this time in a higher part of the computer spectrum, the desktop segment. Sinclair Research Ltd. (50 Staniford Street, Boston, MA 02114) has developed a home/business microcomputer—the Sinclair QL (Quantum Leap) shown in Fig. 1. The machine includes two breakthroughs in the less-than-\$500 category.

The first breakthrough in this \$499 small system is its microprocessor: a member of the powerful Motorola MC-68000 series with its 32-bit internal architecture. The second breakthrough in the less-than-\$500 category is the use of integrated software. The QL is supplied with a word-processing a spreadsheet, database, and graphics programs. We'll look more closely at the software in a few minutes, but right now let's look at what's inside the QL.

# The Sinclair QL

*Sinclair started a revolution with his low-priced ZX80 and ZX81 computer. Will his new Sinclair QL have a similar effect on the business-computer market?*

**MARC STERN**



**FIG.1—THE NEW SINCLAIR QL: at just \$499, a “quantum” leap in computing performance and designed for the serious home, business or educational user.**

### **The MC-68008 microprocessor**

After all the media attention given to the Apple Macintosh microcomputer, you've doubtless heard of the MC-68000 microprocessor. But you probably haven't heard about its variants, which include the 68008.

The 68008 is a 16-bit microprocessor with an 8-bit data bus. Why did Sinclair go with that device? Most likely because it is cost effective. It has the benefits of a 32-bit internal architecture. But because of its 8-bit data bus, you can use byte-wide memories and peripherals. Bus multiplexing is not necessary, as it is with some 16-bit microprocessors. All those factors help to reduce the cost of a system. The memory-addressing capacity of the 68008 is 1 megabyte.

### **The hardware**

One of the most impressive features of the QL is its size. That a computer this powerful can fit in a 5¾ by 1¾ by 18¾-inch unit that weighs about 3 pounds is amazing.

Sitting on the QL system board are four Sinclair-designed semi-custom ICs, as well as the microprocessor itself. The first IC, dual-sourced by



Plessey and Synertek, controls the display and memory; the second, dual-sourced by NCR and Synertek, controls other major system-level functions including the Sinclair Microdrive tape-storage units, local area network and RS-232C transmission, and the third and fourth, made by Ferranti, provide analog functions required by the Microdrives.

Standard in the QL is 128K of RAM, which is expandable externally to 640K via a plug-in cartridge available from Sinclair. As shown in Fig. 2, the cartridge plugs in at the left-hand side of the 65-key keyboard.

The keyboard features five special-function keys, as well as separate cursor-control keys. One drawback a user may find is the lack of a separate numeric keypad on the QL, you must use the number keys at the top of the keyboard. The *Microdrives* are found at the far right of the keyboard.



**FIG.2—THE NEW SINCLAIR QL shown with a prototype of the forthcoming QL 0.5megabyte RAM pack, connected via the QL's internal expansion slot.**


The QL provides two built-in Microdrive units for mass storage. Those tape drives are similar in concept to the tape storage units used in other systems such as the Coleco Adam. Each tiny tape that is inserted into the drive unit—as shown in Fig. 3—has a storage capacity of 100K. Those read-write drives have an access time of 3.5 seconds and a program-loading rate of up to 15 kilobytes-per-second. That's not nearly as fast as a disk drive, but it's a great improvement over cassette-tape storage.

The QL comes with a ROM-resident version of the BASIC programming language called Sinclair SuperBASIC, as well as the QDOS tape-operating system. It is all contained in 32K of ROM.

However, this isn't all that you will find in the QL system. The QL also uses a second processor—the Intel 8048—to handle keyboard I/O, sound, RS-232C reception and real-time clock functions. The inclusion of the second processor means that the 68008 doesn't have to handle housekeeping chores, as well as data-crunching and can thus devote its full capability to handling data.

The QL's video display capabilities are as good as many higher-cost microcomputers on the market. It

features built-in high-resolution graphics capability—512 by 256 pixels in eight colors—and allows the user the flexibility of employing either a dedicated color or monochrome monitor or a home television set. Part of the QL's memory serves as dedicated video RAM: 32K

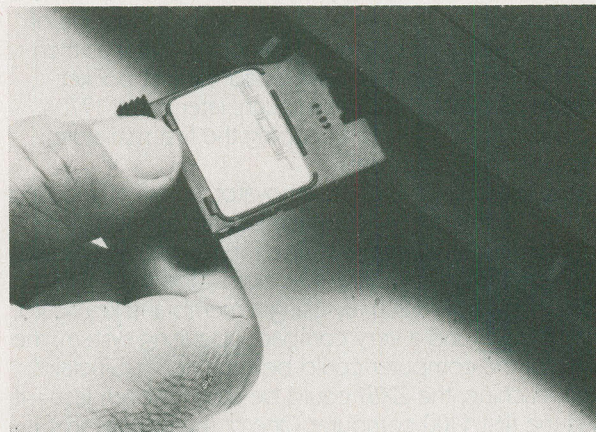

**FIG.3—INSERTING THE MICRODRIVE cartridge in the Sinclair QL.**

(about 8 pages) of memory, are dedicated to video memory locations. That means that each point on the screen is addressable and has a corresponding location in memory so it can be instantly updated or manipulated by an applications program. The QL normally displays the industry-standard 80 columns by 25 lines on a dedicated monitor and it offers you a choice of character sets. When it is used with a television set, its display is 40 to 60 columns, depending on the software used.

The preceding feature shows the impact the QL is likely to have on the computer market. Like its little relative, the ZX81 that is still being offered by Sinclair, it will prove to computer users that a computer doesn't necessarily have to cost a bundle to be a "real" device and not a toy. The ZX81 showed it in the low-end of the market, while the QL will show it in the desktop arena.

The QL also contains nine peripheral/expansion ports. They include one internal expansion port; one microdrive expansion port; a ROM cartridge port; two ports which can be equipped to handle serial interfaces; a local area network port, and two joystick ports. Also included is an RGB-output port and the RF (TV) output.

### The software

As was noted earlier, the QL is aimed at the business or home user with sophisticated needs and comes with a standard set of integrated programs that were developed over a period of 18 months by Psion. The applications include comprehensive word-processing, planning, information handling, and graphics capability that are integrated in style, structure, design and in the sharing of information.

The applications—QL Quill; QL Abacus; QL Archive, and QL Easel—all run under the QDOS operating system that is built into the system's ROM. QDOS, developed by Sinclair, has a number of features that are



only available on a microprocessor as advanced as the 68000 series. For instance, because it is capable of handling a great deal of data very quickly—depending on the timing and system resource sharing requirements—it can have two or more applications resident at one time, although only one of them can be active at any moment (it's still a single-user system, after all). That allows you to have a degree of multitasking capability (handling two tasks at nearly the same time). For instance, let's say you were receiving a file upload from another QL user, while you were processing text. Because the system is so capable, you could halt the word-processing program, bring up the file transfer program, and begin the transfer. Then, you could go back to your text-processing program as the file was transferred in the background and you could continue working. Or, you could just leave the file-transfer program up in the background and another user could call you and leave the file while you were doing something else.

As in everything, though, there is a catch and that is the more you ask the system to do, the more RAM you need and thus it's quite likely, although the company doesn't indicate this, that you need the full complement of RAM for the QL (640K). That is because multitasking—even for a single-user is still a memory-hungry function. The resident programs and the data that might be manipulated, input or output, all require their fair share of RAM.

QDOS also contains a time-sliced priority job scheduler, as well as display handling for multiple screen windows (here's where the dedicated video RAM becomes especially important because you can manipulate it separately and it shouldn't detract from the overhead needed by other functions). Finally, because of the nature of the operating system and the QL, QDOS provides device-independent input and output.

Also contained within ROM is Sinclair SuperBASIC, a good implementation of the standard programming language. It features procedure structuring; extendability, including syntax; a clean machine-code interface; equal capability for strings and arrays; a full-screen editor, and full error-handling facilities. Since it is an interpreted, rather than a compiled language—the system must interpret the source code before it can be used—it tends to be slower than a compiled language, which is written directly to machine code through a compiler routine. However, interpretation speed is independent of the size of the program, so you have fairly fast program execution. Finally, as in other advanced implementations of BASIC, the operating-system facilities are accessible from BASIC.

As for the rest of the software available which operates under QDOS, the key tenet is usability. The software has been designed to make the word-processing, spreadsheet, database and graphics capabilities available and usable by people with no prior training.

That has been achieved by using several interesting concepts: pyramidal; "do-and-see," and "inform and decide." The pyramidal structure of the software takes

you directly to the most commonly used facilities. It enables even the most inexperienced person to perform useful tasks immediately. And, as you become more experienced with the software, you can make the software do more things.

At all times, the software is "do-and-see." In other words, it takes a totally interactive approach and the visual effect is immediately displayed in the video device. For example, the screen always shows exactly what will be output to a printer or plotter. There are no special control characters needed to indicate various type fonts. Instead, the type font itself is shown. In other programs, the only indication of a change in typeface is a special screen symbol.

Finally, the software is self-documented.

Throughout the programs, comprehensive information on the current status and on available actions are displayed. Continuous prompting is directed at the current action being pursued. In addition, a comprehensive help function is available in all the packages at all times.

The integrated software package allows you full text-processing capability, as well as spreadsheet functionality. Further, it allows you to create and manipulate data in a database and it allows you to combine all of the data created into a graphics display.

What does that mean? Suppose you had a report you had to file that needed inputs from a text-processing program; as well as financial data, and other information contained in a database. With an integrated program, you can integrate the text with spreadsheet financial information and database data into a final report and you can also integrate the graphics you need to complete it. Then, if you decide to change something, the report is automatically updated. Isn't it a nice feature? That means you don't need filtration programs and programs that make one data file compatible with a second or third program and it makes your operation more efficient.

The key to this functionality is a common file structure that allows data created under one program to be used by another, which the QL software does.

## The future

As you can see from the foregoing, the Sinclair QL is a powerful machine and it shows that you needn't pay a high price for a high performance machine. That is just what the ZX81 did and it's quite likely that is what this new machine will mean.

The inexpensive pricetag shatters the mystique of the computer marketplace where a high price was equated with quality and functionality. The QL, with its advanced microprocessor, graphics capability and advanced software, has both quality and functionality, but in a price that is lower than \$500. And, it offers users one feature that is a costly add-on in many systems, the ability to tie into a Local Area Network or LAN. The LAN has been touted as the gateway to information sharing in the electronic office of the future and it shows that Sinclair's thinking is on that office. He aims at giving people a quality alternative for a reasonable price. ◀◀▶▶



# PRINTING BUFFERS

*No, you don't have to sit there and glare balefully at your computer while you wait impatiently for the printer to play "catch-up."*

HERB FRIEDMAN

■Pithy sayings and cliches are endemic to all aspects of life and we have our share of them in electronics. The radio amateurs have "If you can't hear 'em you can't work 'em." Generations of hi-fi enthusiasts have had "The system is only as good as the weakest link" drummed into their ears for years. Computerists have "A computer is only as fast as the slowest peripheral."

Among the very slowest of peripherals is the printer. While the computer is all set to zip through a monstrous database in seconds, the printer is putting it all on paper a letter at a time, tick, tick, tick.....tick. And during the time when the printer is doing its tick...tick...tick, the computer sits idle, waiting for the printer to stop.

Depending on the printer's inherent speed, the idle time can be enormous. For example, consider a 3000-word document, which represents 12 pages of text, 25 lines-per-page, 60 characters-per-line—the defacto standard American business format. One of the modern competitively-priced matrix printers can zip along at about 80–120 characters-per-second. This sounds like *Superman* speed, but first, to create enhanced characters the speed is cut approximately in half, so at best we have 60 characters-per-second, which is 10 words, or one full line of print per second. Exclusive of paper feed or changes, 3000 words will take a minimum of 5 minutes to print. Not bad, you could most likely wait 5 minutes to use the computer.

But you don't want your letters to appear computerized by having matrix characters, so you use a letter-quality daisy wheel printer. A competitively priced daisy printer delivers about 12 characters-per-second. Now we have a whole new ballgame as they say. At 12 characters-per-second, not even allowing for changing the paper or the slower carriage returns and linefeeds it will take 25 minutes to print 3000 words, and that's a lot of time for a computer to be out of service just to print a document.

## The spooler

One of the earliest schemes to free the computer from serving as a storage bin for the printer was something called a *spooler*, spooler being an acronym for "Simultaneous Peripheral Operation On-Line," which in plain language means that disk drives and printers can be operational while a program in memory is active with some other function. For example, the spooler might be printing your thesis on perpetual motion while you're composing a letter to the local utility complaining about an electric bill for \$1000 during the month you were away on vacation.

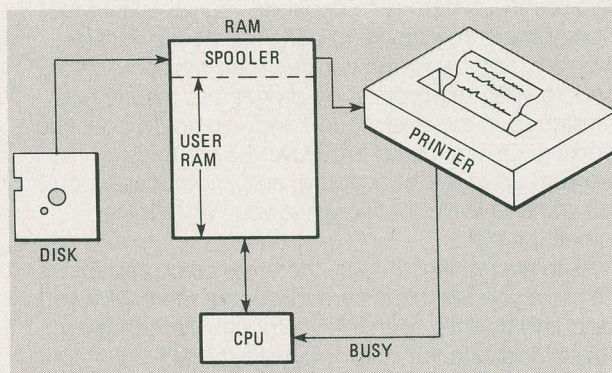


FIG. 1—THERE ARE AS MANY spooler software versions as there are word processors. Most of them work this way.

While there are probably as many versions of spooler software as there are word processors, they all more or less work as shown in Fig. 1. The spooler loads itself into high memory. When the computer "looks up" at the top of memory it sees not the actual top of RAM but the bottom of the spooler. Assuming the computer has 64K RAM, if the spooler requires 10K the computer has only 54K RAM available for the user and the computer "sees" 54K as being the top of RAM.

The spooler functions as a pass-thru for blocks of data from the disk to the printer. If the keyboard is activated it takes preference: the spooler holds off calling for a block of information and the computer functions normally; the user can then utilize user RAM for just about anything else.

Programs or functions in the user RAM are said to be in the *foreground*; the spooler function is said to be in the *background*. Only when the foreground is inactive is the background permitted to operate. Actually, because of the small buffer usually built into the printer, and a small buffer of perhaps less than 1K in the spooler (or even larger), the user rarely realizes it's all happening in fits and starts. With a well-written spooler it's almost impossible to detect any interruption in the printer's throughput even though activating the keyboard might delay the spooler by as much as three seconds.

Spooling is sometimes built into word processing software so the user doesn't have to twiddle his or her thumbs waiting for the printer to finish. With a software spooler the printer goes its merry way—as slow as it wants—while the user power-types through another document. The only thing the user cannot do is access the disk system while the spooler is active. That is not a problem if you're using the foreground to build a



spreadsheet for disk storage after the background spooling is finished, or if you plan to use only non-disk functions until the printing is finished. But, if your foreground task involves the disk system, something's got to give. If you're *boilerplating* a document and the pre-written paragraphs are going to come from disk, the foreground and background tasks are usually going to be mutually exclusive. The few spoolers that can time-share the disk system generally take up so much RAM there's little remaining for the foreground task. So there must always be a compromise of sorts as long as the spooling is done through software.

### Hardware spoolers—the printer buffer

When there's no room for compromise, when you want to print and yet have full access to the disk system, you must totally divorce the printing function from the computer. That is done with a hardware spooler, an electronic device usually called a "printer buffer," or a "printer controller," or a "printer optimizer." To avoid confusion, we'll refer to all of the hardware devices as a *printer buffer* regardless of what it's called by the manufacturer.

The basic concept of a printer buffer is a 4-terminal *black box* full of RAM (memory) which is controlled by its own internal CPU (Central Processing Unit). Two input wires connect to the output printer port of the computer, the remaining two output wires connect to

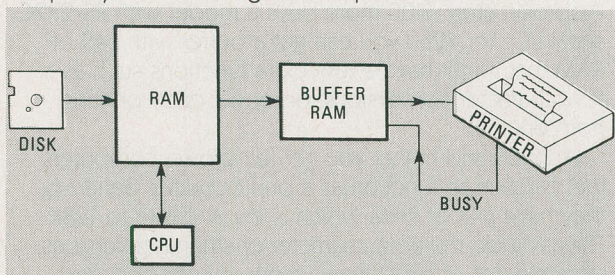


FIG. 2—BLOCK DIAGRAM SHOWS the physical arrangement and interconnections of the printer buffer.

the input of the printer. The physical arrangement is shown in Fig. 2. The internal structure of the buffer is such that, to the computer, it appears to be a printer, while to the printer the buffer appears to be the computer.

When the computer is given the command to PRINT, it dumps to the buffer, filling the buffer's RAM with a mirror image of the signals intended for the printer. Understand this point very clearly: The buffer does not receive a mirror image of the computer's RAM; rather, it receives what is intended for the printer. The data stored in the computer's RAM is what determines the signals sent to the printer, but it is not necessarily the same.

Generally, the buffer outputs immediately to the printer, which thinks it's getting data from the computer. In a matter of seconds—the precise time depending on the amount of data to be transferred from the computer to the buffer—the computer has completed its dump and is free for any other use. The printer chugs along doing its own thing at its own speed using the data from the buffer; it no longer has any effect on

the computer.

Now it's entirely possible that the data in the computer exceeds the RAM available in the buffer; you could have a buffer with 16K RAM while your document takes up 18K in the computer. In this instance, the buffer busies-out the computer until there is free RAM available in the buffer.

It works this way: As shown in Fig. 3, when the buffer's RAM is full, the buffer sends a "busy" signal back to the computer through the handshake connection in exactly the same way as the printer would stop output from the computer. The memory in the buffer is arranged in an overwrite stack, that is, it fills from memory location 0000 and transmits to the printer from 0000. As data in RAM is sent to the printer, the RAM is considered empty and available for new data. After a predetermined block of RAM is free the busy signal to the computer is lifted and the free RAM is loaded with fresh data. As soon as the buffer's RAM is full the computer is busied-out until another block of free RAM is available for data storage. Meanwhile, the buffer's CPU is working its way through the stack. When it gets to address 16K it returns to 0000 and sends the new data, once again moving down the stack through the fresh data. Again, when a sufficiently large block of RAM is cleared, the busy is lifted and the computer fills the free RAM.

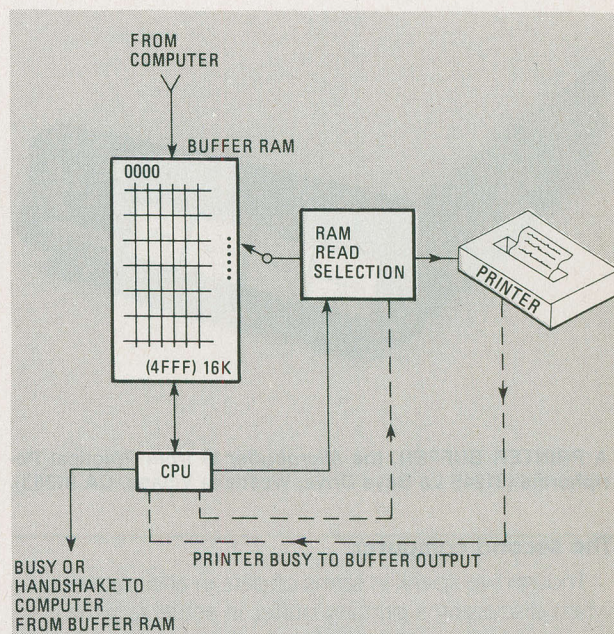



FIG. 3—WHEN THE BUFFER'S RAM IS FULL, the handshake connection sends a "busy" signal back to the computer.

When the computer dumps the remainder of its data, it is free for another purpose even though the buffer is still feeding the printer. So as you see, when the data in the computer's RAM exceeds the capacity of the buffer's RAM it might take somewhat longer than a few seconds to free the computer, but it won't be much longer. Using our previous illustration of 18K of computer data with a 16K buffer, we have 2K of data that cannot be accommodated by the buffer in the initial "fill." The printer runs at, say, 60-bps (bytes per



second). It will take, therefore, an additional 33 seconds for the buffer to release the computer. Actually, 33 seconds is a "nominal value" because the printing commences the instant the buffer's RAM starts to fill, the printer doesn't wait for the RAM to fill. On the other hand, a buffer generally makes its free RAM available to the computer in blocks: it might well accept output from the computer when the first "page" of 256 bytes is free, or 512 bytes, or 1024 bytes, or whatever it's designed to accept as a block of data.

That is really a worst-case scenario because rarely does the computer's stored data exceed the buffer's RAM. In general, few documents exceed 12K bytes, the equivalent of 8 pages of double spaced text at 250 words-per-page. Those who consistently work with larger documents will not use a 16K buffer. More likely, they will use a 64K buffer, which exceeds the total user-available RAM of an 8-bit computer. (In this instance "user-available" means the RAM not used for the computer's operating system and the foreground program.) For example, one of the popular word processors for 64K computers leaves slightly less than 30K available for text storage, so the most the buffer will have to accommodate is 30K of data.

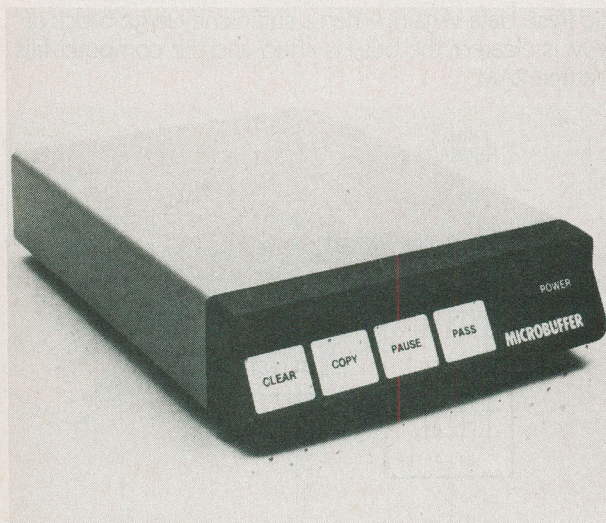

**A PRINTER BUFFER, the *Microbuffer* is from Practical Peripherals (31245 La Baya Drive, Westlake Village, CA 91363).**

### The second computer.

Though we speak in terms of data in and data out when discussing a printing buffer, in actual fact the device is really a somewhat specialized computer, and once something is a computer it's possible to create many diverse functions. The simplest, least expensive buffers serve primarily as RAM storage devices—what flows in flows out unmodified in any way. But the same internal "computer" that handles the data flow can also do things like character and string conversions. For example, assume you are using a Radio Shack *Model 4* computer. This creates a beautiful problem because Radio Shack's own software assumes a printer that does an automatic carriage return after a linefeed, so Radio Shack's software does not transmit a carriage return after a linefeed. On the other hand, most standard CP/

M software that will run on the *Model 4* transmits a line feed after a carriage return. Because of the automatic linefeed of the printer you now have two linefeeds when you want just one. You could probably reprogram the internal switches of the printer each time you changed operating systems (usually requiring some disassembly of the printer), but an easier way is to simply program the buffer (through a keypad) to convert ASCII code 13 (CR) + 10 (LF) to just 13 (CR). The buffer will now straighten out the carriage returns and linefeeds. Each time it comes to a CR + LF command in its own RAM it will output only CR.

Some buffers can also memorize a string of characters, substituting them for a single symbol. For example, an intelligent buffer can be programmed so a single "#" character in a document causes a complete letterhead to print. In effect, # equals: SuperAntenna Repair Co., 12 Howling Wind Rd., Windy City, NH.

When you can't afford to keep your computer tied up just running the printer, or you need some oddball character and string conversions, the easiest way to do the job is most likely to be a printer buffer.

Printer buffers come in all sizes, shapes, and prices that range from about \$200 to well over \$500. The lowest cost models are essentially RAM storage devices of 16K intended for parallel Centronics-compatible input/output ports. Those models can generally be expanded to at least 64K, possibly even 128K or 256K. Approximately \$100 more buys a model with RS-232C serial I/O. For \$250 you can get a buffer with 64K of RAM that might have a few extra functions such as a few character conversions, or repeat copy printing from one fill.

At \$500 and higher you get full-blown computers that happen to function as a printer buffer. Generally, they have 64K of RAM which is expandable to 128K. They will do multiple character or string conversions, store macros of substantial length, merge stock text with mailing address input, directly drive more than one printer, convert from serial to parallel I/O or vice versa, provide two or three printer outputs for a single input...the list of special functions is seemingly endless.

No buffer that we have seen, regardless of price, has all the functions of every other printing buffer. No matter how sophisticated a buffer might be, if it hasn't got the one single feature that's important to you it's not worth the money. If you work with large documents then you need at least 64K of RAM, that's important. If you have several printers with different printer codes maybe a buffer that does extensive conversions is what you need. If you do a lot of form letter mailing, a highlight feature for the printer buffer you need might be extensive (and long) macros or the ability to stack texts so they print one after the other in perfect sequence.

For personal computers, printer buffers are still in the introductory stage, so advertisements vie for your attention with endless lists of functions and features. A good rule of thumb to use when considering a printer buffer is: "If the function or feature isn't clearly listed—if it's implied or assumed—it probably doesn't have it." ◀▶



# PC: "PERSONAL COMMUNICATIONS"

*Your computer's window on the world*

HERB FRIEDMAN

■The concept of "personal communications" as applied to personal computers changes so frequently that it's most difficult to keep up with "what's new" both in terms of services and the software needed to access the services.


Often, what's new and exciting is not what's efficient and practical but what is fashionable. For example, many of the very same magazines that run "in depth" articles on how to join the revolution in on-line computer services get their author's articles on "hardcopy," *hardcopy* being *technese* for a typewritten sheets. Others, which claim to be computerized, actually request their authors supply the article on a disk specifically formatted for a particular computer that uses one particular kind of word processor, usually WordStar.

On the other hand, **Radio-Electronics**, which is a general electronics publication, has been truly computerized almost from the earliest days of personal computing. R-E gets its columns and features by computer to computer transfer; the hardcopy serves only as a reference backup. Better still, an author can dial-up R-E and dump the manuscript using any preferred word processing program, not just WordStar. Standard, generally-available communications software at R-E automatically modifies the author's upload for R-E's preferred word processor. For example, my files are created with TYPIT, which puts a carriage return after every line in the format that I use for ASCII text transfer. R-E's communications software strips off the linefeeds before they ever get to the storage disk.

Until very recently, that kind of data exchange represented typical personal computer communications: Hobbyists exchanged data and programs (let's be honest and call it "pirating" programs), businesses got information from field offices and salespersons, and college students did their computer work from their dormitories (in those schools with an enlightened administration). However, since personal computers became just another appliance found in many households there has been a dramatic shift in the type and kind of personal communications and the required software.
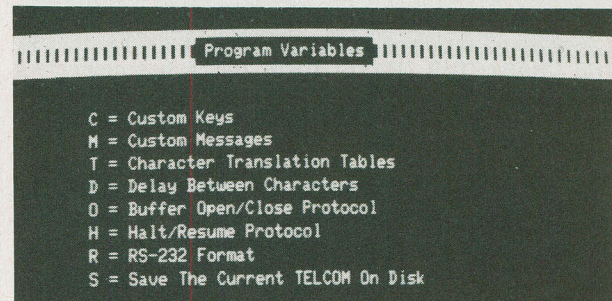
## The communications package.

Today, the fashionable use for personal computer communications is to access the on-line information services, and much of the communications software—what is called the "communications package"—is specifically tailored to access these services.



**MOST MODERN communications software, even the least expensive, permits customization of program variables of TELCOM2, one of the most powerful but least expensive packages.**

For those of you not familiar with the term *on-line*, it originally meant equipment and/or software ready for immediate use. By logical extension to personal computing, it means an information service or network which can be accessed by a personal computer through the dial-up telephone system. All that's needed for on-line access of an information service is a personal computer, a modem, and a software package that programs the computer to emulate a "smart terminal."

A smart terminal is one that can store (download) incoming data and transmit (upload) its own tape or disk files, or data stored in its memory. This contrasts with a "dumb terminal," which is only a keyboard and display, or a computer that emulates only a keyboard and a display.

While a dumb terminal can also access computers and on-line information services it cannot store incoming data, nor can it upload its data. As fast as the incoming information scrolls off the screen it's gone unless fed to a printer. The dumb terminal is simply not adequate for modern on-line or personal communications use, so we will ignore it from here on; we limit our discussion to smart terminals—a full blown computer that also functions for communications.

Dial-up on-line information services—the Source and CompuServe being the best known—have been with us from the early days of personal computing. Today, we also have the Dow Jones News Service for the Wall Street gamblers, even more specialized services for farmers, information networks only for those with IBM computers, and....you name it. If someone thinks people will pay money for information of any kind they start up an on-line information service.



Terminal Output		
FROM		TO
3	----	5
60	----	91
62	----	93
----	0	0
	0	0
	0	0
	0	0
	0	0
	0	0
	0	0
	0	0
	0	0

Up, down, new value (0-255) or <BREAK>:

**THE CHARACTER TRANSLATION TABLE** has characters specified in decimal ASCII and converts outgoing CONTROL-C (3), < (60), and > (62) to CONTROL-E (5), (91), and (93).

Most communications software provide for easy access to the information services through extensive *macros*, a macro being a complete "message" transmitted by touching only a single key. For example, a macro will transmit the telephone number of an on-line information service (assuming use of an auto-dial modem) and wait to receive the required prompt. On receipt of the prompt, the computer then transmits the required response...and repeats this first-you-then-me exchange several times until the local computer is linked and signed into the information service.

If the software is to be used for several on-line services employing different operating codes (called *protocols*), many communications software packages also provide for automatic translation of transmitted or received ASCII characters. For example, assume that many of the on-line services you access require a CONTROL-C to "bail out," but one service requires a CONTROL-E, and you never can seem to remember the one which is not CONTROL-C. If you have a communications package such as TELCOM (Mumford Micro Systems, Box 400 Summerland, CA 93067) or OMNITERM (Lindbergh Systems, 49 Beechmont St., Worcester, MA 01609), you can create a special version that will automatically translate a CONTROL-C to a CONTROL-E. In this way you always use a standardized keyboard entry which the computer translates to the correct characters for the remote computer or information service.

### Introducing E-mail.

In the past year or so there has been a considerable change in the use of personal computers for both on-line information services and what is called E-MAIL (Electronic Mail). The use of those services is increasing at such a rapid rate that software is now being tailored more toward specific on-line/E-Mail use than for the kind of conventional data and program exchange of the early users of personal computers.

First, popular access to on-line services is no longer primarily for entertainment after prime time when on-line information service rates are lowest. Many on-line services cater to business users and access to the service must be at the touch of a button; no one has

time to waste dialing, then punching in strings of access codes, and finally flipping through a menu. So the most modern communications software provides for extended macros; one key dials the service, handles the sign-on protocols, and goes directly to the desired information area of the host computer. True, many older programs had this feature, but the most recent software has macro sign on and automatic E-Mail.

E-Mail is so important a concept to those who can use it efficiently that some New York banks prominently feature E-Mail as one of the highpoints of electronic banking. (Problem is, the pitchman—or is it "pitchperson"—mumbles when they get to the part about how E-Mail can only be sent to other users in the same bank's network.)

One can see the importance of E-Mail by simply looking at the new software packages, such as IBM's "Personal Communications Manager" for the IBM PC/PCjr. Virtually the entire package is oriented towards E-Mail. Like much of the latest communications software, PCM gets involved in unusually sophisticated protocol transfers.

A *protocol transfer* is a method of data transmission that insures an error-free download, upload, or exchange. Until recently, most personal computer protocol transfers involved data and programs, not ASCII text. Instead of exchanging data using ASCII characters, the data is an exact representation of the binary information, and it is transmitted in blocks. Depending on the specific software, error checking is done through a CRC (Cyclic Redundancy Check) or a checksum. Both are means whereby each block of data is followed by a value derived from the data. If a bit gets glitched during transmission the CRC or checksum doesn't match the value of the received data and the host computer automatically requests another transmission. Only when the CRC or checksum matches the data value is the data stored in the computer's memory or written to mass storage.

As a general rule, communications software has some limit on the number of protocol "tries" before it quits and informs the operator there is a data loss.

Smartcom II			Hayes Microcomputer Products, Inc.		
1. Begin Communication	*. Receive File	7. Change Printer Status (OFF)			
2. Edit Set	*. Send File	*. Select Remote Access (OFF)			
3. Select File Command	6. Change Configuration	8. Display Disk Directory (ON)			
A, B - Change Drive		8. End Communication/Program			
	Press F2 For Help				
Enter Selection: 1	Originate, Answer: 0				
Enter Label: 1					
Communication Directory:					
A - THE SOURCE Telenet	J - THE SOURCE Tymnet	S -			
B - DJN/R Telenet	K - DJN/R Tymnet	T -			
C - CompuServe Network	L - CompuServe Tymnet	U -			
D - KNOWLEDGE INDEX TEL	M - KNOWLEDGE INDEX TYM	V -			
E - Peoples Msg System	N -	W -			
F - Access (Phoenix)	O -	X -			
G - FORUM-80 (Kan City)	P -	Y - Remote Access			
H - ABBS (New York)	Q -	Z - Standard Values			
I - ABBS (Chicago)	R -				
Smartmodem: UNAVAILABLE					
20:23:17			Tuesday March 20, 1984		

**THE MENU OF SMARTCOM II** not only lists every function, but also the services programmed for automatic access through the Communications Directory.



Somewhere around 8 to 10 tries is standard before the computer quits and warns the operator that a reliable exchange isn't possible.


Some software entertains the operator with a running count of the number of blocks transmitted or received, the number of errors, the number of tries, etc. None of this information has any real value, but it beats staring at a blank screen.

### The protocols must be compatible.


A protocol exchange requires that both computers recognize exactly the same set of control signals—the "protocol." If one computer uses, say, X-ON/X-OFF (CONTROL-Q/CONTROL-S) to start and stop transmission while the other recognizes only ETX/ACK (CONTROL-C/CONTROL-F), or if the computers use different means of calculating the checksum, they will never be able to do a protocol exchange because they will always be searching for control signals that never arrive.

Unfortunately, manufacturers like to insure that people purchase their products, so few communications software packages employ protocols used by other communications software. TELCOM won't do protocol exchanges with CROSSTALK (Microstuff, Inc., 1845 The Exchange, Atlanta, GA 30339), and SOFTCOM (The Software Store, 706 Chippewa Square, Marquette, MI 49855) won't do protocol exchanges with UNITERM (BT Enterprises, 171 Hawkins Rd., Centereach, NY 11720), etc., etc, ad nauseum. About the only outfit that really gives the user a break is MITE (Mycroft Labs, Inc., Box 6045, Tallahassee, FL 32301), which recognizes the CLINK (Crosstalk), XMODEM (public domain), HAYES (Hayes Microcomputer Products, Inc., 5923 Peachtree Industrial Blvd., Norcross, GA 30092) and IBM PC protocols—which encompasses the majority of the commonly-used CP/M-IBM personal communications software.

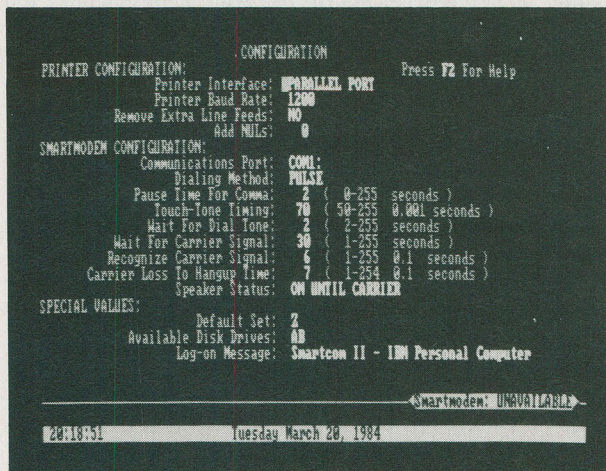
When only interactive text is involved there is usually no need for protocols because the data is exchanged on a character by character basis, not in blocks, and the exchange is continuously viewed. The operator can



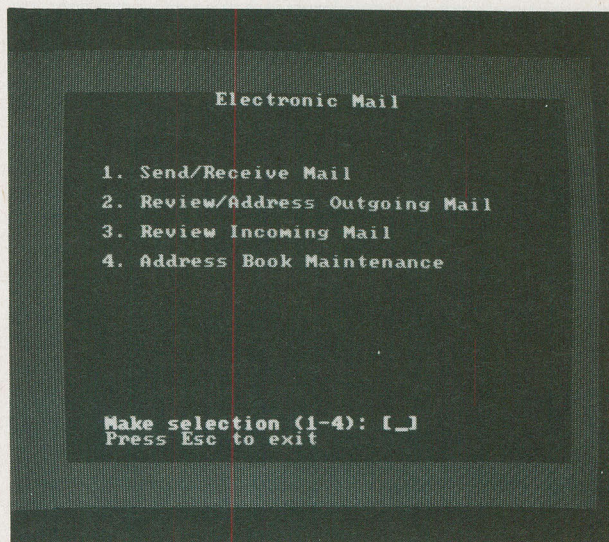**THINK OF ANY CONFIGURATION and SMARTCOM II will probably let you do it. (Smear of screen is caused by automatic highlighting.)**



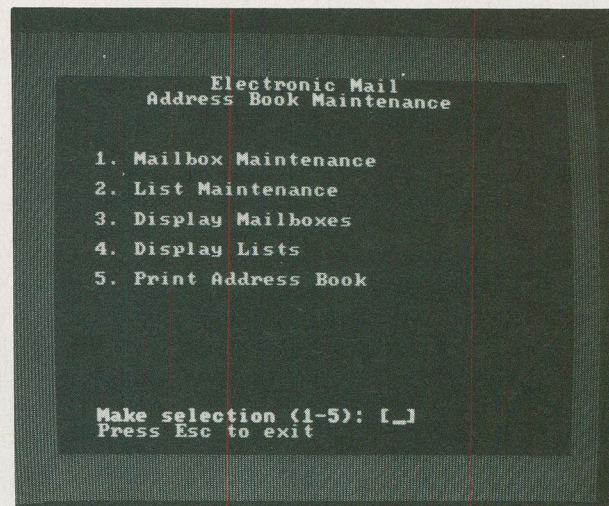**IBM'S PERSONAL COMMUNICATIONS MANAGER is big into E-mail. This sub-menu shows just some of the E-mail options.**



**If you select Address Book Maintenance, you will see this menu that gives you 5 more choices.**


easily recognize a glitch and make an informed guesstimate, or ask for a repeat transmission. The data exchange in this instance uses ASCII because the on-line services and hardware all recognize ASCII. If you access the Source, CompuServe, etc., your computer sends and receives ASCII-encoded characters.

Some software does a checksum or CRC check of ASCII text but doesn't interfere with the exchange. It just informs the user(s) there was an error.

But modern applications of the personal computer have strained the non-protocol ASCII exchange with which most users of personal computers are most familiar. E-Mail is the wave of the present for many business users, and so communications software must provide for error-free data exchange of text. Why error-free? Imagine sending a construction bid by E-Mail and it arrives as \$125,000 instead of \$12,500.

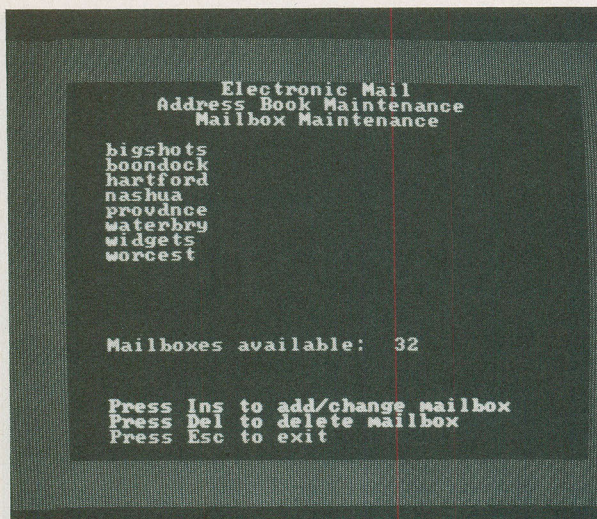E-Mail oriented communications software is more or





**YOU NAME THE MAILBOXES** in IBM's program. To deliver your mail, just enter the name of the mailbox and the computer will auto-dial the remote location and deliver your message—all unattended.

less the same as any other communications software, but it also includes protocol exchange and has many special features specifically intended for E-Mail. Most important, the E-Mail usually referred to is not the E-Mail of the on-line services whereby you leave a message for another subscriber in an "electronic mailbox" at the Source or CompuServe.

### What is E-Mail?

E-Mail is a real document, a letter, data, memo or whatever you would normally put down on paper for exchange between two business offices (at least for the present). True E-Mail oriented communications software is clocked and dated; it will automatically transmit your document at a specific date and time. It will go to an internal Address Book, look up the telephone number of the office for which a message is intended, automatically dial the remote telephone and redial until a link is established, transmit the correct remote access codes, compare the return confirmation codes, then go to the data file, locate the desired file and transmit the document using an unusually precise protocol to virtually eliminate any possibility for transmission error, and finally sign off and disconnect.

Similarly, true E-Mail software will automatically answer the phone, go on-line, test for protocols, receive and store incoming data using the same precise protocol, and then disconnect. The user can even program what time the computer should auto-answer the telephone line to prevent all callers from being greeted with an answer-tone.


Though many E-Mail features are found in conventional high performance communications software, the major differences are the protocols, internal Address Book access, and header-derived transmissions. As for the protocols, IBM's latest personal computer communications package for home and business, "Personal Communications Manager," uses the Microcom Networking Protocol. It matters not whether

this is the best or worst protocol because today, by popular demand, software must be IBM-compatible, hence, the Microcom Networking Protocol will most likely become the defacto E-Mail standard for home and business, just as the XMODEM protocols are the defacto standard for CP/M bulletin boards.

In a typical E-Mail system each office or location is considered to be a mailbox, identified in the Address Book by a specific codeword or identification. The mailbox file contains the identification, the telephone number and access protocols. For example, Super-Shlock Industries, manufacturers of gold-plated widgets, might be identified by the single word WIDGET, while your own home office might be identified as BIGSHOTS, with a field office identified as BOONDOCK.
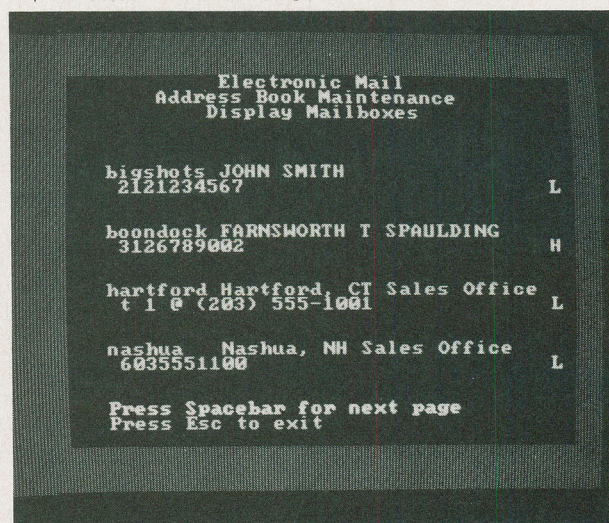
### You need a header.

Each time you selected a document for transmission you would assign a header to the outgoing log that selects the files to be transmitted. Documents to be transmitted after hours to the home office would have the header BIGSHOTS. Orders and requests for bids to Super-Shlock Industries might have the header



**WANT TO SEE WHO PICKS UP THE MAIL** at the mailbox? You can call up the list at the touch of a key. The character L or H at the right means low speed (300 baud) or high speed (1200 baud) modem—again automatically selected.

WIDGETS. Five inquiries to the field office asking for information on how many left-handed screwdrivers were in stock would have the header BOONDOCK.

To transmit your document(s) to the field office you would program the communications package to send files coded BOONDOCK at 1:30 AM. At 1:30 in the morning the computer would start up, locate the phone number identified as BOONDOCK in the Address Book, dial the listed telephone number, and after the communications link was established it would search out and upload all files logged as BOONDOCK.

Same thing with the other files. At 3:00 A.M. the computer might "come-up," find itself programmed to transmit WIDGET files, so it would access the telephone circuit associated with the WIDGET identifier



in the Address Book, and then upload all logged WIDGET files.

An important component of any business operation is "accountability," which is the business-administrator's way of pinning the blame for mistakes on someone else. While general purpose communications software can be used for E-Mail, true E-Mail software keeps a log of incoming and outgoing traffic. It records who sent what to whom at which telephone number at what time. If the Skyhook Antenna Company claims it never received your order for 25 direct broadcast satellite antennas all you need to do is consult the log, if you sent your order by E-Mail. The log will show the date and time the telephone number was dialed, the protocol identifier exchange (if recorded), the subject or name of the transmitted file (your order), and depending on the particular E-Mail software, the


number of tries, failure or success of the protocol exchange, and possibly the disconnect time. It will be difficult for Skyhook Antenna Inc. to deny your order when you have virtually a confirmation in your log.

As with just about everything else in personal computing, new developments are often ready for the marketplace before you even get a chance to become familiar with the hardware and the software you recently purchased. In the field of personal computer communications, be prepared for some startling developments in personal and business E-Mail because it works so well and so easily, and can leave a rather detailed audit trail. Also look at it this way: The junk mail you get through E-Mail doesn't clutter your mailbox and doesn't have to be taken out for the garbage pickup. You get rid of it with the simple command ERASE. ◀▶
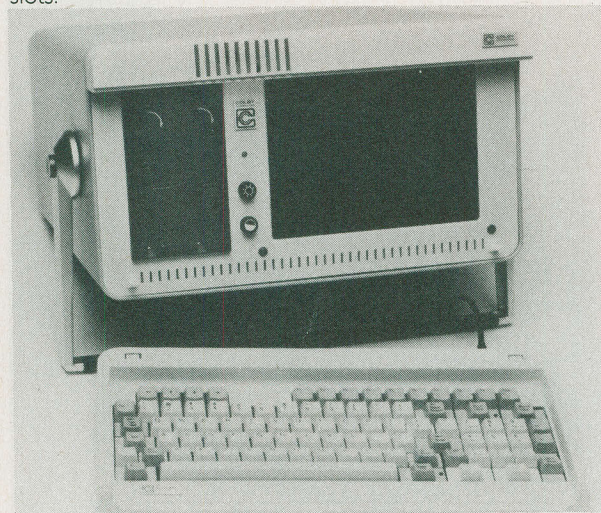
# COMPUTER PRODUCTS

For more details use the free  
information card inside the back cover

**IBM-PC COMPATIBLE COMPUTER**, the Colby PC-3, is a standalone, transportable computer that incorporates Colby's "high density" IBM-PC compatible motherboard with many functions on the motherboard that would ordinarily require additional plug-in boards, taking up space in the expansion slots.



**CIRCLE 121 ON FREE INFORMATION CARD**

The unit weighs 26 lbs., has a 9-inch amber screen and dual 360K double-sided, double-density floppy-disk drives. It measures  $8\frac{1}{2} \times 16 \times 16\frac{1}{2}$  inches, has  $3\frac{1}{2}$  IBM-PC expansion slots, and a full-width carrying handle that doubles as a tilt stand. The computer can be stored under an airline seat.

The PC-3 comes standard with 128K of RAM (but can be upgraded to have as much as one megabyte of RAM on the motherboard), a real-time clock, serial port, parallel port, SASI hard-disk interface, and an 80-column  $\times$  25-line display with IBM-fiPC compatible graphics capability. It is priced at

\$2795.00.—**Colby Computer**, 849 Independence Avenue, Mountain View, CA 94043.

**EQUATION-PROCESSING SOFTWARE**, *TK!Solver* is an equation-processing program that makes it easy to solve mathematical problems without programming. The user simply enters the model (one or more equations), types in the known values, and presses the action key. The program finds all of the unknown values.

All the tools needed for problem-solving are built into the program, including mathematical functions, facilities for converting units of measurement, and the ability to produce graphs and tables. With the program, the user can create his own mathematical functions and use them along with the built-in functions.

File Comment ** ELECTRICAL CIRCUIT **				Copyright 1983	59
*****					
St Input	Name	Output	Unit	Comment	
*****					
** ELECTRICAL CIRCUIT **					
E	U		V	voltage drop over circuit (potential d	
	I	1.8	A	current flow through entire circuit	
	P	18.8	W	power use of circuit	
	R	3.333333	Ohm	overall resistance	
COMPONENT RESISTANCES					
	R1		Ohm	first resistance (in series)	
	R2	3.333333	Ohm	second resistance (in series)	
				also result of 2 parallel resistances	
10	R2a		Ohm	one of two parallel resistances	
5	R2b		Ohm	one of two parallel resistances	
ENERGY AND TIME					
	t	77.168494	h	elapsed time	
000000	work		J	energy used, work done	
	Q	500000	C	charge moved through circuit in elapse	

**CIRCLE 122 ON FREE INFORMATION CARD**

*TK!Solver* applications packages, designed for use with the *TK!Solver* program, solve problems in specific fields. They contain models, which in turn contain the necessary equations, values, and tables for solving a particular problem. The models provided in the applications package can be




modified by the user, if desired.

*TK!SolverPacks* are available for Introductory Science, Mechanical Engineering, Financial Management, and Building Design and Construction. Additional *SolverPacks* are promised in the future, including packages based on educational books published by McGraw-Hill Book Co.

*TK!Solver* has a suggested list price of \$399. The *TK!SolverPack* applications packages are priced at \$100 each—**Software Arts**, Borman/Williams, Inc., 156 Fifth Avenue, New York, NY 10010.

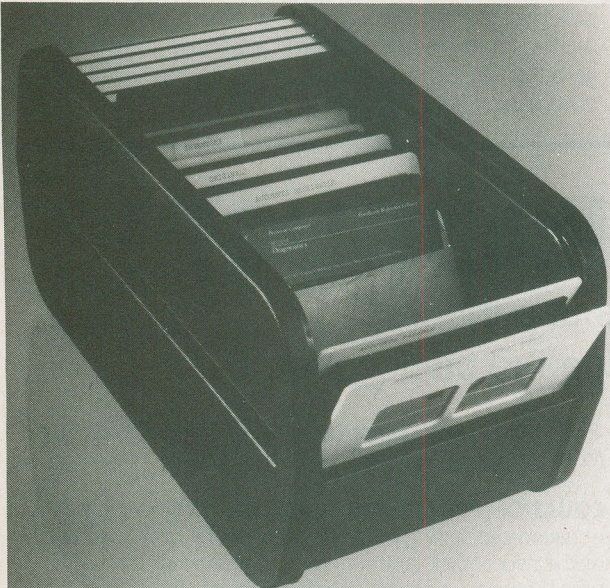**DISK FILE**, the Rolltop 100, known as the "Executive" features a silver rolltop enclosure and a textured black high-impact plastic body. It holds 120 diskettes and comes with 10



CIRCLE 123 ON FREE INFORMATION CARD

dividers and color-coded labels. The Executive Rolltop 100 Disk File is priced at \$39.95 (model *RT100E*). A locking model for securing valuable programs or data (Model *RT100EL*) is priced at \$49.95.—**Microcomputer Accessories, Inc.**, 6721 Buckingham Parkway, Culver City, CA 90230.

**COLOR-GRAPHICS TERMINALS**, *Graphos II* and *Graphos III* feature shiftable cell architecture and 16 independently



CIRCLE 124 ON FREE INFORMATION CARD

managed screen windows that can smooth-scroll in any direction, be used to compare images, and mix graphics and alphanumerics. The windows have individual color tables and are central to device-independent operation.

Both *Graphos II* and *Graphos III* are well suited for the OEM, systems integrator, and software developer. Each terminal communicates through an RS-232 connector with practically any host computer, and attaches to a variety of monitors. Those terminals can be rack-mounted or used on a desk.


The two terminals differ in memory, speed, and number of colors. *Graphos II* runs at 6.25 MHz and has 16 colors displayable on a TTL-input monitor. It is priced at \$3,995.00 (without monitor). *Graphos III* is an enhanced version capable of generating 32,768 colors on an analog RGB monitor, has a speed of 12.5 MHz, and more memory (256K vs 128K graphics RAM; 224K vs 128K local storage RAM). It is priced at \$5,485.00 (without monitor). Complete packages with 13" and 19" monitors are available.—**Ithaca InterSystems**, 1650 Hanshaw Road, Ithaca, New York 14850.

**PRINTER STAND**, *Printer Caddy* is a solid oak-wood container for your printer. The finish comes in light, medium, and dark wood, with the natural markings of the oak wood showing through. There is easy access to printer paper, with two doors front and back; there are also dual fans for cooling,



CIRCLE 125 ON FREE INFORMATION CARD

and an adjustable printer shelf that features 3/4" sound-suppression material.

Overall dimensions are 32" x 27" x 44". The printer stand may be moved about easily on four over-size ball-bearing casters. The "*Printer Caddy*" is priced at \$490.00.—**Daisy-Net International, Inc.**, PO Box 1152, Northbrook, IL 60062. 



sure the resonant frequency.

In order to determine the unknown value of an inductor, place it in parallel with a known capacitor; or for an unknown capacitor, use a known inductor. Measure the resonant frequency with your GDM and you have two of the three values specified in the standard formula:

$$f_r = 1/2\pi\sqrt{LC}$$

Where  $F$  is the frequency in hertz;  $\pi$  is equal to 3.1459;  $L$  is the inductance in henry's, and  $C$  is the capacitance in farads. From that basic formula you can solve for the unknown value. To find the value of an unknown capacitor, for instance, use the equation:

$$C = 1/4\pi^2 f^2 L$$

Let's look at an example: Say that you measure the resonant frequency at 10 kHz and you know the inductance to be 10  $\mu$ H. Substituting the numerical values for their respective symbols in the above equation will yield a capacitance value of 25.33  $\mu$ F.

By reversing the positions of  $L$  and  $C$  in the equation, you can solve for the inductance. Another way, to find the value of an unknown capacitor or inductor would be to use the chart that can be found in any

good radio handbook. Also, keep in mind that building a GDM is a good project.

### Computer tapes revisited

You may recall that the August 1983 Hobby Corner contained a piece about copying computer tapes. The gist of it was that copying from one tape machine to another was an unsatisfactory, if not impossible undertaking. It appears, however, that some of you have had some success with just such copying.

The most informative letter came from Rick Cook (AZ) who is researching this very subject for a book to be published by Sybex. Rick has had the greatest success using relatively inexpensive recorders and high quality tape. He says (as do the others) that finding the right control settings for both machines can require a lot of trial and error. If you are interested in the details, look for Rick's book.


Perhaps my difficulty was a lack of patience in experimenting to get the settings just right. Instead, I got a signal conditioner and then could hardly miss making good copies.

Speaking of signal helpers, P. J. Donnelly (NY) wrote about a passive conditioner for use with Timex/Sinclair tapes. It's call the *Winky Board*, and is available from G. Russel Electronics (RD

*continued on page 75*

## Electronic Troubleshooting

# WINNER

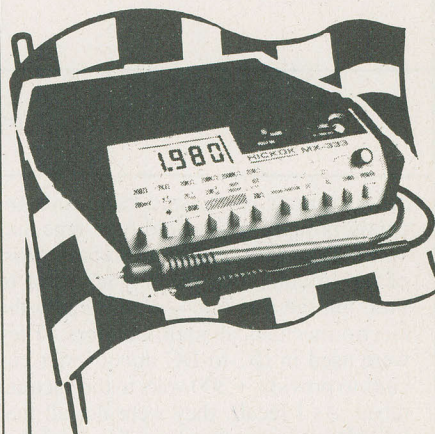

**Hickok's MX333 with  
VARI-PITCH® and LOGI-TRAK®**

Instantaneous VARI-PITCH speeds:

- Voltage tracing
- Troubleshooting in hard-to-reach locations
- Tuning type adjustments
- Resistance checks
- Digital logic troubleshooting

And . . . Detects signal characteristics and abnormalities not possible with digital or analog meters.

LOGI-TRAK replaces the best 100MHz logic probes and offers:

- Eyes on the probe tip, HI/LO indication
- Instant identification of marginal states and fault conditions
- 100MHz response
- 5n sec pulse detection

**LISTEN** to what the MX333 can do for you. Ask about our **NO RISK 30 day Free Trial**.






THE HICKOK ELECTRICAL INSTRUMENT CO.  
10514 Dupont Avenue • Cleveland, Ohio 44108  
(216) 541-8060

**FREE**
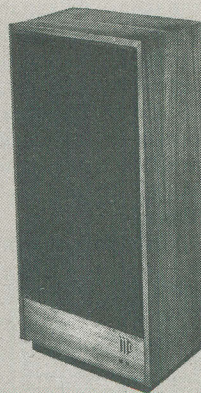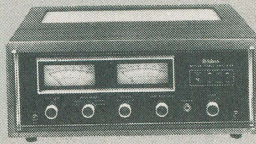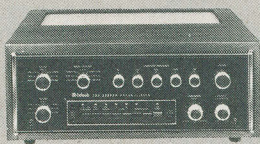
## McIntosh STEREO CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh stereo equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



**SEND  
TODAY!**

McIntosh Laboratory Inc.  
East Side Station P.O. Box 96  
Binghamton, N.Y. 13904-0096

RE

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

If you are in a hurry for your catalog please send the coupon to McIntosh.  
For non rush service send the **Reader Service Card** to the magazine.

CIRCLE 93 ON FREE INFORMATION CARD

CIRCLE 85 ON FREE INFORMATION CARD



# NEW IDEAS

## Restoring tube-type car radios

THE INTEREST IN CLASSIC CARS HAS RECENTLY brought several old tube-type six-volt radios into our shop for repair. Most of the trouble with them is not hard to find, but the parts are—most notably the electro-mechanical multivibrators. They were used in DC-to-DC upconverter circuits to provide +300 volts to the vacuum tubes. As I recall, they were not all that reliable, nor were they long-lived, for that matter. Therefore a substitute was needed.

After some experimenting we finally came up with the circuit shown in Fig. 1. The basic circuit is an astable-multivibrator that is used to drive output power-transistors at the same frequency as the old electro-mechanical vibrator.

### How it works

The circuit is built around IC1, a 4049 hex inverter/driver. Two of the inverters (IC1-b and IC1-e) are used to form an astable-multivibrator, and the others provide the necessary drive for the output transistors. The rest of the circuit consists of several resistors, capacitors, and diodes, and four transistors.

When power is applied to the circuit a pulse is generated through capacitor C4 and is applied to the cathode junction formed by diodes D1 and D2, causing the inverter outputs to alternately go from low to high.

Each of the multivibrator's two outputs are also fed to two separate drive circuits constructed from the four remaining inverters. We will only look at the upper half of the circuit from this point on, because they both do the same thing—only not at the same time.

When the output of IC1-e is low, it causes the output of the paralleled inverters (IC1-c and IC1-d) to go high. Because diodes D3 and D4 are reverse-biased, they will not conduct. But, when IC1-e's output swings in the positive direction, the output of the parallel inverters goes low, thus causing D3 and D4 to be forward-biased and conduct, turning on PNP transistor Q1. Transistors Q1 and Q3 drive output transistors Q2 and Q4.

With Q2 turned off, its collector voltage will be high. Since the collector of Q2 is tied to center-tapped transformer T1, a high will be across it too. (Remember the same action occurs alternately in the bottom half of the circuit with its output also applied to the primary of T1.) Transformer T1 is used to step up the output voltage from the circuit. The two diodes, D9 and D10, connected across the transformer's output leads form a full-wave rectifier. And capacitors C6 and C7 provide filtering for the rectified output-voltage.

Most of the components were mounted

on a small perf-board, about  $1\frac{1}{2} \times 2\frac{1}{2}$  inches. The vacuum-tube multivibrator and rectifier, along with their sockets, were removed from the set to make room for the new circuit. The output transistors, Q2 and Q4, were secured to the chassis using mica insulators and an aluminum heat-spreader plate. Also, ECG 377 transistors may be substituted for Q2 and Q4. Resistor R10 was put where some air could get to it. Also, keep in mind that some old systems require a positive ground. In that case, the hash-choke (L1) should be connected in the negative lead, as was done for the the positive, and tied to the ground point on T1's center-tapped primary. It should also be noted that L1 and T1 are part of the radio's original circuitry. Be sure to check the filter capacitors for shorts before powering up the circuit (sorry to say, we did not).—Dave Maley

### NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, for U.S. residents only, Panavise will donate their model 333—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full ten-inch height adjustment for comfortable working.

I agree to the above terms, and grant **Radio-Electronics Magazine** the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material has not been previously published.

Title of Idea

Signature

Print Name

Date

Street

City

State

Zip

Mail your idea along with this coupon to: **New Ideas Radio-Electronics**,  
200 Park Ave. South,  
New York, NY 10003

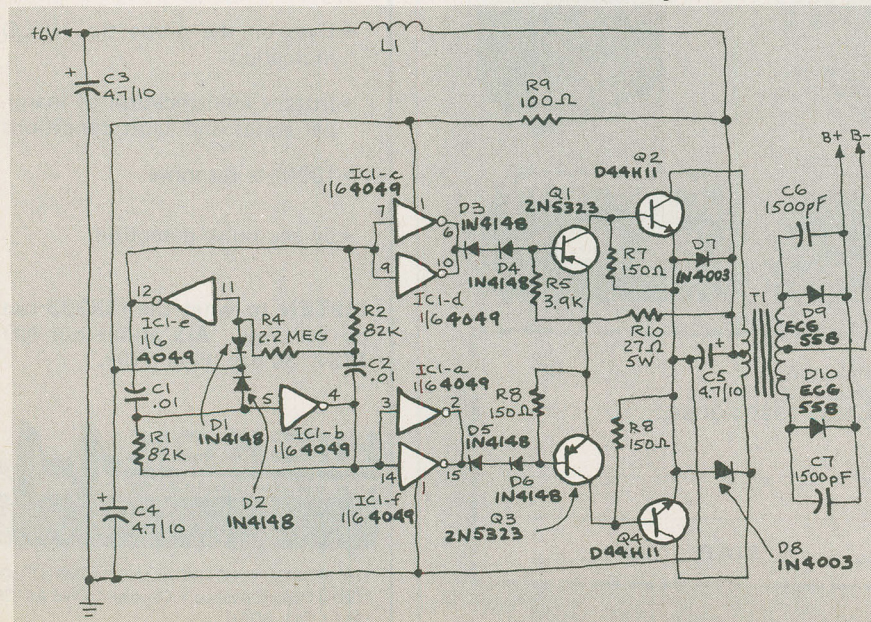


FIG. 1



## HOBBY CORNER

continued from page 73

1 Box 539, Central Hall, PA 16828). According to P.J., that device works extremely well.

You will notice that the *Winky Board*, like the *Data Dubber*, *AcuData*, etc., is machine-specific. In other words, they cannot be used to copy tapes of computers other than the ones for which they were specifically designed.

Those of us with little patience need a device that will work with all, or at least several different, types of computer tapes. Have any of you designed such a circuit, or know of such a versatile device?


### Larger readouts

Bill Murks (TN) has a receiver with a digital readout, but his vision problem makes it difficult to read the numbers. He would like to add a readout with larger digits to the unit. Well, Bill, you already have all the circuitry needed for the readout, so your best bet is to replace the present one. And since I am not familiar with your receiver, I can do no more than point you in the right direction.

The first thing to do is to determine whether the present readouts are of the

common-anode or common-cathode type. Since most display circuits have some "spare" driving capacity, larger digits of the same type should be direct replacements pin-for-pin, even if they do require a bit more current. To be on the safe side, however, you may want to use non-inverting hex drivers between the new digits and the counting circuits.

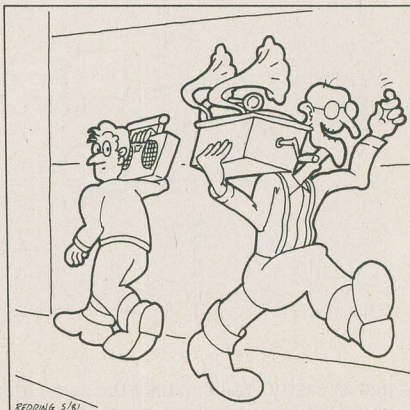Here, your greatest problem is likely to be the larger physical size of the readout. A couple of mounting possibilities are: 1) Place the display outside the cabinet in front of the old readout; 2) Mount the readout in a small case and placed it beside or on top of the receiver. R-E



# ATTENTION TECHNICIANS

## ARE YOU TIRED of being

"only a serviceman"

or

"just a technician"?

THE LETTERS "CET  
AFTER YOUR NAME SPELLS  
"PRIDE"

## TRY IT.

Take pride in  
your profession—  
Decide to be a CET



For information about: — exam dates;  
— requirements; — study guides;  
other \_\_\_\_\_

Send to: NESDA/ISCET  
2708 W. Berry St.  
Fort Worth, TX 76109  
(817) 921-9101

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ St. \_\_\_\_\_ Zip \_\_\_\_\_

## SEI, Inc.

641 Academy Drive • Northbrook, Illinois 60062

For information (312) 564-0104 • To order outside Illinois 1-800-323-1327


### SOLID STATE STEREO REVERBERATION AMPLIFIER



**Specifications:** • Total harmonic distortion less than 0.05% • Frequency response 10 Hz to 50K Hz • IdB • S/N Ratio 90dB • Reverberation time 0 to 3 sec • Input 150MV/50K ohm • Max. input 2V • Accepts input from tape, phono, or aux. • Includes and LED Reverb Level display. Kit comes with all electronic components, transformer and instructions, and 19" rack mount cabinet.

Model TA-2400 ..... \$89.95
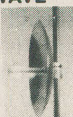
### AMATEUR MICROWAVE Receiver System 1.9-2.5 GHZ MICROWAVE RECEIVER SYSTEM



• Commercial grade construction • Sturdy Parabolic aluminum reflector antenna • High gain 50 dB! • Line of sight distance 45 miles! • Complete system, power supply, cable, assembled reflector antenna, and downconverter. • Downconverter mounted in attractive cabinet.

90 day warranty on PS-5!  
PS5 Assembled .... \$109.95  
Kit Form ..... \$ 79.95

### Microwave Preamp!

### NEW KIT

Use with PS-3 Kit. Adds 20-25 db gain to boost reception distance.

- Low Noise
- High Gain
- Can be used with all existing stop sign board receivers!
- 1.9-2.5 GHz Freq. Range

PS-4 (Kit) ..... \$34.95

### SOLID STATE STEREO GRAPHIC EQUALIZER PRE AMP KIT



**Specifications:** • Total Harmonic Distortion Less than 0.05% • Intermodulation Distortion (70Hz: 7KHz = 4:1 SMPTE Method) Less than 0.03% • Frequency Response: Overall 10Hz-200KHz: 10dB • 2dB • 10dB • RIAA Curve Deviation: (Phono) -0.2dB -0.2dB (30Hz-15KHz) • Channel separation (at rated output 1KHz) • Phono, Tuner, Aux and Tape Monitor better than 70dB • Input sensitivity and impedance (1KHz for rated output).

Phono: 2MV 47K ohms Aux: 130MV 50K ohms. Tuner: 130MV 50K ohms. Tape: 130MV 50K ohms. Graphic Equalizer Control: 10 Band Slide Control. Frequency Bands: 31 5Hz. 33Hz. 125Hz. 250Hz. 500Hz. 1KHz. 2KHz. 4KHz. 8KHz. 16KHz also with on panel selector for Phono, Tuner, Aux 1 and Aux 2. Power Supply: 117 VAC. Kit comes with all electronic components, transformer, instructions and a 19" rack mount type metal cabinet.

TA-2500 (Kit) ..... \$119.00

### 20 STEP LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 40 3-color LED's to indicate sound level output of your amplifier from -57 dB to 0 dB. Comes with an attractive silk screen printed panel. Has selector switch to allow floating or gradual output indicating. Kit includes all parts. Front panel and power supply.

TY-45 (Kit)

\$34.95

### SPY EAR

A very popular device designed to listen to sounds & voices through rooms or 3 ft. thick concrete walls. Place listening sensor against wall and earphone in ear. Adjust volume control! Clearly hear things you may not want to!

CM-8 ..... \$89.95

### INFRA-RED REMOTE CONTROL SWITCH KIT



Infra-red Remote Control switch can be used to control appliances up to 500 W.

The TK-41 has effective control up to 10 meters. No antenna needed. Features latest IC controller which excludes interferences from light or AC pulse signal.

TK-41 Kit ..... \$24.95

### STEREO AMP KIT 160 Watt Total 80W + 80W

This is a solid state all transistor circuitry on board stereo amplifier. Power output employs 2 pairs of matching Darlington transistors. T.H.D. less than 0.05% between DC to 200 KHz. Power supply requires 30 VCT 2 amp • FMR

TA-802

\$39.95

Transformer (optional)

\$9.95

### LOW TIM DC STEREO PRE-AM KIT TA-2800

Incorporates state of D.C. design that gives a frequency response from 0Hz-100KHz + 5dB. • Features tone defeat switch, loudness, treble, midrange, bass, balance. • Contains quad BJT op-amp to develop T.H.D. of 0.05% at rated output • Input sensitivity: phone 2.5 MV, tuner, aux, tape play 100MV 100K • Power supply: 15 volt DC at 2A. Kit comes with regulated power supply, all you need is a 15-20 VCT 2 amp XFMR.

TA-2800

ONLY


\$44.50

XFMR

\$4.50 ea.




### UHF TV PREAMP

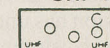

**FEATURES:**  
• 25 dB gain!  
• Kit

Your reception will dramatically improve! This unit will enable you to pull in signals you never knew were there! For both indoor and outdoor use. Input and output impedance 75 ohm. No adjustment! Easy assembly.

JH-0 Kit ..... \$23.95

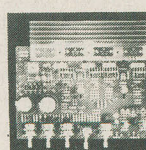

### TA-1500 200 WATT/ CHANNEL STEREO AMP & PREAMP KIT

More power for stereo blaster! 100 watts/channel, stereo preamp built-in. Treble, midrange, bass, mic volume. Balance and volume are standard controls on the pre-amp. Mic input allows you to use it as a P.A. **Specifications:** 100 w x 2 into 8 Ohms. Freq. Range: 0-100KHz ± 3dB. T.H.D.: 0.1%. S/N Ratio: 80 dB. Sensitivity: 3 mu into 42K. Power Requirements: 24-40 VAC.

TA-1500 ..... \$72.00

**160 WATT DC STEREO AMP/PREAMP KIT**  
The TA-800 is an 80 watt/channel preamp and power amp with tone control, high, middle and bass controls. Volume and balance control are built-in. On board power supply requires only 60 volt C.T. XFMR. **Specifications:** 50W x 2 into 8 Ohms. Freq. Range: 0Hz-100 KHz ± 3dB. T.H.D.: 0.1%. S/N Ratio: 80 dB. Sensitivity: 3 mu into 47 K. Power Requirements: 24-40 VAC.

TA-800 ..... \$65.00



Add 10% shipping on orders under \$35.00. Orders over \$35.00, add 5%.

Catalog-\$1.00. Visa & Mastercharge accepted.





# DESIGNER'S NOTEBOOK

## Frequency multiplication

ROBERT GROSSBLATT

ONE OF THE BIGGEST ADVANTAGES THAT A digital approach to circuit problems has over more traditional analog solutions can be summed up in one word—precision. In fact, some of the stickiest problems that come up when dealing with analog circuitry have been just about eliminated, now that a handful of silicon shavings can replace acres of glass epoxy and miles of wiring.

Certainly the area where that has become most outrageously evident is in the whole field of frequency generation and division. At one time, super-precise frequencies could only be generated by using crystal oscillators, expensive hand-picked components, and then building elaborate divide-by networks with components that had names like 12AX7, 6AU6, and so on.

Of course, we're talking about techniques most commonly used by monks and we know about them through ancient hand-illuminated parchment scrolls. Seriously though, the whole idea of frequency-synthesis and division has undergone a major change with the development of the IC.

One of the first experiments that any newcomer to design encounters is building a simple circuit that can generate several frequencies by dividing down a master oscillator. Not only that, but the whole design can be accomplished using less than three IC's! And if you use a binary ripple-counter, like the 4060, you don't even need an external oscillator—it's built right onto the substrate and can be either an R-C type or crystal based. But enough beating around the bush.

The point here is that while everyone knows twelve-million ways to easily divide any frequency by any number, it's sometimes necessary to do exactly the opposite. Multiplying a frequency with the same degree of precision that we can get with division is possible by using things like rate multipliers and some exotic special-purpose IC's. And if you have to multiply a frequency by some "odd-ball" number, special-purpose IC's are the way to go. But suppose your needs are really simple. Just as you can easily divide by two using nothing more exotic than a flip-flop, this month's handy-dandy circuit will multiply a frequency by two

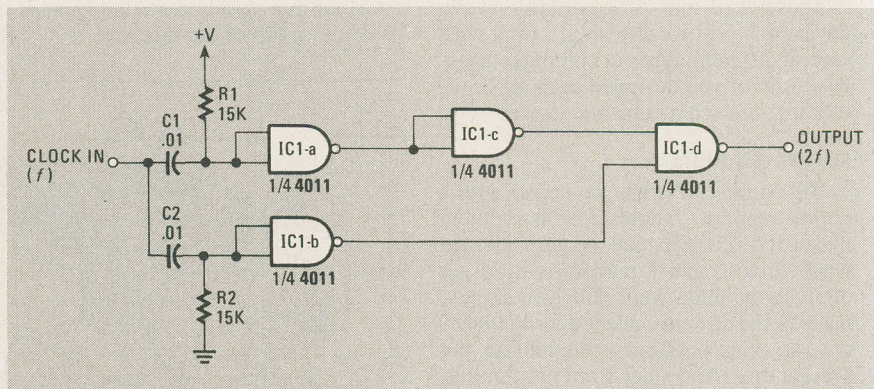


FIG. 1

just as easily. You can take the same ideas even farther and multiply by four, eight, or whatever, by cascading.

### How it works

Figure 1 shows a circuit that can be used as a frequency multiplier. The operation of the circuit is so simple it doesn't require much of an explanation. The whole thing is made from a single quad two-input NAND gate! Two gates, IC1-a and IC1-b, are set up as inverters and their inputs are isolated from each other by two capacitors, C1 and C2. Resistors R1 and R2 hold the inverter inputs high and low respectively. Since IC1-c is on the line between IC1-a and IC1-d, both inputs to IC1-d will be high. As long as there's no signal at the clock input, the output of IC1-d is low.

When a clock pulse shows up at the input, the negative edge will charge capacitor C1 and thus change the output state of IC1-a. The output of that IC is then again inverted by IC1-c. As a result, a low is applied to one leg of IC1-d, causing it to output a high. All the IC's will stay in their present state until either the R-C network times-out or the input clock goes high.

When the input clock goes high, capacitor C2 will charge-up and force IC1-b to output a low on the other leg of IC1-d, forcing its output to go low again. The cycle will repeat over and over again, resulting in an output frequency that is exactly double that of the input clock. Just about the only thing to be careful of is to make sure that the R-C time-constant is well above the maximum frequency that you expect to put through the circuit. If

the input frequency has a period that is shorter than the time constant of the R-C network, the circuit will hang up.

With the component values shown, you should be OK, provided that you don't apply a frequency to the input that is greater than 500 kHz. Also, be certain that the IC that you are using can handle double the input frequency, since IC1-d will be switching at twice the input frequency. It should also be noted, at this point, that the IC used in the circuit should be compatible with the circuitry that it is to feed. For example, if you are using 7400 series TTL's, use a TTL NAND gate such as the 7402; and as for circuits that contain CMOS or low-power Schottky devices, use a CMOS IC such as a 4011 or 74LS00 series TTL respectively.

You should be able to use the same technique to build circuits that will triple or even quadruple an input frequency. All that you need is more inverters and a final gate with the right number of inputs. There are other, even simpler methods to do the same thing. But the operation of this circuit is very reliable over a wide frequency range.

R-E





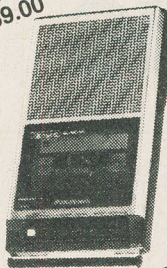
# SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00\*  
14 Hour Model — \$159.00\*

Modified Panasonic Spline.  
high quality, AC-DC  
Recorders provide 5 or 7  
continuous hours of quality  
recording & playback on  
each side of cassette for a  
total of 10 or 14 hours  
depending on model. Built-in  
features include • Voice  
level control, • Digital  
counter, etc. TDK DC 180  
Cassette Furnished.



## PHONE RECORDING ADAPTER

Records calls automatically. All Solid  
state connects to your telephone  
jack and tape recorder. Starts  
recording when phone is lifted.  
Stops when you hang up.

\$24.50\*

FCC APPROVED

## VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjust-  
able sensitivity. Voices or other  
sounds automatically activate and  
control recorder. Uses either re-  
corder or remote mike. \$24.95\*  
• Add for ship & hdg. Phone Adapter & Vox \$1.50 ea.  
Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA,  
M/C, COD's OK. Money Back Guarantee. Qty. disc.  
avail., Dealer Inquiries invited. Free data.  
AMC SALES INC. Dept A 9335 Lubec  
St., Box 928, Downey, CA  
90421 (213) 869-8519

CIRCLE 67 ON FREE INFORMATION CARD

## TROUBLESHOOTING

continued from page 71

shut down the place. It has always been  
my custom when I have test equipment  
hooked up to a live set to shut the set first  
and the equipment last. This time, for no  
accountable reason, I turned off the scope  
first. The screen went white, I went limp. I  
thought I had blown one of the IC's.

But, wait! Turning the scope back on, I  
went to IC101—perfect signal. Back to  
TP12—this time it was not going to sabo-  
tage me—no signal. Back and forth I  
went, as though I wanted to savor every  
delectable moment over and over again.  
On one side of the coil, a signal; on the  
other side, none. Finally, when I felt that I  
had drained out of the moment as much as  
there was to be drained, I put a jumper  
across the coil, and there it was—a pic-  
ture.

It had taken a tiny static discharge that  
was released when the scope switch was  
turned off to open the coil for good and get  
rid of one heck of a headache. R-E



**American Heart  
Association**

WE'RE FIGHTING FOR YOUR LIFE

# cable tv

## DESCRAMBLER PARTS

We stock the exact parts and PC Board for  
Radio Electronic's February Article on building  
your own Cable TV Descrambler.

### #701 PARTS PACKAGE . \$29.95

Includes all resistors, capacitors, diodes, transistors,  
integrated circuits, coils and IF transformers  
(BKAN-K5552AXX).

### #702 PC BOARD ..... \$16.95

Etched and drilled silk-screened PC Board as shown  
in article.

### BOTH #701 & #702 .... \$39.00

Add \$2.50 Postage & Handling



Orders only 1-617-339-6714  
1-617-339-5372

**J & W  
ELECTRONICS, INC.**

P. O. Box 52  
Cumberland, RI 02864

CIRCLE 45 ON FREE INFORMATION CARD

## THE NEW SA-6 DESOLDER IRON



\$19.75\*

Revolutionary new electric  
desoldering iron combines the  
ease and portability of a hand-held,  
manual, desolder pump, with  
performance of an industrial desolder  
station. This unique AC powered compact  
tool features portable, one-hand desoldering  
eliminating the need for separate soldering iron  
and desolder pump. No shop air required. Essential  
for all tool kits, field service technicians, and  
repairmen, as well as production applications. Vacuum  
chamber is easily removed for cleaning or replacement.  
Replacement tips available. Tool is supplied with SAT-6-059  
tip; diameter 0.059 inch (1.5 mm).

### FEATURES:

- Self contained suction power and heating element.
- Economical.
- Lightweight 4oz. (113gms).
- Compact size 10 1/4 inches (26 cm).
- Replacement nozzles available.

\*Does not include shipping  
charges and local taxes.

**dt DAVLE TECH INC**  
ELECTRONIC TOOLS & ACCESSORIES


CIRCLE 54 ON FREE INFORMATION CARD

2-05 BANTA PLACE  
FAIR LAWN, NJ, 07410  
TEL: 201-796-1720  
TELE: 968771

\*\*\*\*\* ANNOUNCEMENT OF OUR NEW ARRIVAL \*\*\*\*\*

SEND FOR OUR  
ELECTRONIC COMPONENTS CATALOG

"ALWAYS IN STOCK"

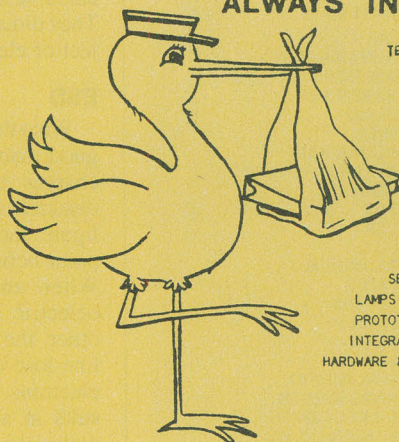

TEST EQUIPMENT  
WIRE & CABLE  
CONNECTORS  
RESISTORS  
BATTERIES  
SWITCHES  
FANS  
FUSES  
CABINETS  
TERMINALS  
CAPACITORS  
SEMICONDUCTORS  
LAMPS & INDICATORS  
PROTOTYPING BOARDS  
INTEGRATED CIRCUITS  
HARDWARE & ACCESSORIES

\*\*\* CALL TOLL-FREE \*\*\*

IN MICHIGAN  
1-800-432-4364

NATIONAL WATS  
1-800-552-9232

**Tubergen**

TUBERGEN & ASSOCIATES, INC.  
3124 N. STATE ST.  
ZEELAND, MI 49464

STOCKING DISTRIBUTORS OF ELECTRONIC COMPONENTS

CIRCLE 37 ON FREE INFORMATION CARD



# SERVICE CLINIC

## Electrostatics and electronics

JACK DARR, SERVICE EDITOR

THE HISTORY OF STATIC ELECTRICITY GOES back about 2500 years to ancient Greece. The theory is that someone rubbed a cat with an amber comb or rod, and found that (after rubbing) the comb attracted small lightweight particles such as lint or dust. That phenomenon was called *trib-ein*, meaning "to rub." Greek philosophers experimented with the force of attraction that amber had on lightweight objects. In fact, our word "electron" comes from "elektron," which was the Greek word for amber.

Since the discovery of the electrostatic phenomenon, many researchers have performed detailed scientific investigations into the property of attraction that many materials display after being rubbed. Among those who performed those experiments was Stephen Grey, an Englishman, who in the 1700's did a considerable amount of work in identifying conductive and nonconductive materials. Other scientists who experimented in this area include Benjamin Franklin, with whom we are all familiar; Alessandro Volta, for whom the volt was named; Charles Augustin De Coulomb,

MATERIALS	
↑ INCREASINGLY POSITIVE	AIR
	HUMAN HANDS
	ASBESTOS
	RABBIT FUR
	GLASS
	MICA
	HUMAN HAIR
	NYLON
	WOOL
	FUR
↓ INCREASINGLY NEGATIVE	LEAD
	SILK
	ALUMINUM
	PAPER
	COTTON
	STEEL
	WOOD
	AMBER
	SEALING WAX
	HARD RUBBER
	NICKEL COPPER
	BRASS SILVER
	GOLD PLATINUM
	SULFUR
	ACETATE RAYON
	POLYESTER
	CELLULOID
	ORLON
	SARAN
	POLYURETHANE
	POLYETHYLENE
	POLYPROPYLENE
	PVC (VINYL)
	KEL-F (CTFE)
	SILICON
	TEFLON

FIG. 1

MEANS OF STATIC GENERATION	ELECTROSTATIC VOLTAGES	
	10 TO 20 PERCENT RELATIVE HUMIDITY	65 TO 90 PERCENT RELATIVE HUMIDITY
WALKING ACROSS CARPET	35,000	1,500
WALKING OVER VINYL FLOOR	12,000	250
WORKER AT BENCH	6,000	100
VINYL ENVELOPES FOR WORK INSTRUCTIONS	7,000	600
COMMON POLY BAG PICKED UP FROM BENCH	20,000	1,200
WORK CHAIR PADDED WITH POLYURETHANE FOAM	18,000	1,500

FIG. 2

for whom the unit of electric charge was named, and many others.

Things went on in much the same way, with little progress being made in that area, until along came a group of dedicated researchers at the 3M Company. They did a complete run-down on the subject of electrostatic discharge (ESD).

### ESD

What those researchers found was that a good many materials can develop static charges; those materials, called the *triboelectric series*, are shown in Fig. 1. That figure shows that cotton is the dividing point between the positive and negative. When any two materials in the triboelectric series are rubbed against each other, the materials above the horizontal line lose electrons and those below gain electrons. That transfer of electrons results in a net positive charge for those materials higher up in the series and a negative charge for materials lower in the series.

The level of static electricity generated is directly related to how closely the materials make contact; how rapidly they are separated; their distance from one another in the triboelectric series, and the relative humidity. Look at Fig. 2: It shows that just walking across a carpet while the humidity is low can generate up to 35,000 volts! Most humans cannot feel static electricity

until it reaches a level of about 3000 volts.

The voltages generated during normal daily activities are stored on materials in much the same way that a capacitor stores a charge. And those voltages are discharged within 20 nanoseconds after they come close to or touch some other material with an unlike charge. That short discharge time causes several watts to be dissipated in a device: And that's not all, the peak current can reach up to 60 amperes! No mistake, we mean amperes! No wonder sensitive devices can arc over internally and be damaged.

The newer generation of semiconductors (such as MOS devices) are faster, more compact, but they are extremely sensitive to heavy static-charges. And when you consider that those devices use single-conductor gate electrodes about a micron wide, it is easy to see why they are so susceptible to ESD damage. For instance, VMOS IC's can be damaged by an electrostatic charge as low as 30 volts. How often have you purchased some static-sensitive device and put it in a circuit only to find that the project or equipment does not work. Very often circuit failure is caused by static charges transferred from the body to sensitive components during handling.

Several types of failure generally occur as a result of ESD. The first and most easily detected is complete component



failure. The second and more serious problem is the degraded or intermittent component. Failures caused by ESD happen very quickly and in many cases protective diodes react too slowly to prevent damage.

Computerists are also plagued by ESD. They often find that after hours of punching in data, along comes an electrostatic surge that completely upsets the whole apple cart. For them, protective products such as *Zap Guard* (from Inmac, 2465 Augustine Drive, Santa Clara, CA 95051) have been introduced. That product is nothing more than a conductive mat that, when placed at a computer station, shunts electrostatic charges away from the computer and prevents possible problems from electrostatic discharge.

It was because of such occurrences that we had to find a way to avoid the damage caused by ESD, if only for the sake of not having to replace so many IC's—a job that nobody likes. Electrostatic discharges can be eliminated when the right precautions are taken.

### ESD control

Some of the stock devices for the elimination of ESD in a manufacturing environment are really quite simple. One such device is a grounded wrist strap, which must always be worn by the technician while he is in the work area. In that way static charges built up during normal activities can drain off before any damage occurs.

Some other devices used to control ESD are conductive covers for the bench top and mats for the floor in front of the work station. Also, it might be a good idea to ground your bench chair: Note the last item in Fig. 2: "Work chair padded with polyurethane foam."

The problem of generating a static charge can be rendered harmless by running new strips of metal tape across the seat and down the sides to the legs. And then removing any rubber or plastic tips from the legs, so that the chair would be grounded to the conductive floor mat; or, if the chair legs are not metal, the strip can be attached to the mat itself. Let's look at some of the simple actions that generate electrostatic voltages.

Almost anything you do *can* cause a static charge to be developed. For instance, did you know that any relative movement resulting in a rubbing action will generate a static charge? An example of that would be walking, and not necessarily across a carpet. The rubbing of clothing against the body as you walk, or simply taking parts out of a PVC bag, or even picking up such a bag from a workbench can generate ESD!

Materials such as plastics, vinyls, and synthetics can generate charges of 60,000 volts or more because of their high insulating properties. Not only that, but

they can also hold their charge for prolonged periods of time. It seems that everything's out to get us, so we have to be extremely careful.

We've mentioned some ESD protective devices, but they are not all that common. However, those items (grounded straps, protective mats, conductive bags, etc.) can be found at NARP CES (North American Philips Consumer Electronics Co., Parts Dept., PO Box 555, Jefferson City, TN 37760). With a few of those protective devices it should be much easier to keep from blowing up sensitive components and equipment.

R-E


## SERVICE QUESTIONS

### RASTER PROBLEMS

*This Motorola TS-915-D11 has me in circles. I have no raster. All cathode voltages on the kine are at B+, cutting off the tube. Collector voltages of the three video drivers measure .5 instead of 6 volts. The base of the ABL driver is at 30 volts when I turn the ABL adjust to maximum. It should be higher, but I can't figure out why it isn't.—R.L., Johnson City, TN*


Although the diagram calls for 34 volts at the ABL driver base, I'm not sure that this is your problem. Still it is an odd circuit, for sure. The ABL adjust is part of a voltage divider that goes back to the screen controls and still further back to the focus control. Stuck in the middle somewhere, you have a 2.7-megohm and a 2.2-megohm resistor. If either of those resistors changes value, you're going to lose some of that voltage. There is DC coupling throughout from the ABL driver through the color outputs, so any off-voltage in that loop could be cutting off the kine.

R-E

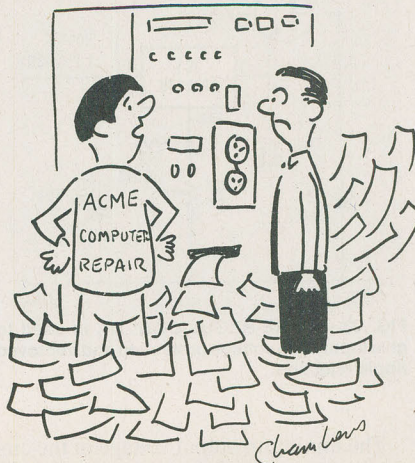

"In technical terms, this is what's known as computer upchuck."

## Versatile Lab Power Supply

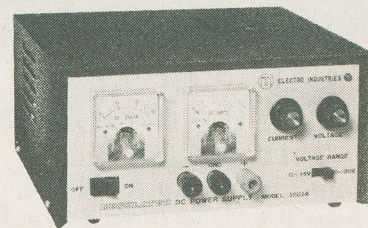

EXCEPTIONAL VALUE!

Only \$125<sup>00</sup>

- 0-30 VDC at 0-2A • Excellent Regulation
- Ripple & Noise - 500  $\mu$ V • Built-in Short-Circuit and Overload Protection

Model 3002A features continuously adjustable current limiting and precision constant voltage/constant current operation with "automatic crossover." This lab-grade unit can also be used as a current regulated power source.

Optional 10-turn voltage & current controls: \$25 each. Add \$3.00 for UPS shipping in Continental U.S. Check, Money Order or C.O.D. accepted. Illinois residents add 6% sales tax.




ELECTRO INDUSTRIES, INC.  
4201 W. IRVING PK., CHICAGO, IL 60641  
312/736-0999

CIRCLE 44 ON FREE INFORMATION CARD

## CABLE TV

Buy Direct & Save

### SUPER SPECIALS

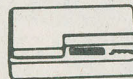


40 CHANNEL  
CONVERTER  
\$29<sup>95</sup>

Advanced Solid State design and circuitry allows you to receive mid & super band channels. Restores programming to Video Recorders.



36 CHANNEL  
REMOTE CONTROL  
CABLE CONVERTER  
\$69<sup>95</sup>

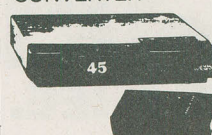JERROLD 400  
THE ULTIMATE CABLE TV  
CONVERTER



60 CHANNEL  
INFRARED  
REMOTE  
CONTROL  
\$129<sup>95</sup>

Send \$5 for Complete Catalog

### DIRECT VIDEO SALES

P.O. BOX 1329  
JEFFERSONVILLE, INDIANA 47130  
CALL  
1-812-282-4766

CIRCLE 53 ON FREE INFORMATION CARD



# CABLE TV


## CONVERTERS DESCRAMBLERS

Largest Selection  
of Equipment Available  
\$ Buy Warehouse Direct & Save \$



36 channel  
converter  
\$4595

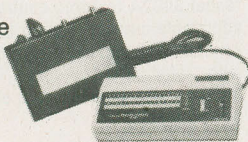36 channel  
wired remote  
converter  
only  
\$8895



Send \$2 for complete catalog  
of converters and unscramblers

Quantity Discounts • Visa • Master Charge  
Add 5% shipping—Mich. residents add 4% sales tax

**C&D Electronics, Inc.**  
P.O. Box 21, Jenison, MI 49428  
(616) 669-2440

## The world of electronics gee-wizardry

Test Equipment • Burglar Fire Alarms • Hobbyist & Automotive Electronics



**-YOURS FREE.**

32-pages of test instruments—from the latest digital multimeters to the famous EICO scopes. Security systems. Automotive and hobbyist products. Kits and assembled. EICO quality. EICO value. For FREE catalog, check reader service card or send 50¢ for first class mail.



108 New South Road  
Hicksville, N.Y. 11801

## POWER SUPPLY

continued from page 68

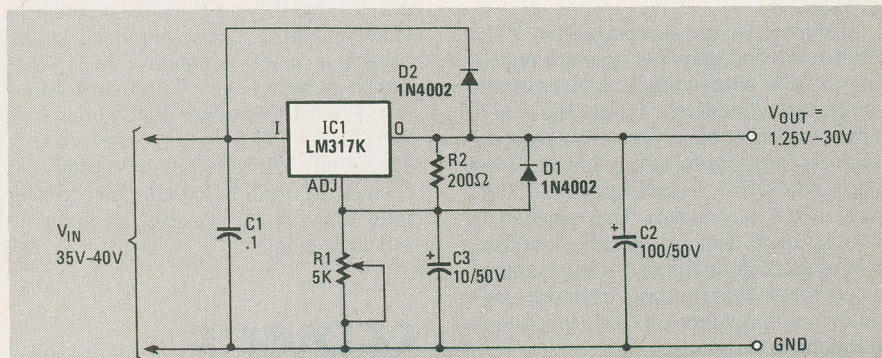


FIG. 21—ADDITIONS TO THE PREVIOUS CIRCUIT has given this regulator a low-impedance transient response and full input and output short-circuit protection.

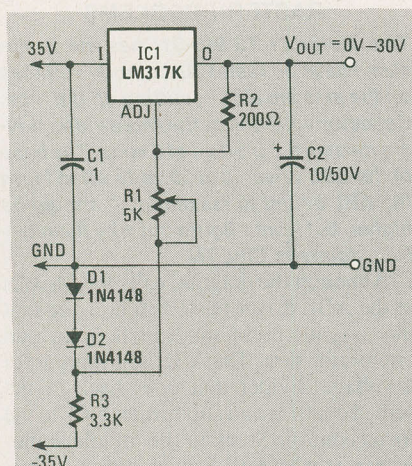


FIG. 22—THE OUTPUT OF THIS REGULATOR is fully variable from zero to 30 volts.

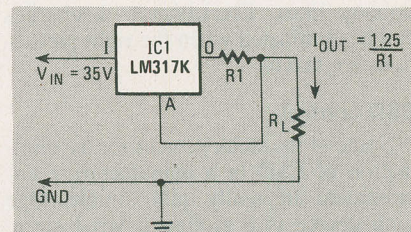


FIG. 24—THE 317K THREE-TERMINAL regulator can be used as a precision current limiter or constant-current generator.

that the "adjust" terminal goes to  $-1.25$  volts when  $R1$  is reduced to zero ohms. Figure 22 shows how that can be achieved, using a 35-volt negative rail and a pair of series-connected diodes to clamp the low end of  $R1$  to  $-1.25$  volts.

If you want to get the maximum possible voltage out of one of these regulators, you'll need to make sure that the input voltage does not exceed the 40-volt rating of the IC. The best way to do that is to use a simple Darlington-plus-Zener pre-regulator circuit, as shown in Fig. 23, which enables you to use any unregulated input in the range 35–55 volts. Note that as well as giving input overvoltage protection, that pre-regulator also gives a further improvement in ripple rejection. If you want to use this circuit with a 5-amp 338K regulator, you may need to reduce the value of  $R2$  and beef up the power rating of the Zener diode.

Finally, to complete this look at regulator circuits, Fig. 24 shows how you can use the 317K as a precision current limiter or constant-current generator in which the output current is determined by  $R1$  and is virtually independent of the external load values. By suitable choice of  $R1$ , the constant-current magnitude can be set at any value between approximately 10 mA ( $R1 = 120 \Omega$ ) and 1.25 A ( $R1 = 1 \Omega$ ). The performance is certainly not bad for a two-component circuit.

R-E

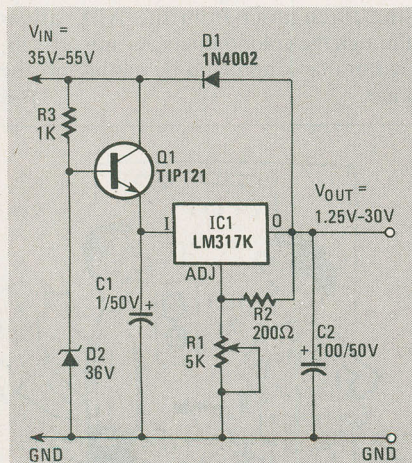


FIG. 23—A PRE-REGULATOR, Q1, is used to give input over-voltage protection and improved ripple rejection.

The minimum output voltage of the circuits in Figs. 19–21 is 1.25 volts. If you want the voltage to vary all the way down to zero, the circuits must be configured so



## PC BOARDS

continued from page 53

brings us to the next disadvantage—the stuff is very expensive. Still in all, you can't beat it for bridging small breaks in a trace and, to be fair about it, a ½ ounce bottle lasts a long time.

We're mentioning the next alternative only so we can tell you to avoid it. Don't ever leave the leg of a component extra long so you can bend it over to bridge a gap in the trace. You'll run into exactly the same horrors you do when you make a sloppy repair with a piece of wire. In this case, the jumper will only be supported by the board at one end. The other end of the component's leg will still be depend on the adhesion of the copper to the board for strength. As was pointed out before, that's a definite no-no.

You can also try to bridge small gaps in a trace with solder but that is too silly to discuss. What you'll be trying to do is create a solder bridge, and even if you manage to do that successfully, its strength will still depend on the bond between the copper and the board. That is really iffy and the chances are good that even trying to make a solder bridge will lift the copper off the board anyway. To make a long story short, don't ever do that—it creates more problems than it solves.

### Changing the pattern

If you have to change the foil pattern because you've discovered that your layout was wrong, the techniques to use are the ones we've already discussed. After all, it's still just a matter of moving the copper around. There are, however, a few other things that should be mentioned.

If you want to change components, you have to remove them from the board without damaging the foil. The ease of removing a component is a direct function of the number of pins it has—the more there are, the harder it will be to remove. Unsocketed IC's are a write-off. There is absolutely no safe way to remove them from the board. If you're faced with that problem, leave the IC where it is and do a cut and paste operation with the traces connected to its pads. However difficult and distasteful that is, it's still better than trying to remove the IC safely.

After the component is removed from the board, the holes have to be cleaned out. Solder will always flow across the hole when the component is removed and it's suicide to try melting the solder and pushing the leg of the replacement part through the hole. The copper will *always* lift off the board. Clean the hole out by melting the solder and pushing a toothpick through the hole from the foil side as

shown in Fig. 11. The solder won't stick to the wood and the hole will be nice and clean. You can get rid of the excess solder with a desoldering tool if you're rich or with left-over braided wire if you're not.

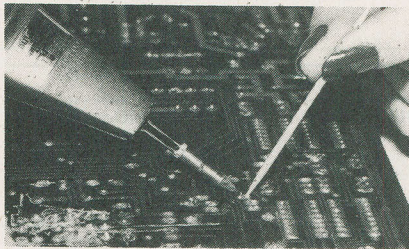


FIG. 11—AFTER A COMPONENT IS REMOVED, solder should be removed from the hole using a toothpick.

We've saved the most horrible sort of repair job for the end. What do you do if you're making a double-sided board and you discover that the two sides are out of register? Well, you cry a lot and bang your head against the wall. There's not much you can do about it—you only have one hope. If things aren't too far off, you can drill through the board at an angle to compensate. If your board is too far off for that, all we have to offer is our deepest sympathy. It's happened to us and if anyone knows a way to solve that problem,

please let us know.


A successful repair to a printed-circuit board is any repair that does the job and doesn't affect the integrity of the board. You can use any or all of the techniques we've discussed and you probably know some that haven't been mentioned. The extra time it takes to make a safe, reliable repair is a small enough price to pay to keep acres of valuable silicon from going up in smoke.

R-E



"It says we'd be in good shape financially if we hadn't bought a computer."
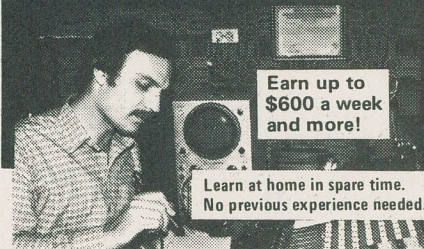
## Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to \$600 a week and more!

Learn at home in spare time. No previous experience needed.

No costly School. No commuting to class. The Original Home-Study course that prepares you for the FCC Radiotelephone license exam in your spare time! An FCC Government license is your "ticket" to thousands of exciting jobs in Communications, Radio & TV, Mobile two-way, Microwave, Computers, Radar, Aerospace and more. You don't need a college degree to qualify, but you do need an FCC License. **No need to quit your job or go to school!** You learn how to pass the FCC License exam at home at your own pace with this easy-to-understand, proven course. It's easy, fast and low cost! **GUARANTEED PASS** - You get your FCC License or money refunded. Write for free details. Soon you could be on your way to being one of the highest workers in the electronics field. **Send for FREE facts now. MAIL COUPON TODAY!**

### COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90  
P.O. Box 2223, San Francisco, CA 94126  
Rush FREE facts on how I can get my FCC License in spare time. No obligation. No salesman will call.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE 23 ON FREE INFORMATION CARD

### SEE YOUR DEALER TODAY

FROM



HERE'S A TIP THAT'S PERFECT!

AM/FM AUTO RADIO AND CB

**'Firestik' II**  
GOLDEN SERIES

**BARE-HANDS TUNABLE  
"NO TOOLS NEEDED"  
HIGH PERFORMANCE ANTENNAS**

ALSO ANTENNAS FOR  
CORDLESS TELEPHONES  
MONITOR SCANNERS

Dealer & Distributor Inquiries Invited  
SEND FOR FREE CATALOG

'Firestik' Antenna Company  
2614 East Adams/Phoenix, AZ 85034

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

Serving the CB and  
Communications Market Since 1962.

**5-YEAR REPLACEMENT WARRANTY**

CIRCLE 40 ON FREE INFORMATION CARD



# MARKET CENTER

## EDUCATION & INSTRUCTION

**EARN your university degree** through evaluation assessment, of existing education, experience, achievements. Call, (614) 863-1791, or write, **ASSESSMENT**, Box 13130R, Columbus, OH 43213.

**HOW a transistor works.** \$4.00. Easy educational experiment. Satisfaction guaranteed. **ANTON**, 1343 W. Belmont, Chicago, IL 60657.

**FCC commercial licence correspondence course.** 60 individual lessons, \$89.50. Payment plan available. Results guaranteed! Information free. **AMERICAN TECHNICAL INSTITUTE**, Box 201, Cedar Mountain, NC 28718.

**UNIVERSITY degrees by mail!** Accredited Bachelors, Masters, Ph.D's. Free facts revealed. **CAREERS-RE7**, Box 470886, Tulsa, OK 74147-0886.

### Be a MICRO-COMPUTER REPAIR TECHNICIAN

No previous experience needed... train at home in spare time for an exciting career. Even beginners can learn how to repair small computers. Everything explained in easy-to-understand language. Test instruments included with course. Easy-to-follow home-study course shows how you can get started in this fast-growing business. Send for free facts. No obligation. No salesman will call.

Write **ICS SCHOOL OF COMPUTER REPAIR**, Dept. DE064 Scranton, PA 18515.

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$2.15 per word (minimum 15 words) to:

**Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003**

### ORDER FORM

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$20.00.

( ) Plans/Kits ( ) Business Opportunities ( ) For Sale  
( ) Education/Instruction ( ) Wanted ( ) Satellite Television

Special Category: \$20.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

PLEASE INCLUDE FOR OUR FILES YOUR PERMANENT ADDRESS AND PHONE NUMBER.

**CLASSIFIED COMMERCIAL RATE** for firms or individuals offering commercial products or services). \$2.15 per word prepaid (no charge for zip code)...MINIMUM 15 WORDS. 5% discount for 6 issues, 10% for 12 issues within one year, if prepaid.

**NON-COMMERCIAL RATE** (for individuals who want to buy or sell a personal item) \$1.50 per word prepaid...no minimum.

**ONLY FIRST WORD AND NAME** set in bold caps. Additional bold face (not available as all caps) at 20¢ per word. All copy subject to publisher's approval. **ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 20th of the third month preceding the date of the issue (i.e., August issue closes May 20th). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

## PLANS & KITS

**PRINTED-circuit boards.** Quick prototypes, production, design, reflow solder send print or description for quote to **KIT CIRCUITS**, Box 235, Clawson, MI 48017.

**CABLE-TV** converters and equipment. Plans and parts. Build or buy. For information send \$2.00. **C & D ELECTRONICS**, PO Box 21, Jenison, MI 49428.

**HI-FI speaker kits**, auto speaker systems and raw drivers from the world's finest manufacturers. For beginners and experts. Free literature. **A&S SPEAKERS**, Box 7462R, Denver, CO 80207 (303) 399-8609.

**NEW!... repair any TV... easy.** Anyone can do it. Write **RESEARCH**, RR No.3, Box 601BR, Colville, WA 99114.

**REPAIRS** of all converters and cable boxes with prompt service. Deluxe sinewave kits \$95.00. 90% complete also available (quantity discounts) UHF converters of all types available. Send SASE (54 cents postage) for information. 1-(312) 637-4408. **HIGGINS ELECTRONICS**, 6014 W. Nelson, Chicago, IL 60641.

**CATALOG:** Hobby, CB, broadcasting! Linears, transmitters, bugs, scramblers, downconverters,

## FREE KIT Catalog

FUNCTION GENERATOR KIT \$59.95  
Auto-Ranging Cap-meter kit \$79.95

Phone 209-772-2076

Write or Phone for FREE CATALOG

**DAGE** SCIENTIFIC INSTRUMENTS  
BOX 144 VALLEY SPRINGS CA 95252

contains  
TEST &  
EXPERI-  
MENTER'S  
EQUIP.

antennas, modifications, more! **PANAXIS**, Box 130-F7, Paradise, CA 95969.

**QUALITY** light chaser/color organ kits. Refundable \$1.00 for flyer. **DESIGN SPECIALTY**, Box 1995, Huntington Beach, CA 92647.

**VEHICLE** security system. Five separate timing circuits. LED monitoring. Many extra features. Plans \$5.00. **D & J ELECTRONICS**, Box 6272, Rosemead, CA 91770.

**CONVERT** three-phase induction motors to single phase at full torque, 1-25 HP, \$6.00 instruction book, **ROTARY CONVERTER SPECIALISTS**, PO Box 1382, Washington, DC 20013.

**ULTRASONIC** remote control to mute unwanted commercials. Photos, schematics parts list, \$5.50. **J. CLARK**, 4720 Fielder, Tampa, FL 33611.

**UHF-STV** using countermeasures (Miami, Chicago)? Unique unpublished add-on circuits for STV, SSAVI, cable, MDS, satellite (Bluemax, Fantasy). Catalog \$1.00 plus SASE. **CAPTAIN VIDEO**, Box 9388, Baltimore, MD 21228.

**CONTROL** your world with your computer! Control up to 48 different devices easily. Complete plans, schematics, programs, \$4.95. **B & W ELECTRONICS**, 3621 Lowden, Kalamazoo, MI 49008.

**FREE Information.** Increase the vertical bandwidth of your 5Mhz oscilloscope to 200Mhz! **WHITE KNIGHT IND.** 3928 Iowa, No.102, San Diego, CA 92104.

**DELUXE** II sine wave descrambler board owners, improve reception distance, picture quality and stability with 7 circuit revisions \$9.95. A pulse suppressed descrambler design for the above board \$7.95. **G & M**, Box 335, Rising Sun, MD 21911.

**ROBOTIC** units kits plans, basic robot kit-\$80.00, interface motor control kit-\$50.00, verbal controlled robot-\$150.00, programmable RAM robot-\$125.00, Information \$1.00. **WENDEL L. DANIELS, ENGINEERING CONSULTANT**, 8450 Anthony Wayne Ave., Cincinnati, OH 45216.

**TOP quality** imported, domestic kits, surplus, discount electronics, computer components. Free catalog. **TEKTRASONIX**, 175 Fifth Ave., Suite 3194, N.Y., NY 10010.

**SECURITY schematics, transistor, ultrasonic** and I.C. designs, \$8.00. For large list of plans send \$2.00 (refundable) to **SELECTIONS**, PO Box 9606, Detroit, MI 48209.

**SILK** screen PC boards, dials & panels yourself! Complete plans \$9.95. **RUS BARLEY**, PO Box 20993, Portland OR 97220.

## CABLE TV

**DEALERS wanted:** Channel 2, 3, and 4 Notch filters. Money back guarantee. Send \$15.00 for sample and quantity price list. Specify channel(s). **LEE KURTZ**, PO Box 291394, Davie, FL 33329

## BUSINESS OPPORTUNITIES

**VIDEO** game repair business. Start your own. Information/parts list \$5.00. **BEST ELECTRONICS**, 4440 Sheena, Phoenix, AZ 85032.

**64K 6502/280** dual processor computer US\$420.00. Hundreds Apple-compatible softwares. Details US\$1.00. **RELIANT**, PO Box 33610, Sheungwan, Hongkong.



# MAKE RADIO SHACK YOUR PARTS PLACE™

Low Prices!

First Quality!

No Mail Order Hassles!

## Power Transformers

### 120VAC Primaries

Type	Volts	Current	Cat. No.	Each
Mini	6.3	300 mA	273-1384	2.59
Mini	12.6	300 mA	273-1385	2.79
Mini	25.2	300 mA	273-1386	2.99
Mini	12.6 CT	450 mA	273-1365	3.59
Mini	25.2 CT	450 mA	273-1366	3.99
Std.	6.3	1.2 A	273-050	3.79
Std.	12.6 CT	1.2 A	273-1505	3.99
Std.	25.2	1.2 A	273-1480	4.39
H-D	12.6 CT	3.0 A	273-1511	5.99
H-D	25.2 CT	2.0 A	273-1512	6.29
H-D	18.0 CT	2.0 A	273-1515	6.99

## Low-Profile DIP Sockets

Quality non-wicking sockets for PC use. Low-resistance contacts.

Type	Cat. No.	Price
8-Pin	276-1995	2/.59
14-Pin	276-1999	2/.89
16-Pin	276-1998	2/.89

Type	Cat. No.	Each
18-Pin	276-1992	.49
20-Pin	276-1991	.59
24-Pin	276-1989	.79
28-Pin	276-1997	.89
40-Pin	276-1996	.99

## Replacement Transistors



Type	Cat. No.	Each
2N1305	PNP 276-2007	1.19
MPS222A	NPN 276-2009	.79
PN2484	NPN 276-2010	.89
MPS3904	NPN 276-2016	.69
TIP31	NPN 276-2017	.99
TIP3055	NPN 276-2020	1.59
MPS2907	PNP 276-2023	.79
MJE34	PNP 276-2027	1.49
2N3053	NPN 276-2030	.89
MPS3638	PNP 276-2032	.79
TIP120	NPN 276-2068	1.29
2N3055	NPN 276-2041	1.99
MJ2955	PNP 276-2043	2.19
2N4124	NPN 276-2057	.59
2N4401	NPN 276-2058	.59
MPSA06	NPN 276-2059	.59
MPSA13	NPN 276-2060	.59
MPSA42	NPN 276-2061	.69
MU4891	UJT 276-2029	.99
2SD313	NPN 276-2048	1.79
2SC945	NPN 276-2051	.79
2SC1308	NPN 276-2055	7.95
2N3819	N-FET 276-2035	.99
MPF102	N-FET 276-2062	.99

## Tantalum Capacitors

- 20% Tolerance
- Standard IC Pin Spacing



μF	WVDC	Cat. No.	Each
0.1	35	272-1432	.49
0.47	35	272-1433	.49
1.0	35	272-1434	.49
2.2	35	272-1435	.59
10	16	272-1436	.69
22	16	272-1437	.79


## Computer Connectors

Repair or make your own RS-232 cables and joystick extension cords and save!

Type	Positions	Cat. No.	Each
ID Card Edge	34	276-1564	4.95
ID Card Edge	50	276-1566	4.95
Card Edge Socket	44	276-1551	2.99
Solderless Sub-D Male	25	276-1559	4.99
Solderless Sub-D Fem.	25	276-1565	4.99
Solder Sub-D Male	9	276-1537	1.99
Solder Sub-D Female	9	276-1538	2.49
Hood for Above	9	276-1539	1.99
Solder Sub-D Male	15	276-1527	2.49
Solder Sub-D Female	15	276-1528	3.49
Hood for Above	15	276-1529	1.99
Solder Sub-D Male	25	276-1547	2.99
Solder Sub-D Female	25	276-1548	3.99
Hood for Above	25	276-1549	1.99

## Ceramic Disc Capacitors

Low As **39¢** Pkg. of 2

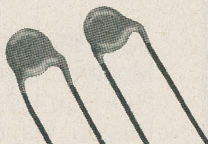

For RF, bypass and coupling. Hi-Q. Moistureproof coating. 50 WVDC minimum.

pF	Cat. No.	Pkg. of 2	μF	Cat. No.	Pkg. of 2
4.7	272-120	.39	.001	272-126	.39
47	272-121	.39	.005	272-130	.39
100	272-123	.39	.01	272-131	.39
220	272-124	.39	.05	272-134	.49
470	272-125	.39	.1	272-135	.49

## Communications ICs

Type	Cat. No.	Each
AY-3-1015 UART	276-1794	5.59
AY-5-8116 Baud Rate Gen.	276-1795	8.95
XR 2206 AFSK Generator	276-2336	5.95
XR 2211 Decoder/PLL	276-2337	5.95
5089 Modem Tone Encoder	276-1301	3.99

## ¼-Watt, 5% Resistors

**39¢** Pkg. of 5



Ohms	Cat. No.	Ohms	Cat. No.
10	271-1301	10k	271-1335
100	271-1311	15k	271-1337
150	271-1312	22k	271-1339
220	271-1313	27k	271-1340
270	271-1314	33k	271-1341
330	271-1315	47k	271-1342
470	271-1317	68k	271-1345
1k	271-1321	100k	271-1347
1.8k	271-1324	220k	271-1350
2.2k	271-1325	470k	271-1354
3.3k	271-1328	1 meg	271-1356
4.7k	271-1330	10 meg	271-1365
6.8k	271-1333		

## Dual Switched Filter

**Slashed 51%**


Reg. 7.99 **388**



**MF10.** Versatile CMOS building block for active filters—eliminates the need for expensive, close-tolerance parts. High performance, yet very easy to use. Hams—build a CW/SSB audio bandpass filter or a RTTY demodulator with a minimum number of parts! Center frequencies up to 20 kHz. Single or split supply. With data.

276-2329 ..... Sale 3.88

## SPST DIP Switches

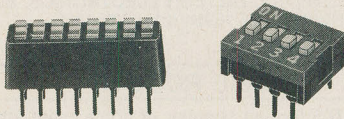

For digital or low current applications. Mount in DIP sockets or on PC boards. Style may vary.

**8-Position.** Fits 16-pin DIP socket.


275-1301 ..... 1.99

**4-Position.** Fits 8-pin DIP socket.

275-1304 ..... 1.49
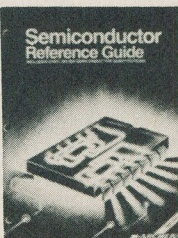
## Semiconductor Reference Guide 349

**1984 Edition.** Cross-reference and substitution section lists 80,000 types and low-cost Radio Shack replacements. Data on Shack transistors, ICs, SCRs, LEDs, diodes, opto devices. Illustrated. 272 pages. 276-4007 .3.49



## Operational Amplifiers



Type	Cat. No.	Each
741 (Single)	276-007	.79
MC1458 (Dual)	276-038	.99
LM324 (Quad)	276-1711	1.29
TL082 (Dual)	276-1715	1.89
TL084 (Quad)	276-1714	2.99
LM3900 (Quad)	276-1713	1.39
LM339 (Quad)	276-1712	1.49

## Voltage Regulator ICs



Type	Adjustable	Cat. No.	Each
LM723	0 to 40 VDC	276-1740	.89
LM317T	1.2 to 37 VDC	276-1778	2.79

Type	Fixed Output	Cat. No.	Each
7805	+5 VDC	276-1770	1.59
7812	+12 VDC	276-1771	1.59
7815	+15 VDC	276-1772	1.59
7905	-5 VDC	276-1773	1.59
7912	-12 VDC	276-1774	1.59

A DIVISION OF TANDY CORPORATION

# Radio Shack®

OVER 8800 LOCATIONS WORLDWIDE

Prices apply at participating Radio Shack stores and dealers

CIRCLE 61 ON FREE INFORMATION CARD



**YOUR own radio station!** AM, FM, cable, licensed, unlicensed, transmitter kits! Write: **BROADCAST-ING**, Box 130-F7, Paradise, CA 95969.

**BUILD** and sell ultrasonic remote control to mute unwanted TV commercials. Photos, schematics, parts list \$5.50. **J. CLARK**, 4720 Fielder, Tampa 33611.

**BIG PROFITS**

## ELECTRONIC ASSEMBLY BUSINESS

Start home, spare time. Investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

**FREE:** Complete illustrated literature  
BARTA, RE-O Box 248  
Walnut Creek, Calif. 94597

**BUY** direct from Taiwan/Hong Kong. Details \$1.00. Refundable. **TONY COLUCCI**, 56 Central Blvd. Merrick, NY 11566.

## GRAPHIC EQUALIZERS, ETC.

**NOISE** eliminators, expanders, power meters, others. Twelve-24 bands/channel equalizers from \$89.00 **Kit** see R-E 5-6/78, 2/80, 3-4/81. Catalog: **SSS**, 856R Lynrose, Santa Rosa, CA 95404. (704) 546-3895.

## SATELLITE TELEVISION

**UNSCRAMBLE** secret satellite channels watch all the good stuff. Plans \$19.95—kits 169.95—complete units \$395.00—Details and order forms \$3.00. **SCRAMCO**, 8688 Royal Dr., Nobleville, IN 46060.

**SATELLITE-TV receiver breakthrough!** Build your own system and save! Instruction manuals, schematics, circuit boards! Send stamped envelope: **XANDI**, Box 25647, Dept. 21A, Tempe, AZ 85282.

**ENJOY** satellite television. Save money with easy, guaranteed, do-it-yourself antenna plans/kits. Electronic knowledge not necessary. Send \$1.00 for catalog. **GFI-22**, Box 9108, Missoula, MT 59807.

**SATELLITES Today**, complete satellite television guide, teaches about purchasing, owning, operating, building earth stations and much more. Learn now and save money. Send \$13.95 (includes shipping) to **CONSOL NETWORK**, Box 12098, Suite E, Boulder, CO 80303.

## SATELLITE TV VIEWERS

Get the most complete weekly listings.  
Send \$1 for sample copy.

**Satellite TV Week**

P.O. Box 308E, Fortuna, California 95540  
800-358-9977 (U.S.) • 800-556-8787 (Calif.)  
707-725-2476 (all others)

## Satellite Descrambler

For West Star 5  
Movies Movies Movies

Send \$5.00 for information  
Modern Technology  
P.O. Box 419 D1  
Boston, Ma. 02186



## TI-99/4A SOFTWARE

**TI-99/4A** owners. Get your free catalog of new, exciting, low cost software. **DYNA**, Box 690, Hicksville, NY 11801.

## SCANNERS

**SCANNERS**—discount prices Bearcat BC-100 \$279.99; Bearcat 210XL \$214.99; Bearcat 300 \$335.99; Regency MX3000 \$186.99; JIL SX100 \$138.99; JIL SX200 \$269.99; Bearcat 20/20 \$275.99; Spectrum radar detector \$214.99; plus \$3.00 Shipping. Free discount catalog. Lowest prices anywhere on scanners, radar detectors, marine radios, two-way accessories. **SCANNER WORLD**, 10-RE New Scotland, Albany, NY 12208 (518) 436-9606.

## REEL-TO-REEL TAPES

**AMPEX** professional series open reel tape, 1800—or 2400—feet on 7-inch reels, used once. Case of 40, \$45.00. 10½ x 3600 feet and cassettes available. MasterCard/Visa. **VALTECH ELECTRONICS**, Box 6-RE, Richboro, PA 18954 (215) 322-4866.

## HOME ROBOTS

**WORLD'S largest supplier of home robot kits/parts.** Build your own. Computerized kits, parts, and publications. Catalog \$3.00. Design handbook \$15.00. Complete kits \$129.95. **ROBOT SHOP**, Dept. 10, PO Box 582, El Toro, CA 92630.

## SINE WAVE PATENT

**INCLUDES** patent complete explanations of authorization and control, video signal correction, audio system, \$20.00. **INTERNAL DESIGN**, Box 2512-P, Culver City, CA 90231.



# Active



1984 Mail Order Catalog

**The One Stop Electronic Shop!**  
**Call Toll FREE 1-800-343-0874**

### In the United States:

**Mail Orders**  
P.O. Box 8000  
Westborough, Mass.  
01581  
(Mass) (617) 366-0500

**Boston**  
133 Flanders Road  
Westborough, Mass.  
01581  
(617) 366-9684

**Seattle**  
13107 Northrup Way  
Bellevue, Wash.  
98004  
(206) 881-8191

### In Canada:

**Montréal**  
5651 Rue Ferrier  
Montréal, Québec  
H4P 1N1  
(514) 731-7441

**Ottawa**  
1023 Merivale Road  
Ottawa, Ontario  
K1Z 6A6  
(613) 728-7900

**Toronto**  
14 Carlton Street  
Toronto, Ontario  
M5B 1K5  
(416) 977-7692

**Calgary**  
3220-5th Ave. N.E.  
Bay 2  
Calgary, Alberta  
T2A 5N1  
(403) 235-5300

**Downsview**  
86 St. Regis Cr. N.  
Downsview, Ontario  
M3J 1Y8  
(416) 630-0400

**Vancouver**  
3070 Kingsway  
Vancouver, B.C.  
V5R 5J7

(604) 438-3321

Visit your nearest Active store, call, write or circle  
the Reader Service Card for your copy of Active's new catalog.

CIRCLE 77 ON FREE INFORMATION CARD





ORDER TOLL FREE

(800)  
538-8800

(CALIFORNIA RESIDENTS)

(800)  
848-8008



**TERMS:** Minimum order \$10.00. For shipping and handling, include \$2.50 for UPS ground or \$3.50 for UPS Blue (air). For each additional air pound, add \$1 for UPS Blue shipping and handling. California residents must include 6% sales tax; Bay area and LA residents include 6½% sales tax. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturers. All merchandise subject to prior sale.

**HOURS:** Mon. - Fri. 7:30 to 5:00  
Saturdays 10:00 to 3:00

VISIT OUR RETAIL STORE

2100 De La Cruz Blvd.  
Santa Clara, CA 95050  
(408) 988-0697

ALL MERCHANDISE IS  
100% GUARANTEED



## STATIC RAMS

2101	256 x 4 (450ns)	1.90
5101	256 x 4 (450ns) (cmos)	3.90
2102-1	1024 x 1 (450ns)	.88
2102L-4	1024 x 1 (450ns) (LP)	.98
2102L-2	1024 x 1 (250ns) (LP)	1.45
2111	256 x 4 (450ns)	2.45
2112	256 x 4 (450ns)	2.95
2114	1024 x 4 (450ns)	8/7.95
2114-25	1024 x 4 (250ns)	8/8.95
2114L-4	1024 x 4 (450ns) (LP)	8/9.95
2114L-3	1024 x 4 (300ns) (LP)	8/10.95
2114L-2	1024 x 4 (200ns) (LP)	8/11.95
2147	4096 x 1 (55ns)	4.90
TMS4044-4	4096 x 1 (450ns)	3.45
TMS4044-3	4096 x 1 (300ns)	3.95
TMS4044-2	4096 x 1 (200ns)	4.45
MK4118	1024 x 8 (250ns)	9.90
TMM2016-200	2048 x 8 (200ns)	4.10
TMM2016-150	2048 x 8 (150ns)	4.90
TMM2016-100	2048 x 8 (100ns)	6.10
HM6116-4	2048 x 8 (200ns) (cmos)	4.70
HM6116-3	2048 x 8 (150ns) (cmos)	4.90
HM6116-2	2048 x 8 (120ns) (cmos)	8.90
HM6116LP-4	2048 x 8 (200ns) (cmos)(LP)	5.90
HM6116LP-3	2048 x 8 (150ns) (cmos)(LP)	6.90
HM6116LP-2	2048 x 8 (120ns) (cmos)(LP)	9.95
Z-6132	4096 x 8 (300ns) (Qstat)	33.95

LP = Low Power Qstat = Quasi-Static

## DYNAMIC RAMS

TMS4027	4096 x 1 (250ns)	1.95
UPD411	4096 x 1 (300ns)	2.95
MM5280	4096 x 1 (300ns)	2.95
MK4108	8192 x 1 (200ns)	1.90
MM5298	8192 x 1 (250ns)	1.80
4116-250	16384 x 1 (250ns)	.49
4116-200	16384 x 1 (200ns)	.89
4116-150	16384 x 1 (150ns)	1.20
2118	16384 x 1 (150ns) (5v)	4.90
4164-250	65536 x 1 (250ns)	4.45
4164-200	65536 x 1 (200ns) (5v)	5.45
4164-150	65536 x 1 (150ns) (5v)	6.45

5V = Single 5 Volt Supply

## EPROMS

1702	256 x 8 (1µs)	4.45
2708	1024 x 8 (450ns)	2.49
2758	1024 x 8 (450ns)	2.49
2716	1024 x 8 (450ns) (5v)	5.90
2716-1	2048 x 8 (350ns) (5v)	2.95
TMS2516	2048 x 8 (450ns) (5v)	5.90
TMS2716	2048 x 8 (450ns)	5.45
TMS2532	4096 x 8 (450ns) (5v)	7.90
2732	4096 x 8 (450ns) (5v)	5.90
2732-250	4096 x 8 (250ns) (5v)	3.95
2732-200	4096 x 8 (200ns) (5v)	8.90
2732-100	4096 x 8 (200ns) (5v)	10.95
2764	8192 x 8 (450ns) (5v)	5.95
2764-250	8192 x 8 (250ns) (5v)	13.95
2764-200	8192 x 1 (200ns) (5v)	23.95
TMS2564	8192 x 8 (450ns) (5v)	16.95
MC68764	8192 x 8 (450ns) (5v) (24 pin)	38.95
27128	16384 x 8 Cell	19.95

5v = Single 5 Volt Supply

## 74LS00

74LS00	.23	74LS92	.54
74LS01	.24	74LS93	.54
74LS02	.24	74LS95	.74
74LS03	.24	74LS96	.88
74LS04	.23	74LS107	.38
74LS05	.24	74LS109	.38
74LS08	.27	74LS112	.38
74LS09	.28	74LS113	.38
74LS10	.24	74LS114	.38
74LS11	.34	74LS122	.44
74LS12	.34	74LS123	.78
74LS13	.44	74LS124	2.85
74LS14	.58	74LS125	.48
74LS15	.34	74LS126	.48
74LS20	.24	74LS132	.58
74LS21	.28	74LS133	.58
74LS22	.24	74LS136	.38
74LS26	.28	74LS137	.98
74LS27	.28	74LS138	.54
74LS28	.34	74LS139	.54
74LS30	.24	74LS145	1.15
74LS32	.28	74LS147	2.45
74LS33	.54	74LS148	1.30
74LS37	.34	74LS151	.54
74LS38	.34	74LS153	.54
74LS40	.24	74LS154	1.85
74LS42	.48	74LS155	.68
74LS47	.74	74LS156	.68
74LS48	.74	74LS157	.64
74LS49	.74	74LS158	.58
74LS51	.24	74LS160	.68
74LS54	.28	74LS161	.64
74LS55	.28	74LS162	.68
74LS63	1.20	74LS163	.64
74LS73	.38	74LS164	.68
74LS74	.34	74LS165	.94
74LS75	.38	74LS166	1.90
74LS76	.38	74LS168	1.70
74LS78	.48	74LS169	1.70
74LS83	.59	74LS170	1.45
74LS85	.68	74LS173	.68
74LS86	.38	74LS174	.54
74LS90	.54	74LS175	.54
74LS91	.88	74LS181	2.10

74LS189	8.90	74LS363	1.30
74LS190	.88	74LS364	1.90
74LS191	.88	74LS365	.48
74LS192	.78	74LS366	.48
74LS193	.78	74LS367	.44
74LS194	.68	74LS368	.44
74LS195	.68	74LS373	1.35
74LS196	.78	74LS374	1.35
74LS197	.78	74LS377	1.35
74LS221	.88	74LS378	1.13
74LS240	.94	74LS379	1.30
74LS241	.98	74LS385	1.85
74LS242	.98	74LS386	.44
74LS243	.98	74LS390	1.15
74LS244	1.25	74LS393	1.15
74LS245	1.45	74LS395	1.15
74LS247	.74	74LS399	1.45
74LS248	.98	74LS424	2.90
74LS249	.98	74LS447	.36
74LS251	.58	74LS490	1.90
74LS253	.58	74LS624	3.95
74LS257	.58	74LS640	2.15
74LS258	.58	74LS645	2.15
74LS259	2.70	74LS668	1.65
74LS260	.58	74LS669	1.85
74LS266	.54	74LS670	1.45
74LS273	1.45	74LS674	9.60
74LS275	3.30	74LS682	3.15
74LS279	.48	74LS683	3.15
74LS280	1.95	74LS684	3.15
74LS283	.68	74LS685	3.15
74LS290	.88	74LS688	2.35
74LS293	.88	74LS689	3.15
74LS295	.98	74LS783	23.95
74LS298	.88	81LS95	1.45
74LS299	1.70	81LS96	1.45
74LS323	3.45	81LS97	1.45
74LS324	1.70	81LS98	1.45
74LS352	1.25	25LS2521	2.75
74LS353	1.25	25LS2569	4.20

## SPRING SPECIALS

4116	250ns	49¢/ea
4116	200ns	89¢/ea

2708	8K EPROMS	2.49
2716	16K EPROMS	2.95
2732	32K EPROMS	3.95
2764	64K EPROMS	5.95
27128	128K EPROMS	19.95

4164	64K DYNAMIC 250ns	4.45
4164	64K DYNAMIC 200ns	5.45
4164	64K DYNAMIC 150ns	6.45
2114	450ns	8/7.95

## 5¼" DISKETTES ATHANA

SSSD	18.95
SSDD	22.95
DSDD	27.95

## BULK DISKETTES 5¼" DISKETTES NO LABEL

SINGLE SIDED DOUBLE DENSITY  
(WITH JACKETS AND HUB RING)

Pack of Ten	\$ 16.95
Pack of 100	\$149.00



### POPULAR CHIPS

NE564	2.75
LM 301	.49
LM 565	.95
MC 1330	1.25
MC 1350	1.15
MC 1458	.49
MC 1496	1.00
LM 1889	1.75
7805	.80
7808	.50
7812	.80
7815	.80
7818	.80
MV 2109	.69
2N2222	.30
MC 1349	1.79

### FUNCTION GENERATOR KIT

Uses XR-2206 IC. 1 Hz to 100 kHz.  
Complete with PC Board & all parts except power supply and enclosure **\$19.95**

### DELUXE PARTS ASSORTMENTS

#### #1 Resistors & Trimpots

68 1/4 watt, 5% resistors & 5 PT-15 10K trimpots, 1 each - 51, 75, 100, 470, 1.5K, 3.6K, 51K, 470K, 13-1.2K, 2-220, 3-100K, 6-330, 6-12K, 7-910, 9-3.3K, & 14-4, 7K.  
**\$4.50 ea, 10/40.00**

#### #2 Capacitor "A"

Monolithics - 1-560pf, 7-1 mfd. & 1-22 mfd. Silver Micas - 2-10pf, & 1 each of 43pf, 110pf, 560pf, 1200pf, 3000 or 3300pf.  
**\$4.95 ea, 10/45.00**

#### #3 Capacitor "B"

Myllars 4-.001, 2-.047, 29-.01. Radial lytics 3-10 mfd 16V, 1-1000 mfd 50V, 1-2200 mfd 35V. Disc Caps 1 each of 5, 12, 27, 36, 110, 330pf, 2-120pf, 3-39pf, 3-220pf, and 1 Vari Cap 5-35pf.  
**\$7.50 ea, 10/70.00**

#### #4 Coil & Chokes

1 each of 15, 33, and 100 (uh) micro henries chokes. 1-variable RF coil (same as #49A537MPC)  
**\$3.25 ea, 10/30.00**

#### #5 IC's Sockets, & Semi's

1 each of: NE564, LM565, MC1330, MC1350, MC1496, LM1889, 7812, 7818, 2N2222A, MV2109, heat sink 2-MC1458, 4-1N4002, 4-8 pin, 2-14 pin, 1-16, & 1-18 pin socket.  
**\$13.50 ea, 10/125.00**

#### #6 Misc Hardware

LED & holder, fuse & holder, line cord, grommet, SPST switch, DPDT switch, 2-F61 conn. & lugs, knob, 4-spacers, 6-screws & nuts, 2'RG-174, matching transformer w/nut.  
**\$5.95 ea, 10/57.50**

### SPECIALS ON PRIME IC's

NE564  
**\$2.75 ea, 10/\$25, 100/\$195**

LM1889  
**\$1.75 ea, 10/16.50, 100/\$150**

MC1496  
**\$1.00 ea, 10/\$9, 100/\$75**

### UHF AMP KIT

25db Gain stripline PC board using (2) BFR-90's  
Complete (no enclosure) **\$10.95**  
Power supply for above **\$3.49**

### POWER TRANSFORMERS

Pri: 115V AC  
Sec: 24 volts @ .350 A  
Dim: 2 1/4 x 1 1/4 x 2 H  
**\$1.95 ea, 10/\$15.00 100/\$125.00**

### NETWORK SALES, INC.

2343 W. BELMONT AVE.  
CHICAGO, IL. 60618  
**312/248-3202**

Phone Orders Welcome.  
QUANTITIES MAY BE LIMITED

TERMS: Visa, M.C., Check, Money Order or COD (addit. \$3.00). Min. Order \$10.00. Add \$2.50 S&H for USA. Ill. add 8% Tax. **MAIL ORDER ONLY.** Prices subject to change without notice.  
WRITE FOR OUR MONTHLY UN-ADVERTISED SPECIALS

©COPYRIGHT 1984 NETWORK SALES, INC.

# DON'T FORGET



USE  
YOUR  
READER  
SERVICE  
CARD

### A SINGER'S DREAM!

### REMOVES VOCALS FROM RECORDS!

Now You can sing with the world's best bands! The Thompson Vocal Eliminator can remove most or virtually all of a lead vocal from a standard stereo record and leave the background!

Write or call for a free brochure and demo record.

**LT Sound, Dept. R-1, P.O. Box 338, Stone Mountain, GA 30086 (404) 493-1258**

### CB EQUIPMENT

**PALOMAR/Pride electronics**—exclusive repair facility. Service—update—improvements on these and similar equipment. **PALOMAR-PRIDE REPAIR, 1320-A Grand, San Marcos, CA 92069 (619) 744-0720.**

### WANTED

**INVENTIONS**, ideas, new products wanted for presentation to industry and exhibition at national technology exposition. **Call 1-800-528-6050.** Arizona 1-800-352-0458. X831.

**HALLICRAFTERS S-40, S-52, S-77.** Any condition. Paying \$20.00-\$40.00 each. **FALA ELECTRONICS, Box 04134-2, Milwaukee, WI 53204.**

# BUY BONDS

# HITACHI

## TEST EQUIPMENT DISCOUNT PRICES

### V-209

DC-20MHz • Dual Trace  
Battery Operated

Reg. \$945  
**\$745** **SAVE \$200**

### V-509

DC-50MHz • Dual Trace  
Delayed Sweep

Reg. \$1399  
**\$1149** **SAVE \$250**

### OSCILLOSCOPES

COMPLETE LINE OF INSTRUMENTATION AT THE MOST COMPETITIVE PRICES  
PRICES INCLUDE \$50.00 PROBES, FREE WITH ALL SCOPES.

### V-650F

60MHz • Dual Trace  
Delayed Sweep

Reg. \$1195  
**\$985** **SAVE \$210**

### V-1050F

100MHz • Quad Trace  
Delayed Sweep

Reg. \$1980  
**\$1280** **SAVE \$600**

### V-222

DC-20MHz • Dual Trace

Reg. \$695  
**\$545** **SAVE \$150**

### V-422

DC-40MHz • Dual Trace

Reg. \$895  
**\$649** **SAVE \$246**

### DIGITAL MULTIMETERS

3 1/2 Digit • 8 Functions • +18" - +28°C Accuracy • AC & DC • Resist • 500 Hours • Data Hold • w/Battery, Test Leads & Fuse • Auto range

**VR-3510** Reg. \$187 **\$137**  
**VR-3525** Reg. \$147 **\$107**  
**VR-3550** Reg. \$127 **\$97** **SAVE UP TO \$50**

### V-6015

1MHz/2 Channels • 1000 Words Per Channel

Reg. \$1995  
**\$1695** **SAVE \$300**

### V-6041

40MHz/2 Channels • 4000 Words Per Channel

**CALL FOR SPECIAL PRICING** **IN STOCK**

**TOTAL ELECTRONICS CENTER • OVER 70,000 ITEMS IN STOCK**

**WM. B. ALLEN SUPPLY CO. INC.**  
**ALLEN SQUARE**  
300 BLOCK NORTH RAMPART STREET, NEW ORLEANS, LOUISIANA 70112

**CALL TOLL FREE**  
**800 535-9593**  
LOUISIANA TOLL FREE 800 462-9529

RADIO-ELECTRONICS





# FORMULA INTERNATIONAL INC.

12603 Crenshaw Blvd., Dept. B, Hawthorne, CA 90250

For information (213) 973-1921 • Orders Only (outside Calif.) (800) 672-8758



## MARK IV — 15 STEP LED POWER LEVEL INDICATOR KIT


This new stereo indicator kit consists of 36 4-color LED's (15 per channel) to indicate the sound level output of your amplifier from -36dB to +3dB. Comes with a well designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6-12VDC with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W. Kit includes 70 pcs driver transistors, 38 pcs matched 4-color LED's, all electronic components, PC Board and front panel. **MARK IV KIT \$31.50**



No FCC License  
Required  
**OUR PRICE \$49.50**  
Additional Microphone  
(Transmitter) Available  
at **\$28.00 ea.**  
**MURA WMS-49**
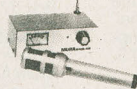
## CRYSTAL CONTROLLED WIRELESS MICROPHONE SYSTEM

Transmitter: FET mic for flat 30Hz-18KHz response. X'tal controlled 49MHz AM Band for drift-free performance. 100mW output (range approx. 1/4 mile) for reliable long range transmission. Powered by a 9V radio battery.



Receiver: X'tal controlled locks on 49MHz transmitter signal. On panel VU meter, monitors the signal strength from the microphone. Standard phone jack outlet connection to a P.A. or other phone input. 9V battery included. This professional set is ideal for on stage, in field, church, in house or outdoor use.


**TA-1000  
KIT  
\$51.95**

**Power  
Transformer  
\$24.00 ea.**
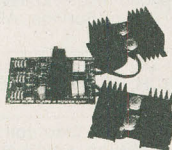
## 100W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low TIM stereo pre-amp.

Specifications • Output power 100W RMS into 8Ω. 125W RMS into 4Ω • Frequency response 10Hz-100KHz • THD less than 0.01% • S/N ratio better than 80dB • Input sensitivity 1V max. • Power supply ±40V at 5A.



## LOW TIM DC STEREO PRE-AMP KIT TA-1020

Incorporates brand-new DC design that gives a frequency response from 0-100KHz ±0.5dB. Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuations!

Specifications: • THD/TIM less than .005% • Frequency response DC to 100KHz ±0.5dB • RIAA deviation ±0.2dB • S/N ratio better than 70dB • Sensitivity: Phone 2mV 47KΩ, Aux 100mV 100KΩ • Output level 1.3V • Max output 15V • Tone controls: Bass ±10dB @ 50Hz, Treble ±10dB @ 15Hz • Power supply ±24VDC @ 0.5A. Kit comes with regulated power supply. All you need is a 48VCT transformer @ 0.5A.

**Only \$44.50  
Transformer  
\$4.50 ea.**



## pinecom™ DP-64



- Dual Processor (6502 and Z80A)
- Detached Keyboard
- 64K RAM Expandable to 192K
- 25 Function Key Keyboard
- Auto Repeat Keys w/Upper/lower Case
- 2 Slim Disk Drives (optional)
- 100% Apple II Compatible
- 40/80 Column Display (optional)
- Runs Both Apple Soft and CP/M Software

**Model DP-64**

**Fully Assembled ...**

**\$650<sup>00</sup>**



**pinecom™**

## Pioneer of Low Cost Apple\* Compatible Computer



**Now  
with New  
Improved  
Keyboard  
and 64K RAM**

No Copyright Problems!

### Compare These Features with Our Competitors:

- Powerful Utility Program (100% Apple Compatible)
- 68-Key Upper & Lower Case Keyboard with Numeric Keypad
- 25 Pre-programmed Function Keys
- 2 Speed Auto Repeat Function
- 64K User Memory—expandable to 192K
- 5A Switching Power Supply (110/220VAC)
- All ICs Are Socketed for Easy Service
- Nation-wide Dealer Network for Convenient Technical Support

*And best of all, the price  
Assembled and Tested is just .....*

**\$499<sup>00</sup>**

SEND ONE DOLLAR  
FOR OUR DETAIL CATALOG

Inside California  
Outside Calif. (incl. Mexico & Canada)  
Overseas

Shipping & Handling Charges	
Under \$50.00	Over \$50.00
Purchase 10%	Purchase 5%
15%	10%
25%	20%

Minimum Order \$10.00/Calif. Residents add 6.5% Sales Tax. Phone Orders Accepted on VISA or MC ONLY. NO C.O.D.'s. Prices subject to change without notice.



**\$59.50 per Kit**

**Model TR88A  
0-15VDC @ 2A**

**Model TR88B  
0-30VDC @ 1A**

## MAGNETIC HEAD EQUALIZER

• Standard RIAA curve for all kinds of magnetic heads • 3 stages crossover circuit for best results • Output voltage guaranteed to be stable without any oscillation • Power Supply: 24 V.D.C.



**MODEL: MA-142  
Part #370-370 ..... \$6.95 ea.**

## PROFESSIONAL REGULATED VARIABLE DC POWER SUPPLY KIT

All solid state circuitry with high efficiency power transistor 2SD388 and IC voltage regulator MC1733. Output voltage can be adjusted from 0-30V at 1A current limited or 0-15V at 2A current limited. Internal resistance is less than 0.005Ω, ripple and noise less than 1mV, dual on panel meters for voltage and current reading, also with on board LED and audible over load indicator. Kit comes with pre-drilled PC Board, instructions, all necessary electronic components, transformer and a professional looking metal cabinet. The best project for school and the most useful instrument for repairmen. Build one today!

## STEREO MIC. AND ECHO MIXER FOR STEREO AMPLIFIER SYSTEM

The circuitry employs all integrated circuits, BBD type echo circuit, echo time can be adjusted (max. 30 Msec.) Also with a microphone preamp on the board. Fully assembled.



**MODEL: MX205  
Part #370-0360 ..... \$29.95 ea.**

## LOW T.I.M. TRANSISTORS 100W + 100W

• Employs Hitachi low noise I.C. for pre-amp • Max. output 16 V P-P (non distortion) • With hi-low filter, and tone defeat circuit • Rear power amp with short circuit protection • Giant heat sink for maximum results • Tone controls ±14dB • All components (except pots for volume, and tone controls) are pre-assembled, the quality is guaranteed. • Power supply DC ±35V-50V



**MODEL: SA802C  
Part #370-0340 ..... \$85.00  
POWER TRANSFORMER  
(68V-80V CT 6 AMP)  
Part #670-0220 ..... \$24.50**



**STORE HOURS  
MON-FRI—10-7  
SAT—10-6**

\*Apple and Apple II are the trademark of APPLE COMPUTERS, INC.

CIRCLE 76 ON FREE INFORMATION CARD



## NEW! MULTI-CHANNEL MICROWAVE

\*\*\*\*\*  
Complete Antenna Systems from \$69<sup>95</sup>


Full 800 Mhz Range  
Tune 1.9-2.7 Ghz  
Includes all  
ITFS Channels

DEALERS WANTED

COD's and Credit Card  
Orders call TOLL FREE

1-800-247-1151

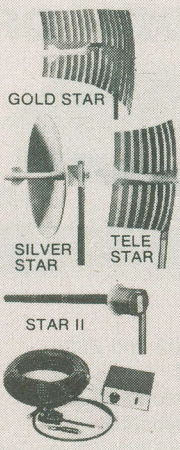**GALAXY**  
ELECTRONICS  
5644 N. 53rd Avenue  
Glendale, AZ 85301  
1-602-247-1151



## CB MODIFICATIONS

Increase channels, range, privacy! We specialize in frequency expanders, speech processors, FM converters, PLL & slider tricks, how-to books, plans, kits. Expert mail-in repairs & conversions. 16-page catalog \$2.

CBC INTERNATIONAL, P.O. BOX 31500RE,  
PHOENIX, AZ 85046 (602) 996-8700

WRITE FOR  
**McGEE'S**  
SPEAKER & ELECTRONICS CATALOG  
1001 BARGAINS IN SPEAKERS  
Tel.: 1 (816) 842 5092  
1901 MCGEE STREET KANSAS CITY, MO. 64108

### FOR SALE

**CABLE-TV SECRETS**—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included. Send \$8.95 to **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

**RESISTORS** ¼ & ½W 5% 3 cents. 1% Metallfilms, precision custom wirewounds, \$1.00 refundable to: **JR INDUSTRIES**, 5834-B Swancreek, Toledo, OH 43614.

**FREE** catalog featuring scanner accessories, carrier/subcarrier detectors, voice scramblers, unusual kits. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520.

**DESCRAMBLERS** for downconverters, high gain. Send \$1.00. **RB ELECTRONICS**, PO Box 643, Kalamazoo, MI 49005.

**THE Intelligence Library**—Restricted technical information & books on **electronic surveillance, surveillance-device schematics, lock-picking, investigation, weapons, identification documents, covert sciences**, etc. The best selection available. **Free brochures**. **MENTOR**, (Dept. Z), 135-53 No. Blvd., Flushing, NY 11354.

**CABLE TV** equipment, notch filters for "beeping" channels. Information \$1.00. **GOLDCOAST**, PO Box 63/6025 RE, Margate, FL 33063.

**RF parts/Motorola transistors**. MRF454 \$16.00, MRF455 \$12.00. Catalog available. **RF PARTS CO.**, 1320 Grand, San Marcos, CA 92069. (619) 744-0720.

THE BEST PLACE to BUY, SELL or  
TRADE NEW and USED EQUIPMENT  
**NUTS & VOLTS MAGAZINE**  
BOX 1111-E • PLACENTIA, CA 92670  
(714) 632-7721  
Join Thousands of Readers Nationwide  
Every Month  
**ONE YEAR U.S. SUBSCRIPTIONS**  
\$7.00 - 3rd Class • \$12.50 - 1st Class  
\$25.00 - Lifetime - 3rd Class

**NUTS & VOLTS**  
NEW & USED EQUIPMENT  
HAM GEAR  
COMPUTERS  
SOFTWARE  
SCANNERS • OPTICS  
TEST EQUIPMENT  
MICROWAVE  
SATELLITE  
AUDIO VISUAL  
NEW PRODUCTS  
COMPONENTS • KITS  
ANTIQUE ELECT.  
PUBLICATIONS  
PLANS • SERVICES

**UP to \$500.00 per month**. Sell computer software in your home. Write to: **COMPUTER SERVICES**, PO Box 7748, Tucson, AZ 85725.

**CABLE-TV** products. Jerrold, Hamlin, and Oak converters. Send \$3.00 for information. **ADDITIONAL OUTLET CORP.**, 111 E. Commercial Blvd., Ft. Lauderdale, FL 33334.

**RECONDITIONED test equipment**. \$1.00 for catalog. **JAMES WALTER TEST EQUIPMENT**, 2697 Nickel, San Pablo, CA 94806.

**POLICE** code unscramblers, other scanner accessories, telephone recording device, **DNE, Inc.**, Rt. 7, Box 257E, Hot Springs, AR 71901, (501) 623-6027.

**NEW!... repair any TV... easy**. Anyone can do it. Write, **RESEARCH**, RR No. 3, Box 601BR, Colville, WA 99114.


**EXACT same PCB and Toko coil set (no. 4) for descrambler in February article** only \$15.00 shipping \$2.00. **JIM RHODES**, 1025 Ransome Lane, Kingsport, TN 37660.

**CONVERTERS** all types for all systems, lowest prices anywhere, quantity discounts, dealer inquiries accepted. Send \$1.00 for catalog. **PG VIDEO CORP.**, PO Box 296, Latham, NY 12110 (518) 274-6593.


**OVER 1200** electronics parts, kits, and computer products. Lowest prices. Send \$1.00 (redeemable) for catalog. Stamp brings flyer. **DAYTAPO ELECTRONICS**, 3029 N. Wilshire, Arlington Hts., IL 60004.

## MICROWAVE TV ANTENNA SYSTEMS

Freq. 2.1 to 2.6 GHz • 34 db Gain +

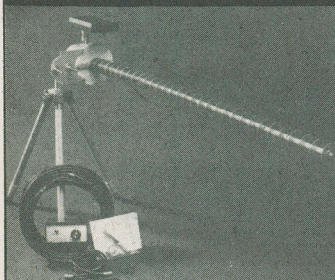

TWO YEAR WARRANTY  
PARTS & LABOR

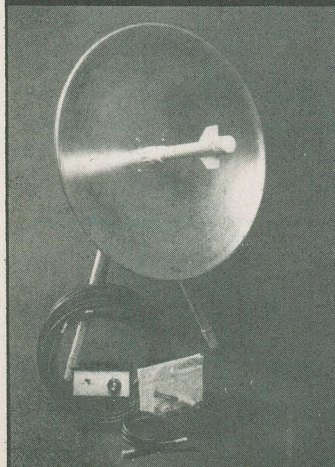

COMPLETE SYSTEMS  
(as Pictured)  
Commercial 40"

Rod Style \$ 89.95

Parabolic 20"

Dish Style \$ 79.95

COMPONENTS

Down Converters  
(both types) \$ 34.95

Power Supplies  
(12V to 16V) \$ 24.95

Data Info (Plans) \$ 9.95

CALL OR WRITE FOR  
KITS, PARTS, INDIVIDUAL  
COMPONENTS

We Repair All Types Down  
Converters & Power Supplies


**Phillips-Tech**  
**Electronics**  
1043 N. STADEM DR.  
TEMPE AZ. 85281  
(602) 967-6972

Special Quantity Pricing  
Dealers Wanted



## NORTH AMERICAN SOAR corporation PEN-STYLE DIGITAL MULTIMETER

MODEL 3100  
GREAT PRICE **\$49.00**

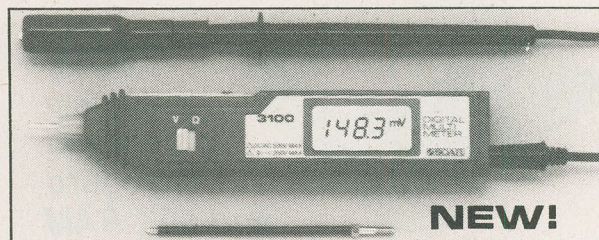

**NEW!**

Hand Held LCD Display - Fast One Hand Operation

### SPECIFICATIONS:

Display: LCD 3½ digits maximum reading of 1999/continuity beeper built-in

Range: Auto ranging

Polarity: Automatic no indication for positive polarity; minus sign for negative polarity

Overrange Indication: MBS 1 or -1 indication

Data Hold: Data hold in all ranges with hold switch on

Low Battery Indication: "B" mark displayed when battery drops below operating voltage

Sampling: 2 Times/second

Power Supply: SR-44 battery (1.55V) X2

Power Consumption: 5.5mW

Size: 6"x1¼" LWH (less probe tips) includes ½" and 2" probes

Add \$2.50 For Shipping

STOCKING DISTRIBUTOR



**KCS ELECTRONICS**  
CORPORATION

SEMICONDUCTOR PARTS AND PRODUCTS

1043 N. STADEM DR.  
TEMPE, AZ 85281

**(602) 967-6945**

Call or Write for **FREE**  
Semiconductor Parts & Products Catalog



# ADVANCED COMPUTER PRODUCTS

## RAM UP-GRADES

64K D RAM (4164-200nS)

9 pcs for \$50<sup>00</sup>

16K D RAM (4116-200nS)

8 pcs for \$12<sup>95</sup>

### REPEAT OF SELL-OUT

#### 58 Key Unencoded Keyboard



\$19<sup>95</sup> ea.

This is a new 58 key terminal Keyboard manufactured by a major manufacturer. It is unencoded with SPST keys unattached to any PC board. Solid molded plastic base measures 11" x 4".

### Unencoded Key Pad

15 key Keypad with 1-10 keys and tab, return, (.), (,) and (.)



Only \$9<sup>95</sup> ea.

### UV "EPROM" ERASER



Model DE-4

\$89<sup>95</sup>

Holds 4 EPROM's at a time.

Model S-52T \$325.00

### CORCOM FILTER



Popular CORCOM Filter

\$4<sup>95</sup>

Compatible Line Cord Add. .... \$3.50

### SWITCHER SPECIAL

by ASTEC

Originally designed for the Apple III

+5 @ 4.0A

-5 @ .25A

+12 @ 2.5A

-12 @ .30A

only \$49<sup>95</sup>

### MISC. HI-TECH

MM5740AAC	9.95	3341FFFO	\$4.75
AYS 2376	13.75	2513-001UC	9.50
AYS 3600	13.75	2513-002LC	9.50
UPD7201	29.95	7107CPL	11.50
ULN2003	2.25		

WE STOCK 74HC & 74C CMOS

### PALS

PAL10H8	\$3.75	PAL14L4	\$3.95
PAL12H6	3.95	PAL16L8	9.95
PAL14H4	3.95	PAL16R8	7.75
PAL10L8	3.95	PAL16R6	7.75
PAL12L6	3.95	PAL16R4	7.75

### FUNCTION GEN.

MC4024	\$3.75	LM566	\$1.95
8038	3.75	XR2208	3.75

### UARTS/USRTS

AYS-1013A	\$3.95	2350	\$9.75
AYS-1014A	6.75	8250	12.50
AYS-1015	6.75	IM6402	8.75
TR1602A	3.75	IM6403	7.75

### BAUD RATE GEN.


MC14411	\$11.50	COM5016	\$15.95
BR1941	10.50	COM8116	11.95
34702	12.75	MM5307	11.95

### SOUND CHIPS

76477	\$3.50	MC3340	\$1.95
76489	5.00	SI-01 Votrac	39.95
76489	8.50	DT1050	
AY38910	8.95	Digitaltr	34.95
AY38912	12.50	MM54104	14.95
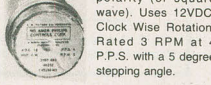
### STEPPER MOTOR


Operates by applying 12VDC in one direction and then reversing polarity (or square wave). Uses 12VDC. Clock Wise Rotation. Rated 3 RPM at 4 P.P.S. with a 5 degree stepping angle.



ACP Price \$3<sup>95</sup>

10 for \$34.95

### RS232 SIGNAL TESTER

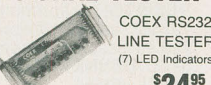

COEX RS232


LINE TESTER

(7) LED Indicators

Only \$24<sup>95</sup>

Other Styles Also Available

### CONNECTORS

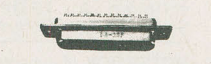

DB25P (RS232)

DB25S Female

1.49

Sel with Hood, Sale

25/50 S/T, Apple

25/50 W/W, Apple

31/62 S/T, IBM

31/62 W/W, IBM

50/100 W/W, S-100 Connector

50/100 S/T, S-100 Connector

3.95

3.95

3.95

3.95

### MICROPROCESSORS

68000	\$47.95	6504	\$6.75	8749	\$49.95
6800	3.95	6505	8.95	8755	39.95
68800	10.50	6507	9.95	Z-80	3.75
6802	7.50	8035	8.95	Z-80A	4.30
6802	20.95	8036	11.95	Z-80B	9.30
6803	18.50	8080	3.50	Z8001	44.95
6808	13.50	8085	4.75	Z8002	49.95
6809E	12.95	8085A-2	11.00	F-83850	19.95
68802E	27.95	8086	29.95	2650	16.95
6809	11.50	8087	199.00	1802	5.95
68809	27.95	8088	29.95	8008-1	16.95
6502	4.75	8089	84.95	2901	6.95
6502A	6.50	8741	3.95	2901A	8.50
6502B	9.75	8748	39.95	Z8671	37.95

WE STOCK IN DEPTH

CALL FOR VOLUME PRICING

### EPROMS

1702	\$4.25	2732	\$4.75	2764-250	\$7.50
2708	3.85	2732-250	8.25	2764-200	16.75
2716	4.95	2732A-200	9.95	89764	39.95
2716	3.85	2732A-200	9.95	89766	41.95
2716-1	5.75	2732A	8.75	27128	27.95
TMS2716	7.50	2732A2	13.00	5203AQ	14.50
TMS2516	5.25	2764	6.75	520AQ	14.50
TMS2532	5.75				

### STATIC RAMS

2101	\$2.75	2147	\$4.75	5516	\$11.95
2102-1	.99	2016-200	4.95	1116-4	4.95
2102L-4	1.29	2016-150	5.95	6116-2	8.75
2102L-2	1.49	2016-100	6.95	6116P-4	5.90
2111	2.75	4044-4	3.95	6116LP2	10.95
2112	2.89	4044-2	6.50	216132	32.50
2114	1.49	4118	9.50	HM6264	47.50
2114L-2	1.89	5514	3.50	6167	9.95

### DYNAMIC RAMS

MK4027	\$1.85	4116-200	\$1.49
UPD410	8.95	4164-200	6.95
UPD411	4.95	4164-150	5.75
MM5280	9.95	MC6505	8.50
MM5290	1.49	TMS4164-15	8.50
MM5298	1.49	41256	79.95

WE STOCK MOST OBSOLETE RAMS.

CALL FOR YOUR HARD TO FIND PARTS.

### 8000 SUPPORT

8155	\$9.95	8238	\$4.75	8271	\$74.95
8156	9.95	8243	5.50	8272	37.50
8202	23.50	8250	10.50	8275	34.95
8203	36.50	8251	9.95	8279	9.95
8205	3.25	8251A	9.95	8279-5	8.95
8212	1.95	8253	6.50	8282	7.95
8214	4.50	8253-5	9.95	8283	7.95
8216	1.95	8255	5.95	8284	7.95
8224	2.20	8255A	9.95	8286	7.95
8226	2.75	8257	7.25	8287	7.95
8228	3.35	8257-5	9.95	8288	24.95
8237	18.50	8259	7.25	8289	48.50
8237-5	21.50	8259-5	37.50		

### 6500 SUPPORT

6520	\$4.25	6532	\$9.75	6545A	\$26.50
6522	6.75	6532A	11.75	6551	11.50
6522A	8.50	6545	21.50	6551A	12.95

### 6800 SUPPORT

6810	\$2.75	6840	\$17.95	6850	\$5.75
68B10	6.75	6843	31.50	6852	5.50
6820	4.25	6844	25.00	6860	7.75
6821	3.75	6845	14.75	6875	6.25
68821	6.75	68845	17.50	6880	2.50
6828	12.50	6847	11.75	68847	22.95
6840	12.50	6850	3.50	68488	19.50

### Z-80 SUPPORT

Z80CTC	\$3.95	Z80DART	\$10.75	Z80ASIO-1	\$12.50
Z80ACTC	4.75	Z80ADART	10.95	Z80ASIO-2	11.50
Z80BCTC	9.75	Z80BART	18.95	Z80ASIO-2	36.00
Z80PIO	3.95	Z80SIO-0	11.50	Z80SIO-2	12.50
Z80PIO	4.75	Z80SIO-10	12.50	Z80SIO-9	11.50
Z80PIO	12.50	Z80SIO-1	11.50	Z80ASIO-9	12.50

### SOCKETS



### LOW PROFILE SOCKETS (TIN)

	1-24	24-49	50-100
8 pin LP	.16	.15	.14
14 pin LP	.20	.19	.18
16 pin LP	.22	.21	.20
18 pin LP	.29	.28	.27
20 pin LP	.34	.32	.30
22 pin LP	.39	.37	.36
24 pin LP	.38	.37	.36
28 pin LP	.45	.44	.43
40 pin LP	.60	.59	.58


### 3L WIREWRAP SOCKETS (GOLD)

	1-24	25-49	50-100
8 pin WW	.55	.54	.49
10 pin WW (Tin)	.65	.63	.58
14 pin WW	.75	.73	.70
16 pin WW	.80	.77	.70
18 pin WW	.95	.90	.81
20 pin WW	1.15	1.08	.99
22 pin WW	1.45	1.35	1.23
24 pin WW	1.35	1.26	1.14
28 pin WW	1.60	1.53	1.38
40 pin WW	2.20	2.09	1.89

### CLOCK CHIPS


MM5369	\$3.50	MM58174	\$10.95
MM58167	11.95	MSM5832	3.95

### OSCILLATORS

		
32.768KHz	\$1.95	2.4576
1.000MHz	3.75	3.2768MHz
1.842MHz	3.75	3.5795MHz
2.000MHz	2.95	4.000MHz
2.010MHz	2.95	5.000MHz
2.097152MHz	2.95	5.0688MHz



## Worlds Most Remarkable Radar Jammer!

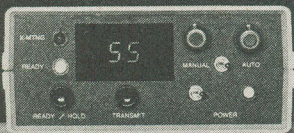

Causes speed radar guns and devices to read out your choice of either a percentage of your true speed when in automatic mode (example: Your speed; 76 mph, auto mode set for 75%, speed displayed — 57 mph), or the speed that you dial in when in manual mode. Transmits only in the presence of speed radar, or by manual override. Operates on both X and K bands. WARNING: The device described in this literature is not legal for use against police radar, and is not FCC approved.

For complete literature and plan package, send \$14.95 to:

**Phillips Instrument Design Co. Inc.**  
9560 S.W. Barbur Blvd., Suite #109 S  
Portland, Oregon 97219

**RARE** parts and surplus electronics bargains. RF, linear, digital computers, robotics. Free catalog. **ODD BALL ELECTRONICS**, PO Box 879R, Duncanville, TX 75116.

**VCR protective cover** clear vinyl 18 1/2 x 15 1/2 x 5 beautifully made \$11.95. **WINDOW MOODS**, 8228 Scotts Level Road, Baltimore, MD 21208.

**CONNECTORS**—audio, co-axial, aviation, computer, industrial, and many other types. Send \$2.00 for complete price list and ordering information. Largest inventory in country. **CONNECTOR TECHNOLOGY INC.**, 5A Veronica Ave., Somerset, NJ 08873.

**DELUXE Cable/UHF converters.** All systems. Zenith SSAVI-1 \$225.00, SB-3 \$89.95, N-12 \$79.95. \$2.00 catalog. **PRECISION VIDEO**, PO Box 1323, Elgin, IL 60121.

**WHOLESALE** indoor antenna \$14.00. Master video control center \$30.00. (212) 897-0509. **D&WR**, 68-12 110 St., Flushing, NY 11375.

**TUBES**—All types, discount prices. Many antique and hard-to-find types. Send \$1.00 for 16-page cata-

## WERSI electronics ORGAN & PIANO KITS

### ALPHA DX 300



### fully DIGITAL RS232 Interface

For Free Sound Info  
Call 1-800-233-3865  
or write WERSI USA  
Dept. M 8 P.O. Box 5318  
Lancaster, PA 17601

log. We buy antique tubes. **ANTIQUE ELECTRONIC SUPPLY**, 1725 W. University, Tempe, AZ 85281.

**CHANNEL 3**—60dB notch filter. 63.5MHz. \$32.00. **CROSLLEY**, Dept., 763, Box 840, Champlain, NY 12919.

**FREE** pay-TV reception. "How-to" book. HBO, Showtime, Cinemax. \$4.95. **DIPTRONICS**, PO Box 80E, Lake Hiawatha, NJ 07034.

**SENSATIONAL!** feature loaded three channel light chaser/color organ w/dimmer, 800 watts/channel, \$295.00. **DESIGN SPECIALTY**, Box 1995, Huntington Beach, CA 92647.

## DESCRAMBLERS

AMERICAN—CANADIAN  
New Satellite Descramblers

### C-1000 / ZENITH TYPE

Descrambles "over the air" and "cable" sync suppressed active video inversion signals.

Ready to go C-1000 ..... 379.95  
Complete Kit C-1000K ..... 274.95  
Printed Circuit & Manual ..... 24.95

### C-100 / JERROLD TYPE

Cable Descrambler for in-band gated suppressed systems

Ready to go C-100 ..... 119.95  
Complete Kit C-100K ..... 54.95

SEND \$2 FOR COMPLETE INFORMATIVE CATALOG TO DETERMINE WHAT TYPE YOU NEED.

**J & D ENGINEERING**  
P.O. Box 6099  
Falmouth, Maine 04105

Buy 1 kit  
Get 2nd kit  
at 1/2 price

Dealers Wanted  
Special Quantity Pricing  
COD's—OK

All J & D products are engineered, not copied, all are guaranteed 90 days & we stand behind our products where others fail to

**LATEST** bug-detection equipment for home or office. Literature, \$1.00. **CLIFTON**, Box 220-X, Miami, FL 33168.

**RESISTOR** assortment. 2200pcs. 1/4w5% C-film. 110 std. values, 20pcs. each individually packed. \$29.95 postpaid. Check/MO accepted. COD add \$2.00. **BENNETT CO.** 1271 Merchandise Mart, Chicago, IL 60654.

**TRANSISTORIZED** soft start, incandescent lamp adapter. No dimming, greatly increased life, reduced, "EMI". \$4.95, 60 watt control. Free description. **AL TEMPS ENTERPRISES**, 720 Smithtown Ave., Bohemia, NY 11716.

**NOTEBOOK** of subscription TV descrambler technique (sinewave system). TV Companies descramblers technique. 38 pages full of things. NE 564 substitute, video improvement, Mitsumi, Amnec tuner modification, waveforms, troubleshooting and more. \$21.50. **ADVANCE ELECTRONICS**, PO Box 3298, Culver City, CA 90231.

**CABLE-TV** manual: How to turn on cable TV. Converters and descramblers for all programmable and addressable systems. Send \$10.00 cash or money order to **MODERN TECHNOLOGICS**, PO Box 419-A1, Boston, MA 02186.

**CCTV** package: B/W camera, 16mm lens, 9" monitor, camera mount, 50 ft. coaxial cable—\$325.00. **A. LIPTON INC.** 29 West 47th St. New York, NY 10036 (212) 944-1373. Your CCTV headquarters!

**SCOTCHFLEX** breadboard IC sockets and tools. Free price list. **A. HARTMANN**, 9118 Hipkins Rd. SW, Tacoma, WA 98498.

**NEWEST cable-TV facts.** Manual includes: scrambling and descrambling theory, schematics of popular descramblers and converters, secret techniques and more. \$9.95 plus \$1.50 shipping. Free catalog. **ELECTRON**, Box 169, 17 N. State St., rm 1222, Chicago, IL 60602

**BRADFORD** parts 50% off—"JOE" TROY TV PARTS, 76 Second Ave., Troy, NY 12180

**PROFESSIONAL** quality solder, soldering irons, hardware, at discount prices. Free gift with purchase. Send stamp for prices to **TECHNICAL ELECTRONIC PRODUCTS**, PO Box 295, Purdy's NY 10578.

**MICROWAVE** generators. Manual tuned—3.7-4.2GHz, \$51.16; 2.1-2.2GHz, \$61.16. Voltage tuned (1" x 2" PCB)—2.1-2.5GHz, \$24.95; 18-21GHz, \$24.95. Send **SASE ROENSCHE MICROWAVE**, RR No.1 Brookfield, MO 64628.

**HIGH-gain** UHF antenna: outperforms most UHF antennas of its size: includes hardware, 50' cable, and balun; guaranteed. Send \$64.95 to **ERD**, 26 Meadow Street, Littleton, NH 03561 (603) 444-5559.



**A WHOLE NEW WORLD OF TV VIEWING WITH TUSA'S NEW MODEL CVU-40, 40 CHANNEL CABLE TV CONVERTER**  
Receive all the EXTRA CABLE TV "MIDBAND" & SUPERBAND CHANNELS on your UHF DIAL.  
Eliminates the need for renting or leasing. This system takes the "midband" and "superband" channels your TV, VCR or projector can't receive and converts them to standard UHF channels that any set can tune in.  
**A MUST FOR VIDEO-TAPING FROM CABLE TV!**  
The system allows you to program both pay per view TV decoder required and standard cable channels for taping on any VCR — while you are watching a different channel on your TV.  
Simple to install and operate on any make of TV with UHF.  
Now \$28.95 ea.  
PLUS POSTAGE

**NOW AVAILABLE**  
**NEW TUNEABLE DELUXE MODEL CVU-1000** \$34.95 ea.

**WINEGARD 7-ELEMENT**  
75 OHM UHF YAGI ANTENNAS

**OPTIONAL**  
12 db GAIN  
UHF Antenna  
Preamp  
18db Gain  
NF - 1.8db  
\$39.95 ea.  
6 OR MORE  
\$7.95 ea.  
Specify Channel  
\$8.95 ea.  
Now!  
MODEL 115-B-403A  
\$16.95 EACH  
All units are brand new from Sanyo  
Call for Quantity Price



### UHF TUNERS

45 MHz Output

Click Stop Detent Tone model. Excellent for replacement use or experimental work building UHF receivers for ham or TV.

**WHILE THEY LAST**  
\$3.95 ea.  
10 or more \$2.99 ea.

**POPULAR MICROWAVE PARTS**


MRF-901 ..... \$2.39  
9-Up ..... 1.95  
MRF-911 ..... 3.45  
9-Up ..... 3.12  
MBO-101 ..... .58  
CHIP CAPS - .001 mld ..... .50  
26-Up ..... .30  
2N6603 (formerly MRF-902) ..... 11.95

### POPULAR IC's

TOP QUALITY NO SECONDS

TYPE	DESCRIPTION	1-9	10-Up
LM-3800	2 watt Audio Power Amp	\$1.49	\$ .89
LM-3800N-3	Low Voltage Audio Amp	1.59	1.19
LM-3559N	Phase Locked Loop	1.49	.99
LM-733N	Video Amp	1.69	.98
MC-1330	Video Detector	2.29	1.69
MC-1349	Video If Amp	2.06	1.55
MC-1350	Video If Amp	1.75	1.19
MC-1352	Video If Amp AGC	2.69	2.09
MC-1358	Audio If Amp	1.75	1.64
MC-1374P	R.F. Modulator	3.19	2.39
MC-1456	Dual Comp. Op Amp	.89	.59
LM-146N	Balanced Mod/Demodulator	1.79	1.34
LM-1889	Video Modulator	2.79	1.95
LM-7805	5 Volt Positive Volt. Reg.	1.19	.89
LM-7808	8 Volt Positive Volt. Reg.	1.19	.89
LM-7812	12 Volt Positive Volt. Reg.	1.19	.89
LM-7815	15 Volt Positive Volt. Reg.	1.19	.89
LM-7818	18 Volt Positive Volt. Reg.	1.19	.89
LM-7824	24 Volt Positive Volt. Reg.	1.19	.89
LM-7805	LINEAR VOLTAGE REGULATORS		
LM-7805	5 Volt Positive Volt. Reg.	1.19	.89
LM-7808	8 Volt Positive Volt. Reg.	1.19	.89
LM-7812	12 Volt Positive Volt. Reg.	1.19	.89
LM-7815	15 Volt Positive Volt. Reg.	1.19	.89
LM-7818	18 Volt Positive Volt. Reg.	1.19	.89
LM-7824	24 Volt Positive Volt. Reg.	1.19	.89

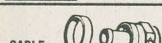THE ORIGINAL NE-564 IS NOW BACK IN STOCK!  
\$3.50 Each No minimum order



### CABLE CONNECTOR

F-69 Male connector for RG-59U cable. Complete with ferrule. Mates with female "F" connectors.  
100 for \$10.50  
20e ea.



### QUALITY POWER TRANSFORMERS

24V CT, 500 mA.  
\$3.19 ea. 10-49 \$2.75 ea.  
50 or more \$2.25 ea.  
For Larger Quantities Call




### NEW 1984 B&K AUTO/MANUAL RANGING MULTIMETER

MODEL 2807

**SPECIAL PRICE!**  
\$94.00 ea.

**BK PRECISION**

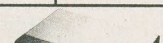

### WAHL SOLDERING IRONS

Your Choice \$42.50

MODEL 7470  
Temperature-Adjustable  
Micro Soldering Station

Compact. 500° to 700°  
Perfect for micro circuits  
and fine mfg. Grounded  
tip. Comes with 3/32"  
B type tip, tip wiping  
sponge & stand.  
3 wire grounded  
power supply cord.

**NEW VERSION OF THE JERROLD 400**  
GEN. INSTRUMENT LCC58  
58 CHAN. CATV CONVERTER

Receive all the standard VHF, Mid and Superband cable TV channels. Provides excellent reception on any channels that are not being scrambled by your local cable company. Converts all cable channels to channel 3 for viewing on your regular TV set. Hand held wireless remote control allows remote channel change and on/off control. Installs in minutes on any set. Note: To receive the cable frequencies you must subscribe to your local cable company.

\$119.95 \$104.95  
EACH 2 OR MORE  
15 for \$10.00... 100 for \$5.00  
For Larger Quantities Call

**SURPLUS SYLVANIA**  
VHF VARACTOR TUNERS

45 MHz output. Channels 2 through 13 as well as the mid-band channels. Schematic included.

**WHILE THEY LAST!**  
\$13.95 ea.



### PROJECT BOXES

Woodgrain


This box is 1 1/4" W. 4 1/4" H. 6 1/2" D with a removable aluminum U-shaped chassis 1 1/4" W. 3 1/4" H. 6 1/2" D inside.

4 or more \$12.50 ea.  
PREPUNCHED & SILICONE-PAINTED \$14.95 ea.  
For Larger Quantities Call

**DELUXE A-B SWITCHES**  
Specify Pushbutton or lever type

For CATV - MATV - VCR  
75 ohm - 90 db Isolation

\$5.95 ea.  
2 or more \$5.50 ea.

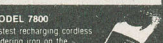

### Phone-A-Tenna

EXTENDS CORDLESS TELEPHONE RANGE UP TO 3 TIMES!

Here's the best quality, best working phone antenna on the market. Simple installation. Mounts outdoors. Does not void telephone warranty.

COMPLETE KIT includes antenna, 40' coaxial cable, adaptor and easy instructions.

Introductory Special \$37.95  
List Price \$62.25

### ORDER NOW TOLL FREE

800-854-4655

OUTSIDE CALIFORNIA

714-635-5090

INSIDE CALIFORNIA

### R.F. ELECTRONICS

1086-C N. STATE COLLEGE BLVD., DEPT. R

ANAHEIM, CALIFORNIA 92806

PERSONAL CHECKS HELD FOR CLEARANCE — NO MINIMUM ORDER

ALL PREPAID ORDERS 2 LBS OR LESS MUST INCLUDE \$2.50 SHIPPING & HANDLING — SHIPPED SAME DAY RECEIVED

OPEN TUES - FRI 10 - 6

SAT 10 - 5


CLOSED SUN & MON

SEND FOR FREE Mail Order Catalog



# RAMSEY

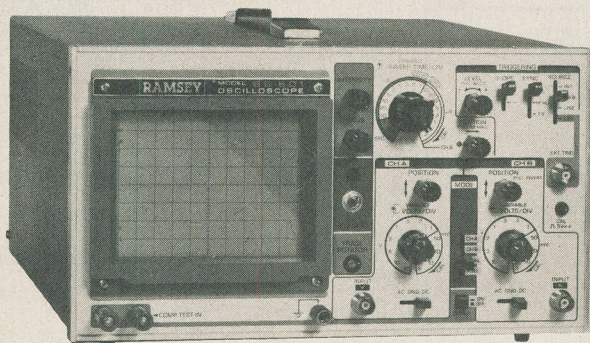
## THE FIRST NAME IN ELECTRONIC TEST GEAR


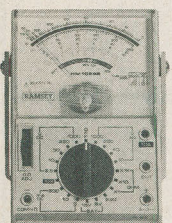
### NEW FROM RAMSEY-20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit that will allow you to easily test resistors, capacitors, digital circuits and diodes • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • high quality rectangular CRT • front panel trace rotator • Z axis • high sensitivity x-y mode • very low power consumption • regulated power supply • built-in calibrator • rock solid triggering • high quality hook-on probes

**\$399.95** high quality hook-on probes included




#### RAMSEY D-1100 VOM-MULTIESTER

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit.

**\$1.995**

test leads and battery included

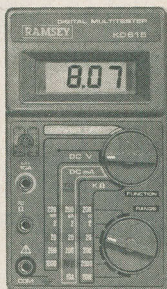


#### RAMSEY D-2100 DIGITAL MULTITESTER

A compact easy to use unit designed to operate like a pro. Featuring • 3 1/2 digit LCD • low BAT. indicator • all range overload protection • overrange indication • auto-polarity • Transistor tester • dual-slope integration • vinyl carrying case

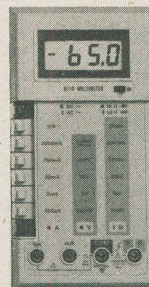**\$54.95**

hFE test leads, battery & vinyl carrying case included



#### RAMSEY D-3100 DIGITAL MULTITESTER

Reliable, accurate digital measurements at an amazingly low cost • In-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed input jacks • overload protection on all ranges • 3 1/2 digit LCD display with auto zero, auto polarity & low BAT. indicator

**\$59.95**

test leads and battery included



#### CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy

**\$119.95**

wired includes AC adapter

CT-70 kit ..... \$99.95  
BP-4 nicad pack ..... 8.95



#### CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy

**\$149.95**

wired includes AC adapter

CT-90 kit ..... \$129.95  
OV-1 0.1 PPM oven timebase ..... 59.95  
BP-4 nicad pack ..... 8.95




#### CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps

**\$169.95**

wired includes AC adapter

BP-4 nicad pack ..... 8.95

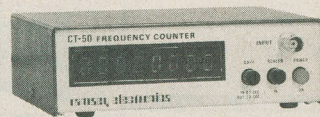

#### CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy

**\$169.95**

wired

CT-50 kit ..... \$139.95  
RA-1 receiver adapter kit ..... 14.95




#### DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity

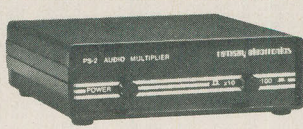**\$119.95**

wired includes AC adapter

DM-700 kit ..... \$99.95  
MP-1 probe set ..... 4.95




#### PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies UP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01Hz resolution & built-in signal preamp/conditioner

**\$49.95**

wired

PS-2 kit ..... \$39.95

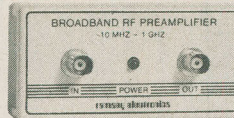

#### PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for sniffing RF • ideal receiver/TV preamp

**\$44.95**

wired includes AC adapter

PR-2 kit ..... \$34.95



#### PS-1B 600 MHz PRESCALER

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 circuitry • sensitivity: 25mV @ 150 MHz • BNC connectors • drives any counter

**\$59.95**

wired includes AC adapter

PS-1B kit ..... \$49.95

#### ACCESSORIES FOR RAMSEY COUNTERS

Telescopic whip antenna—BNC plug ..... \$ 8.95  
High impedance probe, light loading ..... 16.95  
Low pass probe, audio use ..... 16.95  
Direct probe, general purpose use ..... 13.95  
Tilt bail, for CT-70, 90, 125 ..... 3.95



PHONE ORDERS CALL  
**716-586-3950**

TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.

**RAMSEY**

**RAMSEY ELECTRONICS, INC.**  
2575 Baird Rd.  
Penfield, N.Y. 14626

CIRCLE 79 ON FREE INFORMATION CARD

JULY 1984

91







# CORPORATION

In Mn., AK., HI. Call 218-681-6674

**NATIONAL SEMICONDUCTOR • PANASONIC • ARIES • CHEMIV • ATLANTIC DIODES • ARIES • PLESSEY • MOLEX • AVID • E.F. J. • CHEMIV • ATLANTIC DIODES • ARIES • PLESSEY • MOLEX • AVID • E.F. J.**  
**QUALITY - Name brand products from nationally recognized manufacturers.**  
**SERVICE - Computerized order processing and inventory control.**  
**SAVINGS - Volume Discounts • OEM Quantity Pricing • Toll Free 800 Number Chemicals • ARIES • PLESSEY • MOLEX • E.F. J.**

## INTEGRATED CIRCUITS

7400 TTL 74LS00 TTL 7490 TTL 4000 CMOS 74LS00 TTL 74LS00 TTL

Part Price Part Price Part Price Part Price Part Price Part Price

7400 42 74LS00 41 7490 41 4000 42 74LS00 41 74LS00 41

7401 41 74LS01 40 7491 40 4001 41 74LS01 40 74LS01 40

7402 41 74LS02 40 7492 40 4002 41 74LS02 40 74LS02 40

7403 41 74LS03 40 7493 40 4003 41 74LS03 40 74LS03 40

7404 41 74LS04 40 7494 40 4004 41 74LS04 40 74LS04 40

7405 41 74LS05 40 7495 40 4005 41 74LS05 40 74LS05 40

7406 41 74LS06 40 7496 40 4006 41 74LS06 40 74LS06 40

7407 41 74LS07 40 7497 40 4007 41 74LS07 40 74LS07 40

7408 41 74LS08 40 7498 40 4008 41 74LS08 40 74LS08 40

7409 41 74LS09 40 7499 40 4009 41 74LS09 40 74LS09 40

7410 41 74LS10 40 74910 40 4010 41 74LS10 40 74LS10 40

7411 41 74LS11 40 74911 40 4011 41 74LS11 40 74LS11 40

7412 41 74LS12 40 74912 40 4012 41 74LS12 40 74LS12 40

7483 41 74LS83 40 74983 40 4083 41 74LS83 40 74LS83 40

## TEXAS INSTRUMENTS I.C. SOCKETS

Body - 8K V.O. polyester with Copper Alloy contacts. Accommodates standard I.C. leads up to 0.04" thick and 0.025" wide. Contact is designed and oriented in the insulator to allow maximum retention force. Socket is designed to allow maximum retention force. Socket is designed to allow maximum retention force.

**SOLDER TAIL DIP SOCKETS**

• Single lead • Low profile • YOUR CHOICE: TIN OR GOLD • Minimum: 100 sockets gold plated (see below)

TIN PLATED SOLDER TAIL 100 100 100 100 100 100

Part No. Description 1 10 100 1000

C9018 8 pin solder tail, tin 13 115 1000

C9019 16 pin solder tail, tin 13 115 1000

C9020 24 pin solder tail, tin 13 115 1000

C9021 32 pin solder tail, tin 13 115 1000

C9022 40 pin solder tail, tin 13 115 1000

C9023 48 pin solder tail, tin 13 115 1000

C9024 56 pin solder tail, tin 13 115 1000

C9025 64 pin solder tail, tin 13 115 1000

C9026 72 pin solder tail, tin 13 115 1000

C9027 80 pin solder tail, tin 13 115 1000

C9028 88 pin solder tail, tin 13 115 1000

C9029 96 pin solder tail, tin 13 115 1000

C9030 104 pin solder tail, tin 13 115 1000

C9031 112 pin solder tail, tin 13 115 1000

C9032 120 pin solder tail, tin 13 115 1000

C9033 128 pin solder tail, tin 13 115 1000

C9034 136 pin solder tail, tin 13 115 1000

C9035 144 pin solder tail, tin 13 115 1000

C9036 152 pin solder tail, tin 13 115 1000

C9037 160 pin solder tail, tin 13 115 1000

C9038 168 pin solder tail, tin 13 115 1000

C9039 176 pin solder tail, tin 13 115 1000

C9040 184 pin solder tail, tin 13 115 1000

C9041 192 pin solder tail, tin 13 115 1000

C9042 200 pin solder tail, tin 13 115 1000

C9043 208 pin solder tail, tin 13 115 1000

C9044 216 pin solder tail, tin 13 115 1000

C9045 224 pin solder tail, tin 13 115 1000

C9046 232 pin solder tail, tin 13 115 1000

C9047 240 pin solder tail, tin 13 115 1000

C9048 248 pin solder tail, tin 13 115 1000

C9049 256 pin solder tail, tin 13 115 1000

C9050 264 pin solder tail, tin 13 115 1000

C9051 272 pin solder tail, tin 13 115 1000

C9052 280 pin solder tail, tin 13 115 1000

C9053 288 pin solder tail, tin 13 115 1000

C9054 296 pin solder tail, tin 13 115 1000

C9055 304 pin solder tail, tin 13 115 1000

C9056 312 pin solder tail, tin 13 115 1000

C9057 320 pin solder tail, tin 13 115 1000

C9058 328 pin solder tail, tin 13 115 1000

C9059 336 pin solder tail, tin 13 115 1000

C9060 344 pin solder tail, tin 13 115 1000

C9061 352 pin solder tail, tin 13 115 1000

C9062 360 pin solder tail, tin 13 115 1000

C9063 368 pin solder tail, tin 13 115 1000

C9064 376 pin solder tail, tin 13 115 1000

C9065 384 pin solder tail, tin 13 115 1000

C9066 392 pin solder tail, tin 13 115 1000

C9067 400 pin solder tail, tin 13 115 1000

C9068 408 pin solder tail, tin 13 115 1000

C9069 416 pin solder tail, tin 13 115 1000

C9070 424 pin solder tail, tin 13 115 1000

C9071 432 pin solder tail, tin 13 115 1000

C9072 440 pin solder tail, tin 13 115 1000

C9073 448 pin solder tail, tin 13 115 1000

C9074 456 pin solder tail, tin 13 115 1000

C9075 464 pin solder tail, tin 13 115 1000

C9076 472 pin solder tail, tin 13 115 1000

C9077 480 pin solder tail, tin 13 115 1000

C9078 488 pin solder tail, tin 13 115 1000

C9079 496 pin solder tail, tin 13 115 1000

C9080 504 pin solder tail, tin 13 115 1000

C9081 512 pin solder tail, tin 13 115 1000

C9082 520 pin solder tail, tin 13 115 1000

C9083 528 pin solder tail, tin 13 115 1000

C9084 536 pin solder tail, tin 13 115 1000


C9085 544 pin solder tail, tin 13 115 1000

C9086


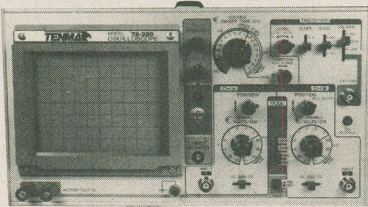
# TECHNICIANS!

We Have What You Need At  
The Prices You Want!




**TENMA**  
20MHz DUAL TRACE  
OSCILLOSCOPE

**\$389.95**

Backed By Our 2 Year Warranty  
High Quality Hook-On Probes Included

#72-320

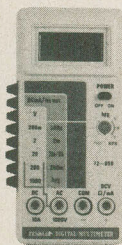

**TENMA**  
DIGITAL  
MULTIMETER  
HFE TEST  
0.5" LCD display  
DC input impedance  
10MΩ

**\$39.80**


#72-050

AGC FUSES  
STANDARD  
1 1/4x1 1/4

25A 4A  
5A 5A  
75A 6A  
1A 7A  
1.5A 8A  
2A 10A  
2.5A 15A  
3A 20A  
(100-up pcs.)  
(NO MIXED QTYS.)


**3.5¢**  
each

36 PIN PARALLEL  
CONNECTOR

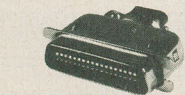

**\$3.95**  
#83-310

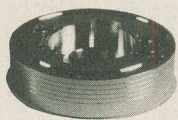PANASONIC 2-4 HOUR  
VIDEO HEAD REPLACES  
PANASONIC PART #VEH-0070



#32-160

**\$39.95**

## JAPANESE SEMICONDUCTORS

•D1341 1.92 •M51515BL 2.49  
•BUY69A 2.99 •STK0050 3.95  
•HA1377 2.49 •4116-200NS 1.38

(min. 10 pcs.)

We have the Largest  
Selection of Original  
Japanese Semiconductors  
in the Country!

**We Also Have...** a full line of: test equipment,  
computer accessories, telephone accessories, speakers,  
television parts, flybacks, yokes, switches, fuses, lamps,  
capacitors, resistors, cartridges, styli, wire, CATV equipment,  
and many more. **Over 4,500 items AT THE LOWEST PRICES  
AROUND!**

**Terms:** •\$10 minimum order. \$1.00 charge for orders under \$10.  
•\$20 minimum charge card order.  
•Orders shipped UPS C.O.D.  
•Most orders shipped within 24 hours.  
•Sales office open 8:30am to 6:00pm. Saturdays 10:00am to  
3pm, EST.



**CALL TOLL FREE  
1-800-543-4330**

(in Ohio, 1-800-762-4315)

**mcm**  
ELECTRONICS

THE ONLY  
ELECTRONICS  
PARTS COMPANY  
YOU'LL EVER  
NEED  
858 East Congress Park Drive  
Centerville, Ohio 45459  
513-434-0031

**CALL OR WRITE TODAY  
FOR YOUR FREE 120 PAGE  
CATALOG! OVER 4500 ITEMS!**

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



SOURCE NO. RE-1

CIRCLE 19 ON FREE INFORMATION CARD

REPLACEMENT FOR

## ECG®/TRIPLERS/MULTIPLIERS

(MIN. 50 PC. PER TYPE)

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
500A.....	7.65	530.....	10.65	537.....	11.73
521.....	10.98	531.....	10.45	538.....	9.84
522.....	9.50	532.....	12.40	539.....	9.84
523.....	7.75	533.....	9.90	549.....	14.55
526A.....	7.75	534.....	10.48	550.....	10.05
528.....	9.40	535.....	11.48	556.....	11.90
529.....	8.90	536A.....	13.85	557.....	11.75
				564.....	11.55

## REPLACEMENT FOR ECG® TYPES

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
85.....	FOUR for .99	125.....	SEVEN for .99
102A.....	THREE for .99	159AP.....	FOUR for .99
123A.....	FIVE for .99	177.....	EIGHT for .99
123AP.....	SIX for .99	199.....	FIVE for .99

## SUPER SPECIAL (MIN. 5 PC. EACH)

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
124.....	.85	165.....	2.25	375.....	.90
128.....	.45	171.....	.65	506.....	.55
129.....	.45	184.....	.45	500A.....	8.95
130.....	.80	185.....	.45	523.....	9.95
152.....	.40	238.....	2.25	526A.....	10.20
153.....	.40	276.....	6.95	529.....	13.75
154.....	.60	291.....	.95	712.....	1.25

## JAPANESE TYPES (MIN. 5 PC. EACH)

2SC867A.....	2.75	HA1366W.....	1.85	STK0029.....	3.80
2SC1114.....	3.25	HA1377A.....	2.90	STK0080.....	9.99
2SC1308K.....	1.95	LA4102.....	1.25	TA7205AP.....	1.50
AN214Q.....	1.45	M51515BL.....	2.95	TA7208P.....	1.85
AN239A.....	4.60	STK433.....	3.95	TA7222AP.....	1.95
BA532.....	1.80	STK435.....	3.95	UPC1181H.....	1.25
GH3F.....	.89	STK437.....	6.25	UPC1182H.....	1.25
HA1342A.....	2.30	STK439.....	6.50	UPC1185H.....	2.99

COD ORDERS WELCOME (\$25 MIN. ORDER)

For Complete Component Catalog Call or Write

**DIGITRON ELECTRONIC**

110 HILLSIDE AVENUE, SPRINGFIELD, N.J. 07081

TOLL FREE: 800-526-4928

In N.J.: 201-379-9016

\*ECG IS A TRADE MARK OF PHILIPS ECG.  
DIGITRON ELECTRONIC IS NOT ASSOCIATED IN ANY WAY WITH PHILIPS ECG.

CIRCLE 11 ON FREE INFORMATION CARD

## SURPLUS BARGAINS

Dataproducts D-50 Daisy Wheel Terminal:

SUPPLY LIMITED

- "35" Character per second print rate.
- RS-232 Input ("Receive-only" configured).
- 300-9600 Baud rate for fast print speed.
- Takes standard Diablo Daisywheels.
- Offers 10 pitch and 12 pitch.
- Full 13 1/2" carriage width.
- 6 & 8 lines per inch.

BUY NOW



These off-lease Daisy Wheel terminals are cleaned and adjusted and ready to use. Built in the U.S. by master printer manufacturer: DATAPRODUCTS. Ideal for use as a high speed Word Processor Printer. With data and info.

NOW ONLY **\$695.00** ea.

**CRT Terminals** Built by a major OEM, these terminals

include 3 microprocessor boards (Interface, CPU & CRT) plus composite video & switching power supply 48K or more. "Ergonomic" design and more. Experimenter special, includes Data, Keyboard, RS-232 I/O plus much more. Seems to be quite powerful.



Only!!

**\$289.00** ea.

**Parallel, TTL Input I/O "Selectric"**

**TYPEWRITER/PRINTER** These machines have built-in driver and decoder circuitry and take TTL level, 6-bit character, plus a 4-bit function input signals. Easily driven by most any micro. Use as a typewriter (with add'l "repeat" circuitry) or as a KSR I/O printer or both. "Table Top" style case.



Only!!

**\$299.00** ea.

TESTED AND OPERATIONAL!

**9" Composite Video Input CRT Monitor**

Requires approx. 12 VDC @ 1-2A VDC in attractive case. With schematics.




Only!!

**\$89.00** ea.

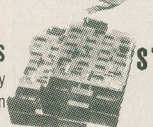**Shugart SA-400 "Mini-Floppy" Drives**

Model SA-400, used, whole, untested, less power supply & case. Data and schematics included. Removed from Equipment.



Only!!

**\$119.00** ea.

Prices do not include packaging and shipping.

Write or Call for Our Latest Flyer NOW!!!

"Selectric" is a registered trademark of IBM Corporation

**Computer  
Products &  
Peripherals  
Unlimited**

WAREHOUSE: 18 Granite St., Haverhill, Mass. 01830  
MAIL ORDERS: Box 204, Newton, New Hampshire 03858

**617/372-8637**

Sorry No Collect Calls  
MasterCard & VISA Accepted



CIRCLE 68 ON FREE INFORMATION CARD



# WE HAVE QUALITY PARTS, DISCOUNT PRICES AND FAST SHIPPING!

## TRANSFORMERS

**120 volt primaries**

5.6 VOLTS @ 750 MA	\$3.00
6 VOLTS @ 150 MA	\$1.25
12 VCT @ 200 MA	\$2.00
16.5 V @ 3 AMPS	\$6.50
18 V @ 650 MA	\$3.50
18 VOLTS @ 1 AMP	\$4.50
24 VOLTS @ 250 MA	\$2.50
24 VCT @ 1 AMP	\$4.50
42 VCT @ 1.2 AMP	\$4.50

## WALL TRANSFORMER

ALL ARE 115 VAC PLUG IN

4 VDC @ 70 MA	\$2.00
6 VDC @ 100 MA	\$2.50
6 VDC @ 500 MA	\$5.00
9 VDC @ 225 MA	\$3.00
14 VDC @ 300 MA	\$3.50
15 VAC @ 300 MA	\$3.00
16.5 VAC @ 10 VA	\$3.50
17 VAC @ 500 MA	\$4.00

## SPRING LEVER TERMINALS

TWO COLOR CODED TERMINALS ON A STURDY 2 3/4" x 3 3/4" BAKELITE PLATE. GREAT FOR SPEAKER ENCLOSURES OR POWER SUPPLIES.

**\$1.00 EACH 10 FOR \$9.00**

## 2 CHANNEL LIGHT ORGAN

EASILY HOOKS INTO STEREO SPEAKERS AND ALLOWS 110 VAC LIGHTS TO DANCE WITH MUSIC. TWO SEPARATE 110 VAC OUTPUTS FOR HIGH AND LOW FREQUENCY AUDIO SIGNALS. USE TWO ORGANS FOR STEREO.

**\$6.50 PER UNIT**

COLOR LIGHT STRING AVAILABLE \$1.75 EA

## HELPING HAND

WILL HOLD P.C. BOARD OR OTHER SMALL ITEMS AND ALLOW BOTH YOUR HANDS FREEDOM TO WORK.

**\$6.50 EACH**

## MIKE CONNECTOR

5 CONDUCTOR IN-LINE PLUG AND CHASSIS MOUNT JACK. TWIST LOCK STYLE. SAME AS SWITCHCRAFT 12CL5M.

**\$2.50 PER SET**

## METER

0 - 15 V.D.C. THIS 2-1/4" SQUARE METER MEASURES 0-15 VDC.

**\$4.50 EACH**

## SUB-MINIATURE D TYPE CONNECTOR

SOLDER TYPE SUB-MINIATURE CONNECTORS USED FOR COMPUTER HOOK UPS.

DB-15 PLUG	\$2.75
DB-15 SOCKET	\$4.00
DB-15 HOOD	\$1.50
DB-25 PLUG	\$2.75
DB-25 SOCKET	\$3.50
DB-25 HOOD	\$1.25

## "PARALLEL" PRINTER CONNECTOR

SOLDER STYLE 36 PIN MALE USED ON "PARALLEL" DATA CABLES.

**\$5.50 EACH**

## LIGHTS

### GRAIN OF WHEAT

**T1 SIZE** 125" DIA. (3.15mm)

3 to 6 VOLTS	3 for \$1.00
Rated: 55ma @ 5 VOLTS	
6 to 12 VOLTS	3 for \$1.00
Rated: 55ma @ 8 VOLTS	
12 to 24 VOLTS	3 for \$1.00
Rated: 45ma @ 14 VOLTS	

### T1 SIZE

**WITH WIRE LEADS**

3 to 6 VOLTS	2 for \$1.00
Rated: 55ma @ 5 VOLTS	
6 to 12 VOLTS	2 for \$1.00
Rated: 55ma @ 8 VOLTS	
12 to 24 VOLTS	2 for \$1.00
Rated: 45ma @ 14 VOLTS	

### T1 - 3/4 SIZE WITH WIRE LEADS

.163" DIA. (4.14mm)

3 to 6 VOLTS	2 for \$1.00
Rated: 45ma @ 6 VOLTS	
6 to 12 VOLTS	2 for \$1.00
Rated: 55ma @ 8 VOLTS	
12 to 24 VOLTS	2 for \$1.00
Rated: 45ma @ 14 VOLTS	

### NEON W/ RESISTOR

DIRECT OPERATION FROM 120 VOLT

**7 for \$1.00**


### 120V INDICATOR

NEON INDICATOR. RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE. RED LENS.

**75¢ EACH**

10 FOR \$7.00  
100 FOR \$65.00

## 8 TRACK RECORD/PLAY TAPE DECK

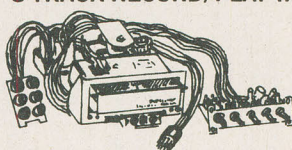

MORSE MODEL 94-A

8 TRACK RECORD WITH AUTO STOP. NOT FULLY FUNCTIONAL. REMOVED FROM ASSEMBLY LINE FOR MINOR PROBLEMS. IDEAL FOR PARTS. EACH UNIT CONTAINS SWITCHES, LIGHTS, TAPE MOTOR, BELT, WHEELS, PULLEYS, PRE AMPS, TAPE HEADS, ETC.

**\*SPECIAL PRICE\* \$4.00 EACH 10 for \$35.00**

## 2K 10 TURN

MULTI-TURN POT

SPECTROL #MOD 534-7161

**\$5.00 EACH**

## EDGE CONNECTORS

ALL ARE .156" SPACING

**18/36 GOLD SOLDER EYELET \$2.00 EACH**

**22/44 TIN P.C. STYLE, NO MOUNTING EARS. \$1.50 EACH 10 FOR \$14.00**

**22/44 GOLD P.C. STYLE \$2.00 EACH 10 FOR \$18.00**

**28/56 GOLD 28/56 GOLD PLATED CONTACTS .156 CONTACT SPACING. \$2.50 EACH 10 FOR \$22.00**

**50/100 GOLD STANDARD S-100 CONNECTOR. .125" SPACING. GOLD PLATED P.C. MOUNT. \$3.75 EACH 10 FOR \$35.00**

## SWITCHES

### MINI-PUSH BUTTON

S.P.S.T. MOMENTARY NORMALLY OPEN 1/4" BUSHING

**35¢ EACH**

10 FOR \$3.25  
100 FOR \$30.00

SPECIFY COLOR: RED, BLACK, WHITE, GREEN, YELLOW.

### KEY SWITCH

S.P.S.T. 4 AMPS @ 125 VAC KEY REMOVES BOTH POSITIONS

**\$3.50 EA**

### LIGHTED PUSH BUTTON

RED LIGHTED 120 VAC 10 AMP. S.P.S.T.

"POWER" PRINTED ON FACE. MOUNTS IN 7/8" SQUARE HOLE.

**\$1.50 EA 10 FOR \$13.50**

**FREE! FREE! FREE! SEND FOR NEW LARGER! 48 PAGE CATALOG FREE! FREE! FREE!**

## LINE CORDS

**TWO WIRE** 6' 18ga TWO WIRE **3 FOR \$1.00**

**THREE WIRE** 18 INCH 18ga THREE WIRE **2 for \$1.00**

8 FOOT 18ga THREE WIRE **\$2.00 EACH**

## SOLDERING IRON STAND

SPRING STEEL IRON HOLDER ON WEIGHTED BASE.

**\$5.00 EACH**

## TRANSISTORS

2N706	5 for \$1.00
2N2222A	4 for \$1.00
PN2222	8 for \$1.00
2N2904	4 for \$1.00
2N2905	4 for \$1.00
2N2907	4 for \$1.00

## POWER SUPPLY W/ PRE-AMP

THIS SUPPLY WAS USED TO POWER AN 8 TRACK/CASSETTE UNIT. IT WILL SUPPLY APPROX. 18 VDC AND INCLUDES A SMALL PRE-AMP TO BOOST SIGNAL LEVEL. RCA PLUGS FOR LINE IN/OUT.

**\$4.50 EACH**

## KEY ASSEMBLY

**5 KEY** **\$1.00 EACH**

CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 3 3/4" LONG

**6 KEY** **\$1.25 EACH**

CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 4 1/4" LONG.

## BATTERY OPERATED SMOKE DETECTOR

BRK MODEL #79R UL APPROVED 9 VOLT BATTERY OPERATION FOR CEILING OR WALL MOUNT.

**\$8.00 EACH 2 FOR \$15.00**

## ROTARY SWITCH

**1 POLE 6 POSITION** 1 1/4" DIA x 1 1/2" HIGH

**75¢ EACH 10 for \$6.00**

## RELAYS

**MINIATURE 6 VDC RELAY**

SUPER SMALL SPDT RELAY. GOLD COBALT CONTACTS.

RATED 1 AMP AT 30 VDC. HIGHLY SENSITIVE. TTL DIRECT DRIVE POSSIBLE. OPERATES FROM 4.3 TO 6 V. COIL RES. 220 OHM.

1 3/16" x 13/32" x 7/16" AROMAT # RSD-6V

**\$1.50 EACH 10 FOR \$13.50**

## 13 VDC RELAY

CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO OPEN CONTACT...

COIL: 13 VDC 650 OHMS

**SPECIAL PRICE \$1.00 EACH**

## 4 PDT RELAY

14 pin style  
3 amp contacts  
24 volt d.c. or 120 volt a.c. coil  
Used but fully tested

**\$1.70 EACH**

specify coil voltage

LARGE QUANTITIES AVAILABLE

SOCKETS FOR RELAY 50¢ each

## COMPUTER GRADE CAPACITORS

2,000 mfd. 200 VDC	\$2.00
13/4" DIA. x 5" HIGH	
3,600 mfd. 40 VDC	\$1.00
13/8" DIA. x 3 3/4" HIGH	
6,400 mfd. 60 VDC	\$2.50
13/8" DIA. x 4 1/4" HIGH	
21,000 mfd. 50 VDC	\$4.00
2 1/2" DIA. x 5" HIGH	
22,000 mfd. 40 VDC	\$3.00
2" DIA. x 6" HIGH	
31,000 mfd. 15 VDC	\$2.50
13/4" DIA. x 4" HIGH	
44,000 mfd. 35 VDC	\$4.00
2" DIA. x 5" HIGH	
72,000 mfd. 15 VDC	\$3.50
2" DIA. x 4 3/8" HIGH	
185,000 mfd. 6 VDC	\$1.50
2 1/2" DIA. x 4 1/2" HIGH	

CLAMPS TO FIT CAPACITORS 50¢ ea.

## SLIDE POTS

**100K linear tape** 2" LONG

1 5/8" TRAVEL **75¢ EACH**

**500K linear taper** 2 7/8" LONG

1 3/4" TRAVEL **75¢ EACH**

**DUAL 100K audio taper** 3 1/2" LONG

2 1/2" TRAVEL. **\$1.50 EACH**

## CRYSTALS

CASE STYLE HC33/U

2 MHZ **\$3.50 EACH**

COLORBURST 3579.545 KC **\$1.00 EACH**

## METAL OXIDE VARISTOR

G.E. # V82A12 50 VOLTS, NOMINAL D.C. VOLTAGE. 5/8" DIAMETER.

**2 FOR \$1.50**

## L.E.D.'S STANDARD JUMBO DIFFUSED

RED 10 FOR \$1.50  
GREEN 10 FOR \$2.00  
YELLOW 10 FOR \$2.00

## FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE \$1.00 EACH

## BI POLAR LED 2 FOR \$1.70

## SUB MINI LED

079" x .098"

RED 10 FOR \$1.00  
200 FOR \$18.00

GREEN 10 FOR \$1.50

## LED HOLDERS

TWO PIECE HOLDER FOR JUMBO LED

10 FOR 65¢ 200 FOR \$10.00

## PHOTO-FLASH CAPACITORS

**35 MFD 330 VOLT**

1" x 5/8" DIA. **45¢ EACH...**

10 FOR \$4.00

**170 MFD 330 VOLT**

1 1/8" x 7/8" **2 FOR \$1.50 10 FOR \$7.00**

**750 MFD 330 VOLT**

2" HIGH x 1 1/4" DIA. **\$1.25 EACH 10 FOR \$11.00**

TOLL FREE ORDERS ONLY  
1-800-826-5432  
(ORDER ONLY)  
(IN CALIFORNIA: 1-800-258-6666)  
ALASKA, HAWAII, OR INFORMATION  
(213) 380-8000

**ALL ELECTRONICS CORP.**

905 S. Vermont Ave. P.O. BOX 20406 Los Angeles, Calif. 90006

CIRCLE 12 ON FREE INFORMATION CARD

QUANTITIES LIMITED  
MINIMUM ORDER \$10.00  
USA: \$2.50 SHIPPING  
FOREIGN ORDERS:  
INCLUDE SUFFICIENT  
SHIPPING  
CALIF. RES. ADD 6 1/2%  
NO C.O.D.!



JULY 1984



# 7400

Part No.	**Pins	Price	Part No.	**Pins	Price	Part No.	**Pins	Price
SN7400N	14	25	SN7472N	14	29	SN74156N	16	59
SN7401N	14	25	SN7473N	14	35	SN74157N	16	59
SN7402N	14	25	SN7474N	14	35	SN74160N	16	69
SN7403N	14	25	SN7475N	16	35	SN74161N	16	69
SN7404N	14	25	SN7476N	16	35	SN74162N	16	69
SN7405N	14	25	SN7477N	14	49	SN74163N	16	69
SN7406N	14	25	SN7478N	14	49	SN74164N	16	69
SN7407N	14	25	SN7479N	14	49	SN74165N	16	69
SN7408N	14	25	SN7480N	14	49	SN74166N	16	69
SN7409N	14	25	SN7481N	14	49	SN74167N	16	69
SN7410N	14	25	SN7482N	14	49	SN74168N	16	69
SN7411N	14	25	SN7483N	14	49	SN74169N	16	69
SN7412N	14	49	SN7484N	14	49	SN74170N	16	29
SN7413N	14	49	SN7485N	16	29	SN74171N	16	29
SN7414N	14	49	SN7486N	14	29	SN74172N	16	29
SN7415N	14	49	SN7487N	14	29	SN74173N	16	29
SN7416N	14	49	SN7488N	14	29	SN74174N	16	29
SN7417N	14	49	SN7489N	14	29	SN74175N	16	29
SN7418N	14	49	SN7490N	14	29	SN74176N	16	29
SN7419N	14	49	SN7491N	14	29	SN74177N	16	29
SN7420N	14	49	SN7492N	14	29	SN74178N	16	29
SN7421N	14	49	SN7493N	14	29	SN74179N	16	29
SN7422N	14	49	SN7494N	14	29	SN74180N	16	29
SN7423N	14	49	SN7495N	14	29	SN74181N	16	29
SN7424N	14	49	SN7496N	14	29	SN74182N	16	29
SN7425N	14	49	SN7497N	14	29	SN74183N	16	29
SN7426N	14	49	SN7498N	14	29	SN74184N	16	29
SN7427N	14	49	SN7499N	14	29	SN74185N	16	29
SN7428N	14	49	SN7500N	14	29	SN74186N	16	29
SN7429N	14	49				SN74187N	16	29
SN7430N	14	49				SN74188N	16	29
SN7431N	14	49				SN74189N	16	29
SN7500N	14	49				SN74258N	16	29

# MICROPROCESSOR COMPONENTS

IC80102	40	CPU	102	18	1024K1 (300ns)	99
2650	40	MPU (2MHz)	4116N-2	16	16.384K1 (150ns)	2.49
MC68050	40	MPU w/ Clock	4116N-3	16	16.384K1 (200ns)	1.89/8/12/95
MC68050B	40	MPU w/ Clock @ 3MHz	4116N-4	16	16.384K1 (250ns)	1.49/8/12/95
6809	40	CPU—8-bit (Internal Clock) 1MHz	4164N-150	16	65.536K1 (150ns)	6.95/8/48/95
6809E	40	CPU—8-bit (External Clock) 1MHz	4164N-200	16	65.536K1 (200ns)	5.95/8/48/95
INS8030N	40	MPU—8-bit (6MHz)	MSM5261	24	2048K1 (300ns)	49/8/1.95
INS8036N	40	CPU-Sp. chip 8-bit (280ns) RAM	MSM5262	22	1024K1 (95ns)	99
INS8040N-6	40	CPU (64 bytes RAM)	MSM5270	18	4096K1 (250ns) MK4096	4.95
INS8070N	40	CPU (64 bytes RAM)	MSM5290-2	16	4096K1 (250ns) 2107	3.95
INS8073N	40	CPU w/ Basic Micro Interpreter	MSM5290-3	16	16.384K1 (150ns)	1.89/8/12/95
RO80A	40	CPU	MSM5290-4	16	16.384K1 (200ns)	1.49/8/12/95
8088	40	CPU 16-bit 5MHz	MSM5290-5	16	16.384K1 (250ns)	1.89
8088	40	CPU 8-bit 16-bit	2110	16	256K1 (650ns)	1.49
8155	40	HMS RAM I/O Port-Timer	2102	16	1024K1 (450ns) 8101	2.49
8748	40	HMS EPROM MPU	2112	16	1024K1 (450ns) L.P.	1.49

STATIC RAMS

# Z80, Z80A, Z80B, Z8000 SERIES


Z80-P10	40	Parallel I/O Interface Controller	3.95	2114	16	1024K4 (450ns)	1.49	8/9/95
Z80-SIO/0	40	Serial I/O (TxCB and RxCB Bonded)	12.95	2114L	16	1024K4 (450ns) L.P.	1.95	8/9/95
Z80-SIO/1	40	Serial I/O (Latched Data)	12.95	2114L	16	1024K4 (450ns) L.P.	1.95	8/9/95
Z80-SIO/2	40	Serial I/O (Latched Data)	12.95	2114L-2	16	1024K4 (450ns) L.P.	2.25	8/9/95
Z80A	40	CPU (MC3808N-4) 780C1 4MHz	4.49	2114	16	1024K8 (70ns)	2.95	8/9/95
Z80A-CTC	28	Counter Timer Circuit	4.95	IMS4045	16	1024K4 (450ns)	2.95	8/9/95
Z80A-DART	40	Dual Asynchronous Rec./Trans.	9.95	IMS4046/47-45	20	1024K4 (450ns)	2.95	8/9/95
Z80A-DMA	40	Direct Memory Access Circuit	12.95	2101	16	1024K4 (450ns)	2.95	8/9/95
Z80A-P10	40	Parallel I/O Interface Controller	3.95	IMS5257	16	1024K1 (450ns) 4044	2.95	8/9/95
Z80A-SIO/0	40	Serial I/O (TxCB and RxCB Bonded)	12.95	IMS5258	16	1024K1 16P-2 4044	2.95	8/9/95
Z80A-SIO/1	40	Serial I/O (Latched Data)	12.95	IMS6116P-1	24	2048K8 (200ns) CMOS	3.95	8/9/95
Z80A-SIO/2	40	Serial I/O (Latched Data)	12.95	IMS6116P-4	24	2048K8 (200ns) CMOS	3.95	8/9/95
Z80A-SIO/3	40	Serial I/O (Latched Data)	12.95	IMS6264P-15	24	8048K8 (200ns) CMOS	3.95	8/9/95
Z80B	40	CPU (MC3808N-6) 6MHz	5.95	27L500	16	256K1 (450ns)	2.95	8/9/95
Z80B-CTC	28	Counter Timer Circuit	12.95	4848	16	16K4 (450ns) 3101	2.25	8/9/95
Z80B-DART	40	Dual Asynch. Rec./Trans/Controller	19.95	25A20	16	256K4 (450ns) CMOS	2.95	8/9/95
Z80B-P10	40	Parallel I/O Interface Controller	4.95	AC0281	16	256K4 (450ns) CMOS	2.95	8/9/95
Z80C1	40	CPU Segmented	34.95	AC0289	16	1024K1 (250ns) CMOS (6501)	1.95	8/9/95
Z80C2	40	CPU Non-Segmented	34.95	AC0330	16	256K4 (450ns) CMOS (6501)	1.95	8/9/95
Z80C3	40	Serial Comm. Controller	45.95	45S189	16	16K4 (35ns) 934045	2.95	8/9/95
Z80C4	40	Serial Time & Date I/O Interface	45.95					



## HOME COMPUTER ACCESSORIES

## RS232 ADAPTER FOR VIC-20 AND COMMODORE 64

New!

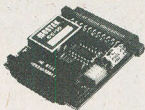

New!

The JE232CM allows connection of standard RS232C printers, modems, etc. to your VIC-20 and C-64. A 4-pole switch allows the inversion of the 4 control lines. Complete installation and operation instructions included.

• Plugs into User Port • Provides Standard RS232C signal levels • Uses 6 signals (Transmit, Receive, Clear to Send, Request to Send, Data Terminal Ready, Data Set Ready).  
**JE232CM . . . . . \$39.95**

## VOICE SYNTHESIZER FOR APPLE AND COMMODORE

NEW!



JE520CM


JE520AP

• Over 250 word vocabulary affixes allow the formation of more than 500 words • Built-in amplifier, speaker, volume control, and audio jack • Recreates a clear, natural male voice • Plug-in user ready with documentation and sample software • Case size: 7 1/4" L x 3 3/4" W x 1-3/8" H

APPLICATIONS: • Security Warning • Telecommunication • Teaching • Handicap Aid • Instrumentation • Games

The JE520.VOICE SYNTHESIZER will plug right into your computer and allow you to enhance almost any application. Utilizing National Semiconductor's DIGITALIZER™ Speech Processor IC (with four custom memory chips), the JE520 compresses natural speech into digital memory, including the original inflections and emphases. The result is an extremely clear, natural vocalization.

Part No.	Description	Price
JE520CM	For Commodore 64 & VIC-20	\$114.95
JE520AP	For Apple II, II+, and IIe	\$149.95

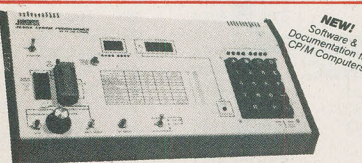

NEW! Software &amp; Documentation for CPM Computers

## JE664 EPROM PROGRAMMER 8K to 64K EPROMS — 24 &amp; 28 Pin Packages

Completely Self-Contained — Requires No Additional Sockets for Operation

- Programs and validates EPROMs • Checks for properly erased EPROMs
- Emulates PROMs or EPROMs • RS232C Computer Interface for editing and program loading • Loads data into RAM by keyboard • Changes data in RAM by keyboard • Loads RAM from the JE664 • Compares EPROMs for content differences • Copies EPROMs • Power Input: 115VAC, 60Hz, less than 10W power consumption • Enclosure: Color-coordinated, light tan panels with molded end panels in mocha brown • Size: 15 1/2" L x 8 3/4" W x 3 1/4" H • Weight: 5 1/2 lbs.

The JE664 EPROM Programmer emulates and programs various 8-Bit Word EPROMs from 8K to 64K-Bit memory capacity. Data can be entered into the JE664's internal 8K x 8-Bit RAM in three ways: (1) from a ROM or EPROM; (2) from an external computer via the optional JE664 RS232C BUS; (3) from its panel keyboard. The JE664's RAM may be accessed for emulation purposes from the panel's test socket to an external microprocessor. In programming and emulation, the JE664 allows for examination, change and validation of program content. The JE664's RAMs can be programmed quickly to all "1"s (or any value), allowing unused addresses in the EPROM to be programmed later without necessity of "0V" erasing. The JE664 displays DATA and ADDRESS in convenient hexadecimal (alphanumeric) format. A "DISPLAY EPROM DATA" button changes the DATA readout from RAM word to EPROM word and is displayed in both hexadecimal and binary code. The front panel features a convenient operating guide. The JE664 Programmer includes one JM16A Jumper Module (as listed below).

**JE664-A EPROM Programmer . . . . . \$995.00**  
Assembled & Tested (Includes JM16A Module)

**JE665 — RS232C INTERFACE OPTION** — The RS232C Interface Option implements computer access to the JE664's RAM. This allows the computer to manipulate, store and transfer EPROM data to and from the JE664. A sample program listing is supplied in M6800C for CPM computers. Documentation is provided to adapt the software to other computers with an RS232C port, 9600 Baud, 8-bit word, odd parity and 2 stop bits.

FOR A LARGE TIME A SAMPLE OF SOFTWARE WRITTEN IN BASIC FOR THE TRS-80™ MODEL I, LEVEL II COMPUTER WILL ALSO BE PROVIDED.

**JE664-ARS EPROM Prog. w/JE665 Option. . . . . \$1195.00**  
Assembled & Tested (Includes JM16A Module)

EPROM JUMPER MODULES — The JE664 JUMPER MODULE (Personality Module) is a plug-in Module that pre-sets the JE664 for the proper programming pulses to the EPROM and configures the EPROM socket connections for that particular EPROM.


JUMP EPROM	Manufacturer	Part No.	Price
JM16A	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16B	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16C	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16D	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16E	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16F	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16G	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16H	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16I	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16J	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16K	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16L	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16M	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16N	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16O	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16P	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16Q	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16R	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16S	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16T	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16U	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16V	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16W	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16X	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16Y	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95
JM16Z	25V	AMD, Motorola, Nat. Intel, TI, AMD, Hitachi, Matsushita	\$14.95

## KEYBOARDS



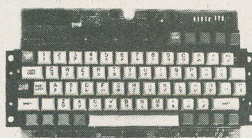
## HI-TEK 14-KEY NUMERIC KEYPAD

• Great keypad for many home and business computer applications • SPST switching • Mounted on PC board • Size 5" L x 3" W x 1 1/2" H • Color: Grey • Weight: 1 lb. • Spec available  
**K-14 . . . . . \$9.95**


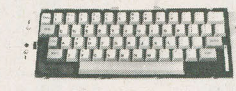
## MICRO SWITCH KB-MISC Encoded Keyboards

• Large selection of keyboards • Hall effect switching • Some have parallel interfaces • Some have serial interfaces • All have status LEDs and a minimum of 68 keys • Some with numeric keypad capabilities, cursor controls, or both • Styles may vary • Weight: 2 lbs. • No specs available  
**KB-MISC . . . . . \$9.95**




**Mitsumi 54-Key Unencoded Matrix All-Purpose Keyboard**  
• SPST keyswitches • 20 pin ribbon cable connection • Low profile keys • Features: cursor controls, control, caps (lock), function, enter and shift keys • Color (keycaps): grey • Wt.: 1 lb. • Pinout included  
**KB54 . . . . . \$14.95**



**76-Key Serial ASCII Keyboard**  
• Simple serial interface • SPST mechanical switching • Operates in upper and lower case • Five user function keys: F1-F5 • Six finger edge card connection • Color (keys): tan • Weight: 2 lbs. • Data incl.  
**KB76 . . . . . \$29.95**



**106-KEY 8-BIT SERIAL ASCII KEYBOARD**  
• The terminals were designed to be daisy chained around a central host computer and used as individual work stations • Hall effect switching • numeric and cursor keypad • 10 user definable keys • 50" interface cable with 9-pin sub-miniature connector • 7 LED function display • Security lock • N-key rollover • Automatic key repeat function • Color: (case): white w/black panel • (key caps): grey and blue • Weight: 6 1/2 lbs. • Data included.  
**KB139 . . . . . \$59.95**

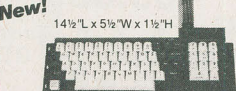

**68-Key Keyboard with Numeric Keypad for Apple II and II+**  
• Plugs directly into Apple II or II+ motherboard with 16-pin ribbon cable connector • 26 special functions • Color (keys): white/grey • Weight: 2 lbs.  
**KB-A68 . . . . . \$99.95**

## POWER SUPPLIES



## TRANSACTION TECHNOLOGY, INC.

**5VDC @ 1 AMP Regulated Power Supply**  
• Output: +5VDC @ 1.0 amp (also +30VDC regulated) • Input: 115VAC, 60 Hz • Two-tone (black/beige) self-enclosed case • 6 foot, 3-conductor black power cord • Size: 6 1/2" L x 7" W x 2 1/4" H • Weight: 3 lbs.  
**PS51194 . . . . . \$14.95**



**Power/Mate Corp. REGULATED POWER SUPPLY**  
• Input: 105-125/210-250 VAC at 47-63 Hz • Line regulation: ±0.05% • Three mounting surfaces • Overvoltage protection • UL recognized • CSA certified  
**Part No. Output Protection Size Weight Price**  
**EMA5/6B 5V@3A/6V@2.5A 4 1/2" L x 4" W x 2 1/4" H 2 lbs. \$29.95**  
**EMA5/6C 5V@6A/6V@5A 5 1/2" L x 4" W x 2 1/4" H 4 lbs. \$39.95**




**ASTEC SWITCHING REGULATED POWER SUPPLY**  
• Apple III Power Supply • Multiple outputs for bench top uses and other applications • Input: 115VAC, 50-60 Hz @ 3.0 amps • Output: +5VDC @ 1.0 amp, +12VDC @ 1.0 amp, -12VDC @ 1.0 amp, +24VDC @ 2.5 amp, -24VDC @ 2.5 amp • Size: 15 1/2" L x 3 3/4" W x 3 1/4" H • Weight: 2 1/2 lbs.  
**AS1155 . . . . . \$39.95**



**POWER SUPPLY +5VDC @ 7.6 AMP 12VDC @ 1.5 AMP SWITCHING**  
• Input: 115VAC, 50-60 Hz @ 3.0 amp/230VAC • Output: +5VDC @ 7.6 amp, +12VDC @ 1.5 amp, -12VDC @ 1.5 amp • Line regulation: ±0.2% • Ripple: 30mV p-p • Load regulation: ±1% • Overcurrent protection • Adj: 5V main output • +10% • Size: 6 1/2" L x 1 1/2" W x 4-15/16" H • Weight: 1 1/2 lbs.  
**PS94VOS . . . . . \$39.95**



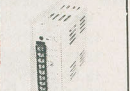**KEPCO/TKD 4-OUTPUT SWITCHING POWER SUPPLY**  
• Ideal for disk drive needs of CRT terminals, microcomputers and video games • Input: 115/230VAC, 50/60Hz • Output: +5V @ 5 Amp, +12V @ 1.5 Amp, -12V @ 2 Amp, -12V @ 0.5 Amp • UL recognized • CSA certified • Size: 7 1/4" L x 6-3/16" W x 1 1/4" H • Weight: 2 lbs.  
**MRM 174KF . . . . . \$59.95**



**4-CHANNEL SWITCHING POWER SUPPLY**  
• Microprocessor, mini-computer, terminal, medical equipment and process control applications • Input: 90-130VAC, 47-440Hz • Output: +5VDC @ 5A, +5VDC @ 1A, +12VDC @ 1A, -12VDC @ 1A • Line regulation: ±0.2% • Ripple: 30mV p-p • Load regulation: ±1% • Overcurrent protection • Adj: 5V main output • +10% • Size: 6 1/2" L x 1 1/2" W x 4-15/16" H • Weight: 1 1/2 lbs.  
**FCS-604A . . . . . \$69.95 each**



**Switching Power Supply for APPLE II, II+ & IIe™**  
• Can drive four floppy disk drives and up to eight expansion cards • Short circuit and overload protection • Fits inside Apple computer • Fully regulated +5V @ 5A, +12V @ 1.5A, -5V @ 5A, -12V @ 5A • Direct plug-in power cord included • Size: 9 1/2" L x 3 1/2" W x 2 1/4" H • Weight: 2 lbs.  
**KHP4007 . . . . . \$79.95**

\$10.00 Minimum Order — U.S. Funds Only  
California Residents Add 6 1/2% Sales Tax  
Shipping — Add 5% plus \$1.50 Insurance  
Send S.A.S.E. for Monthly Sales Flyer!


Spec Sheets — 30¢ each  
Send \$1.00 Postage for your  
FREE 1984 JAMECO CATALOG  
Prices Subject to Change



Mail Order Electronics • Worldwide  
**Jameco ELECTRONICS**  
1355 SHOREWAY ROAD, BELMONT, CA 94002  
7/84 PHONE ORDERS WELCOME — (415) 592-8097 Telex: 176043



## 4-Digit Fluorescent Alarm Clock Kit

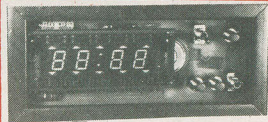

NEW!

• AM/PM indicator • Automatic display dimmer • Bright 4-digit 0.5" high display • 10 minute snooze alarm

The JE750 Clock Kit is a versatile 12-hour digital clock with 24-hour alarm. The clock has a bright 0.5" high blue-green fluorescent display. The display will automatically dim with changing light conditions. The 24-hour alarm allows the user to disable the alarm and immediately re-enable the alarm to activate 24 hours later. The kit includes all documentation, components, case and wall transformer. Size: 6 1/2" L x 3 1/4" W x 1 3/4" D.

**JE750 Alarm Clock Kit. . . . . \$29.95**


## DISK DRIVES AND SUPPLIES



## 5 1/4" APPLE™ Direct Plug-In Compatible Disk Drive

• Uses Shugart SA390 mechanics • 148K formatted storage • 25 tracks — compatible with Apple controller • Complete with connector and cable — just plug into your disk controller card • Size: 6 1/2" L x 3 3/4" W x 8-9/16" D • Weight: 4 1/4 lbs.

**ADD-514...\$195.95**

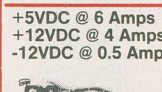


**Microcomputer Power Inc. Regulated Power Supply**  
• Perfect for computer or disk drive systems • Supply has AMP connectors for direct connection to two 5 1/4" disk drives • Cooling fan • Input: 100/115/200/230VAC, 47-63Hz • Output (above) • Weight: 9 lbs.




**+5VDC @ 6 Amps +12VDC @ 4 Amps -12VDC @ 0.5 Amps**  
**CP167 . . . . . \$59.95**



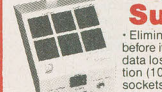**INDUSTRIES Protect Yourself... DATASHIELD® Surge Protector**  
• Eliminates voltage spikes and EMI-RFI noise before it can damage your equipment or cause data loss • 6 month warranty • Power dissipation (100 microsecond) • 1,000,000 watts • 6 sockets • 6 foot power cord • Normal line voltage indicator light • Brown out/black out reset switch • Weight: 2 lbs.



**DATASHIELD® Back-Up Power Source**  
Provides up to 30 minutes of continuous 120 VAC 60Hz power to your computer system (load dependent) when you have a black out or voltage sag • Output rating: 200 watts • Six month warranty • Weight: 24 lbs.

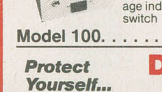

**Model 100 . . . . . \$69.95**



**Model 200 (PC200) . . . . . \$349.95**



**IBM MEMORY EXPANSION KIT COMPAQ COMPATIBILITY**

## SAVE HUNDREDS OF \$\$\$ BY UPGRADING MEMORY BOARDS YOURSELF!

Most of the popular memory boards allow you to add an additional 64K, 128K, 192K, or 256K. The IBM64K Kit will populate these boards in 64K byte increments. The kit is simple to install — just insert the nine 64K RAM chips in the provided sockets and set the two groups of switches. Directions are included.

**IBM64K (Nine 200ns 64K RAMs) . . . . . \$49.95**

## TRS-80 MEMORY EXPANSION KIT

**TRS-80 to 16K, 32K, or 48K**  
\*\*Model 1 = From 4K to 16K Requires (1) One Kit  
\*\*Model 3 = From 4K to 48K Requires (3) Three Kits  
Color = From 4K to 16K Requires (1) One Kit  
\*\*Model 1 equipped with Expansion Board up to 4K Two Kits Required — One Kit Required for each 16K of Expansion —

**TRS-16K3 \*200ns for Color & Model III . . . . . \$12.95**  
**TRS-16K4 \*250ns for Model I . . . . . \$10.95**

## TRS-80 Color 32K or 64K Conversion Kit

Easy to install kits comes complete with 8 ea. 4164-2 (200ns) 64K dynamic RAMs and conversion documentation. Converts TRS-80 color computers with D, E, F, T and NC circuit boards to 32K. Also converts TRS-80 color computer II to 64K. Flex DOS or OS-9 required to utilize full 64K RAM on all computers.

**TRS-64K2 . . . . . \$44.95**

## UV-EPROM Eraser



**8 Chips — 51 Minutes**  
**1 Chip — 37 Minutes**  
Erases 2708, 2716, 2732, 2764, 2516, 2532, 2564. Erases up to 8 chips within 51 minutes (1 chip in 37 minutes). Maintains constant exposure distance of one inch. Special conductive foam liner eliminates static build-up. Built-in safety lock to prevent UV exposure. Compact — only 9.00" x 3.70" x 2.60". Complete with holding tray for 8 chips.

**DE-4 UV-EPROM Eraser . . . \$79.95**  
**UVS-11EL Replacement Bulb . . \$16.95**



**4164** 64K DYNAMIC \$5<sup>95</sup>  
200 ns

**4116** 16K DYNAMIC 8/\$7<sup>95</sup>  
250 ns

### STATIC RAMS

2101	356 x 4	(45ns)	1.95
5101	256 x 4	(45ns) (cmos)	3.95
2101-1	1024 x 1	(45ns)	.89
2102L-4	1024 x 1	(45ns) (LP)	.99
2102L-2	1024 x 1	(250ns) (LP)	1.49
2125	1024 x 1	(45ns)	2.95
2111	256 x 4	(45ns)	2.49
2111L	256 x 4	(250ns) (LP)	2.95
2112	256 x 4	(45ns)	2.99
2114	1024 x 4	(45ns)	8/9.95
2114-25	1024 x 4	(250ns)	8/10.95
2114L-4	1024 x 4	(45ns) (LP)	8/12.95
2114L-3	1024 x 4	(300ns) (LP)	8/13.45
2114L-2	1024 x 4	(200ns) (LP)	8/13.95
TC5514	1024 x 4	(650ns) (cmos)	2.49
TC5516	2048 x 4	(250ns) (cmos)	9.95
2147	4096 x 1	(55ns)	4.95
TMS4044-4	4096 x 1	(45ns)	3.49
TMS4044-3	4096 x 1	(300ns)	3.99
TMS4044-2	4096 x 1	(200ns)	4.49
UPD410	4096 x 1	(100ns)	3.95
MK4118	1024 x 8	(100ns)	9.95
TMM2016-200	2048 x 8	(200ns)	4.15
TMM2016-150	2048 x 8	(150ns)	4.95
TMM2016-100	2048 x 8	(100ns) (cmos)	6.15
HM6116-4	2048 x 8	(200ns) (cmos)	4.75
HM6116-3	2048 x 8	(150ns) (cmos)	4.95
HM6116-2	2048 x 8	(120ns) (cmos)	8.95
HM6116LP-4	2048 x 8	(200ns) (cmos) (LP)	5.95
HM6116LP-3	2048 x 8	(150ns) (cmos) (LP)	6.95
HM6116LP-2	2048 x 8	(120ns) (cmos) (LP)	10.95
TMS4016	2048 x 8	(200ns) (cmos)	6.95
Z-6132	4096 x 8	(300ns) (Qstat)	34.95
HM6264P-15	8192 x 8	(150ns) (cmos)	39.95
HM6264LP-15	8192 x 8	(150ns) (cmos) (Qstat)	49.95

LP = Low Power Qstat = Quasi-Static

### DYNAMIC RAMS

TMS4027	4096 x 1	(250ns)	1.99
2107	4096 x 1	(200ns)	1.85
MMS280	4096 x 1	(300ns)	1.95
TMS4060	4096 x 1	(300ns)	1.95
UPD411	4096 x 1	(300ns)	1.95
TMS4050	4096 x 1	(300ns)	1.95
MK4108	8192 x 1	(200ns)	1.95
MMS298	8192 x 1	(250ns)	1.85
4116-300	16384 x 1	(300ns)	8/11.75
4116-250	16384 x 1	(250ns)	8/12.95
4116-200	16384 x 1	(200ns)	8/12.95
4116-150	16384 x 1	(150ns)	8/14.95
4116-120	16384 x 1	(120ns)	8/29.95
2118	16384 x 1	(150ns) (5v)	4.95
MK4332	32768 x 1	(200ns)	9.95
4164-200	65536 x 1	(200ns) (5v)	5.95
4164-150	65536 x 1	(150ns) (5v)	6.95
4164-120	65536 x 1	(120ns) (5v)	8.95
MCM6665	65536 x 1	(200ns) (5v)	8.95
TMS4164-15	65536 x 1	(150ns) (5v)	8.95
TMS4416	16384 x 4	(150ns) (5v)	9.95
41256	262144 x 1	(200ns) (5v)	CALL

5v = Single 5 volt supply

### EPROMS

1702	256 x 8	(1us)	4.50
2708	1024 x 8	(450ns)	3.95
2758	1024 x 8	(450ns) (5v)	5.95
2716-6	2048 x 8	(650ns)	2.95
2716	2048 x 8	(450ns) (5v)	3.95
2716-1	2048 x 8	(350ns) (5v)	5.95
TMS2516	2048 x 8	(450ns) (5v)	5.50
TMS2716	2048 x 8	(450ns)	7.95
TMS2532	4096 x 8	(450ns) (5v)	5.95
2732	4096 x 8	(450ns) (5v)	4.95
2732-250	4096 x 8	(250ns) (5v)	8.95
2732-200	4096 x 8	(200ns) (5v)	11.95
2732A-4	4096 x 8	(450ns) (5v) (21vPGM)	6.95
2732A	4096 x 8	(250ns) (5v) (21vPGM)	9.95
2732A-2	4096 x 8	(200ns) (5v) (21vPGM)	13.95
2764	8192 x 8	(450ns) (5v)	6.95
2764-250	8192 x 8	(250ns) (5v)	7.95
2764-200	8192 x 8	(200ns) (5v)	19.95
TMS2564	8192 x 8	(450ns) (5v)	14.95
MCM68764	8192 x 8	(450ns) (5v) (24pin)	39.95
MCM68766	8192 x 8	(350ns) (5v) (24pin)	42.95
27128-30	16384 x 8	(300ns) (5v)	29.95
27128	16384 x 8	(250ns) (5v)	34.95

5v = Single 5 Volt Supply 21vPGM Program at 21 Volts

### ★ ★ ★ ★ HIGH-TECH ★ ★ ★ ★

## SSI 263 SPEECH SYNTHESIZER

- ★ MICROPROCESSOR COMPATIBLE
- ★ 5 8-BIT CONTROL REGISTERS
- ★ ENHANCE YOUR MOCKINGBOARD OR BUILD STEVE CIARCIA'S SWEET TALKER II (BYTE MARCH '84)

### ★ ★ ★ ★ SPOTLIGHT ★ ★ ★ ★

- ★ Computer managed inventory — virtually no back orders!
- ★ Very competitive prices!
- ★ Friendly staff!
- ★ Fast service — most orders shipped within 24 hours!

### CRYSTALS

32.768 khz	1.95
1.0 mhz	3.95
1.8432	3.95
4002	.25
4006	.89
4007	.29
4008	.95
4009	.39
4010	.45
4011	.25
4012	.25
4013	.38
4014	.79
4015	.39
4016	.39
4017	.69
4018	.79
4019	.39
4020	.75
4021	.79
4022	.79
4023	.29
4024	.65
4025	.29
4026	1.65
4027	.45
4028	.69
4029	.79
4030	.39
4034	1.95
4035	.85
4040	.75
4041	.75
4042	.69
4043	.85
4044	.79
4046	.85
4047	.95
4049	.35
4050	.35
4051	.79
4053	.79
4060	.89
4066	.39
4068	.39
4069	.29
4070	.35
4071	.29
4072	.29
4073	.29
4075	.29
4076	.79
4078	.29
4081	.29
4082	.29
4085	.95
4086	.95
4093	.49
4098	2.49
4099	1.95
14409	12.95
14410	12.95
14411	11.95
14412	12.95
14419	7.95
14433	14.95
4502	.95
4503	.65
4508	1.95
4510	.85
4511	.85
4512	.85
4514	1.25
4515	1.79
4516	1.55
4518	.89
4519	.39
4520	.79
4522	1.25
4526	1.25
4527	1.95

### UARTS

AY5-1013	3.95
AY3-1015	6.95
PT1472	9.95
TR1602	3.95
2350	9.95
2651	8.95
IM6402	7.95
IM6403	8.95
INS8250	10.95

### GENERATORS BIT-RATE

MC14411	11.95
BR1941	11.95
4702	12.95
COM5016	16.95
COM8116	10.95
MM5307	10.95

### FUNCTION

MC4024	3.95
LM566	1.49
XR2206	3.75
8038	3.95

### MISC.

UPD7201	29.95
TMS99532	29.95
ULN2003	2.49
3242	7.95
3341	4.95
MC3470	4.95
MC3480	9.00
11C90	13.95
95H90	7.95
2513-001 UP	9.95
2513-002 LOW	9.95

### CLOCK CIRCUITS

MM5314	4.95
MM5369	3.95
MM5369-EST	4.25
MM5375	4.95
MM58167	12.95
MM58174	11.95
MSM5832	3.95

### KEYBOARD CHIPS

AY5-2376	11.95
AY5-3600	11.95
AY5-3600 PRO	11.95

### 6800

68000	49.95
6800	2.95
6802	7.95
6803	19.95
6808	13.90
6809E	14.95
6809	11.95
6810	2.95
6820	4.35
6821	2.95
6828	14.95
6840	12.95
6843	34.95
6844	25.95
6845	14.95
6847	11.95
6850	3.25
6852	5.75
6860	7.95
6875	6.95
6880	2.25
6883	22.95
68047	24.95
68488	19.95

### 6800 = 1MHZ

68B00	10.95
68B02	22.25
68B09E	29.95
68B09	29.95
68B10	6.95
68B21	6.95
68B40	19.95
68B45	19.95
68B50	5.95

### 68B00 = 2 MHZ

### 6500

6502	1 MHZ	4.95
6504	6.95	
6505	8.95	
6507	9.95	
6520	4.35	
6522	6.95	
6532	9.95	
6545	22.50	
6551	11.85	

### 2 MHZ

6502A	6.95
6522A	9.95
6532A	11.95
6545A	27.95
6551A	11.95

### 3 MHZ

6502B	9.95
-------	------

### DISC CONTROLLERS

1771	16.95
1791	24.95
1793	26.95
1795	29.95
1797	49.95
2793	54.95
2795	59.95
2797	59.95
6843	34.95
8272	39.95
UPD765	39.95
MB8876	29.95
MB8877	34.95
1691	17.95
2143	18.95

### 8000

8035	5.95
8039	5.95
INS-8060	17.95
INS-8073	49.95
8080	3.95
8085	4.95
8085A-2	11.95
8086	24.95
8087	CALL
8088	29.95
8089	89.95
8155	6.95
8155-2	7.95
8156	6.95
8185	29.95
8185-2	39.95
8741	29.95
8748	24.95
8755	24.95

### CRT CONTROLLERS

6845	14.95
68B45	19.95
HD46505SP	15.95
6847	11.95
MC1372	6.95
68047	24.95
8275	29.95
8270	99.95
CRT5027	19.95
CRT5037	24.95
TMS9918A	39.95
DP8350	49.95

### 8200

8202	24.95
8203	39.95
8205	3.50
8212	1.80
8214	3.85
8216	1.75
8224	2.25
8226	1.80
8228	3.49
8237	19.95
8237-5	21.95
8238	4.49
8243	4.45
8250	10.95
8251	4.49
8253	6.95
8255	7.95
8255-5	5.25
8257	7.95
8257-5	8.95
8259	6.90
8259-5	7.50
8271	79.95
8272	39.95
8275	29.95
8279	8.95
8279-5	10.00
8282	6.50
8283	6.50
8284	5.50
8286	6.50
8287	6.50
8288	25.00
8289	49.95
8292	14.95

### Z-80

2.5 Mhz	
Z80-CPU	3.95
Z80-CTC	3.95
Z80-DART	10.95
Z80-DMA	14.95
Z80-PIO	3.95
Z80-SIO/0	11.95
Z80-SIO/1	11.95
Z80-SIO/2	11.95



TMM2016

2K x 8 STATIC  
200 ns\$4<sup>15</sup>

HM6264

8K x 8 STATIC  
150 ns\$39<sup>95</sup>

## 74LS00

74LS00	.24	74LS173	.69
74LS01	.25	74LS174	.55
74LS02	.25	74LS175	.55
74LS03	.25	74LS181	2.15
74LS04	.24	74LS189	8.95
74LS05	.25	74LS190	.89
74LS08	.28	74LS191	.89
74LS09	.29	74LS192	.79
74LS10	.25	74LS193	.79
74LS11	.35	74LS194	.69
74LS12	.35	74LS195	.69
74LS13	.45	74LS196	.79
74LS14	.59	74LS197	.79
74LS15	.35	74LS221	.89
74LS20	.25	74LS240	.95
74LS21	.29	74LS241	.99
74LS22	.25	74LS242	.99
74LS26	.29	74LS243	.99
74LS27	.29	74LS244	1.29
74LS28	.35	74LS245	1.49
74LS30	.25	74LS247	.75
74LS32	.29	74LS248	.99
74LS33	.55	74LS249	.99
74LS37	.35	74LS251	.59
74LS38	.35	74LS253	.59
74LS40	.25	74LS257	.59
74LS42	.49	74LS258	.59
74LS47	.75	74LS259	2.75
74LS48	.75	74LS260	.59
74LS49	.75	74LS266	.55
74LS51	.25	74LS273	1.49
74LS54	.29	74LS275	3.35
74LS55	.29	74LS279	.49
74LS63	1.25	74LS280	1.98
74LS73	.39	74LS283	.69
74LS74	.35	74LS290	.89
74LS75	.39	74LS293	.89
74LS76	.39	74LS295	.99
74LS78	.49	74LS298	.89
74LS83	.60	74LS299	1.75
74LS85	.69	74LS323	3.50
74LS86	.39	74LS324	1.75
74LS90	.55	74LS352	1.29
74LS91	.89	74LS353	1.29
74LS92	.55	74LS363	1.35
74LS93	.55	74LS364	1.95
74LS95	.75	74LS365	.49
74LS96	.89	74LS366	.49
74LS107	.39	74LS367	.45
74LS109	.39	74LS368	.45
74LS112	.39	74LS373	1.39
74LS113	.39	74LS374	1.39
74LS114	.39	74LS375	.95
74LS122	.45	74LS377	1.39
74LS123	.79	74LS378	1.18
74LS124	2.90	74LS379	1.35
74LS125	.49	74LS385	3.90
74LS126	.49	74LS386	.45
74LS132	.59	74LS390	1.19
74LS133	.59	74LS393	1.19
74LS136	.39	74LS395	1.19
74LS137	.99	74LS399	1.49
74LS138	.55	74LS424	2.95
74LS139	.55	74LS447	.95
74LS145	1.20	74LS490	1.95
74LS147	2.49	74LS624	3.99
74LS148	1.35	74LS640	2.20
74LS151	.55	74LS645	2.20
74LS153	.55	74LS668	1.69
74LS154	1.90	74LS669	1.89
74LS155	.69	74LS670	1.49
74LS156	.69	74LS674	14.95
74LS157	.65	74LS682	3.20
74LS158	.59	74LS683	3.20
74LS160	.69	74LS684	3.20
74LS161	.65	74LS685	3.20
74LS162	.69	74LS688	2.40
74LS163	.65	74LS689	3.20
74LS164	.69	81LS95	1.49
74LS165	.95	81LS96	1.49
74LS166	1.95	81LS97	1.49
74LS168	1.75	81LS98	1.49
74LS169	1.75	25LS2521	2.80
74LS170	1.49	25LS2569	4.25

## 74S00

74S00	.32	74S124	2.75	74S197	1.49
74S02	.35	74S132	1.24	74S201	6.95
74S03	.35	74S133	.45	74S225	7.95
74S04	.35	74S134	.50	74S240	2.20
74S05	.35	74S135	.89	74S241	2.20
74S08	.35	74S138	.85	74S244	2.20
74S09	.40	74S139	.85	74S251	.95
74S10	.35	74S140	.55	74S253	.95
74S11	.35	74S151	.95	74S257	.95
74S15	.35	74S153	.95	74S258	.95
74S20	.35	74S157	.95	74S260	.79
74S22	.35	74S158	.95	74S273	2.45
74S30	.35	74S161	1.95	74S280	1.95
74S32	.40	74S162	1.95	74S287	1.90
74S37	.88	74S163	1.95	74S288	1.90
74S38	.85	74S168	3.95	74S289	6.89
74S40	.35	74S169	3.95	74S301	6.95
74S51	.35	74S174	.95	74S373	2.45
74S64	.40	74S175	.95	74S374	2.45
74S65	.40	74S181	3.95	74S387	1.95
74S74	.50	74S182	2.95	74S412	2.98
74S85	1.99	74S188	1.95	74S471	4.95
74S86	.50	74S189	6.95	74S472	4.95
74S112	.50	74S194	1.49	74S474	4.95
74S113	.50	74S195	1.49	74S570	2.95
74S114	.55	74S196	1.49	74S571	2.95

VOLTAGE  
REGULATORS

7805T	.75	7905T	.85
78M05C	.35	7908T	.85
7808T	.75	7912T	.85
7812T	.75	7915T	.85
7815T	.75	7924T	.85
7824T	.75		
7805K	1.39	7905K	1.49
7812K	1.39	7912K	1.49
7815K	1.39	7915K	1.49
7824K	1.39	7924K	1.49
78L05	.69	79L05	.79
78L12	.69	79L12	.79
78L15	.69	79L15	.79
78H05K	9.95	LM323K	4.95
78H12K	9.95	UA78S40	1.95

C, T = TO-220 K = TO-3  
L = TO-92

## SOUND CHIPS

76477	3.95	AY3-8910	12.95
76488	5.95	AY3-8912	12.95
76489	8.95	MC3340	1.49
		SSI-263	39.95

## BYPASS CAPS

.01 UF DISC	100/6.00
.01 UF MONOLITHIC	100/12.00
.1 UF DISC	100/8.00
.1 UF MONOLITHIC	100/15.00

## INTERFACE

8T26	1.59
8T28	1.89
8T95	.89
8T96	.89
8T97	.89
8T98	.89
DM8131	2.95
DP8304	2.29
DS8833	2.25
DS8835	1.99
DS8836	.99
DS8837	1.65
DS8838	1.30

## CENTRONICS

IDCEN36  
Ribbon Cable  
36 Pin Male 8.95IDCEN36/F  
Ribbon Cable  
36 Pin Female 8.95CEN36  
Solder Cup  
36 Pin Male 7.95

## CONNECTORS

RS232 Male	2.50
RS232 Female	3.25
RS232 Hood	1.25
S-100 ST	3.95

## EXAR

XR 2206	3.75
XR 2207	3.75
XR 2208	3.75
XR 2211	5.25
XR 2240	3.25

## INTERSIL

ICL7106	9.95
ICL7107	12.95
ICL7660	2.95
ICL8038	3.95
ICM7207A	5.59
ICM7208	15.95

## 9000

9316	1.00
9334	2.50
9368	3.95
9401	9.95
9601	.75
9602	1.50
96S02	1.95

EPROM ERASERS  
SPECTRONICS  
CORPORATION

	Timer	Capacity Chip	Intensity (uW/Cm <sup>2</sup> )	
PE-14		9	8,000	83.00
PE-14T	X	9	8,000	119.00
PE-24T	X	12	9,600	175.00
PL-265T	X	30	9,600	255.00
PR-125T	X	25	17,000	349.00
PR-320T	X	42	17,000	595.00

## DATA ACQUISITION

ADC0800	15.55	DAC0800	4.95
ADC0804	3.49	DAC0808	2.95
DAC0806	1.95	DAC1020	8.25
DAC0809	4.49	DAC1022	5.95
ADC0816	14.95	MC1408L6	1.95
ADC0817	9.95	MC1408L8	2.95

## LINEAR

LM301	.34	LM348	.99	LM567	.89	LM1812	8.25
LM301H	.79	LM350K	4.95	NE570	3.95	LM1830	3.50
LM307	.45	LM350T	4.60	NE571	2.95	LM1871	5.49
LM308	.69	LM358	.69	NE590	2.50	LM1872	5.49
LM308H	1.15	LM359	1.79	NE592	2.75	LM1877	3.25
LM309H	1.95	LM376	3.75	LM709	.59	LM1889	1.95
LM309K	1.25	LM377	1.95	LM710	.75	LM1896	1.75
LM310	1.75	LM378	2.50	LM711	.79	ULN2003	2.49
LM311	.64	LM379	4.50	LM723	.49	LM2877	2.05
LM311H	.89	LM380	.89	LM723H	.55	LM2878	2.25
LM312H	1.75	LM380N-8	1.10	LM733	.98	LM2900	.85
LM317K	3.95	LM381	1.60	LM741	.35	LM2901	1.00
LM317T	1.19	LM382	1.60	LM741N-14	.35	LM2917	2.95
LM318	1.49	LM383	1.95	LM741H	.40	LM3900	.59
LM318H	1.59	LM384	1.95	LM747	.69	LM3905	1.25
LM319H	1.90	LM386	.89	LM748	.59	LM3909	.98
LM319	1.25	LM387	1.40	LM1014	1.19	LM3911	2.25
LM320 (see 7900)		LM389	1.35	LM1303	1.95	LM3914	3.95
LM322	1.65	LM390	1.95	LM1310	1.49	LM3915	3.95
LM323K	4.95	LM392	.69	MC1330	1.69	LM3916	3.95
LM324	.59	LM393	1.29	MC1349	1.89	MC4024	3.95
LM329	.65	LM394H	4.60	MC1350	1.19	MC4044	4.50
LM331	3.95	LM399H	5.00	MC1358	1.69	RC4136	1.25
LM334	1.19	NE531	2.95	MC1372	6.95	RC4151	3.95
LM335	1.40	NE555	.34	LM1414	1.59	LM4250	1.75
LM336	1.75	NE556	.65	LM1458	.59	LM4500	3.25
LM337K	3.95	NE558	1.50	LM1488	.69	RC4558	.69
LM337T	1.95	NE561	24.95	LM1489	.69	LM13080	1.29
LM338K	6.95	NE564	2.95	LM1496	.85	LM13600	1.49
LM339	.99	LM565	.99	LM1558H	3.10	LM13700	1.49
LM340 (see 7800)		LM566	1.49	LM1800	2.37	MPQ2907	1.95

H = TO-5 CAN      T = TO-220      K = TO-3

H = TO-5 CAN

T = TO-220

K = TO-3

## RCA

CA 3023	2.75	CA 3082	1.65
CA 3039	1.29	CA 3083	1.55
CA 3046	1.25	CA 3086	.80
CA 3059	2.90	CA 3089	2.99
CA 3060	2.90	CA 3096	3.49
CA 3065	1.75	CA 3130	1.30
CA 3080	1.10	CA 3140	1.15
CA 3081	1.65	CA 3146	1.85
CA 3160	1.19		

## TI

TL494	4.20	75365	1.95
TL496	1.65	75450	.59
TL497	3.25	75451	.39
75107	1.49	75452	.39
75110	1.95	75453	.39
75150	1.95	75454	.39
75154	1.95	75491	.79
75188	1.25	75492	.79
75189	1.25	75493	.89
75494	.89		

## BI FET

TL071	.79	TL084	2.19
TL072	1.19	LF347	2.19
TL074	2.19	LF351	.60
TL081	.79	LF353	1.00
TL082	1.19	LF355	1.10
TL083	1.19	LF356	1.10
LF357	1.40		



2764

8K x 8 EPROM  
450 ns\$6<sup>95</sup>

27128-30

16K x 8 EPROM  
300 ns\$29<sup>95</sup>

## BARGAIN HUNTERS CORNER

2732A 350ns

- "A" VERSION PROGRAMS AT 21 VOLTS.
- FAST! 350ns ACCESS TIME

4.95 EACH 100/4.45 EACH

## Z-80 SPECIALS!


Z-80A-CPU	2.95
Z-80A-CTC	2.95
Z-80A-PIO	2.95

SPECIALS END 7/31/84

## IC SOCKETS

	1-99	100
8 pin ST	.13	.11
14 pin ST	.15	.12
16 pin ST	.17	.13
18 pin ST	.20	.18
20 pin ST	.29	.27
22 pin ST	.30	.27
24 pin ST	.30	.27
28 pin ST	.40	.32
40 pin ST	.49	.39
64 pin ST	4.25	call
ST = SOLDER TAIL		
8 pin WW	.59	.49
14 pin WW	.69	.52
16 pin WW	.69	.58
18 pin WW	.99	.90
20 pin WW	1.09	.98
22 pin WW	1.39	1.28
24 pin WW	1.49	1.35
28 pin WW	1.69	1.49
40 pin WW	1.99	1.80
WW = WIREWRAP		

## ZIF SOCKETS

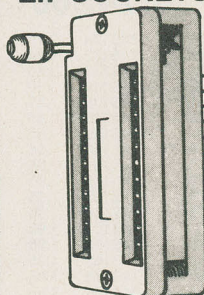

LEADS	UNIT PRICE
14	5.95
16	5.95
24	7.95
28	8.95
40	10.95
ZIF = Zero Insertion Force	

## OPTO-ISOLATORS

4N26	1.00	MCA-7	4.25
4N27	1.10	MCA-255	1.75
4N28	.69	IL-1	1.25
4N33	1.75	ILA-30	1.25
4N35	1.25	ILQ-74	2.75
4N37	1.25	H11C5	1.25
MCT-2	1.00	TIL-111	1.00
MCT-6	1.50	TIL-113	1.75

## MUFFIN FANS

4.68" Square	14.95
3.125" Square	14.95

## HEAT SINKS

TO-3 style	.95
TO-220 style	.35

## SWITCHES

SPDT mini-toggle	1.25
DPDT mini-toggle	1.50
SPST mini-pushbutton	.39

## DIODES

1N751	5.1 volt zener	.25
1N759	12.0 volt zener	.25
1N4148	(1N914) switching	25/1.00
1N4004	400PIV rectifier	10/1.00
KBP02	200PIV 1.5amp bridge	.45
KBP04	400PIV 1.5amp bridge	.55
VM48	Dip-Bridge	.35

## TRANSISTORS

2N918	.50	MPS3706	.15
MPS918	.25	2N3772	1.85
2N2102	.75	2N3903	.25
2N2218	.50	2N3904	.10
2N2218A	.50	2N3906	.10
2N2219	.50	2N4122	.25
2N2219A	.50	2N4123	.25
2N2222	.25	2N4249	.25
PN2222	.10	2N4304	.75
MPS2369	.25	2N4401	.25
2N2484	.25	2N4402	.25
2N2905	.50	2N4403	.25
2N2907	.25	2N4857	1.00
PN2907	.125	PN4916	.25
2N3055	.79	2N5086	.25
3055T	.69	PN5129	.25
2N3393	.30	PN5139	.25
2N3414	.25	2N5209	.25
2N3583	.40	2N6028	.35
2N3585	.40	2N6043	1.75
PN3585	.25	2N6045	1.75
MPS3638	.25	MPS-A05	.25
MPS3640	.25	MPS-A06	.25
PN3643	.25	MPS-A55	.25
PN3644	.25	TIP29	.65
MPS3704	.15	TIP31	.75
		TIP32	.79




ORDER TOLL FREE

VISA


## DISK DRIVES

TANDON	
TM100-1 5 1/4" (FOR IBM) SS/DD	199.00
TM100-2 5 1/4" (FOR IBM) DS/DD	219.00
MPI	
MP-52 5 1/4" (FOR IBM) DS/DD	249.00
TEAC	
FD-55B 1/2" HEIGHT DS/DD	189.00
SHUGART	
SA 400L 5 1/4" (40 TRACK) SS/DD	199.95
8" DISK DRIVE	
FD 100-8 BY SIEMENS, SHUGART 801 EQUIV.	
SS/DD — 10/\$149 EA.	\$169.00
FD 200-8 BY SIEMENS, SHUGART 851 EQUIV.	
SS/DD — 10/\$220 EA.	\$239.00

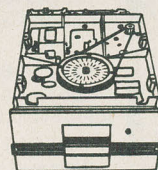Please include sufficient amount for shipping on above items.



TANDON 5 1/4"

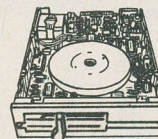

TEAC HALF HEIGHT

## CABINETS FOR 5 1/4" DISK DRIVES

## CABINET #1 \$29.95

- ★ Dimensions 8 1/2 x 5 1/8 x 3 1/16"
- ★ Color matches Apple
- ★ Fits standard 5 1/4" drives, inc. Shugart

- ★ Includes mounting hardware and feet

## CABINET #2 \$79.00

- ★ Complete with power supply, switch, line cord, fuse & standard power connector
- ★ Dimensions: 11 1/2 x 5 1/2 x 3 1/16"
- ★ + 5V @ 1 AMP, + 12V @ 1.5 AMP
- ★ Please specify gray or tan


NOTE: Please include sufficient amount for shipping on above items.

## D-SUBMINIATURE

DESCRIPTION	ORDER BY	CONTACTS				
		9	15	25	37	50
SOLDER CUP	MALE DPxxP	2.08	2.69	2.50	4.80	6.06
	FEMALE DBxxS	2.66	3.63	3.25	7.11	9.24
RT. ANGLE	MALE DBxxPR	1.65	2.20	3.00	4.83	---
PC HOLDER	FEMALE DBxxSR	2.18	3.03	4.42	6.19	---
IDC RIBBON CABLE	MALE IDBxxP	3.37	4.70	6.23	9.22	---
	FEMALE IDBxxS	3.69	5.13	6.84	10.08	---
HOODS	BLACK HOOD-B	---	---	1.25	---	---
	GREY HOOD	1.60	1.60	1.25	2.95	3.50

MOUNTING HARDWARE - \$1.00

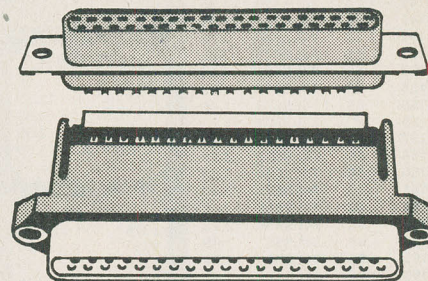
For order instructions see "IDC Connectors" below.



## IDC CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS				
		10	20	26	34	40
SOLDER HEADER	IDHxxS	.82	1.29	1.68	2.20	2.58
RT. ANGLE SOLDER HEADER	IDHxxSR	.85	1.35	1.76	2.31	2.72
WW HEADER	IDHxxW	1.86	2.98	3.84	4.50	5.28
RT. ANGLE WW HEADER	IDHxxWR	2.05	3.28	4.22	4.45	4.80
RIBBON HEADER SOCKET	IDSxx	1.15	1.86	2.43	3.15	3.73
RIBBON HEADER	IDMxx	---	5.50	6.25	7.00	7.50
RIBBON EDGE CARD	IDExx	2.25	2.36	2.65	3.25	3.80

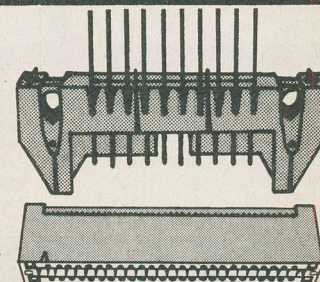ORDERING INSTRUCTIONS: Insert the number of contacts in the position marked "xx" of the "order by" part number listed. Example: A 10 pin right angle holder style header would be IDH10SR.




© Copyright 1984 JDR Microdevices

CIRCLE 49 ON FREE INFORMATION CARD



# FOR APPLE COMPUTER USERS

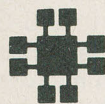

**JDR Microdevices**

**THOUSANDS SOLD!**

## JDR 16K RAM CARD FOR APPLE II+


- ★ Expand your 48K Apple to 64K
  - ★ Fully compatible with Apple Language System — Use in place of Apple Language card
  - ★ Highest quality card features: gold edge connector, sockets for all IC's.
  - ★ 2 YEAR WARRANTY
- Kit with Instructions ..... \$40.95 **\$44.95**  
Bare PC Card ..... \$14.95

## GET SLIM IN 1984!


### JDR HALF-HEIGHT DISK DRIVE

- ★ 35 Track if used with Apple Controller
- ★ 40 Track Controller and DOS Available (Call for Price)

**\$209.95**

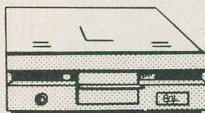

## MA SYSTEMS FD-35 DISK DRIVE

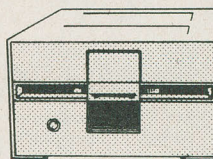

**\$199.95**

- ★ Shugart Mechanism — Made in U.S.A.
- ★ Direct Replacement for Apple Disk II
- ★ Compatible with Apple Controller or other Apple compatible controllers
- ★ Specially designed electronics with **low power** consumption
- ★ DOS 3.3 and 3.2 compatible
- ★ One Year Warranty

### CONTROLLER CARD

**\$69.95**



## APPLE COMPATIBLE POWER SUPPLY


- ★ Use To Power Apple Type Systems
- ★ +5V @ 4A +12V @ 2.5A
- ★ -5V @ .5A -12V @ .5A
- ★ Instructions and Apple Power Connector Included.

**\$79.95**

## BMC BMX-80 PRINTER

- ★ 80 CPS Dot Matrix Printer
- ★ Prints Bi-Directional in 40, 80, 71 or 142 Columns in Normal, Double Width or Compressed Text.
- ★ Print Superscript As Well As Superb Graphics in Character or Bit Image

**\$279**

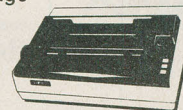

**micromax**

## VIEWMAX-80

**NOW ONLY \$159.95**

- ★ 80 Column Card for Apple II+
- ★ Video Soft Switch
- ★ Inverse Video
- ★ 2 Year Warranty

## VIEWMAX-80e

**NEW \$129.95**

- ★ 80 Column Card for Apple IIe
- ★ 64K RAM Expandable to 128K
- ★ 64K RAM Upgrade **\$47.60**

**GRAPHMAX \$129.95**

- ★ Hi Resolution Graphics
- ★ Printer Card
- ★ Centronics Parallel Interface
- ★ Zoom, Rotation and More

Graphmax with Color Option ..... **149.95**

## NASHUA DISKETTES

5 1/4" WITH HUB RING

MD1 SOFT SECTOR, SS/SD	19.95
MD1D SOFT SECTOR, SS/DD	26.25
MD2D SOFT SECTOR, DS/DD	30.75
MD2F SOFT SECTOR, DS/QUAD DENSITY	45.00
MD110 10 SECTOR HARD, SS/SD	19.95
MD210D 10 SECTOR HARD, DS/DD	30.75
8" WITHOUT HUB RING	
FD1 SOFT SECTOR, SS/SD	24.75
FD1D SOFT SECTOR, SS/DD	30.00
FD2D SOFT SECTOR, DS/DD	36.75

## VERBATIM

### DATALIFE DISKETTES

SS/DD SOFT SECTOR

**\$29.95**

SS/DD 10 HARD SECTOR

**\$29.95**

## 5 1/4" DISKETTE FILE

- ★ ATTRACTIVE, FUNCTIONAL DISK STORAGE SYSTEM
  - ★ 75 DISK STORAGE CAPACITY
  - ★ MOLDED FROM DURABLE SMOKED PLASTIC WITH FRONT CARRYING HANDLE
- \$16.99**

## OTHER ACCESSORIES FOR APPLE II

### THUNDERCLOCK \$129.95


- ★ Real-Time Clock Calendar
- ★ Software Included
- ★ Mountain Software Compatible
- ★ BSR Control Options Available

### KRAFT JOYSTICK \$39.95

## MONITORS
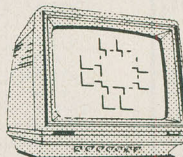
### BMC MONITOR STAND MODEL PA-900

Your Display Will  
Tilt & Swivel **\$29.95**




### MONOCHROME

BMC BM 12AUW GREEN 12"	\$89.95
BMC BM 12EUY 18 MHZ AMBER	\$139.95
BMC BM 12EUN 18 MHZ HIGH RES GREEN	\$115.00
NEC JB1201M-20 MHZ GREEN	\$169.00
ZENITH ZVM-123-15 MHZ GREEN	NEW \$105.00

### COLOR

BMC BM-AU9191U COMPOSITE 13"	\$279.00
------------------------------	----------

NO C.O.D. ORDERS PLEASE

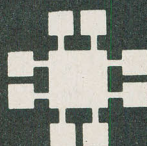

**JDR Microdevices**

1224 S. Bascom Avenue, San Jose, CA 95128

800-538-5000 • 800-662-6279 (CA)

(408) 995-5430 • Telex 171-110

Apple is a trademark of Apple Computer Corporation

## VISIT OUR RETAIL STORE

HOURS: M-W-F, 9-5 T-Thu., 9-9 Sat. 10-3

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: Minimum order \$10. For shipping and handling include \$2.50 for UPS Ground and \$3.50 for UPS Air. Orders over 1 lb. and foreign orders may require additional shipping charges — please contact our sales department for the amount. CA residents must include 6% sales tax. Bay Area and LA residents include 6 1/2%. Prices subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sale.

© Copyright 1984 JDR Microdevices



**MICRO-PROFESSOR**  
MPF-1 USER'S AND EXPERIMENTAL MANUAL

Dear Electronic Enthusiast:  
Now, let the Micro-Professor usher you into the microcomputer revolution.  
The Micro-Professor™ is the first really low-cost learning system designed for personal use. It will truly become your "Personal Computer".  
Sincerely,  
Chris Johnson  
Chris Johnson, Customer Service

only **\$12995**

**Z-80 BASED**

## MICROCOMPUTER

**A superb learning tool for students, instructors, hobbyists.**

Nothing else needed. Just plug in and start learning! Complete experimenters manual, easy instructions. 18 experiments. Fully expandable for Z80-CTC, Z80-PIO, EPROM, Breadboarding and prototyping. Invest with confidence. Now only \$129.95, two for only \$239.95. 2KB BASIC interpreter now available, only \$19.00. Full money back guarantee!

**Plus-FREE GIFT**  
☐ Check this box for **FREE Z-80 Microprocessor Programming and Interfacing textbook** when you order within 7 days. \$12.95 value.

**ETRONIX**  
Dept. RE074  
14803 N.E. 40th  
Redmond, WA 98052

For immediate action call TOLL FREE: **1-800-426-1044**

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ST \_\_\_\_\_ ZIP \_\_\_\_\_  
☐ VISA ☐ MSTRCD ☐ EXP. \_\_\_\_\_  
ACCT. NO. \_\_\_\_\_

CIRCLE 39 ON FREE INFORMATION CARD

# ACTIVE RECEIVING ANTENNA

**Gives excellent reception, 50 KHz to 30 MHz.**

**New MFJ-1024 Active Receiving Antenna** mounts outdoors away from electrical noise for maximum signal. **Gives excellent reception of 50 KHz to 30 MHz signals.** Equivalent to wire hundreds of feet long. Use any SWL, MW, BCB, VLF or Ham receiver.

**High dynamic range RF amplifier.** 54 in. whip. 50 foot coax. 20 dB attenuator prevents receiver overload. Switch between two receivers. Select auxiliary or active antenna. Gain control. "ON" LED. Remote unit, 3x2x4 in. Control, 6x2x5 in. 12 VDC or 110 VAC with optional adapter, MFJ-1312, \$9.95.

**\$129.95** (+\$4.00 shipping)

Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping). **One year unconditional guarantee.**

Order today. Call TOLL FREE 800-647-1800. Charge VISA, MC. Or mail check, money order. Write for free catalog. Over 100 products.

**CALL TOLL FREE 800-647-1800**

Call 601-323-5869 in Miss., outside continental USA, tech/order/repair info. TELEX 53-4590.

**MFJ ENTERPRISES, INCORPORATED**  
Box 494, Mississippi State, MS 39762

CIRCLE 66 ON FREE INFORMATION CARD

**DC TO OVER 1000 MHz**  
with any  
**OSCILLOSCOPE**

**HIGH PERFORMANCE SAMPLING SCOPE.** Litco GS-1 will convert, with a simple external connection, any DC scope to a high performance sampling scope. It will outperform for repetitive waveforms, any conventional scope regardless of price. Rise time 150ps max. Bandwidth DC to well over 1000 MHz. Useful to several gigahertz. Time base - 12 steps from 200ps to 1us/div. Noise or signal aberrations 10 mV max. Input signal range 10 Vp-p, 100 Vp-p with X10 probe attenuator sold below. Remote active sampling probe with 10 Meg, 1pF input. Stable trigger with slope and level controls. Manual scan for X-Y plotter operation. Quality construction with all BNC connectors. Internal fused power supplies.

**TIME DOMAIN REFLECTOMETER (TDR).** GS-1 can be combined with Litco ST-1 100ps, 2 Vp-p step generator to form a TDR - a powerful tool for analysis of UHF, VHF & microwave striplines, coax cables, antennas & networks.

**MICROPROCESSOR INTERFACE.** If X voltage is impressed on "SCAN IN" terminal of GS-1 (DC 1000KHz rate), Y voltage will appear on "VERT OUT" terminal for any waveform observed. Ideal for digitizing of voltage, frequency, delay & risetime in microprocessor based test systems.

GS-1 Gigahertz sampler	\$349.00
PA-10 X10 probe tip attenuator	29.00
ST-1 100 ps, 2 Vp-p step generator	195.00
IN-12 Booklet - Sampling, TDR, GS-1 & ST-1 theory & applications.	9.00
Shipping, handling & insurance	4.00
Check or COD (NJ res. add 6% sales tax)	

**LITCO SYSTEMS, INC., Box 90, E. Hanover, NJ 07936**  
(717) 689-7835

### ELECTRONIC KITS FROM HAL-TRONIX

2304 MHZ DOWN CONVERTERS. TUNES IN ON CHANNELS 2 TO 7 ON YOUR OWN HOME T.V. HAS FREQUENCY RANGE FROM 2000 MHZ TO 2500 MHZ. EASY TO CONSTRUCT AND COMES COMPLETE WITH ALL PARTS INCLUDING A DIE-CAST ALUM CASE AND COAX FITTINGS, REQUIRE A VARIABLE POWER SUPPLY AND ANTENNA (Antenna can be a dish type or coffee can type depending on the signal strength in your area.)

2304 MOD 1 (Basic Kit)	\$19.95
(Less case & fittings)	
2304 MOD 2 (Basic/Pre-amp)	\$29.95
(Less case & fittings)	
2304 MOD 3 (Hi-Gain Pre-amp)	\$39.95
(Includes case & fittings)	

POWER SUPPLY FOR EITHER MODEL ABOVE IS AVAILABLE. COMES COMPLETE WITH ALL PARTS, CASE, TRANSFORMER, ANTENNA SWITCH AND CONNECTORS (Kit) \$24.95  
Assembled.....\$34.95  
Slotted Microwave Antenna For Above Downverters.....\$39.95

### PREAMPLIFIERS

HAL PA-19—1.5 mhz to 150 mhz. 19db gain operates on 8 to 18 volts at 10ma. Complete unit \$8.95.  
HAL PA-1.4—3 mhz to 1.4 ghz. 10 to 12 db gain operates on 8 to 18 volts at 10 ma. Complete unit \$12.95.  
(The above units are ideal for receivers, counters, etc.)

16 LINE TOUCH TONE DECODE KIT WITH P.C. BOARD AND PARTS	\$69.95
12 LINE TOUCH TONE DECODE KIT WITH P.C. BOARD AND PARTS	\$39.95
16 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS	\$39.95
12 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS	\$29.95

Complete Sets of P.C. Boards Available For: Unicorn Robot Project and Heart-A-Matic Project.  
MANY, MANY OTHER KITS AVAILABLE

Send 20 cents stamp or S.A.S.E. for information and flyer on other HAL-TRONIX products. To order by phone: 1-313-285-1782.



**HAL-TRONIX**  
P.O. Box 1101  
Southgate, MI 48195

SHIPPING INFORMATION: ORDERS OVER \$25.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$25.00 PLEASE INCLUDE ADDITIONAL \$2.50 FOR HANDLING AND MAILING CHARGES.

CIRCLE 75 ON FREE INFORMATION CARD

**HIGH QUALITY up to 75dB GAIN**

# MICROWAVE TV SYSTEM

Variable from 1.9 to 2.5 GHz

**The latest advance in microwave technology with a SNOW-FREE PICTURE.**

Two Models to choose from.  
**Both Models Include:**

- 20" Parabolic Dish
- Pre-assembled Probe with Down Converter

- Power Supply and Coax Switch
- 60' of RG-59/U Coax with Connector
- Transformer for 75 to 300 Ohms
- All Mounting Hardware for Fast and Easy Installation

<b>20" Fiberglass Dish</b> Up to 55dB Gain Special <b>\$98.95</b>	<b>20" Aluminum Dish</b> Up to 55dB Gain Low Priced <b>\$98.95</b>
---	--

Add 10% for Foreign orders or U.S. Parcel Post

High Gain Yagi Antenna with Down Converter and Power Supply. Complete System, Ready to Use. **\$89.95**

Send \$2.00 for Catalog. Refundable with first purchase. Available thru Mail and Phone Orders Only. 20% deposit for COD. CA Res add 6 1/2% Tax. Send Cashiers Check or Money Order to: (Personal Checks, allow 2-5 weeks to clear)

**PROFESSIONAL VIDEO, Inc.**  
4670 Hollywood Blvd., Hollywood, Calif. 90027

For C.O.D. Orders Call (213) 219-0227

CIRCLE 21 ON FREE INFORMATION CARD

# DON'T BLAME THE SOFTWARE!

Our Isolators eliminate equipment interaction, clean up interference, curb damaging power line spikes and lightning bursts.



### ISO-1 ISOLATOR

3 isolated sockets; quality spike suppression; basic protection. . \$81.95

### ISO-3 SUPER-ISOLATOR

3 dual isolated sockets; suppressor; commercial protection. . . . . \$122.95

### ISO-17 MAGNUM ISOLATOR

4 quad isolated sockets; suppressor; laboratory grade protection. . \$213.95

**ESP Electronic Specialists, Inc.**  
171 S. Main, Natick, MA 01760 (617) 655-1532  
Toll Free Order Desk 1-800-225-4876  
MasterCard, VISA, American Express

CIRCLE 6 ON FREE INFORMATION CARD





**NEW!**

**The complete  
BREADBOARDING  
SOURCE at the  
lowest prices  
ANYWHERE!**

## HB-0100 Buss Strip

Each buss strip contains four groups of labeled contact points (25 per group) providing multipoint distribution for Vcc, ground and signal paths. When interconnected, HB-0100's can simulate Micro-Processor's data or address busses simplifying ROM, RAM, UART, etc. to processor interconnects.

Competition Price: \$3.00!

**\$2.25**

HB-0100

## HB-1000 Socket

With HANDY sockets, breadboarding is easy because you always know where you're at. Each group of 5 contacts is labeled from 1-64 and each position within a group is labeled from a-j. With 64 groups of 5 contacts each you have more than enough room for infield and lab mock-ups that always come up when you least expect them.

Competition Price: \$12.50!

**\$9.95**

HB-1000

## HB-1210

One socket and one buss strip with self-adhesive backing and metal ground plate. Big nine 14-pin DIP capacity.

Competition Price: \$18.50!

**\$13.95**

HB-1210

## HB-1110

One socket and two buss strips with self-adhesive backing and metal ground plate. Big nine 14-pin DIP capacity.

Competition Price: \$15.49!

**\$11.95**

HB-1110

## HB-2112

A compact breadboard ideal for beginners, students, professionals and hobbyists. It's quick and easy to use and immediately becomes the most useful tool on your workbench. Includes: • 2 sockets • 1 buss strip • 2 binding posts and is mounted on an 8.7"x5.4" aluminum ground plate. 18 14-Pin DIP capacity.

**\$24.95**

HB-2112

**ORDER  
NOW!**

## HB-2313

Holds enough IC's to meet any quick-fix situation. Includes: • 2 sockets

• 3 buss strips • 3 binding posts and is mounted on an 8.7"x5.9" aluminum ground plate. 18 14-Pin DIP capacity.

Competition Price: \$51.50!

**\$31.00**

HB-2313

## HB-3514

Ideal for light industrial as well as secondary level educational and hobbyist experimentation. Includes: • 3 sockets

• 5 buss strips • 4 binding posts and is mounted on a 9.4"x7.7" aluminum ground plate. 27 14-Pin DIP capacity.

Competition Price: \$66.00!

**\$47.95**

HB-3514

## HB-4714

Largest HANDY breadboard available today. Complete PCB or even system mock-ups can easily fit on this breadboard. This high capacity, heavy duty board is a must for industrial users where time is money ... Great for advanced educational and hobbyist applications.




Includes: • 4 sockets • 7 buss strips • 4 binding posts and is mounted on a 10.3"x9.5" aluminum ground plate.

Giant 36 14-Pin DIP capacity.

Competition Price: \$89.00!

**\$63.95**

HB-4714

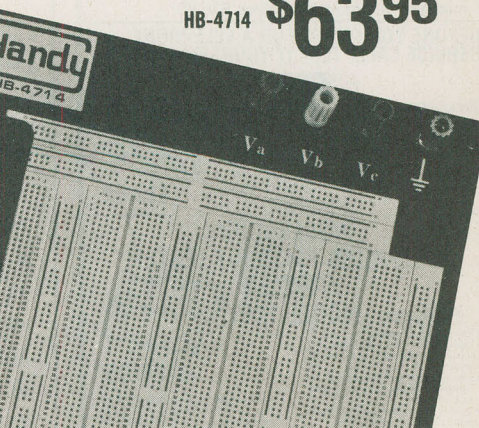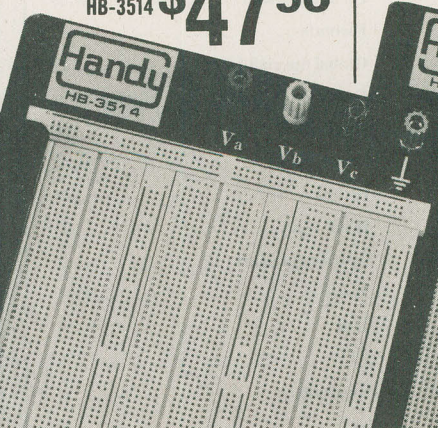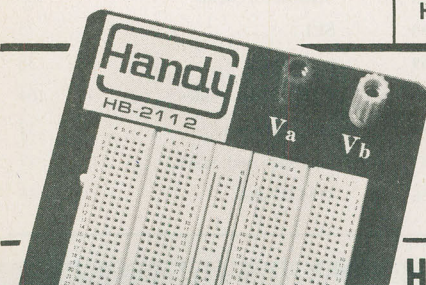

**Mail Orders:** Please add \$3 (Canada & Int'l add \$5) to cover cost of shipping/handling.

**Charge Cards:** (Min. \$15). Please include Acct. No., Exp. Date, Bank No. (M/C only) and your signature.

**Checks:** Drawn in U.S. Dollars on U.S. banks only.

**Conn Residents:** Add 7 1/2% Sales Tax. Sorry! No C.O.D. orders.



To order...call **1-800-34-HANDY**

...charge with **VISA, MasterCard or American Express.**

**All items off-the-shelf for Immediate Shipment!**

a division of RSP Electronics Corp.

7 Business Park Drive • P.O. Box 699 • Branford, CT 06405 • (203) 488-6603 • TWX: (910) 997-0684

Easy Link Mail Box: 62537580 • CompuServe: 71346, 1070

U.S. and Canadian Distributor inquiries welcomed.

CIRCLE 95 ON FREE INFORMATION CARD




# SPARTAN Electronics Inc



CALL (516) 499-9500  
MAIL 6094 Jericho Tpke.  
Commack, N.Y. 11725

CTC9R

## Philips Remote Cable Converter

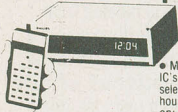

**\$139.95**

• Micro computer technology • Quartz controlled IC's lock in picture & prevent drift • 60 channel selections • Programmable time on & off • 24 hour LED digital clock • Favorite channel memory & recall plus scan • Wireless hand held "infra-red" transmitter system • Automatic fine tune • Adaptable to any brand television • One year warranty service.

## SGL WABER \$35.95


Protect your computer and electronic equipment from voltage spikes

DG115P

DG115S  
(6 Outlet)  
\$45.95



## WINEGARD FM CAR ANTENNA BOOSTER

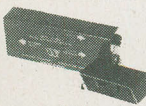

\$26.95

Amplifies FM radio signals an average of 18dB (8 times) Improves car radio reception and extends range to allow greater selection of stations. Switch and indicator light attaches to lower edge of dash. 24" cable with Motorola plugs provided. Installs in minutes. Great for window antennas.

## REFURBISHED MONITORS

9" and 12" Bell & Howells or GBC Commercial Grade as low as \$10.00 off with a purchase of 2 refurbished monitors



**\$39.95**

## BECKMAN CIRCUITMATE DM73

- .5% basic Vdc Accuracy probe-sized dmm
- 4 ac/dc voltage ranges (autoranging)
- 4 resistance ranges (autoranging)
- continuity beeper
- "touch hold" button
- Other Circuitmate Meters Available.

**\$63.95**



## Jerrold 58 Channel Wireless Remote Converter \$109.95

Jerrold 36 Channel Remote CATV Converter w/on/off Fine Tuning \$94.95



## 40 Channel VHF to UHF Block Converter



28.95 Ea.  
24.95 4 & up

Deluxe Version - Features fine tuning knob, matching X former & 2 cables \$38.95

## BEFORE YOU PAY \$\$ FOR A TELEPHONE SERVICE CALL, TEST IT YOURSELF

BK PRECISION

Telephone Line Analyze Model #1042

- Tests telephone line functions that affect telephone operation
- Verifies line and ring voltage levels
- Checks condition of telephone line from central office to user's telephone jack
- Verifies telephone line polarity that can affect polarity sensitive telephones




**\$19.95**

## PROFESSIONAL TELEPHONE PRODUCT TESTER

BK PRECISION

Features: MODEL 1045

- Provides basic operation tests for corded and cordless telephones, answering machines, and automatic dialers
- Checks telephone line cords and handset cords for continuity, shorts and intermittents
- Verifies number dialed and redialed for pulse or touch-tone telephones
- Provides low and normal level ring test sequence
- Verifies that voice and DTMF (Dual Tone Multiple Frequency) levels are above minimum required level
- Can be used by the consumer without the aid of a salesperson—an easy-to-follow instruction card is provided with the tester
- Can be used by the salesperson to demonstrate operation and features of telephone products and to screen returns before making an exchange

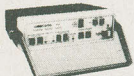

**\$335.95**

## Volume Discounts

Min. Order \$25.00	to 75.00	\$2.50
International shipping Add'l.	76.00 to 250.00	\$4.50
Prices subject to change without notice.	251.00 to 500.00	\$6.00
COD 2.00 Extra	501.00 to 750.00	\$8.50
*Add'l. shipping for monitors	751.00 to 1000.00	\$12.00
	Over 1000.00	\$12.50

(516) 499-9500 Mon Th 9-8 Tu W F 9-6 Sa 9:30-5

CIRCLE 36 ON FREE INFORMATION CARD

## ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	7	OK Industries	26
77	Active Electronics	84	Philips ECG	17
80	Advanced Computer Products	89	Philips Tech Electronics	88
—	Advance Electronics	5	Pomona	15
12	All Electronics	95	Priority One	7
67	AMC Sales	77	Professional Video	102
—	Appliance Service	23	PTS	42
87	AP Products	Cover 3	Radio Shack	83
22	Beta Electronics	23	Ramsey	91
16	B&K	13	Random Access	23
—	C&D	80	RCA Dis. and Special Prod.	14
18	CEI	16	RF Electronics	90
—	CIE	18-21	R&M Distributors	23
—	Command Productions	81	RSP Handy	103
35	Communications Electronics	2	Sams Book Store	24-25
50	Contact East	23	Scientific Systems	104
68	CPU	94	SEI	75
24	Deco Industries	23	Sony Video	33
65	Digikey	92,93	Spartan Electronics	104
11	Digitron	94	Trio Kenwood	32
53	Direct Video	79	Tubergen and Assoc.	77
99	Dokay	85	WM B Allen	86
54	DTI	77		
92	EICO	80		
58	EKI	37		
44	Electro Industries	79		
6	Electronic Specialists	102		
39	Etronix	102		
40	Firestik	81		
—	Fluke Manufacturing	Cover 4		
—	Fordham Radio	34,35		
76	Formula	87		
33	Global Specialties	27		
—	Grantham College of Engineering	1		
75	Haltronix	102		
15	Heath	Cover 2		
85	Hickok	73		
38	HMR Sales	23		
8	Instrument Mart	36		
41	Jameco	96,97		
49	JDR	98-101		
45	J&W	77		
63	Kashiwagi	23		
83	KCS	88		
19	Litco Systems	102		
—	McGraw Hill Book Club	39-41		
93	McIntosh Labs	73		
66	MFJ	102		
90	Network Sales	86		
—	Newtone Electronics	22		
—	NRI	8-11		
—	NTS	28-31		

## AMAZING DEVICES

PERSONAL DEFENSE AND PROPERTY PROTECTION UTILIZE SPACE AGE TECHNOLOGY. CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.

POCKET PAIN FIELD GENERATOR — IPG50

Assembled.....\$59.50

IPG5.....Plans.....\$7.00 IPG5K.....Kit/Plans.....\$39.50

PHASOR PAIN FIELD CROWD CONTROLLER — PPF10

Assembled.....\$250.00

PPF1.....Plans.....\$15.00 PPF1K.....Kit/Plans.....\$175.00

BLASTER — Provides a plasma discharge capable of puncturing a can.

BLS10.....Assembled.....\$79.50

BLS1.....Plans.....\$10.00 BLS1K.....Kit/Plans.....\$59.50

SHOCKER/PARALYZING DEVICE — Very intimidating and effective.

SHG60.....Assembled.....\$99.50

SHG6.....Plans.....\$10.00 SHG6.....Kit/Plans.....\$79.50

RUBY LASER RAY GUN — Intense visible red beam burns and welds hardest of metals. MAY BE HAZARDOUS.

RUB3All Parts Available for Completing Device \$15.00

CARBON DIOXIDE BURNING, CUTTING LASER — Produces a continuous beam of high energy. MAY BE HAZARDOUS.

LC5. All Parts Available for Completing Device. \$15.00

VISIBLE LASER LIGHT GUN — produces intense red beam for sighting, spotting, etc. Hand held complete.

LGU3.....Plans.....\$10.00 (Kit & Assembled Units Available)

IR PULSED LASER RIFLE — Produces 15-30 watt infra-red pulses at 200-2000 per sec.

LRG3.....All Parts & Diodes Available.....\$10.00

BEGINNERS LOW POWER VISIBLE LASER — Choice of red, yellow, green — provides an excellent source of monochromatic light.

LHC2.....Plans.....\$5.00 LHC2K.....Kit.....\$29.50

SNOOPER PHONE — Allows user to call his premises and listen in without phone ever ringing.

SNP20.....Assembled.....\$89.50

SNP2.....Plans.....\$9.00 SNP2K.....Plans/Kit.....\$59.50

LONG RANGE WIRELESS MIKE — Miniature device clearly transmits well over one mile. Super sensitive, powerful.

MFT1.....Plans.....\$7.00 MFT1K.....Plans/Kit.....\$39.50

WIRELESS TELEPHONE TRANSMITTER — Transmits both sides of phone conversation over one mile, shuts off automatically.

VWPM5.....Plans.....\$8.00 VWPM5K.....Plans/Kit.....\$34.50

TALK & TELL AUTOMATIC TELEPHONE RECORDING DEVICE — Great for monitoring telephone use.

TAT20.....Assembled.....\$24.50

TAT2.....Plans.....\$5.00 TAT2K.....Plans/Kit.....\$14.50

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send for free catalog of hundreds more similar devices. Send check, cash, MO, Visa, MC, COD to: INFORMATION UNLIMITED

DEPT R8, P.O. Box 716, Amherst, N. H. 03031 Tel: 603-673-4730

CIRCLE 88 ON FREE INFORMATION CARD



FOR FREE INFORMATION USE THESE POST-PAID CARDS


Print your name, address and Zip Code on one of the attached postage-paid cards.

Circle the number (or numbers) on the card that matches the number at the bottom of each ad or editorial item that you want information on. Advertisers' free information numbers also appear in the ad index on the facing page.

Mail the card. It's Postage-Paid.

At the bottom free-information card is a BUSINESS/PROFESSIONAL CARD. If you use this card you MUST complete the spaces for Company Name, Title, and Phone Number. If these are not filled in, the card will not be processed.

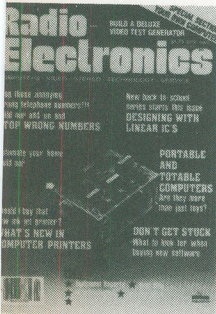NOTE: Use the postcard address for Free Product Information only. Address all editorial inquiries to Editor, Radio-Electronics, 200 Park Ave. South, New York, NY 10003.



Radio-Electronics Your favorite electronics magazine and still getting better

POSTAGE-PAID FREE INFORMATION CARD

Radio-Electronics

Name (please print) \_\_\_\_\_ Title \_\_\_\_\_  
Company Name (if applicable) \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Unclear or incomplete mailing info will prevent our processing this request.

- 2 ☐ Please send me 12 issues of RADIO-ELECTRONICS for \$14.97 and bill me. (Canada \$17.97—US Funds only)  
4 ☐ Please send me 4 issues of HANDS-ON ELECTRONICS for \$10.00 and bill me. (Canada \$13.00—US Funds only)

25	49	73	97	121	145	169	193	217	241	265	289	313	337	361
26	50	74	98	122	146	170	194	218	242	266	290	314	338	362
27	51	75	99	123	147	171	195	219	243	267	291	315	339	363
28	52	76	100	124	148	172	196	220	244	268	292	316	340	364
5	29	53	77	101	125	149	173	197	221	245	269	293	317	341
6	30	54	78	102	126	150	174	198	222	246	270	294	318	342
7	31	55	79	103	127	151	175	199	223	247	271	295	319	343
8	32	56	80	104	128	152	176	200	224	248	272	296	320	344
9	33	57	81	105	129	153	177	201	225	249	273	297	321	345
10	34	58	82	106	130	154	178	202	226	250	274	298	322	346
11	35	59	83	107	131	155	179	203	227	251	275	299	323	347
12	36	60	84	108	132	156	180	204	228	252	276	300	324	348
13	37	61	85	109	133	157	181	205	229	253	277	301	325	349
14	38	62	86	110	134	158	182	206	230	254	278	302	326	350
15	39	63	87	111	135	159	183	207	231	255	279	303	327	351
16	40	64	88	112	136	160	184	208	232	256	280	304	328	352
17	41	65	89	113	137	161	185	209	233	257	281	305	329	353
18	42	66	90	114	138	162	186	210	234	258	282	306	330	354
19	43	67	91	115	139	163	187	211	235	259	283	307	331	355
20	44	68	92	116	140	164	188	212	236	260	284	308	332	356
21	45	69	93	117	141	165	189	213	237	261	285	309	333	357
22	46	70	94	118	142	166	190	214	238	262	286	310	334	358
23	47	71	95	119	143	167	191	215	239	263	287	311	335	359
24	48	72	96	120	144	168	192	216	240	264	288	312	336	360

FREE INFORMATION CARD

VOID after September 30, 1984  
Allow 6-8 weeks for delivery of first issue

BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 597 BOULDER, COLORADO

Radio-Electronics

SUBSCRIPTION SERVICE

P.O. Box 2520

BOULDER, COLORADO 80321

NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

BUSINESS/PROFESSIONAL FREE INFO CARD  
For business information requests

4-784

Radio-Electronics

Name \_\_\_\_\_ Title \_\_\_\_\_  
Company \_\_\_\_\_  
Dept./MS \_\_\_\_\_ Phone ( ) \_\_\_\_\_  
Company Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Unclear or incomplete mailing info will prevent our processing this request.


- 2 ☐ Please send me 12 issues of RADIO-ELECTRONICS for \$14.97 and bill me. (Canada \$17.97—US Funds only)  
4 ☐ Please send me 4 issues of HANDS-ON ELECTRONICS for \$10.00 and bill me. (Canada \$13.00—US Funds only)

25	49	73	97	121	145	169	193	217	241	265	289	313	337	361
26	50	74	98	122	146	170	194	218	242	266	290	314	338	362
27	51	75	99	123	147	171	195	219	243	267	291	315	339	363
28	52	76	100	124	148	172	196	220	244	268	292	316	340	364
5	29	53	77	101	125	149	173	197	221	245	269	293	317	341
6	30	54	78	102	126	150	174	198	222	246	270	294	318	342
7	31	55	79	103	127	151	175	199	223	247	271	295	319	343
8	32	56	80	104	128	152	176	200	224	248	272	296	320	344
9	33	57	81	105	129	153	177	201	225	249	273	297	321	345
10	34	58	82	106	130	154	178	202	226	250	274	298	322	346
11	35	59	83	107	131	155	179	203	227	251	275	299	323	347
12	36	60	84	108	132	156	180	204	228	252	276	300	324	348
13	37	61	85	109	133	157	181	205	229	253	277	301	325	349
14	38	62	86	110	134	158	182	206	230	254	278	302	326	350
15	39	63	87	111	135	159	183	207	231	255	279	303	327	351
16	40	64	88	112	136	160	184	208	232	256	280	304	328	352
17	41	65	89	113	137	161	185	209	233	257	281	305	329	353
18	42	66	90	114	138	162	186	210	234	258	282	306	330	354
19	43	67	91	115	139	163	187	211	235	259	283	307	331	355
20	44	68	92	116	140	164	188	212	236	260	284	308	332	356
21	45	69	93	117	141	165	189	213	237	261	285	309	333	357
22	46	70	94	118	142	166	190	214	238	262	286	310	334	358
23	47	71	95	119	143	167	191	215	239	263	287	311	335	359
24	48	72	96	120	144	168	192	216	240	264	288	312	336	360

FREE INFORMATION CARD

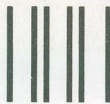VOID after September 30, 1984  
Allow 6-8 weeks for delivery of first issue





NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

## BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 27346 PHILADELPHIA, PA.


POSTAGE WILL BE PAID BY ADDRESSEE

## Radio-Electronics®

FREE PRODUCT INFORMATION

P.O. Box 13775

PHILADELPHIA, PA. 19101

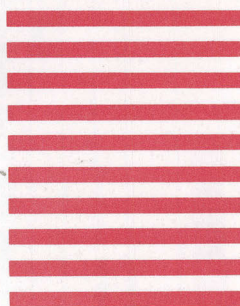

## Radio-Electronics

4SG47

Subscribe today to the magazine that keeps you up-to-date with the newest ideas and innovations in electronics. (If you already are a subscriber, do a friend a favor and pass this subscription card along to him.)

### check offer preferred

- |   |  |
|---|--|
| <input type="checkbox"/> 1 Year—12 issues <b>ONLY \$14.97</b><br>(You save \$6.03 over newsstand) | <input type="checkbox"/> 2 Years ( <b>SAVE MORE</b> )—24 issues \$28.97<br>(You save \$13.03 over newsstand) |
| <input type="checkbox"/> Canada—12 issues \$17.97   | <input type="checkbox"/> Canada—24 issues \$34.97  |
| <input type="checkbox"/> All other countries—12 issues \$22.47                                    | <input type="checkbox"/> All other countries—24 issues \$43.97   |

☐ Payment enclosed

☐ Bill Me

☐ Check here if you are extending or  
renewing your subscription

Name (Please Print) \_\_\_\_\_

Company Name (If applicable) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Allow 6-8 weeks for delivery of first issue

Offer valid in US \$ Only.



NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

## BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 27346 PHILADELPHIA, PA.


POSTAGE WILL BE PAID BY ADDRESSEE

## Radio-Electronics®

FREE PRODUCT INFORMATION

P.O. BOX 13775

PHILADELPHIA PA. 19101

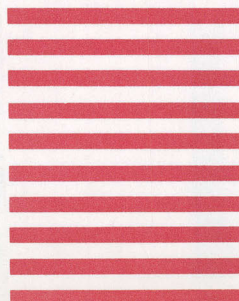

**For New  
Ideas  
In Electronics  
read Radio-  
Electronics  
every month.**

**During the next  
12 months**

Radio-Electronics will carry up to  
the minute articles on:

- Computers • Video
- Solid-state technology
- Outstanding construction projects
- Satellite TV • Telephones
- Radio • Stereo • Equipment reports
- Test equipment • VCR's
- Servicing • Industrial electronics



**NEW IDEAS AND INNOVATIONS  
IN ELECTRONICS APPEAR IN EVERY  
ISSUE OF RADIO-ELECTRONICS**


**KEEP UP TO DATE! DON'T MISS  
ANY ISSUES!**

**SUBSCRIBE TODAY!**

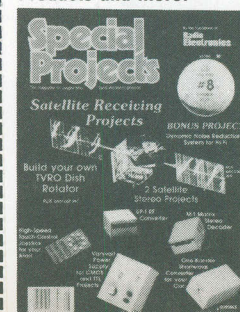**USE THE ORDER CARD ON YOUR LEFT**



**Delivers construction article after  
construction article.....Exciting col-  
umns including Jensen on DXing,  
Friedman on computers, Test bench  
tips, Noll with Calling All Hams, New  
Products and more.**




**SUBSCRIBE TODAY!**

**USE THE REPLY CARDS ON YOUR LEFT**



# WHAT IF

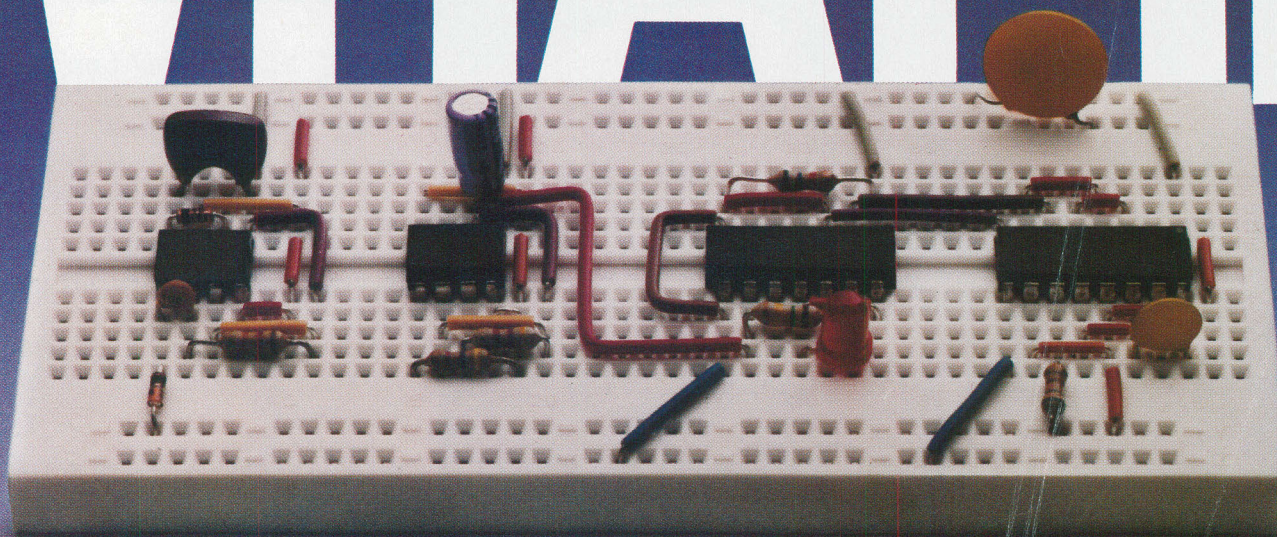

## What if there were a faster way to build and test circuits?

There is. Circuit-Strip from A P PRODUCTS makes circuit building a snap, giving you more time to experiment, to create. With a Circuit-Strip solderless breadboard, all you have to do is plug in components and interconnect them with ordinary #22 AWG solid hook-up wire. If you want to make a circuit change, just unplug the components involved and start over. It's just that easy. Circuit-Strips feature 610 plug-in tie-points and have a capacity of up to 6 14-pin DIPs. Four separate distribution buses of 35 tie-points each give you access for power, ground or signal.

## What if it were easier to identify tie-point locations in a circuit?


It is. Circuit-Strip has a molded-in alpha-numeric grid for instant identification of every tie-point. Schematics can be labeled with each tie-point location to make circuit building faster and troubleshooting easier. Circuit-Strip is ideal for electronic training programs as well as laboratory use.

## What if Circuit-Strip had a new low price?

It does. Circuit-Strip now carries a suggested resale price of only \$12. That means that the best tool for the job now has the best price ever.
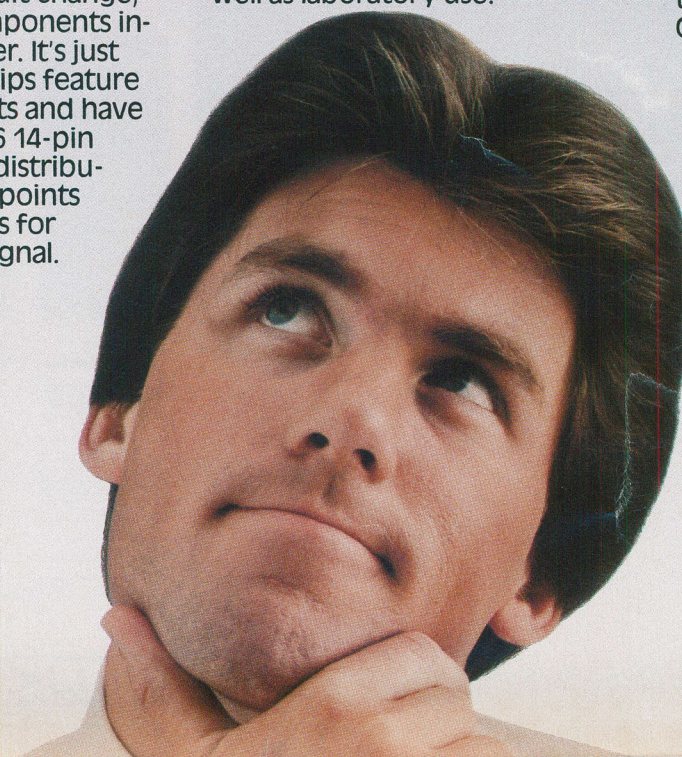
## What if you need more information?

That's easy, too. Just call toll free 800-321-9668 for the name of the distributor near you. (In Ohio, call collect (216) 354-2101.)



A P PRODUCTS INCORPORATED  
9450 Pineneedle Dr. • Box 540  
Mentor, Ohio 44061-0540  
[216] 354-2101  
TWX: 810-425-2250  
In Europe, contact A P PRODUCTS  
GmbH Baumslesweg 21  
D-7031 Weil 1 • West Germany  
Phone: [07157] 62424  
TLX: 841 07 23384

CIRCLE 87 ON FREE INFORMATION CARD



# The Digital vs. Analog battle is over.

**\$85\*** buys you the new champion.  
**The new Fluke 70 Series.**

They combine digital and analog displays for an unbeatable two-punch combination.

Now, digital users get the extra resolution of a 3200-count LCD display.

While analog users get an analog bar graph for quick visual checks of continuity, peaking, nulling and trends.

Plus unparalleled operating ease, instant autoranging, 2,000+ hour battery life and a 3-year warranty.

All in one meter.

Choose from three new models. The Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own multipurpose protective holster and unique "Touch Hold" function (patent pending) that captures and holds readings, then beeps to alert you.

Each is Fluke-tough to take a beating. American-made, to boot. And priced to be, quite simply, a knockout.

For your nearest distributor or a free brochure, call toll-free anytime **1-800-227-3800, Ext. 229**. From outside U.S., call 1-402-496-1350, Ext. 229.

FROM THE WORLD LEADER  
IN DIGITAL MULTIMETERS.



**Fluke 73**

\$85\*  
Analog/digital display  
Volts, ohms, 10A, diode test  
Autorange  
0.7% basic dc accuracy  
2000+ hour battery life  
3-year warranty



**Fluke 75**

\$99\*  
Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
Autorange/range hold  
0.5% basic dc accuracy  
2000+ hour battery life  
3-year warranty



**Fluke 77**

\$129\*  
Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
"Touch Hold" function  
Autorange/range hold  
0.3% basic dc accuracy  
2000+ hour battery life  
3-year warranty  
Multipurpose holster

\* Suggested U.S. list price, effective October 1, 1983.

